



COURSE FILE

ACADEMIC YEAR : 2022-23


SUBJECT : Electronic Circuits- Analysis & Design

YEAR/SEM : II B. Tech II-Sem

DEPARTMENT : Electronics & Communication Engineering

FACULTY NAME : Dr. Y. Madhu Sudhana Reddy

S. No	Contents	Page No.
1	Time Table	1
2	Syllabus & Lesson Plan	2-5
3	Register & Sample Mid Script	6-20
4	Assignment Questions with solutions	21-64
5	Mid Question Papers	65-87
6	External Question Papers with solutions	88-150
7	CO-PO Calculation	151-167
8	External Exam Student Answer Script	168-201
9	Course Materials	202-447
10	Contents covered beyond Syllabus	448-470
11	Expert Suggestion	471
12	Result Analysis	472-473

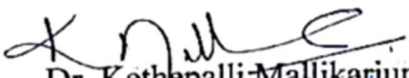
Dr. Kethapalli Mallikarjuna
B. E., M. Tech., M. Ed., M. A., M. E., M. I. E., M. I. E., M. I. E.
Professor & HOD
Department of ECE
RGM College of Engg. & Tech. (Autonomous)
NANDYAL - 518 501, Kurnool (Dist), A.P.


Dr. T. Jayachandra Prasad
Principal
M. E. Ph. D.,
PRINCIPAL
R. G. M. College of Engg. & Tech.,
(Autonomous)
NANDYAL-518 501, Nandyal (Dt), A.P.

R.G.M.COLLEGE OF ENGINEERING & TECHNOLOGY, NANDYAL – 518 501
DEPARTMENT OF ELECTRONICS AND COMMUNICATION ENGINEERING

II B.Tech., II-Semester
w.e.f: 16-03-2023

Academic Year: 2022-23

A-Section : RB2130 B-Section : RB2010
 C-Section : RB2020 D-Section : RB2030

Period/ Day	Section	1	2	3	4	5	6	7
		9.00 AM To 9.50 AM	9.50 AM To 10.40 AM	11.00 AM To 11.50 AM	11.50 AM To 12.40 PM	1.50 PM To 2.40 PM	2.40 PM To 3.30 PM	3.30 PM To 4.20 PM
MON	A	RVRP	ECA&D	EMFT&L	COU	PP	ARMMCI	AARC
	B	ARMMCI	PP Lab			RVRP	PP	EMFT&L
	C	ECA&D	AMRP Lab/ECA&D Lab			AARC	RVRP	ARMMCI
	D	PP	ECA&D	RVRP	AARC	ARMMCI	EMFT&L	LIB
TUE	A	RVRP	AMRP Lab/ECA&D Lab			ECA&D	EMFT&L	PP
	B	ECA&D	EMFT&L	PP	AARC	AMRP Lab/ECA&D Lab		
	C	PP	ECA&D	COU	ARMMCI	EMFT&L	RVRP	LIB
	D	ARMMCI	EMFT&L	ECA&D	PP	PP Lab		
WED	A	PP	EMFT&L	ECA&D	ARMMCI	AMRP Lab/ECA&D Lab		
	B	RVRP	ARMMCI	EMFT&L	PP	COU	ECA&D	LIB
	C	PP	EMFT&L	AARC	RVRP	PP Lab		
	D	RVRP	AMRP Lab/ECA&D Lab			ARMMCI	AARC	ECA&D
THU	A	PP	ECA&D	RVRP	AARC	ARMMCI	EMFT&L	LIB
	B	PP	ECA&D	ARMMCI	EMFT&L	RVRP	IEI/ISTE	AARC
	C	PP	EMFT&L	ECA&D	ARMMCI	AMRP Lab/ECA&D Lab		
	D	ECA&D	ARMMCI	IEI/ISTE	EMFT&L	PP	RVRP	COU
FRI	A	ARMMCI	PP Lab			ARRC	PP	RVRP
	B	ECA&D	RVRP	ARRC	ARMMCI	AMRP Lab/ECA&D Lab		
	C	RVRP	EMFT&L	IEI/ISTE	AARC	ARMMCI	ECA&D	PP
	D	EMFT&L	AMRP Lab/ECA&D Lab			RVRP	PP	AARC
SAT	A	ARMMCI	IEI/ISTE	ECA&D	EMFT&L	RVRP	EAA	
	B	RVRP	EMFT&L	PP	ARMMCI	ECA&D		
	C	ECA&D	PP	ARMMCI	EMFT&L	RVRP		
	D	PP	EMFT&L	ECA&D	RVRP	ARMMCI		

Subject	Section	Name of the Faculty
PP	A	Dr.A.Sathish
ARMMCI	A	Smt.R.Sireesha
ECA&D	A	Mr.P.Anand Rao
EMFT&L	A	Dr.M.Chennakesavulu
RVRP	A	Mr.T.Tirumalesh
AARC	A	Smt.Y.Akhila
PP Lab	A	Dr.AS/Dr.NR/Dr.AKS/DBKR
ARMP Lab	A	Smt.RS/Mr.JLMK
ECA&D Lab	A	Smt.VS/Mr.YSPD/Smt.KSR
COU	A	Mr.D.Rajesh Setty
IEI/ISTE	A	Smt.V.Saraswathi

Subject	Section	Name of the Faculty
PP	B	Mr.D.B Krishna Reddy
ARMMCI	B	Smt.R.Sireesha
ECA&D	B	Mr.Y.M Sudhana Reddy
EMFT&L	B	Mr.K.Mastan Vali
RVRP	B	Smt.V.Saraswathi
AARC	B	Smt.Y.Akhila
PP Lab	B	Mr.DBKR/Dr.AS/Dr.AKS
ARMP Lab	B	Mr.PR/Smt.RS
ECA&D Lab	B	Mr.YMSR/Smt.VS/Smt.KSR
COU	B	Mr.D.Rajesh Setty
IEI/ISTE	B	Smt.V.Saraswathi

Subject	Section	Name of the Faculty
PP	C	Dr.Ajit Kumar Singh
ARMMCI	C	Dr.P.V.Gopi Krishna Rao
ECA&D	C	Smt.B.Geetha Rani
EMFT&L	C	Dr.V.N.V.Satya Prakash
RVRP	C	Mr.P.Chandra Sekar
AARC	C	Mr.E.V.Raghavendra
PP Lab	C	Dr.AKS/Dr.NR/Dr.AS/DBKR
ARMP Lab	C	Mr.JLMK/Mr.YSPS(MON)
ECA&D Lab	C	Smt.BGR/Mr.TT/Smt.GILP
COU	C	Smt.B.Nazma
IEI/ISTE	C	Smt.V.Saraswathi

Subject	Section	Name of the Faculty
PP	D	Dr.N.Ramanjaneyulu
ARMMCI	D	Mrs.P.Prasanthi
ECA&D	D	Dr.C.Venkataiah
EMFT&L	D	Mrs.G.I.Lakshmi Prasanna
RVRP	D	Mr.P.Chandra Sekar
AARC	D	Mr.E.V.Raghavendra
PP Lab	D	Dr.NR/Mr.DBKR/Dr.AKS
ARMP Lab	D	Dr.PVGKR/Mr.DBKR(FRI)
ECA&D Lab	D	Dr.CV/Smt.BGR/Mr.TT
COU	D	Smt.B.Nazma
IEI/ISTE	D	Smt.V.Saraswathi


Dr.K.Mallikarjuna
HOD OF ECE
 B.E., M.Tech, Ph.D, MISTE, FIETE, MIE
 Professor & HOD
 Department of ECE


Dr.T.Durga Chandra Prasad
Principal
 M.E., Ph.D.,
PRINCIPAL

R G M COLLEGE OF ENGINEERING AND TECHNOLOGY
AUTONOMOUS
ELECTRONICS AND COMMUNICATION ENGINEERING

II B.Tech, II-Sem(ECE)

L	T	C
2	1	3

(A0409204) ELECTRONIC CIRCUITS – ANALYSIS AND DESIGN

COURSE OBJECTIVES:

- ❖ To study the analysis and design of single stage and multistage amplifiers at low and high frequencies.
- ❖ Electrical equivalent model of transistor at low and high frequencies.
- ❖ Study of small signal and large signal amplifiers and their area of applications.
- ❖ To understand the concepts of feedback and their applications (Voltage feedback amplifiers and oscillators)

COURSE OUTCOMES:

- ❖ Design and analyze single stage amplifiers using BJT and MOSFET at low frequencies.
- ❖ Design and analyze multi stage amplifiers using BJT and MOSFET at low frequencies.
- ❖ Discuss frequency response of single stage BJT and MOSFET amplifiers at low and high frequencies.
- ❖ Explain effect of negative feedback on amplifier characteristics.
- ❖ Discuss basic principles for analyzing RC & LC oscillator circuits using BJT and MOSFET.
- ❖ Design and analyse different types of large signal amplifiers.

MAPPING WITH COs & POs:

	PO1	PO2	PO3	PO4	PO5	PO6	PO7	PO8	PO9	PO10	PO11	PO12	PSO1	PSO2	PSO3
CO1	1	3	2		1							1	3	1	
CO2	2	2			2							2	3	2	
CO3	2	3	2	2	1							2		2	1
CO4	1	3	2	2								1	1	2	1
CO5	3	1	2		1							2		2	1
CO6	2	1	2	2	1								2	1	1

UNIT I

Small Signal Analysis of BJT: Basic CE amplifier circuit. Circuit with Emitter resistance, AC load line analysis. Small signal analysis-input and output impedances. Voltage gain. Current gain of CE, CB, CC amplifiers using h-parameter model and simplified model, Problem solving.

Small Signal Analysis of MOSFETs: Graphical and Load line analysis, small signal parameters, Small signal equivalent circuit, Small signal analysis of Common source, Common drain, Common gate amplifiers, Comparison of the three basic amplifier configurations, Problem solving.

UNIT II**Differential and Multistage Amplifiers:**

The MOS Differential Pair, Small-Signal Operation of the MOS Differential Pair, The BJT Differential Pair, Other Non-ideal Characteristics of the Differential Amplifier, The Differential Amplifier with Active Load, Multistage Amplifiers – RC coupled amplifier – Darlington pair – Cascode amplifier, Problem solving.

UNIT III**Frequency Response:**

Introduction. Low-Frequency Response of the CS and CE Amplifiers. Internal Capacitive Effects and the High-Frequency Model of the MOSFET and the BJT. High-Frequency Response of the CS and CE Amplifiers. Useful Tools for the Analysis of the High-Frequency Response of Amplifiers. A Closer Look at the High-Frequency Response of the CS and CE Amplifiers. High-Frequency Response of the CG and Cascode Amplifiers. High-Frequency Response of the Source and Emitter Followers. High-Frequency Response of Differential Amplifiers. Other Wideband Amplifier Configurations. Multistage Amplifier Examples, Problem solving.

UNIT IV**Feedback Amplifiers:**

Introduction, The General Feedback Structure, Some Properties of Negative Feedback, The Four Basic Feedback Topologies, The Feedback Voltage Amplifier (Series—Shunt), The Feedback Transconductance

R G M COLLEGE OF ENGINEERING AND TECHNOLOGY
AUTONOMOUS
ELECTRONICS AND COMMUNICATION ENGINEERING

Amplifier. The Feedback Transresistance Amplifier (Shunt—Shunt). The Feedback Current Amplifier (Shunt—Series). Summary of the Feedback Analysis Method. Determining the Loop Gain, Problem solving.

UNIT V**Power Amplifiers:**

Introduction, Classification of Output Stages, Class A Output Stage, Class B Output Stage, Class AB Output Stage, Biasing the Class AB Circuit, CMOS Class AB Output Stages, Power BJTs, Variations on the Class AB Configuration, IC Power Amplifiers, MOS Power Transistors, Problem solving.

UNIT VI**Oscillators and Tuned Amplifiers:**

Oscillators: General Considerations, Classification of Oscillators, LC Oscillators using BJT and FET-Healy and Colpit's Oscillators, RC Oscillators using BJT and FET- Phase Shift and Wien-Bridge Oscillators, Crystal Oscillators, Illustrative Problems.

Tuned Amplifiers: Basic Principle, Inductor losses, use of transformers, Amplifiers with multiple tuned circuits.

TEXT BOOKS:

- 1) Adel S. Sedra and Kenneth C. Smith, "Micro Electronic Circuits". Oxford University Press International 6th edition. 2013.
- 2) Donald A Neamen. "Electronic Circuits – analysis and design", 3rd Edition. McGraw Hill (India), 2019.

REFERENCES:

- 1) J. Milliman and C Halkias, "Integrated electronics", 2nd Edition, Tata McGraw Hill, 1991.
- 2) Behzad Razavi, "Microelectronics", Second edition, Wiley, 2013.
- 3) R.L. Boylestad and Louis Nashelsky, "Electronic Devices and Circuits," 9th Edition, Pearson, 2006.
- 4) Jimmie J Cathey, "Electronic Devices and Circuits," Schaum's outlines series, 3rd edition, McGraw-Hill (India), 2010.

(AUTONOMOUS)

DAPARTMENT OF ECE

LESSON PLANName of the Faculty: **Dr. Y. MADHU SUDHANA REDDY**Academic Year: **2022-23**Class and Semester: **II B.Tech II-Sem**Branch: **ECE - B**Subject: **ELECTRONIC CIRCUITS- ANALYSIS & DESIGN**Regulation: **RGM-R20**

UNIT NO.	TOPIC	NO. OF PERIODS
I	Small Signal Analysis of BJT:	
	Basic CE amplifier circuit and Circuit with Emitter resistance,	01
	AC load line analysis	01
	Small signal analysis-input and output impedances, Voltage gain, Current gain of CE, CB, CC amplifiers using h-parameter model and simplified model of CE, CC and CB configurations and its analysis	03
	Problem solving.	02
	Small Signal Analysis of MOSFETs: Graphical and Load line analysis	02
	small signal parameters and small signal equivalent circuit	01
	Small signal analysis of Common source, Common drain, Common gate amplifiers	02
	Comparison of the three basic amplifier configurations	02
	Problem solving.	01
II	Differential and Multistage Amplifiers:	
	The MOS Differential Pair	01
	Small-Signal Operation of the MOS Differential Pair	02
	The BJT Differential Pair	01
	Other Non-ideal Characteristics of the Differential Amplifier	01
	The Differential Amplifier with Active Load	02
	Multistage Amplifiers – RC coupled amplifier – Darlington pair – Cascode amplifier	02
	Problem solving.	02
III	Frequency Response:	
	Introduction	01
	Low-Frequency Response of the CS and CE Amplifiers	02
	Internal Capacitive Effects and the High-Frequency Model of the MOSFET and the BJT	01
	High-Frequency Response of the CS and CE Amplifiers	01
	Useful Tools for the Analysis of the High-Frequency Response of Amplifiers	01
	A Closer Look at the High-Frequency Response of the CS and CE Amplifiers	01
	High-Frequency Response of the CG and Cascode Amplifiers	01
	High-Frequency Response of the Source and Emitter Followers	01
	High-Frequency Response of Differential Amplifiers	01

	Other Wideband Amplifier Configurations Multistage Amplifier Examples Problem solving.	01 01 01
IV	Feedback Amplifiers: Introduction The General Feedback Structure Some Properties of Negative Feedback The Four Basic Feedback Topologies The Feedback Voltage Amplifier (Series—Shunt) The Feedback Transconductance Amplifier The Feedback Transresistance Amplifier (Shunt—Shunt) The Feedback Current Amplifier (Shunt—Series) Summary of the Feedback Analysis Method Determining the Loop Gain, Problem solving.	01 01 01 01 01 01 01 01 01 01
V	Power Amplifiers: Introduction Classification of Output Stages Class A Output Stage Class B Output Stage Class AB Output Stage Biasing the Class AB Circuit CMOS Class AB Output Stages Power BJTs Variations on the Class AB Configuration IC Power Amplifiers, MOS Power Transistors Problem solving.	01 01 01 01 01 01 01 01 01 01 01
VI	Oscillators and Tuned Amplifiers: Oscillators: General Considerations Classification of Oscillators LC Oscillators using BJT and FET-Healy and Colpit's Oscillators RC Oscillators using BJT and FET- Phase Shift and Wien-Bridge Oscillators Crystal Oscillators Illustrative Problems. Tuned Amplifiers: Basic Principle Inductor losses, use of transformers Amplifiers with multiple tuned circuits.	01 01 02 02 01 01 01 01 01 01

TOTAL CLASSES REQUIRED: 71


Signature of the Faculty


Signature of the HOD

**RGM COLLEGE OF ENGINEERING & TECHNOLOGY
(AUTONOMOUS)**

NANDYAL - 518 501, Kurnool (Dist.) A.P.



ATTENDANCE REGISTER

ACADEMIC YEAR	: 2022-23	SEM	: I / II
COURSE	: B.Tech	CLASS	: B.Tech
BRANCH / SECTION	: ECE - B		
SUBJECT &	: 03		
CREDITS	: Electronic Circuit - Analysis & Design		
FACULTY	: Mr. Y. Madhu Sudhana Reddy.		

R.G.M. COLLEGE OF ENGINEERING ATTENDANCE

Class : B.Tech

Branch : ECE - B

Semister / Year II / II

Roll No.	Name	Date											
		16/03/23	16/03/23	17/03/23	18/03/23	21/03/23	23/03/23	24/03/23	25/03/23	03/04/23	04/04/23	05/04/23	11/04/23
		1	2	3	4	5	6	7	8	9	10	11	12
21091A0 465	Y. Jaya Sreenivas Reddy	A	A	A	A	A	A	A	A	1	2	3	4
466	P. Jayasurya	A	A	A	A	A	A	A	A	1	2	3	4
467	P. Jithendra Reddy	A	A	A	A	A	A	A	1	2	3	A	4
468	N. Johnson Kumar	A	A	A	A	A	A	A	1	A	2	A	A
469	B. Kailashnath Reddy	A	A	A	A	A	A	A	1	2	3	4	5
470	K. Kalyani	A	A	1	A	2	3	4	5	6	7	8	9
471	Y. Karthik Kumar Reddy.	A	A	A	A	A	A	A	A	1	2	3	A
472	U. Karthik	A	A	A	A	A	A	A	A	1	2	A	A
473	B. Kasi Eswari	A	A	A	A	1	2	3	4	5	6	7	8
474	D. Kasim Saheb	A	A	A	A	A	A	A	1	2	3	4	5
475	N. Keerthi	A	A	A	A	A	A	1	2	3	4	A	5
476	P. Khadar Basha	A	A	A	A	A	A	A	A	1	2	A	3
477	K. Kiran Kumar Naik	A	A	A	A	A	A	A	A	1	2	3	4
478	B. Krupakar	A	A	A	A	A	1	2	A	3	4	5	6
479	M. Lakshmi Devi	A	A	A	A	A	1	2	3	4	5	6	7
480	S. Lakshmi Narasimhulu	A	A	1	A	2	A	A	A	3	4	A	A
481	B. Lavanya	1	2	A	A	A	A	A	3	4	5	6	A
482	K. Lavanya	A	A	1	A	2	3	4	5	6	7	8	9
483	K. Likhitha	A	A	A	A	A	A	1	2	A	3	4	5
484	B. Lomith Reddy.	1	2	3	4	5	A	6	7	8	9	10	11
485	P. Mabulkussain	A	A	A	A	A	1	2	3	4	5	6	7
486	B. Madhavi	A	A	1	A	2	3	4	5	6	7	8	9
487	M. Madhu	A	A	A	A	A	A	A	1	2	3	4	5
488	G. Madhusudhan Reddy	A	A	A	A	A	A	1	2	3	4	5	6
489	E. Madhusudhan Goud	A	A	A	A	A	A	A	1	2	3	4	5
490	G. Madhu Sudhan	A	A	A	A	A	A	A	1	2	A	3	
491	G.G. Mahammad Basha	A	A	A	A	A	A	1	2	3	4	5	6
493	U. Mahesh	A	A	A	A	A	A	1	A	2	3	4	5
494	Y. Mahesh	A	A	A	A	A	A	A	1	2	3	4	
495	S. Mahitha	A	A	A	A	A	A	1	2	3	4	A	5

Signature of Teacher

Signature of II.O.D.

Signature of Principal

& TECHNOLOGY (Autonomous) REGISTER

Academic Year from

Roll No.	Date																							
	05/10/23	07/10/23	09/10/23	11/10/23	13/10/23	15/10/23	17/10/23	19/10/23	21/10/23	23/10/23	25/10/23	27/10/23	29/10/23	31/10/23	02/11/23	04/11/23	06/11/23	08/11/23	10/11/23	12/11/23	14/11/23	16/11/23	18/11/23	
65	5	6	A	7	8	9	10	11	12	13	14													
66	5	A	6	7	8	9	10	11	12	13	14													
67	5	A	6	7	8	9	10	11	12	13	14													
68	3	4	5	6	7	8	9	10	11	12	13	14	15											
69	6	7	A	8	9	10	11	12	13	14	15													
70	10	11	A	12	13	14	15	16	17	18	19													
71	4	5	6	7	8	9	10	11	12	13	14													
72	3	4	5	6	7	8	9	10	11	12	13													
73	9	10	A	11	12	13	14	15	16	17	18													
74	6	7	A	8	9	10	11	12	13	14	15													
75	6	7	A	8	9	10	11	12	13	14	A													
76	4	5	A	6	7	8	9	10	11	12	13													
77	5	6	7	8	9	10	11	12	13	14	15													
78	7	8	A	9	10	11	12	A	13	14	15													
79	8	9	10	11	12	13	14	15	16	17	18													
80	5	6	A	7	8	9	10	11	12	13	14													
81	7	8	9	10	11	12	13	14	15	16	17													
82	10	11	A	12	13	14	15	16	17	18	19													
83	6	7	A	8	9	10	11	12	13	14	15													
84	12	13	A	14	15	16	17	18	19	20	21													
85	8	9	10	11	12	13	14	15	16	17	18													
86	10	11	A	12	13	14	15	16	17	18	19													
87	6	7	A	8	9	10	11	A	12	13	14													
88	7	8	9	10	11	12	13	14	15	16	17													
89	6	7	A	8	9	10	11	A	12	13	14													
90	4	5	A	A	A	6	7	8	9	10	11													
91	7	8	9	10	11	12	13	14	15	16	17													
92	6	7	8	9	10	11	12	13	14	15	16													
94	5	6	A	7	8	9	10	11	12	13	14													
95	6	7	A	8	9	10	11	12	13	14	15													

R.G.M. COLLEGE OF ENGINEERING ATTENDANCE

Class : B.Tech
Branch : ECE - B

Roll No.	Name	Date	
		16/05/23	17/05/23
465	Y. Jaya Sreenivas Reddy	A	
466	P. Jayasurya	A	
467	P. Jithendra Reddy	A	
468	N. Johnson Kumar	A	
469	B. Kailashnath Reddy	A	
470	K. Kalyani	A	
471	Y. Karthik Kumar Reddy	A	
472	U. Karthik	A	
473	B. Kasi Eswari	A	
474	D. Kasim Sahab	A	
475	N. Keerthi	A	
476	P. Khadar Basha	A	
477	K. Kiran Kumar Naik	A	
478	B. Krupakar	A	
479	M. Lakshmi Devi	A	
480	S. Lakshmi Narasimhulu	A	
481	B. Lavanya		
482	K. Lavanya	A	
483	K. Likhitha	A	
484	B. Lomith Reddy		
485	P. Mabulkussain	A	
486	B. Madhavi	A	
487	M. Madhu	A	
488	G. Madhusadhan Reddy	A	
489	E. Madhusadhan Goud	A	
490	G. Madhu Sadhan	A	
491	G.G. Mahammad Basha	A	
493	U. Mahesh	A	
494	Y. Mahesh	A	
495	S. Mahitha	A	

Signature of Teacher _____
Signature of II.O.D. _____
Signature of Principal _____

Roll No.	24	25	26	27	28	29	30	31	32	33	34	
55	A	15	16	17	18	19	20	A	A	A	21	22
66	A	16	17	18	19	20	A	A	A	A	21	22
67	A	15	A	A	16	17	18	A	A	19	20	
68	A	14	15	16	17	18	19	A	A	A	20	
69	16	17	18	19	20	A	21	A	A	22	A	
70	20	21	22	23	24	25	26	27	28	29	30	
71	15	16	17	18	19	A	A	A	A	A	A	
72	15	16	17	18	A	A	19	A	A	20	21	
73	A	19	20	21	22	23	24	25	26	27	28	
74	16	17	18	19	20	21	A	A	A	22	23	
75	15	16	17	18	A	19	A	20	21	22	23	
76	14	A	A	A	15	16	17	A	A	18	19	
77	16	17	18	19	20	21	22	A	A	23	24	
78	16	17	18	19	20	21	22	A	A	23	24	
79	19	20	21	22	23	A	24	A	A	25	26	
80	15	16	17	18	19	A	A	A	A	A	A	
81	18	19	20	21	A	22	A	A	A	23	24	
82	20	21	22	23	24	25	26	A	27	A	28	
83	16	17	18	19	20	21	22	A	23	24	25	
84	22	23	24	25	26	27	A	28	29	30	31	
85	19	A	20	21	A	22	A	23	24	25	26	
86	A	20	21	22	23	24	25	26	27	28	29	
87	15	16	17	18	19	20	A	A	A	21	22	
88	18	19	A	A	20	21	22	23	24	15	26	
89	15	16	17	18	19	20	21	A	22	23	24	
90	12	13	14	15	16	17	18	A	A	19	20	
91	18	19	20	21	22	23	24	25	26	27	28	
93	17	18	19	20	21	22	23	A	A	24	A	
94	15	16	17	18	19	A	20	A	A	A	21	
95	16	17	18	19	20	21	A	A	A	A	22	

& TECHNOLOGY (Autonomous) REGISTER Academic Year from

Roll No.	14/06/23	15/06/23	16/06/23	17/06/23	18/06/23	19/06/23	20/06/23	21/06/23	22/06/23	23/06/23	24/06/23	25/06/23	26/06/23	27/06/23	28/06/23	29/06/23
65	23	24	25	26	27	28	29	30	31	32	33					
66	23	24	25	26	27	28	29	30	31	32	33					
67	21	22	A	23	24	25	26	27	28	29	30					
68	21	22	A	23	24	A	A	25	A	A	A					
69	23	24	25	26	27	28	29	30	31	32	33					
70	31	32	33	34	35	36	37	38	39	40	41					
71	20	21	22	23	24	A	A	25	A	26	27					
72	22	23	24	25	26	27	28	29	30	31	32					
73	29	30	31	32	33	34	35	36	37	38	39					
74	24	25	26	27	28	29	30	31	A	32	33					
75	24	25	26	27	28	29	30	31	32	33	34					
76	20	21	22	23	24	25	26	27	28	29	30					
77	25	26	27	28	29	30	31	32	A	33	34					
78	25	26	A	A	A	27	28	29	A	30	31					
79	27	28	29	30	31	A	A	32	33	34	35					
80	A	A	20	21	22	23	24	25	26	27	28					
81	25	A	26	27	28	29	30	31	32	A	A					
82	29	30	31	32	33	34	35	36	37	38	39					
83	26	27	28	29	30	31	32	33	34	35	36					
84	32	A	33	34	35	36	37	38	39	40	41					
85	27	A	A	28	29	A	A	30	31	32	33					
86	30	31	32	33	34	35	36	37	38	A	A					
87	23	A	24	25	26	27	28	29	30	31	32					
88	27	28	29	30	31	32	33	34	35	36	37					
89	A	25	26	27	28	29	30	31	A	32	33					
90	21	22	A	A	23	24	25	26	27	28	29					
91	29	30	31	32	33	34	35	36	37	38	A					
93	25	26	27	28	29	30	31	32	33	34	35					
94	22	23	24	25	26	27	28	29	30	31	32					
95	23	24	25	26	27	28	29	30	31	32	33					

R.G.M. COLLEGE OF ENGINEERING ATTENDANCE

Class : B.Tech

Branch : ECE - B

Roll No.	Name	Date	
		16/03/23	1
21091A0 465	Y. Jaya Sreenivas Reddy	A	
466	P. Jayasurya	A	
467	P. Jithendra Reddy	A	
468	N. Johnson Kumar	A	
469	B. Kailashnath Reddy	A	A
470	K. Kalyani	A	A
471	Y. Karthik Kumar Reddy.	A	A
472	U. Karthik	A	A
473	B. Kasi Eswari	A	A
474	D. Kasim Saheb	A	A
475	N. Keerthi	A	A
476	P. Khadar Basha	A	A
477	K. Kiran Kumar Naik	A	A
478	B. Krupakar	A	A
479	M. Lakshmi Devi	A	A
480	S. Lakshmi Narasimhulu	A	A
481	B. Lavanya		
482	K. Lavanya	A	A
483	K. Likhitha	A	A
484	B. Lomith Reddy.		
485	P. Mabu Hussain	A	A
486	B. Madhavi	A	A
487	M. Madhu	A	A
488	G. Madhusudhan Reddy.	A	A
489	E. Madhusudhan Soud	A	A
490	G. Madhu Sudhan	A	A
491	G.G. Mohammad Basha	A	A
493	U. Mahesh	A	A
494	Y. Mahesh	A	A
495	S. Mahitha	A	A
Signature of Teacher			
Signature of II.O.D.			
Signature of Principal			

Roll No.	28/06/23	30/06/23	01/07/23	02/07/23	05/07/23	06/07/23	07/07/23	07/07/23	54	55	56
46											
47											
48											
49											
50											
51											
52											
53											
54											
55											
56											
65	34	35	36	37	38	39	40	41			
66	34	35	36	37	38	39	40	41			
67	31	32	33	34	35	36	A	A			
68	26	27	A	28	29	30	31	32			
69	34	35	36	37	38	39	40	41			
70	42	43	44	45	46	47	48	A			
71	28	29	30	31	32	33	34	35			
72	33	34	35	36	37	38	39	40			
73	A	40	41	42	43	44	45	A			
74	32	35	36	37	38	39	40	41			
75	35	36	37	38	39	40	A	A			
76	31	32	A	33	34	35	36	37			
77	35	36	37	38	39	40	41	A			
78	32	33	34	35	36	37	38	39			
79	36	37	38	A	39	40	A	A			
80	29	30	31	32	33	34	35	36			
81	33	34	35	A	36	37	A	A			
82	40	41	42	43	44	45	46	47			
83	37	38	39	40	41	42	43	A			
84	42	43	A	44	45	46	47	A			
85	34	35	36	37	38	39	40	A			
86	39	40	A	41	42	43	44	45			
87	33	34	35	36	37	38	39	40			
88	38	39	40	41	42	43	44	A			
89	34	35	36	37	38	39	40	A			
90	30	31	32	33	34	35	36	37			
91	39	40	41	42	43	44	45	46			
93	36	37	38	39	40	41	42	43			
94	A	33	34	35	36	37	38	A			
95	34	35	36	37	38	39	A	A			

R.G.M. COLLEGE OF ENGINEERING & TECHNOLOGY (Autonomous)

REGISTER

Class : B.Tech
Branch : ECE-B

Semester / Year 5 / 15

Roll No.	Name	Date											
		16/03/23	16/03/23	17/03/23	18/03/23	21/03/23	23/03/23	04/04/23	05/04/23	05/04/23	06/04/23	07/04/23	08/04/23
		1	2	3	4	5	6	7	8	9	10	11	12
496	R.B.N.R.G. Maniswari	A	A	A	A	A	A	A	A	1	2	3	4
497	G. Manasa	A	A	A	A	A	A	1	2	3	4	A	5
498	M. Manasa	A	A	A	A	A	A	A	1	2	3	4	5
499	M. Manikumar Naik	A	A	A	A	A	A	A	A	1	2	3	A
4A0	U. Manikanta	A	A	A	A	A	A	A	A	1	2	3	A
4A1	P. Manisha	A	A	A	A	A	A	A	A	1	2	A	3
4A2	G. Manjula	A	A	A	A	A	A	1	2	3	4	5	A
4A3	B. Manoj Kumar Reddy	A	A	A	A	A	A	A	A	1	2	3	A
4A4	M. Manoj Kumar	A	A	A	A	A	A	A	1	2	3	4	5
4A5	K. Manoj	A	A	A	A	A	A	A	1	2	3	A	4
4A6	V. Maria Dhathri	A	A	A	A	1	A	2	3	4	5	A	6
4A7	V. Maruthi	A	A	A	A	A	A	A	A	1	2	A	3
4A8	M. Meenakshi	A	A	A	A	A	A	A	A	1	2	A	A
4A9	A. Meghana	A	A	A	A	1	2	3	4	A	5	6	7
4B0	C.T. Mithunteja	A	A	A	A	A	A	A	A	A	A	A	1
4B1	S. Mohamād Abbas	A	A	A	A	1	A	2	3	A	A	4	A
4B2	S. Mohammad Irfan	A	A	A	A	1	A	2	3	A	4	5	A
4B3	S. Mohammad Arif	A	A	A	A	1	2	3	4	5	6	7	8
4B4	P. Maunika	A	A	A	A	1	A	2	3	A	4	5	6
4B5	M. Mythili	A	A	A	A	1	2	3	4	A	5	A	6
4B6	B. Naga Sujanya	A	A	A	A	A	A	1	A	A	2	A	A
4B7	B. Naga Udayaswar Reddy	A	A	A	A	A	A	1	2	3	4	5	A
4B9	B. Nagaraju.	A	A	A	A	A	A	1	2	3	4	5	A
4C0	R.G. Nagesh	A	A	A	A	A	A	A	A	1	2	A	3
4C1	B. Naveen	A	A	A	A	1	2	3	4	5	A	A	6
4C2	R. Naveen	A	A	A	A	1	2	3	4	5	6	7	P
4C3	D. Nisheth	A	A	A	A	A	A	A	1	2	3	4	5
4C4	P. Nishitha	A	A	A	A	A	A	1	2	3	4	5	A
4C5	R. Pavan Kumar Reddy	A	A	A	A	A	A	A	1	2	3	A	A
4C6	S. Pavan Kumar Reddy	A	A	A	A	A	A	A	1	2	3	4	A

Signature of Teacher

Signature of H.O.D.

Signature of Principal

Roll No.	13	14	15	16	17	18	19	20	21	22	23
96	5	6	7	8	9	10	11	12	13	14	15
97	6	7	A	8	9	10	11	12	13	14	15
98	6	7	8	9	10	11	12	13	14	15	16
99	4	5	A	6	7	8	9	10	11	12	13
A0	4	5	A	A	A	6	7	8	9	10	11
A1	4	5	6	7	8	9	10	11	12	13	14
A2	6	7	8	9	10	11	12	13	14	15	16
A3	4	5	A	6	7	A	A	8	9	10	11
A4	6	7	8	9	10	11	12	A	13	14	15
A5	5	6	A	7	8	9	10	11	12	13	14
A6	7	8	A	9	10	11	12	13	14	15	16
A7	4	5	A	A	A	6	7	8	9	10	11
A8	3	4	A	5	6	7	8	9	10	11	12
A9	2	3	A	4	5	A	A	12	13	14	15
B0	2	3	A	4	5	6	7	8	9	10	11
B1	5	6	7	8	9	10	11	12	A	A	13
B2	6	7	8	9	10	11	12	13	A	A	14
B3	9	10	11	12	13	14	15	16	17	18	19
B4	7	8	A	9	10	11	12	13	14	15	16
B5	7	8	9	10	11	12	13	A	14	15	16
B6	3	4	5	6	7	8	9	10	A	A	A
B7	6	7	8	9	10	11	12	13	14	15	16
B9	6	7	8	9	10	11	12	13	14	15	16
C0	4	5	6	7	8	9	10	11	12	13	14
C1	7	8	9	10	11	12	13	14	15	16	17
C2	8	9	10	11	12	13	14	15	16	17	18
C3	6	7	8	9	10	11	12	13	14	15	16
C4	6	7	8	9	10	11	12	13	14	15	16
C5	4	5	6	7	8	9	10	11	12	13	14
C6	5	6	7	8	9	10	11	12	13	14	15

R.G.M. COLLEGE OF ENGINEERING ATTENDANCE

Class : B.Tech
Branch : ECE-B

Roll No.	Name	Date	
		16/03/23	17/03/23
496	R.B.N.R.G. Mahiswari	A	A
497	G. Manasa	A	A
498	M. Manasa	A	A
499	M. Mani Kumar Naik	A	A
4A0	V. Mani kanta	A	A
4A1	P. Manisha	A	A
4A2	G. Manjula	A	A
4A3	B. Manoj Kumar Reddy	A	A
4A4	M. Manoj Kumar	A	A
4A5	K. Manoj	A	A
4A6	V. Maria Dhathri	A	A
4A7	V. Maruthi	A	A
4A8	M. Meenakshi	A	A
4A9	A. Meghana	A	A
4B0	C.T. Mithuntela	A	A
4B1	S. Mohamad Abbas	A	A
4B2	S. Mohammad Sirfan	A	A
4B3	S. Mohammad Arif	A	A
4B4	P. Mounika	A	A
4B5	M. Mythili	A	A
4B6	B. Naga Sujanya	A	A
4B7	B. Naga Udayeswar Reddy	A	A
4B9	B. Nagaraju	A	A
4C0	R.G. Nagesh	A	A
4C1	B. Naveen	A	A
4C2	R. Naveen	A	A
4C3	D. Nisheth	A	A
4C4	P. Nishitha	A	A
4C5	R. Pavan Kumar Reddy	A	A
4C6	S. Pavan Kumar Reddy	A	A

Signature of Teacher: _____
Signature of H.O.D.: _____
Signature of Principal: _____

Roll No.	24	25	26	27	28	29	30	31	32	33	34
96	16	17	18	19	20	21	22	A	23	24	25
97	16	17	18	19	A	20	A	A	A	A	21
98	17	18	19	20	21	22	A	A	A	A	A
99	A	14	15	16	17	18	19	A	20	21	22
A0	A	12	13	14	15	16	17	18	19	20	21
A1	15	16	17	18	A	19	A	A	A	20	21
A2	17	18	19	20	21	22	A	A	23	24	25
A3	12	13	14	15	16	A	17	18	19	20	21
A4	A	17	A	A	18	A	19	A	20	21	A
A5	15	16	17	18	19	A	20	A	A	21	22
A6	17	A	18	19	20	A	A	22	23	24	25
A7	13	14	15	16	17	18	19	A	A	20	21
A8	13	14	15	16	A	17	A	A	A	18	19
A9	16	17	18	19	20	21	A	22	23	24	25
B0	12	13	14	15	16	17	18	A	19	20	21
B1	A	14	A	A	A	A	A	A	A	15	16
B2	15	16	17	18	19	A	20	A	21	A	22
B3	20	21	22	23	24	25	26	27	28	29	30
B4	17	A	A	A	18	19	20	21	22	A	23
B5	A	17	A	A	A	18	19	20	21	22	23
B6	A	A	A	A	A	11	12	A	13	14	15
B7	17	18	A	A	A	A	A	A	19	20	21
B9	17	18	19	20	21	A	22	A	A	23	24
C0	15	16	17	18	19	20	21	A	22	23	24
C1	18	19	20	21	22	23	A	24	25	26	27
C2	19	A	20	21	22	A	23	24	25	A	26
C3	17	18	19	20	21	A	22	A	23	24	25
C4	A	17	18	19	20	21	22	23	24	25	26
C5	A	16	17	18	19	20	21	A	A	A	22
C6	16	17	18	19	20	21	22	A	A	A	23

& TECHNOLOGY (Autonomous) REGISTER

Academic Year from _____ to _____

Roll No.	35	36	37	38	39	40	41	42	43	44	45
96	26	27	28	29	30	31	32	33	34	35	36
97	22	23	24	25	26	27	28	29	30	31	32
98	A	A	A	A	A	A	A	A	A	A	23
99	23	24	25	26	27	28	29	30	31	32	33
A0	22	23	24	25	26	27	28	29	30	31	32
A1	22	23	24	25	26	27	28	29	30	31	32
A2	26	27	28	29	30	31	32	33	34	35	36
A3	22	23	A	24	25	26	27	28	29	30	31
A4	A	22	23	A	24	25	26	27	28	29	30
A5	23	24	25	26	27	28	29	30	31	32	33
A6	26	27	28	29	30	A	A	31	32	33	34
A7	22	23	24	25	26	27	28	29	30	31	32
A8	20	21	22	23	24	25	26	27	28	29	30
A9	26	27	28	29	30	31	32	33	34	35	36
B0	22	23	24	A	25	26	27	28	29	30	31
B1	17	18	19	20	21	22	23	24	25	26	27
B2	23	24	25	A	26	27	28	29	A	30	31
B3	31	32	33	34	35	36	37	38	39	40	41
B4	A	24	25	26	27	28	29	30	31	32	33
B5	24	25	26	27	28	29	30	31	A	32	33
B6	16	17	18	19	20	21	22	23	24	25	26
B7	22	23	24	25	26	27	28	29	30	31	32
B9	25	26	27	28	29	30	31	32	A	33	34
C0	25	26	27	28	29	30	31	32	33	34	35
C1	28	29	30	31	32	33	34	35	36	37	38
C2	27	A	28	29	30	31	32	33	34	35	36
C3	26	27	28	29	30	31	32	33	34	35	36
C4	27	28	A	29	30	31	32	33	34	35	36
C5	23	24	25	26	27	28	29	30	31	32	33
C6	24	25	26	27	28	29	30	31	32	33	34

R.G.M. COLLEGE OF ENGINEERING ATTENDANCE

Class : B.Tech

Branch : ECE-B

Roll No.	Name	Date	
		16/03/23	17/03/23
496	R.B.N.R.G. Mahiswari	A	A
497	G. Manasa	A	A
498	M. Manasa	A	A
499	M. Mani Kumar Naik	A	A
4A0	V. Mani Kanta	A	A
4A1	P. Manisha	A	A
4A2	G. Manjula	A	A
4A3	B. Manoj Kumar Reddy	A	A
4A4	M. Manoj Kumar	A	A
4A5	K. Manoj	A	A
4A6	V. Maria Dhathri	A	A
4A7	V. Maruthi	A	A
4A8	M. Meenakshi	A	A
4A9	A. Meghana	A	A
4B0	C.T. Mithunteja	A	A
4B1	S. Mohamād Abbas	A	A
4B2	S. Mohammad Srfan	A	A
4B3	S. Mohammad Arif	A	A
4B4	P. Maunika	A	A
4B5	M. Mythili	A	A
4B6	B. Naga Sujanya	A	A
4B7	B. Naga Udayeswar Reddy	A	A
4B9	B. Nagaraju	A	A
4C0	R.G. Nagesh	A	A
4C1	B. Naveen	A	A
4C2	R. Naveen	A	A
4C3	D. Nisheth	A	A
4C4	P. Nishitha	A	A
4C5	R. Pavan Kumar Reddy	A	A
4C6	S. Pavan Kumar Reddy	A	A

Signature of Teacher _____
 Signature of II.O.D. _____
 Signature of Principal _____

Roll No.	16/03/23	17/03/23	18/03/23	19/03/23	20/03/23	21/03/23	22/03/23	23/03/23	24/03/23	25/03/23	26/03/23	27/03/23	28/03/23	29/03/23	30/03/23	31/03/23	01/04/23	02/04/23	03/04/23	04/04/23	05/04/23	06/04/23	07/04/23	08/04/23	09/04/23	10/04/23	11/04/23	12/04/23	13/04/23	14/04/23	15/04/23		
96	32	38	39	40	41	42	A	A																									
97	33	34	35	36	37	38	A	A																									
98	25	26	27	28	29	30	31	32																									
99	34	35	36	37	38	39	40	A																									
100	33	34	35	36	37	38	39	A																									
A1	33	34	35	36	37	38	A	A																									
A2	37	38	39	40	41	42	43	44																									
A3	32	33	34	35	36	37	38	A																									
A4	31	32	33	34	35	36	37	38																									
A5	34	35	36	37	38	39	40	41																									
A6	35	A	36	37	38	39	40	A																									
A7	A	A	33	34	35	36	37	38																									
A8	31	32	33	34	35	36	A	37																									
A9	37	38	39	40	41	42	43	A																									
B0	32	33	34	35	36	37	38	39																									
B1	28	29	30	31	32	33	34	35																									
B2	32	A	33	34	35	36	37	38																									
B3	42	43	44	45	46	47	48	A																									
B4	34	A	35	36	37	38	39	40																									
B5	34	A	35	36	37	38	A	39																									
B6	27	28	29	30	31	32	33	34																									
B7	33	34	35	36	37	38	39	40																									
B9	35	A	36	37	38	39	40	41																									
C0	A	36	37	38	39	40	41	A																									
C1	39	40	41	42	43	44	A	A																									
C2	37	38	39	40	41	42	43	A																									
C3	37	38	39	40	41	42	43	44																									
C4	37	38	39	40	41	42	43	44																									
C5	34	35	36	37	38	39	40	A																									
C6	35	36	37	38	39	40	41	A																									

R.G.M. COLLEGE OF ENGINEERING ATTENDANCE

Class : B.Tech
Branch : ECE-B

Roll No.	Name	Date	
		16/03/23	1
2109110 407	C. Pavan Kumar	A	
22091510 407	K. Deveswar Reddy	A	
408	S. Dharma Teja	A	
409	K. Elizabeth Rani	A	
411	S. Gangotri	A	
413	K. Hanika	A	
415	Z. Hemant Kumar	A	
417	J. Jayavardan	1	
422	P. Mani Teja	A	
428	P. Rameeja	A	
429	S. Ruksana	A	
435	K. Sreenivas	A	
436	N. Varun Kumar	A	
Signature of Teacher		[Signature]	
Signature of I.O.D.			
Signature of Principal			

& TECHNOLOGY (Autonomous) REGISTER

Academic Year from.....

Roll No.	06/05/23	08/05/23	10/05/23	10/05/23	11/05/23	12/05/23	23/05/23	08/06/23	09/06/23	12/06/23	13/06/23
24	25	26	27	28	29	30	31	32	33	34	
25	18	19	20	21	22	23	A	A	A	24	A
27	15	16	17	18	19	20	21	A	22	23	24
28	16	17	18	19	20	A	A	A	A	A	21
29	19	13	14	15	16	A	17	A	18	19	20
31	17	18	19	20	21	A	22	23	24	25	26
32	16	17	18	19	20	21	22	A	23	24	25
33	A	18	19	20	21	22	23	A	24	25	A
34	23	24	A	A	A	A	A	25	26	27	A
35	13	14	15	16	17	A	18	A	19	20	21
36	A	A	A	A	A	A	A	A	A	A	A
37	A	16	17	18	19	A	20	A	21	22	23
38	A	17	18	19	20	A	21	A	A	22	23
39	A	16	17	18	19	20	A	21	22	23	24
<div style="display: flex; justify-content: space-around;"> [Signature] [Signature] [Signature] [Signature] [Signature] [Signature] [Signature] [Signature] [Signature] [Signature] [Signature] [Signature] </div>											

Roll No.	14/06/23	15/06/23	16/06/23	17/06/23	20/06/23	21/06/23	21/06/23	22/06/23	23/06/23	24/06/23	25/06/23
35	36	37	38	39	40	41	42	43	44	45	
35	25	26	A	27	28	29	30	31	32	33	34
36	25	26	27	28	29	30	31	32	33	34	35
37	22	23	24	25	26	27	28	29	30	31	32
38	21	22	23	24	25	26	27	28	29	30	31
39	27	28	29	30	31	32	33	34	35	A	A
40	26	27	28	29	30	31	32	33	34	35	36
41	26	27	28	A	29	30	31	32	33	34	35
42	A	28	29	30	31	32	33	34	35	36	37
43	22	23	24	25	26	27	28	29	30	31	32
44	A	A	A	A	A	A	A	A	A	A	A
45	24	25	26	27	28	29	30	31	32	33	34
46	24	25	26	A	27	28	29	30	31	32	33
47	25	26	27	A	28	29	30	31	32	33	34
<div style="display: flex; justify-content: space-around;"> [Signature] [Signature] [Signature] [Signature] [Signature] [Signature] [Signature] [Signature] [Signature] [Signature] [Signature] [Signature] </div>											

& TECHNOLOGY (Autonomous), NANDYAL.

REGISTER

Academic Year from 2022-23 to Teacher YMSR

Subject & Credits ECA & D Dept FCE

INTERNAL / RECORD MARKS

Roll No.	Assignments			Internal Test		Internal Marks			Final Internal (I+A)	Remarks
	1	2	Average (A)	1	2	75% of MAX	25% of MIN	Total (I)		
65	10	10	10	07	16	12	1.75	13.75	24	
66	10	10	10	06	13	9.75	1.5	11.25	22	
67	10	10	10	07	12	9	1.75	10.75	21	
68	10	10	10	03	05	3.75	0.75	4.5	15	
69	10	10	10	13	12	9.75	3	12.75	23	
70	10	10	10	13	19	14.25	3.25	17.5	28	
71	10	10	10	10	11	8.25	2.5	10.75	21	
72	10	10	10	07	10	7.5	1.75	9.25	20	
73	10	10	10	14	19	14.25	3.5	17.75	28	
74	10	10	10	05	07	5.25	1.25	6.5	17	
75	10	10	10	13	19	14.25	3.25	17.5	28	
76	10	10	10	10	07	7.5	1.75	9.25	20	
77	10	10	10	09	10	7.5	2.25	9.75	20	
78	10	10	10	05	10	7.5	1.25	8.75	19	
79	10	10	10	08	09	6.75	2	8.75	19	
80	9	8	9	01	07	5.25	0.25	5.5	15	
81	10	10	10	13	16	12	3.25	15.25	26	
82	10	10	10	13	19	14.25	3.25	17.5	28	
83	10	10	10	09	10	7.5	2.25	9.75	20	
84	10	10	10	03	09	6.75	0.75	7.5	18	
85	10	10	10	09	11	8.25	2.25	10.5	21	
86	10	10	10	14	18	13.5	3.5	17	27	
87	10	10	10	11	16	12	2.75	14.75	25	
88	10	10	10	11	16	12	2.75	14.75	25	
89	10	10	10	03	11	8.25	0.75	9	19	
90	10	08	9	09	14	10.5	2.25	12.75	22	
91	10	10	10	10	17	14.75	2.5	17.25	26	
93	10	10	10	13	19	14.25	3.25	17.5	28	
94	10	10	10	15	12	11.25	3.25	14.5	25	
95	10	10	10	09	18	13.5	2.25	15.75	26	

LECTURE RECORD

Subject	: ECA 2D	Total Exams.....	2
Credits	: 03	Each for.....	2 hrs.
Internal Mid Exam Marks	: 02	Total quizzes	-
Internal Quiz Marks	: -	No. of Assignment.....	2

S.No.	Date	Topic Covered / Exercise Completed	Remarks
1	18/03/23	No class due to less strength	1
2	16/03/23	No class due to less strength	2
3	17/03/23	No class due to less strength	3
4	18/03/23	Introduction to electronic circuits	4
5	21/03/23	Introduction to diode, transistors	5
6	23/03/23	Review of EDC	6
7	24/03/23	Introduction to ECA 2D	7
8	25/03/23	IEEE Seminar on usage of IEEE membership	8
9	03/04/23	Basic CE and CC with the amplifier	9
10	04/04/23	Analysis of DC and AC load line	10
11	06/04/23	Introduction to h-parameters	11
12	11/04/23	Definitions & typical values of h-parameters	12
13	25/04/23	Analysis of general transistor amplifier	13
14	27/04/23	Analysis of CE amplifier using exact model	14
15	28/04/23	Analysis of CB amplifier using exact model	15
16	02/05/23	Problems on CE & CC	16
17	02/05/23	Simplified model of CE	17
18	03/05/23	CE amplifier with R _e resistor	18
19	05/05/23	Problems on CE, CC, CB.	19
20	04/05/23	Analysis of CS amplifier	20
21	05/05/23	Analysis of CO amplifier	21
22	09/05/23	Analysis of CG amplifier	22
23	05/05/23	Introduction to multistage amplifier & classification.	23 - Unit - II
24	06/05/23	RC coupled, transformer coupled, Direct coupled amplifier	24
25	09/05/23	Analysis of CE-CE, CE-CC amplifiers	25
26	10/05/23	Analysis of CE-CB, CC-CC Amplifier	26
27	10/05/23	Introduction to differential amplifier - classification	27
28	11/05/23	Modes of MOSFET differential amp.	28
29	12/05/23	Modes of BJT differential amp.	29
30	23/05/23	Introduction to feedback Amplifier	30 Unit - IV
31	08/06/23	Classification & Block diagram	31
32	09/06/23	Characteristics of -ve fb on gain & stability	32
33	12/06/23	Noise, Distortion & B.C.B	33
34	13/06/23	Change in i/p & o/p impedances	34
35	14/06/23	Problems.	35

K. Mallikarjun
13/4/23

LECTURE RECORD

S.No.	Date	Topic Covered / Exercise Completed	Remarks
36	15/06/23	Analysis of voltage series fb amp.	36
37	16/06/23	Analysis of current series fb amp.	37
38	17/06/23	Analysis of voltage shunt fb amp.	38
39	20/06/23	Analysis of current shunt fb amp.	39
40	21/06/23	Introduction to oscillators & classification	40 Unit - VI
41	21/06/23	RC phase shift oscillator	41
42	22/06/23	Wien bridge oscillator	42
43	23/06/23	Problems on above two oscillators	43
44	27/06/23	LC oscillators - Hartley	44
45	27/06/23	Colpitts oscillator	45
46	28/06/23	Crystal oscillator	46
47	30/06/23	Frequency & Amplitude stability	47
48	01/07/23	Tuned amplifier	48
49	04/07/23	Introduction to power amplifier & classification	49 Unit - VII
50	05/07/23	Class A power Amplifier - direct fed & transformer coupled	50
51	06/07/23	Class B PA - Pushpull & complementary & symmetry	51
52	07/07/23	Class AB power amplifier	52

X Roll No
26/6/23

 X Roll No
21/7/23

Assignment - I

Name :- M. Shanni

Regd no :- 21091A00413

Year :- II / II Sem


Subject :- Eca&id

Branch :- ECE


10

2

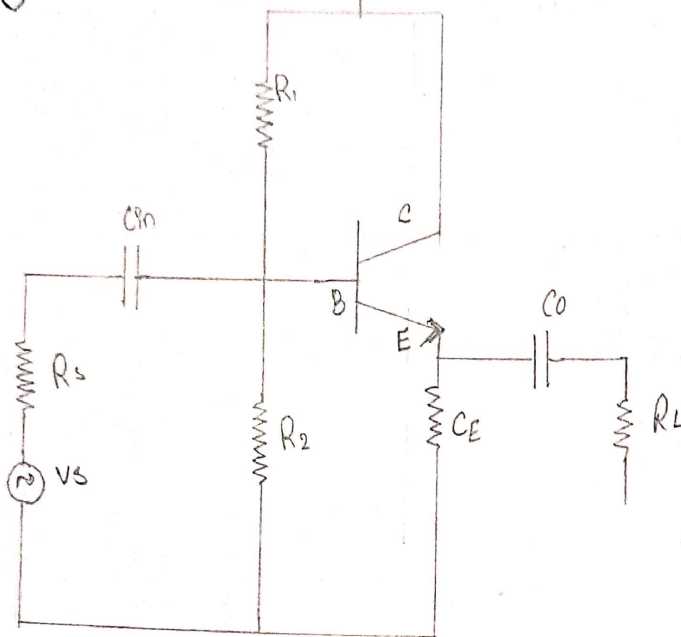1) Analysis of cc amplifier in Exact Model.





AC Equivalent circuit :-

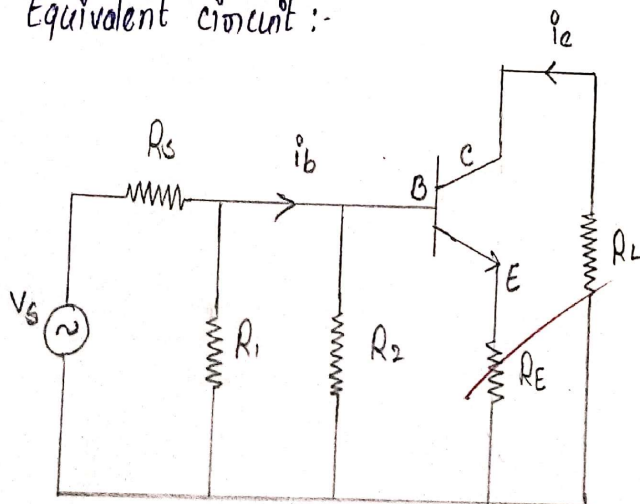

- * Reduce all dc sources are connected to ground
- * All capacitors are short circuited

Hybrid Model :-

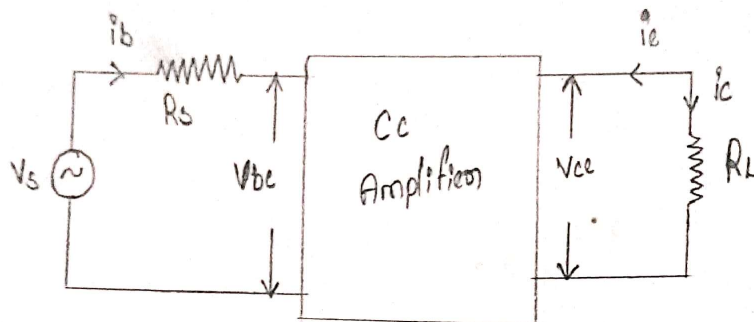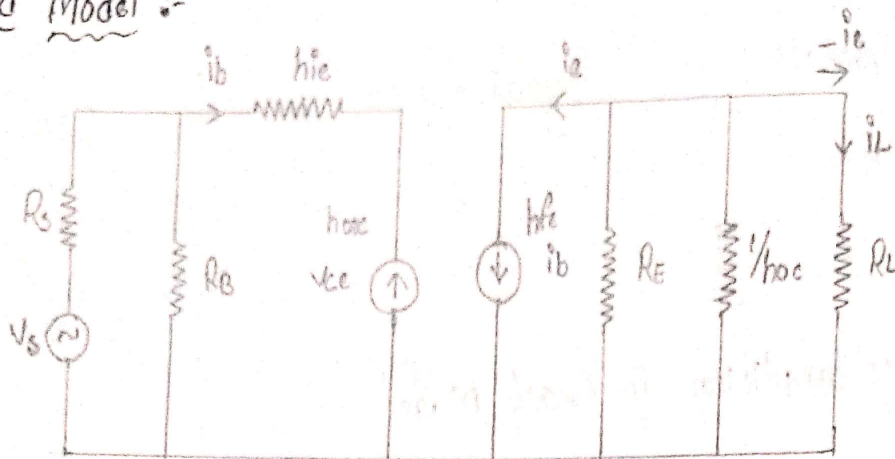

$$V_1 = h_{11} i_1 + h_{12} V_2$$

$$i_2 = h_{21} i_1 + h_{22} V_2$$

$$V_{be} = h_{ie} i_b + h_{oe} V_{ce} \rightarrow (1)$$

$$i_e = h_{fe} i_b + h_{oe} V_{ce} \rightarrow (2)$$

$$i_L \text{ (or) } i_2 = -\frac{V_{ce}}{R_L} \rightarrow (3)$$

Input impedance :-

$$Z_{in} = \frac{V_{be}}{i_b} \rightarrow (4)$$

Sub eqn (3) in eqn (4)

$$Z_{in} = \frac{h_{ie} i_b + h_{oe} V_{ce}}{i_b}$$

$$Z_{in} = h_{ie} + \frac{h_{oe} V_{ce}}{i_b} \rightarrow (5)$$

From eqn (2) and eqn (3)

$$\frac{-V_{ce}}{R_L} = h_{fe} i_b + h_{oe} V_{ce}$$

$$h_{fe} i_b = \frac{-V_{ce}}{R_L} - h_{oe} V_{ce}$$

$$h_{fe} i_b = -V_{ce} \left(\frac{1}{R_L} + h_{oe} \right)$$

$$\frac{V_{ce}}{i_b} = \frac{-h_{fe}}{\frac{1}{R_L} + h_{oe}} \rightarrow (6)$$

eqn (6) in eqn (5)

$$Z_{in} = h_{ie} + h_{oe} \left(\frac{-h_{fe}}{\frac{1}{R_L} + h_{oe}} \right)$$

$$Z_{in} = h_{ie} - \frac{h_{fe} h_{oe}}{\frac{1}{R_L} + h_{oe}}$$

Current gain :-

$$A_I = i_e / i_b$$

From eqn (3) $i_e = \frac{-V_{ce}}{R_L}$

$$V_{ce} = -i_e R_L$$

eqn (2) $i_e = h_{fe} i_b + h_{oe} V_{ce}$

$$i_e = h_{fe} i_b + h_{oe} (-i_e R_L)$$

$$i_e = h_{fe} i_b - h_{oe} i_e R_L$$

$$h_{fe} i_b = i_e (1 + h_{oe} R_L)$$

$$\frac{i_e}{i_b} = \frac{-h_{fe}}{1 + h_{oe} R_L}$$

$$A_I = \frac{-h_{fe}}{1 + h_{oe} R_L}$$

Voltage gain :-

$$A_V = \frac{V_{ce}}{V_{be}}$$

From eqn (4) $Z_{in} = \frac{V_{be}}{i_b}$

$$V_{be} = Z_{in} i_b$$

$$A_V = \frac{V_{ce}}{Z_{in} i_b}$$

$$A_V = \frac{-h_{fe}}{1/R_L + h_{oe}} \times \frac{1}{Z_{in}}$$

Output Impedance :

$$Z_o = \frac{V_{ce}}{i_e}$$

From eqn (2)

$$i_e = h_{fe} i_b + h_{oe} V_{ce}$$

divide by V_{ce}

$$\frac{i_e}{V_{ce}} = \frac{h_{fe} i_b + h_{oe} V_{ce}}{V_{ce}}$$

$$\frac{i_e}{V_{ce}} = \frac{h_{fe} i_b}{V_{ce}} + h_{oe} \rightarrow (7)$$

From eqn (1)

$$V_{bc} = h_{ie} i_b + h_{oe} V_{ce}$$

$$V_{bc} = 0$$

$$h_{ie} i_b = -h_{oe} V_{ce}$$

$$\frac{i_b}{V_{ce}} = \frac{-h_{oe}}{h_{ie}} \rightarrow (8)$$

From (7) and (8)

$$\frac{i_e}{V_{ce}} = h_{fe} \left(\frac{-h_{oe}}{h_{ie}} \right) + h_{oe}$$

$$\frac{i_e}{V_{ce}} = \frac{-h_{fe} h_{oe} + h_{oe} h_{ie}}{h_{ie}}$$

$$Z_o = \frac{h_{ie}}{h_{oe} h_{ie} - h_{fe} h_{oe}}$$

Input effective impedance $Z_{in}' = R_B \parallel Z_{in}$

Effective output impedance $Z_o' = R_E \parallel R_L \parallel Z_o$

Input impedance with source $Z_{is} = R_s + Z_i$

A_{is} = current gain including source

$$A_{is} = A_z \times \frac{R_s'}{R_s' + Z_i}$$

A_{vs} = voltage gain including source


$$A_{vs} = A_v \times \frac{R_i'}{R_i' + R_s} \quad [R_i' = Z_i']$$

Z_o'' = output impedance with load


$$Z_o'' = Z_o' \parallel R_L$$

2) Analysis of FET CS Amplifier

circuit Diagram of CS amplifier :-

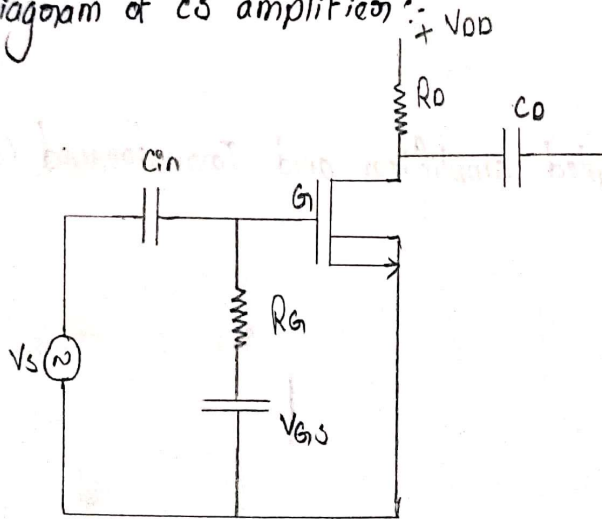

Hybrid Model

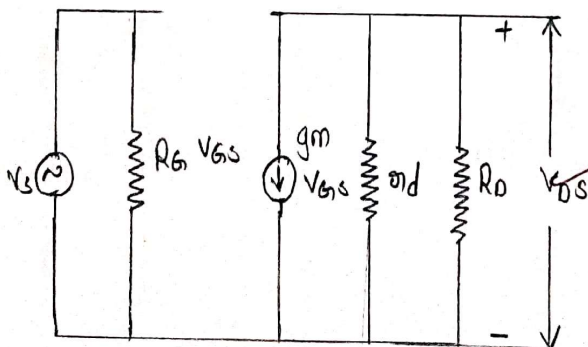

Current gain :-

$$\frac{i_d}{i_g} = i_d / 0 = \infty$$

Input impedance :-

$$i_g = 0$$

$$Z_i = \frac{V_{GS}}{i_g} = \infty$$

Effective input impedance

$$Z_i' = Z_i \parallel R_g$$

$$= \infty \parallel R_g$$

$$Z_i' = R_g$$

Output impedance :

$$Z_o = \frac{V_{os}}{i_d} \Big|_{V_{GS}=0, R_d = \text{disconnected}}$$

$$Z_o = r_{od}$$

Voltage gain :

$$A_v = \frac{V_{os}}{V_{GS}}$$

$$A_v = -g_m (r_{od} \parallel R_D)$$

$$V_{os} = -g_m V_{GS} (r_{od} \parallel R_D)$$


$$A_v = -g_m (r_{od} \parallel R_D)$$

$$g_m = i_d / V_{GS}$$


$g_m = \text{Transconductance}$

Effective output impedance :-

$$Z_o' = Z_o \parallel R_D$$

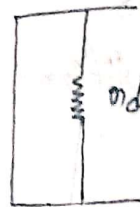

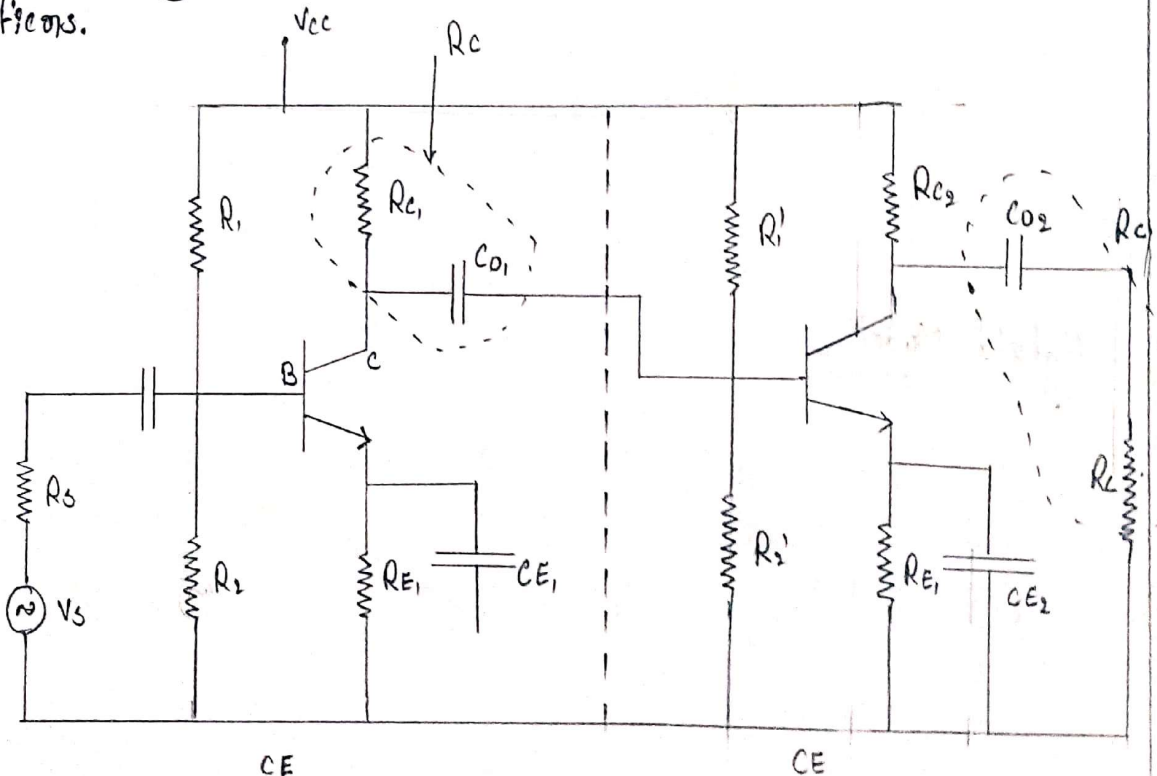3) Explain Two stage R.c coupled amplification and Transformer Coupled Amplifiers.



* This is the most popular type of Coupling because of amplification and this is cheap and provide excellent amplification.

* In the above fig we consider CE-CE amplification 1st stage is CE and

2nd stage is also CE amplifier is called cascading.

- * Coupling capacitor is used to transfer output signal from one stage to next stage.
- * output is taken from coupling capacitor, this o/p is given to next CE amplifier as input.

Disadvantages


- * It has low voltage and power gain

Advantages :-

- * Easy to construct
- * less cost

Applications:- used in voltage amplification

Hybrid Model :-

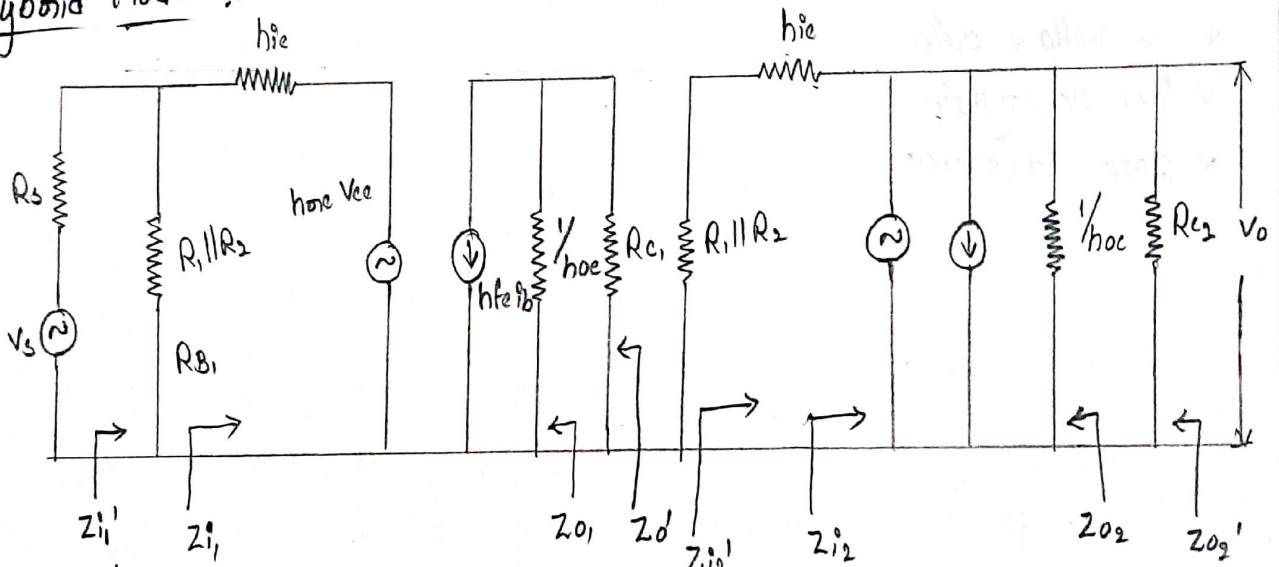

If condition $h_{oe} R_L' \leq 0.1$ satisfies below formulas

- 1) $A I_2 = -h_{fe} = A I_1$
- 2) $Z_{in2} = h_{ie} = Z_{in1}$
- 3) $Z_{i2}' = Z_{i2} || R_E = Z_{i1}'$
- 4) $A V_2 = \frac{-h_{fe} R_L'}{Z_{i2}} = A V_1$

If condition does not satisfies we use below formulas

- 1) $Z_{i1} = h_{ie} - \frac{h_{fe} h_{oe}}{1/R_L + h_{oe}} = Z_{i2}$
- 2) $A I_1 = \frac{-h_{fe}}{1 + h_{oe} R_L'} = A I_2$
- 3) $A V_1 = \frac{-h_{fe}}{1/R_L + h_{oe}} \times \frac{1}{Z_{i1}} = A V_2$
- 4) $Z_{o1} = \frac{h_{ie}}{h_{oe} h_{ie} - h_{fe} h_{oe}} = Z_{o2}$

5) $Z_{O1} = \infty = Z_{O2}$

6) $Z_{O1}' = Z_{O1} \parallel R_C = Z_{O2}'$

6) $Z_{O2}' = Z_{O2} \parallel R_C = Z_{O1}'$

overall:

$A_I = A_{I1} * A_{I2}$

$A_V = A_{V1} * A_{V2}$

$Z_I = Z_{i1}'$


$Z_{O2} = Z_{O2}'$

Transformer Coupled Amplifier

The drawback of RC coupled amplifier is overcome by using Transformer coupled Amplifier.

⇒ Drawbacks of RC Coupled Amplifier

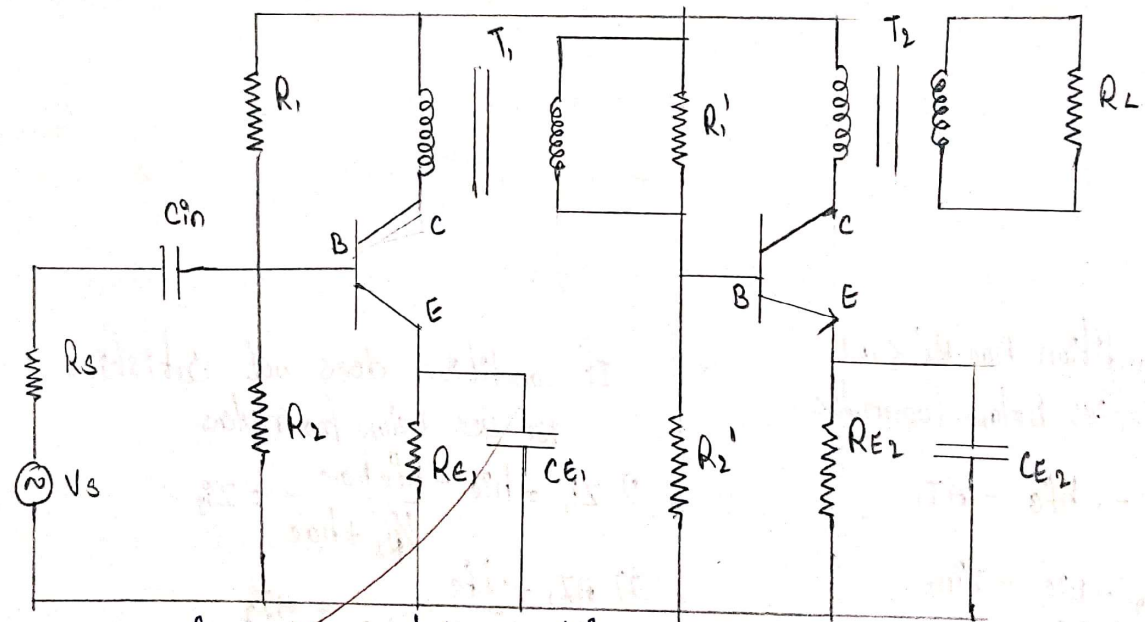- * low voltage gain
- * low power gain
- * poor impedance



* In Transformer Coupled amplifier when the collector resistor R_C is replaced by Transformer operation:-

* When AC signal is applied to the base of 1st Transformer it

appears amplified form across the primary of the coupling transformer.

* The amplified signal is transformed to input to the next stage by secondary transformer.

* In 2nd stage it is further amplified and appears across primary of 2nd transformer.

* From secondary transformer the output is transformed.

* In this Amplifier frequency response is poor because transformer losses and gain is also unstable.

Advantages:-

* High Voltage gain and high power gain

* It has good impedance match

* No signal losses in collector or base resistor

Disadvantages:-

* poor frequency response

* Because of that RC coupled resistor transformer is expensive and bulky.

Applications:-

* used in impedance matching.

* It is used in Radio and TV receivers to amplify RF signal.

4) Explain differential modes in Mos Differential Amplifier.

There are four modes in Mos differential Amplifier.

1. common i/p mode

2. differential i/p mode

3. large signal i/p mode

4. small signal i/p mode

1. Common i/p mode :-

When same i/p voltage is applied to two transistors Q_1, Q_2 the differ.

ential amplifier is operates in common mode
 ⇒ when the two transistors operate in saturation region the total current Equally distribute into $I_{D1} = I_{D2} = I/2$

$$I = I_{D1} + I_{D2}$$

$$V_S = V_{cm} - V_{GS}$$

$$I_{D1} = I/2 = \frac{kn'}{2} \frac{W}{L} (V_{GS} - V_T)^2$$

WRT drain current Equation of MOSFET

$$V_{GS} - V_T = V_{OV}$$

V_{OV} = overdrive voltage

$$I_{D1} = I = \frac{kn'W}{L} (V_{OV})^2$$

$$V_{OV} = \sqrt{\frac{I}{\frac{kn'W}{L}}} \quad \begin{matrix} V_S = V_T \\ V_S = -V_T \end{matrix}$$

From Drain side

$$V_{D1} = V_{DD} - I/2 R_{D1} \quad V_{D1} = V_{D2}$$

$$V_{D2} = V_{DD} - I/2 R_{D2} \quad V_D = 0 \text{ voltage}$$

⇒ Because of some voltage output 'becomes 0'

⇒ common mode voltage range $V_{cm}(max) = V_D + V_T$

$$V_{cm}(min) = -V_{SS} + V_{CS} + V_{GS}$$

$$V_{cm}(min) \leq V_{cm} \leq V_{cm}(max)$$


2) Differential i/p mode

⇒ In differential i/p mode the i/p voltage applied to Q_1 transistor and Q_2 transistor is connected to ground

$$I = I_{D1} + I_{D2}$$

$$I = I_{D1} + I_{D2} = 0$$
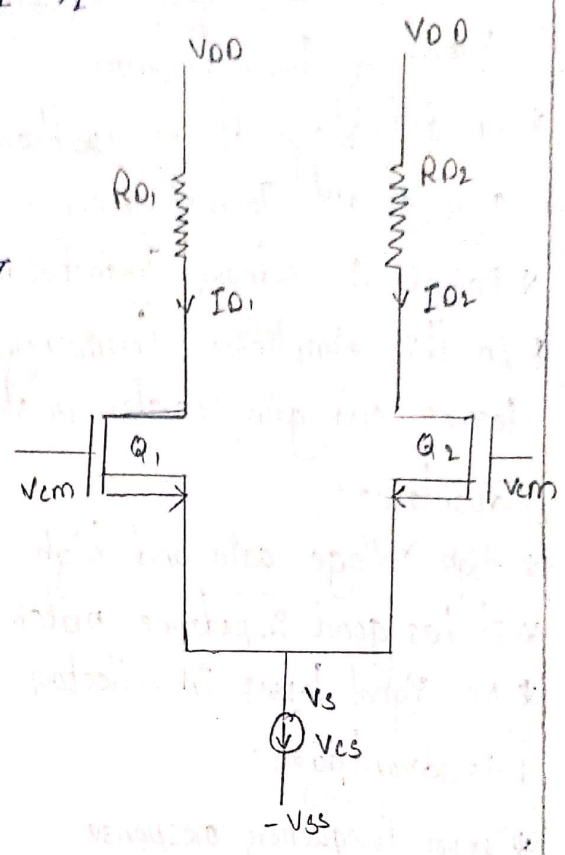
$$V_{OV} = \sqrt{\frac{2I}{\frac{kn'W}{L}}}$$



If v_{id} is +ve $I_{D1} > I_{D2}$ then

$$V_o = V_{GS2} - V_{GS1} \text{ is +ve}$$

⇒ If v_{id} is -ve then $V_{GS1} < V_{GS2}$ (or) $V_{GS2} > V_{GS1}$

$$I_{D1} = I = \frac{kn'k}{2L} [V_{GS1} - V_t]^2$$

By solving this

$$V_{GS1} = V_t + \sqrt{\frac{2I}{kn'k/L}}$$

$$\frac{I}{kn'k/L} = V_{ov} \text{ when } I_{D1} = I/2$$

$$V_{GS1} = V_t + \sqrt{2} V_{ov}$$

$$v_{id} = V_{GS1} - V_t$$

$$= \sqrt{2} V_{ov} - V_t$$

$$\boxed{v_{id} = \sqrt{2} V_{ov}}$$

if $v_{id} = -ve$ so it is from $-\sqrt{2} V_{ov} \leq v_{id} \leq \sqrt{2} V_{ov}$

$$v_{id} = -\sqrt{2} V_{ov}$$

3) Differential Amplifier in large small signal i/p mode:-

In large signal mode the current equations are derived in terms of V_{GS1} and V_{GS2} in terms of V_{GS1} and V_{GS2} or in terms of V_{ov}



$$I_{D1} = \frac{I}{2} = \frac{kn'k}{2L} (V_{GS1} - V_t)^2 \rightarrow (1)$$

$$I_{D2} = \frac{I}{2} = \frac{kn'k}{2L} (V_{GS2} - V_t)^2 \rightarrow (2)$$

Apply square roots on both sides for two equations

$$\sqrt{I_{D1}} = \sqrt{\frac{kn'k}{L}} (V_{GS1} - V_t) \rightarrow (3)$$
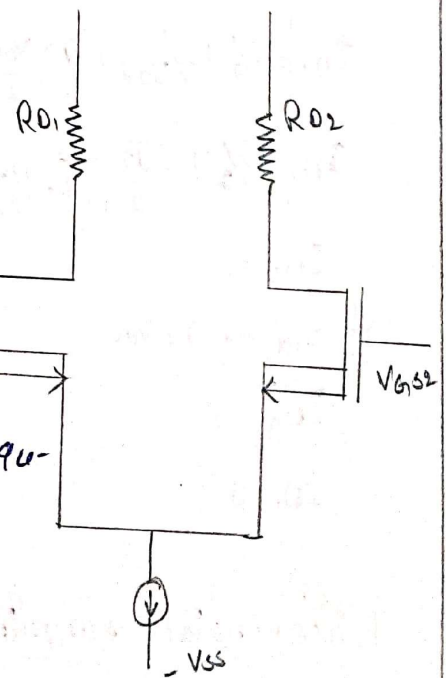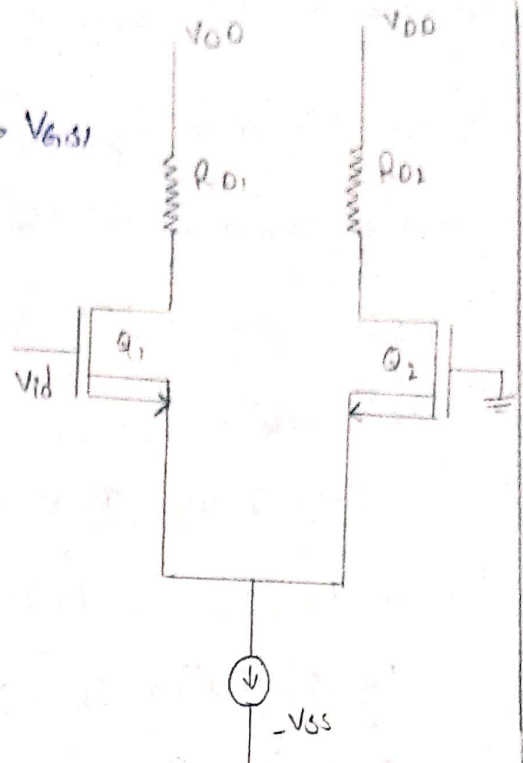
$$\sqrt{I_{D2}} = \sqrt{\frac{kn'k}{L}} (V_{GS2} - V_t) \rightarrow (4)$$



$$\sqrt{I_{D1}} - \sqrt{I_{D2}} = \sqrt{\frac{kn'w}{L}} (V_{GS1} - V_t) - \sqrt{\frac{kn'w}{L}} (V_{GS2} - V_t)$$

$$= \sqrt{\frac{kn'w}{L}} (V_{GS1} - V_{GS2}) \rightarrow (5)$$

Apply square on both sides

$$(\sqrt{I_{D1}} - \sqrt{I_{D2}})^2 = \frac{kn'w}{L} (V_{GS1} - V_{GS2})^2$$

$$\sqrt{I_{D1}}^2 + \sqrt{I_{D2}}^2 - 2\sqrt{I_{D1}I_{D2}} = \frac{kn'w}{L} v_{id}^2$$

$$I - 2\sqrt{I_{D1}I_{D2}} = \frac{kn'w}{L} v_{id}^2 \rightarrow (6)$$

$$\text{By } 2\sqrt{I_{D1}I_{D2}} = I - \frac{kn'w}{L} v_{id}^2 \rightarrow (6)$$

By substituting $I_{D2} = I - I_{D1}$

$$2\sqrt{I_{D1}(I - I_{D1})} = I - \frac{kn'w}{L} v_{id}^2$$

By simplifying this we get

$$I_{D1} = \frac{I}{2} + \frac{I}{V_{OV}} \left(\frac{v_{id}}{2}\right) \sqrt{1 - \left(\frac{v_{id}/2}{V_{OV}}\right)^2}$$

$$I_{D2} = \frac{I}{2} - \frac{I}{V_{OV}} \left(\frac{v_{id}}{2}\right) \sqrt{1 - \left(\frac{v_{id}/2}{V_{OV}}\right)^2}$$

$$\text{If } v_{id} = \sqrt{2} V_{OV}$$

$$I_{D1} = \frac{I}{2} + \frac{I}{V_{OV}} \left(\frac{\sqrt{2} V_{OV}}{2}\right) \sqrt{1 - \frac{\sqrt{2} V_{OV}/2}{V_{OV}}^2}$$


$$I_{D1} = \frac{I}{2} + \frac{I\sqrt{2}}{2} \sqrt{(1 - 1/2)^2}$$

$$I_{D1} = I$$

$$\text{If } v_{id} = -\sqrt{2} V_{OV}$$

$$I_{D2} = I$$

$$I_{D1} = 0$$

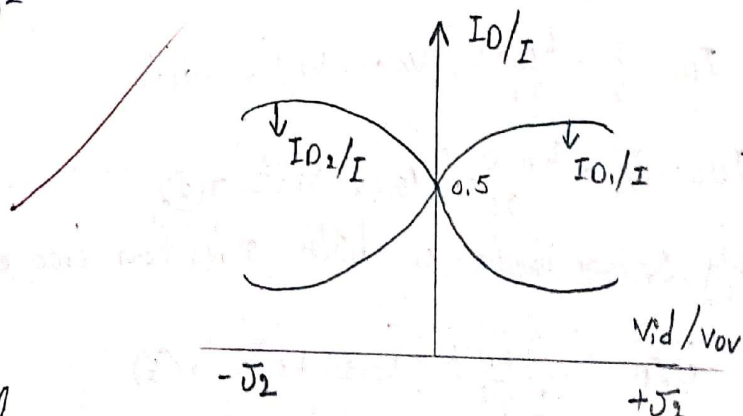


Differential Amplifier in Small Signal i/p mode:

⇒ In this small signal mode we are applying $v_{cm} \pm v_{id}/2$



For Q_1 transistor we applying $V_{em} + v_{id}/2$
 For Q_2 transistor we applying $V_{em} - v_{id}/2$

→ In this mode the MOS transistors are operated in active region
 → V_{em} is required to set DC voltage of MOSFET

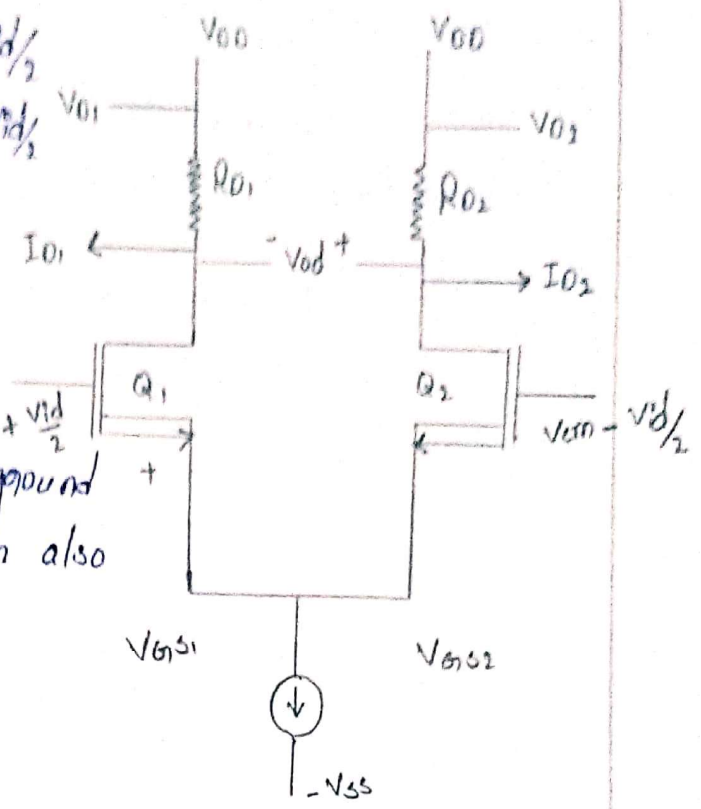By considering all dc voltages are ground and capacitors are become short, V_{em} also zero and current source to zero.



Ac Equivalent CRT :-

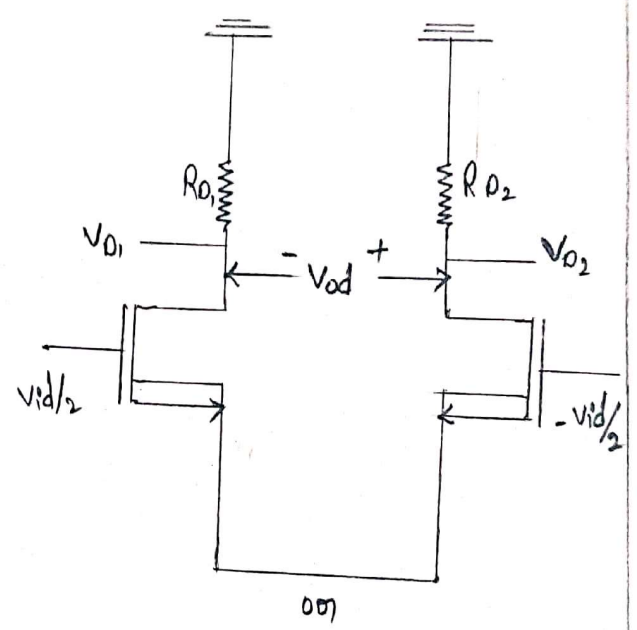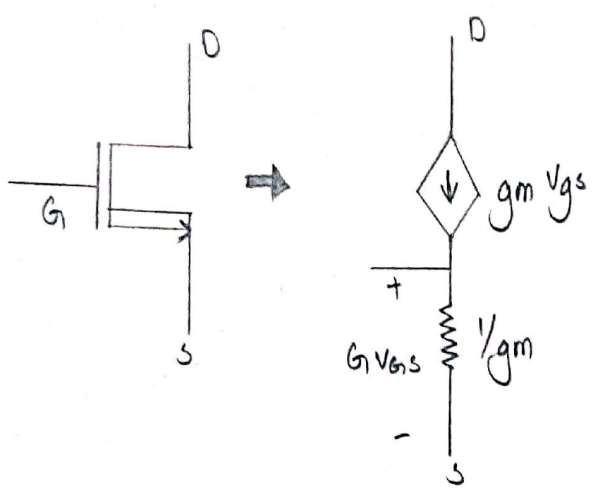

$$V_{D1} = -g_m \frac{v_{id}}{2} R_D$$

$$V_{D2} = g_m \frac{v_{id}}{2} R_D$$

$$V_o = V_{D2} - V_{D1}$$

$$= g_m \frac{v_{id}}{2} R_D + g_m \frac{v_{id}}{2} R_D$$

$$V_o = 2 g_m \frac{v_{id}}{2} R_D$$

$$V_o = g_m v_{id} R_D$$


$$\frac{V_o}{v_{id}} = g_m R_D$$

$A_d = \text{differential gain}$

$A_d = g_m R_o$ by consider 'od'

$A_d = g_m (R_o || r_{od})$
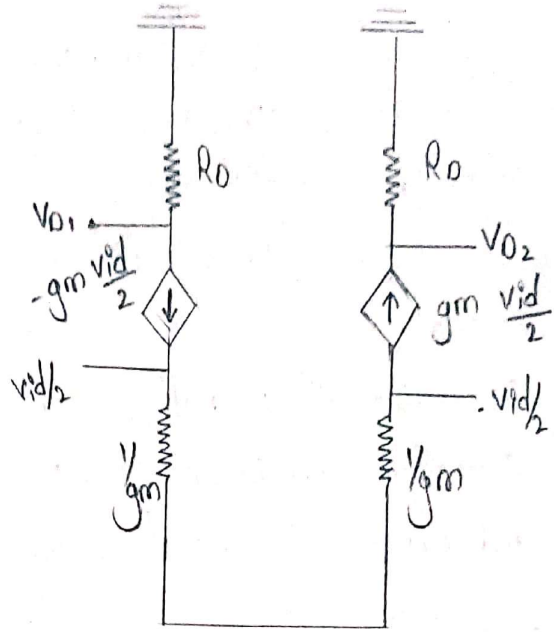
$$g_m = \frac{2I_D}{V_{ov}} ; r_{od} = \frac{2VA}{I}$$



Assignment - 1

Name: P. Hemalatha

SUBJECT: ECAKD

Reg No: 22095400114


10

Branch: ECE (C)

Year: II year

P

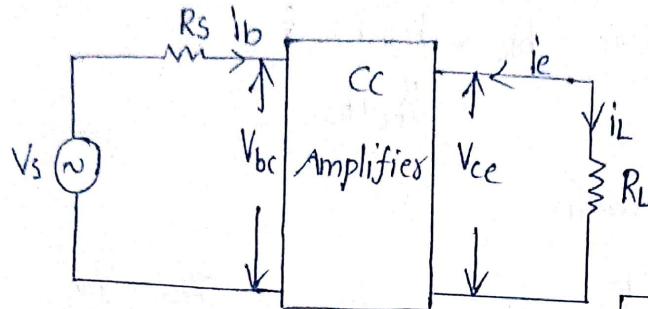1) Analysis of CC Amplifier in exact Model.




$$V_1 = h_{11} i_1 + h_{12} V_2$$

$$i_2 = h_{21} i_1 + h_{22} V_2$$

$$V_{bc} = h_{ic} i_b + h_{rc} V_{ce} \rightarrow \textcircled{1}$$

$$i_e = h_{fc} i_b + h_{oc} V_{ce} \rightarrow \textcircled{2}$$
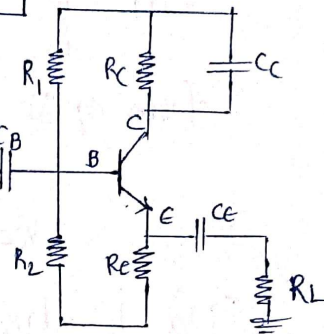
$$i_L \text{ (or) } i_2 = -\frac{V_{ce}}{R_L} \rightarrow \textcircled{3}$$



ckt diagram

Input impedance :-

$$Z_{in} = \frac{V_{bc}}{i_b} \rightarrow \textcircled{4}$$

sub eq ③ in eq ④

$$Z_{in} = \frac{h_{ic} i_b + h_{rc} V_{ce}}{i_b}$$

$$Z_{in} = h_{ic} + \frac{h_{rc} V_{ce}}{i_b} \rightarrow \textcircled{5}$$

from eq ② & ③

$$-\frac{V_{ce}}{R_L} = h_{fc} i_b + h_{oc} V_{ce}$$

$$h_{fc} i_b = -\frac{V_{ce}}{R_L} - h_{oc} V_{ce}$$

$$h_{fc} i_b = -V_{ce} \left(\frac{1}{R_L} + h_{oc} \right)$$

$$\frac{V_{ce}}{i_b} = \frac{-h_{fc}}{1/R_L + h_{oc}} \rightarrow \textcircled{6}$$


Voltage gain :-

$$A_v = \frac{V_{ce}}{V_{bc}}$$

from eq ④ $Z_{in} = \frac{V_{bc}}{i_b}$

$$V_{bc} = i_b Z_{in}$$

$$A_v = \frac{V_{ce}}{i_b Z_{in}}$$

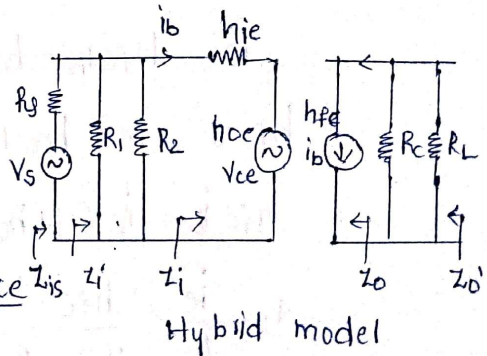

Hybrid model

eq (2) in eq (3)

$$Z_{in} = h_{ic} + h_{rc} \left(\frac{-h_{fc}}{1/R_L + h_{oc}} \right)$$

$$Z_{in} = h_{ic} - \frac{h_{fc} h_{rc}}{1/R_L + h_{oc}}$$

$$Z_{in} = h_{ic} - \frac{h_{fc} h_{rc}}{1/R_L + h_{oc}}$$

$$A_v = \frac{-h_{fc}}{1/R_L + h_{oc}} \times \frac{1}{Z_{in}}$$

$$A_v = \frac{-h_{fc}}{1/R_L + h_{oc}} \times \frac{1}{h_{ic} - \frac{h_{fc} h_{rc}}{1/R_L + h_{oc}}}$$

Current Gain :-

$$A_I = \frac{i_e}{i_b}$$

from eq (2) $i_e = \frac{-V_{ce}}{R_L}$

$$V_{ce} = -i_e R_L$$

eq (2) $i_e = h_{fc} i_b + h_{oc} V_{ce}$

$$i_e = h_{fc} i_b + h_{oc} (-i_e R_L)$$

$$i_e = h_{fc} i_b - h_{oc} i_e R_L$$

$$h_{fc} i_b = i_e + h_{oc} i_e R_L$$

$$h_{fc} i_b = i_e (1 + h_{oc} R_L)$$

$$A_I = \frac{i_e}{i_b} = \frac{h_{fc}}{1 + h_{oc} R_L}$$

$$A_I = \frac{h_{fc}}{1 + h_{oc} R_L}$$

$$Z_o = \frac{V_{ce}}{i_e}$$

from eq (2)

$$i_e = h_{fc} i_b + h_{oc} V_{ce}$$

divide by V_{ce}

$$\frac{i_e}{V_{ce}} = \frac{h_{fc} i_b}{V_{ce}} + h_{oc} \rightarrow (7)$$

from eq (1)

$$V_{bc} = h_{ic} i_b + h_{rc} V_{ce}$$

$$V_{bc} = 0$$

$$h_{ic} i_b = -h_{rc} V_{ce}$$

$$\frac{i_b}{V_{ce}} = \frac{-h_{rc}}{h_{ic}} \rightarrow (8)$$

from (7) \times (8)



$$\frac{i_e}{V_{ce}} = h_{fc} \left(\frac{-h_{rc}}{h_{ic}} \right) + h_{oc}$$

$$\frac{i_e}{V_{ce}} = \frac{-h_{fc} h_{rc} + h_{oc} h_{fc}}{h_{ic}}$$

$$Z_o = \frac{V_{ce}}{i_e} = \frac{h_{ic}}{h_{oc} h_{ic} - h_{fc} h_{rc}}$$

2) Analysis of ~~CC~~ FET CS Amplifier in exact Model.

Analysis of CS Amplifier:-

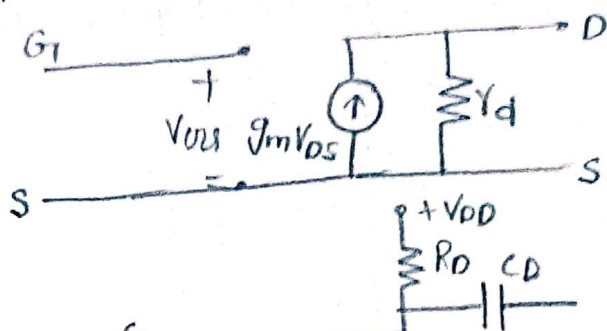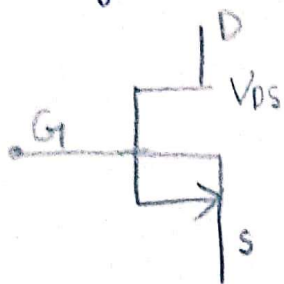

current gain :-

$$\frac{i_d}{i_g} = \frac{i_d}{0} = \infty$$


ilp impedance :-

$$Z_i = \frac{V_{gs}}{i_g} = \infty$$

$$Z_i' = Z_i \parallel R_g = R_g$$

o/p impedance :-

$$Z_o = \frac{V_{ds}}{i_d} \Big|_{V_{gs}=0, R_d \text{ disconnected}}$$

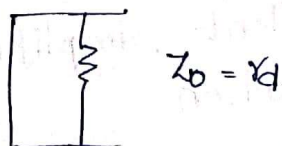

$$Z_o' = Z_o \parallel R_D$$

Voltage Gain:-

$$A_v = \frac{V_{ds}}{V_{gs}}$$



$$A_v = \frac{V_{ds}}{V_{gs}} = -g_m (Y_d \parallel R_D)$$

$$V_{ds} = -g_m V_{gs} [Y_d \parallel R_D]$$

$$A_v = -g_m (Y_d \parallel R_D)$$


$$g_m = i_d / V_{gs}$$

g_m = transconductance

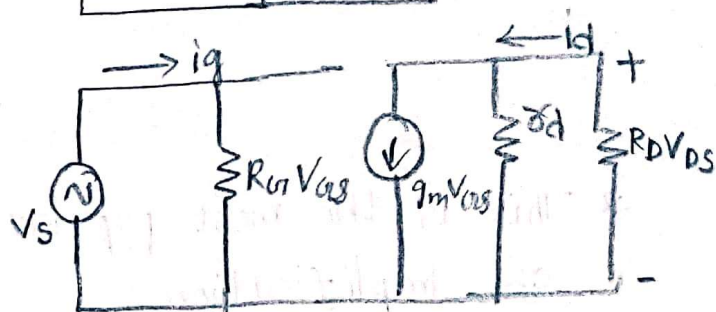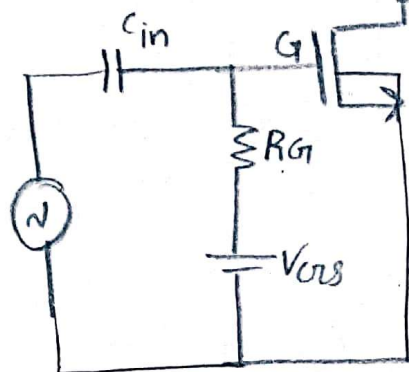


3) Explain two stage RC coupled Amplifier & transformed coupled Amplifiers.

Two stage RC coupled Amplifiers:-

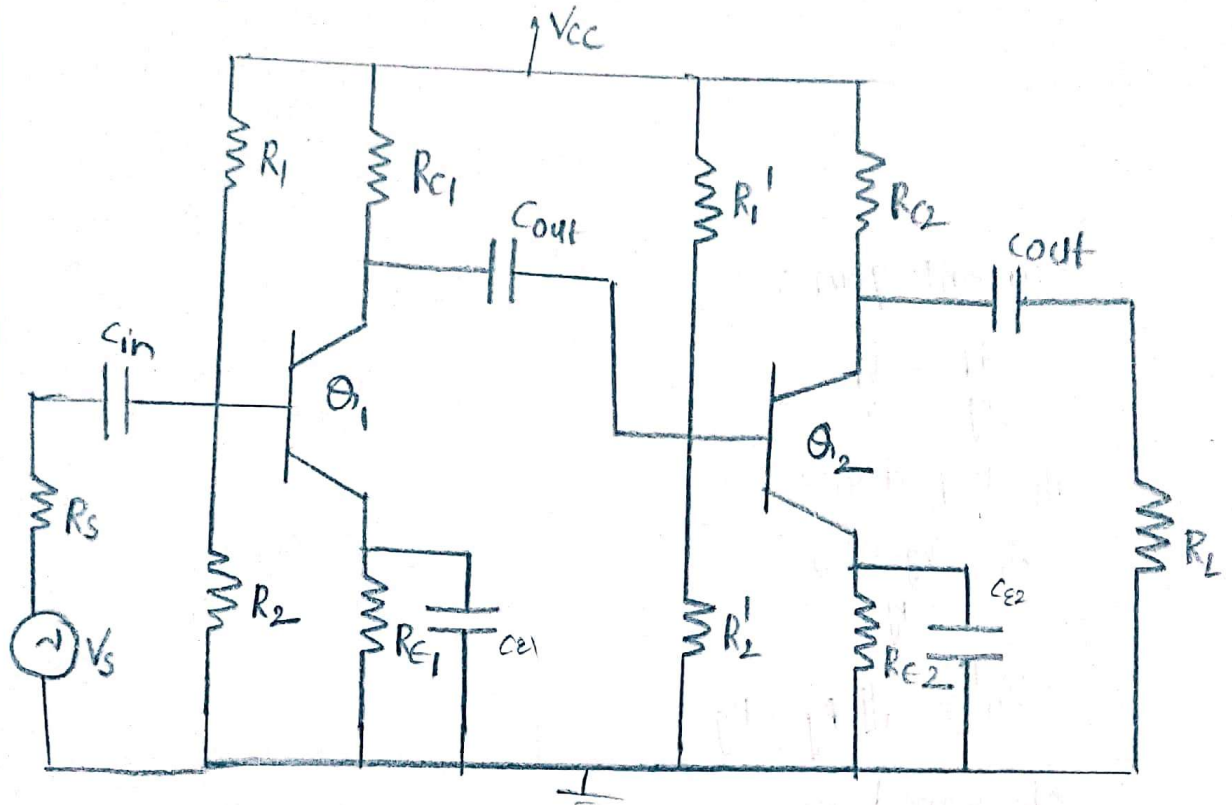

- * This is the most popular type of coupling because of Amplification
- * cheap and provides excellent Amplifications
- * Used in Voltage Amplification
- * coupling capacitor is used to transfer o/p from one stage to next stage.

Frequency response:-

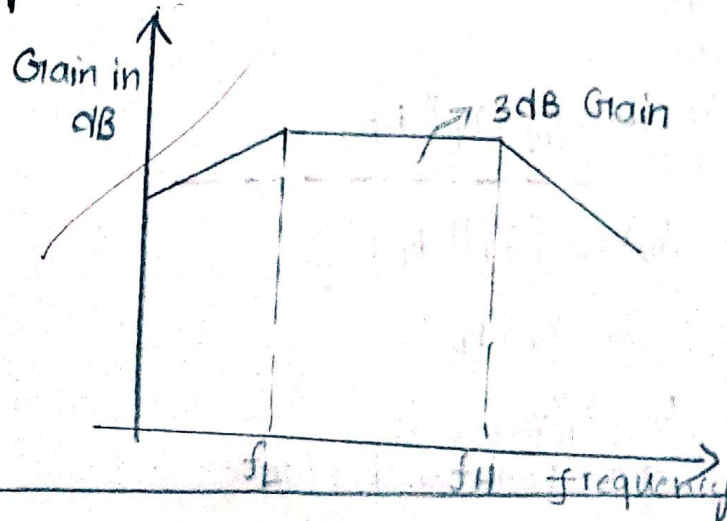

Analysis of CE Amplifier in exact & Simplified Model

Model :-

In Exact Model :-

$$\text{i/p impedance} = Z_{in} = h_{ie} - \frac{h_{re} h_{fe}}{\frac{1}{R_L} + h_{oe}}$$

$$\text{current gain} = A_I = \frac{-h_{fe}}{1 + h_{oe} R_L'}$$

$$\text{voltage gain} = A_v = \frac{-h_{fe}}{\frac{1}{R_L} + h_{oe}} \times \frac{1}{h_{ie} - \frac{h_{re} h_{fe}}{\frac{1}{R_L} + h_{oe}}}$$

$$\text{o/p impedance} = Z_o = \frac{h_{ie}}{h_{ie} h_{oe} - h_{fe} h_{re}}$$

In simplified Model :-

1) current Gain :- $A_I = -h_{fe}$

2) i/p impedance :- $Z_{in} = h_{ie}$

3) effective i/p impedance :- $Z_{in}' = R_B / Z_{in}$

4) i/p impedance with R_s :- $Z_{is} = R_s + Z_{in}$


5) Voltage Gain (A_v) :- $A_I \frac{R_L'}{Z_{in}}$

6) Voltage Gain with source :- $A_{vs} = A_v \frac{Z_i'}{Z_i' + R_s}$

7) current Gain with source :- $A_{Is} = A_I \cdot \frac{R_s'}{R_s' + Z_i}$

8) o/p impedance :- $Z_o = \alpha$, $Z_o' = R_c$, $Z_o'' = R_L'$


Transformed Coupled Amplifiers:-

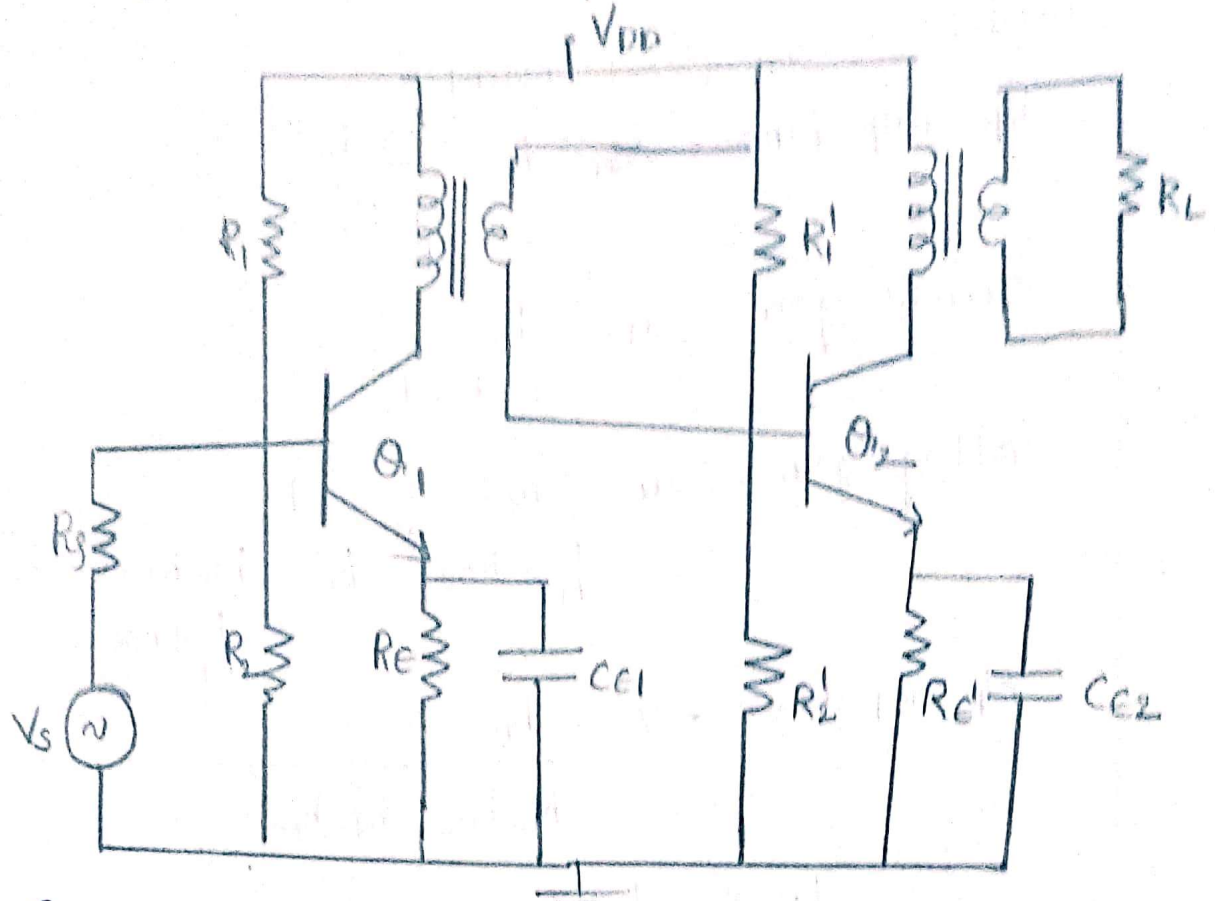

Operation:-

- 1) When an AC signal is applied to base of 1st amplifier it appears as amplified across the primary of coupling Amplifier
- 2) The Amplified signal is transferred to the ip of next stage by using secondary transformer.
- 3) In 2nd stage further Amplification from secondary transformer the o/p is transferred to R_L .

Frequency response:-

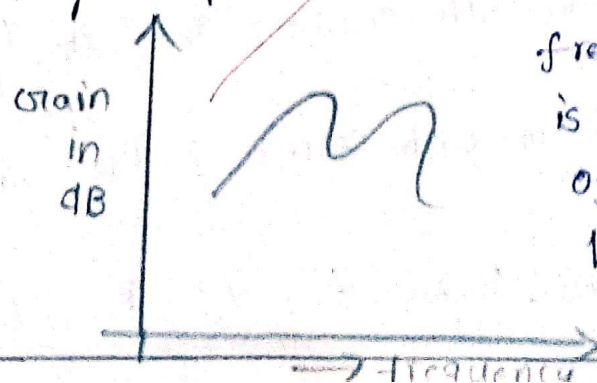

* In this Amplifier frequency response is poor because of transformer losses & gain is also unstable.

Advantages:

- 1) It has high Voltage Gain
- 2) High power Gain
- 3) Good i/p impedance matching
- 4) No signal loss in collector / base resistors.

Disadvantages:

- 1) Gain is not stable
- 2) transformer are expensive
- 3) poor frequency response
- 4) provides frequency distortion.

Applications:-

- 1) used in impedance matching
- 2) it is used in Radio frequencies (20 KHz - 200 KHz)
* TV receivers to amplify RF signals.

4) Explain different modes in Mos differential amplifier.

Mos differential Amplifiers are operated in 4 modes

- 1) common i/p mode
- 2) differential i/p mode
- 3) large signal i/p mode
- 4) small signal i/p mode.

1) Common i/p Mode:-

1) When same i/p voltage is applied to 2 transistors θ_1 & θ_2 the differential amplifier operates in common mode.

2) When two transistors are switch on operating saturated region total current is distributed equally.

$$I_{D1} = I_{D2} = I/2$$

$$I = I_{D1} + I_{D2}$$

$$V_s = V_{cm} - V_{ovs}$$

We know the drain current of MOSFET is

$$I_{D1} = \frac{I}{2} = \frac{k_n'}{2} \frac{w}{L} (V_{ovs} - V_t)^2$$

$$I_{D1} = I = \frac{k_n' w}{L} (V_{ov})^2$$

$$\therefore V_{ovs} - V_t = V_{ov}$$

V_{ov} = over drive voltage

$$V_{ov} = \sqrt{\frac{I}{k_n' \frac{w}{L}}}$$

from drain side

$$V_{D1} = V_{DD} - \frac{I}{2} R_{D1}$$

$$V_{D2} = V_{DD} - \frac{I}{2} R_{D2}$$

under this condition the difference btw two voltages is zero

so the o/p voltage is zero


$$V_{D1} = V_{D2}$$

$$V_o = 0$$

Common mode voltage range is

$$V_{cm}(\max) = V_D + V_s$$
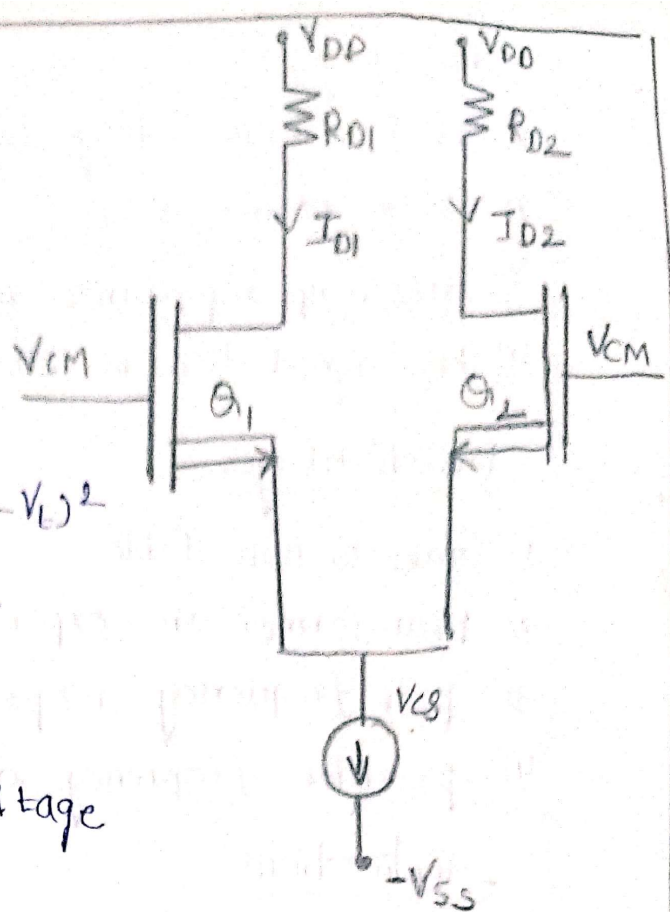
$$V_{cm}(\min) = -V_{SS} + V_{cs} + V_{ovs}$$



2) Differential i/p mode:-

In differential i/p mode the i/p voltage is given to Q_1 transistor & Q_2 transistor is connected to ground (0).


$$I_{D1} + I_{D2} = I$$

$$I_{D1} + 0 = I$$

$$I = I_{D1}$$

$$I_{D1} = I = \frac{kn' \omega}{2} \frac{\omega}{\mu} (V_{ov})^2$$
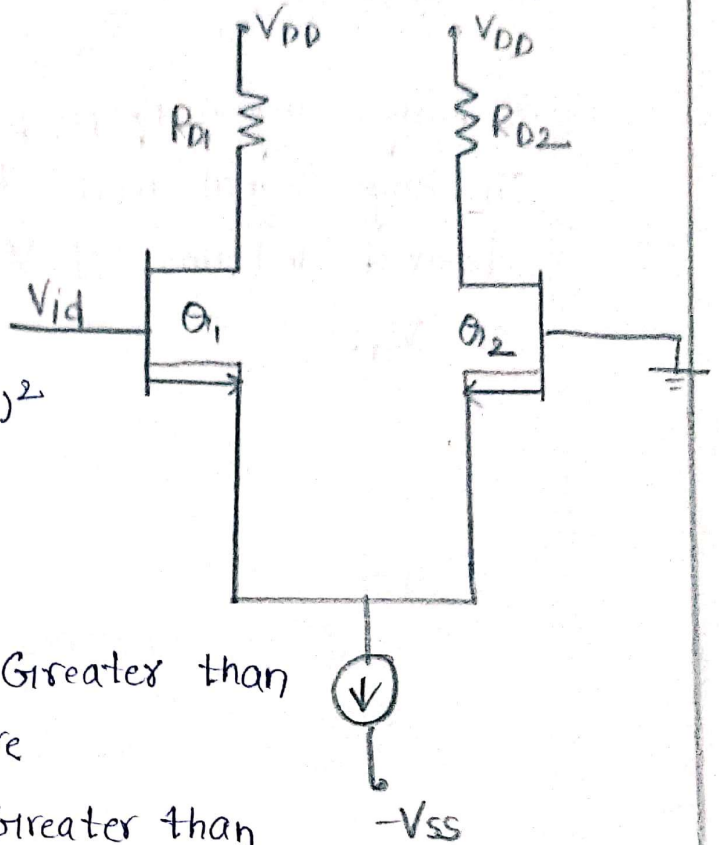
$$V_{ov} = \sqrt{\frac{2I}{\frac{kn' \omega}{\mu}}}$$



⇒ When V_{ID} is +ve I_{D1} is Greater than I_{D2} & also $V_{O12} - V_{O11} = +ve$

⇒ When V_{id} is -ve I_{D1} is Greater than I_{D2} & also $V_{O11} - V_{O12} = +ve$

⇒ When V_{id} is -ve, then $V_{O11} - V_{O12}$ is -ve ($V_{O11} < V_{O12}$)

$$I_{D1} = I = \frac{kn' \omega}{2} \frac{\omega}{\mu} [V_{GS} - V_t]^2$$

$$V_{GS1} = V_t + \sqrt{\frac{2I}{\frac{kn' \omega}{\mu}}} = V_t + \sqrt{2} V_{ov}$$

$$\left\{ \frac{I}{kn' \frac{\omega}{\mu}} = V_{ov} \text{ When } I_{D1} = I/2 \right\}$$

⇒ if V_{id} is +ve

$$V_{id} = V_{GS1} - V_t$$

$$V_{id} = V_t + \sqrt{2} V_{ov} - V_t$$

$$V_{id} = \sqrt{2} V_{ov}$$


→ if $V_{id} = V_e$

$$V_{id} = -\sqrt{2} V_{ov}$$

$$\therefore -\sqrt{2} V_{ov} \leq V_{id} \leq \sqrt{2} V_{ov}$$

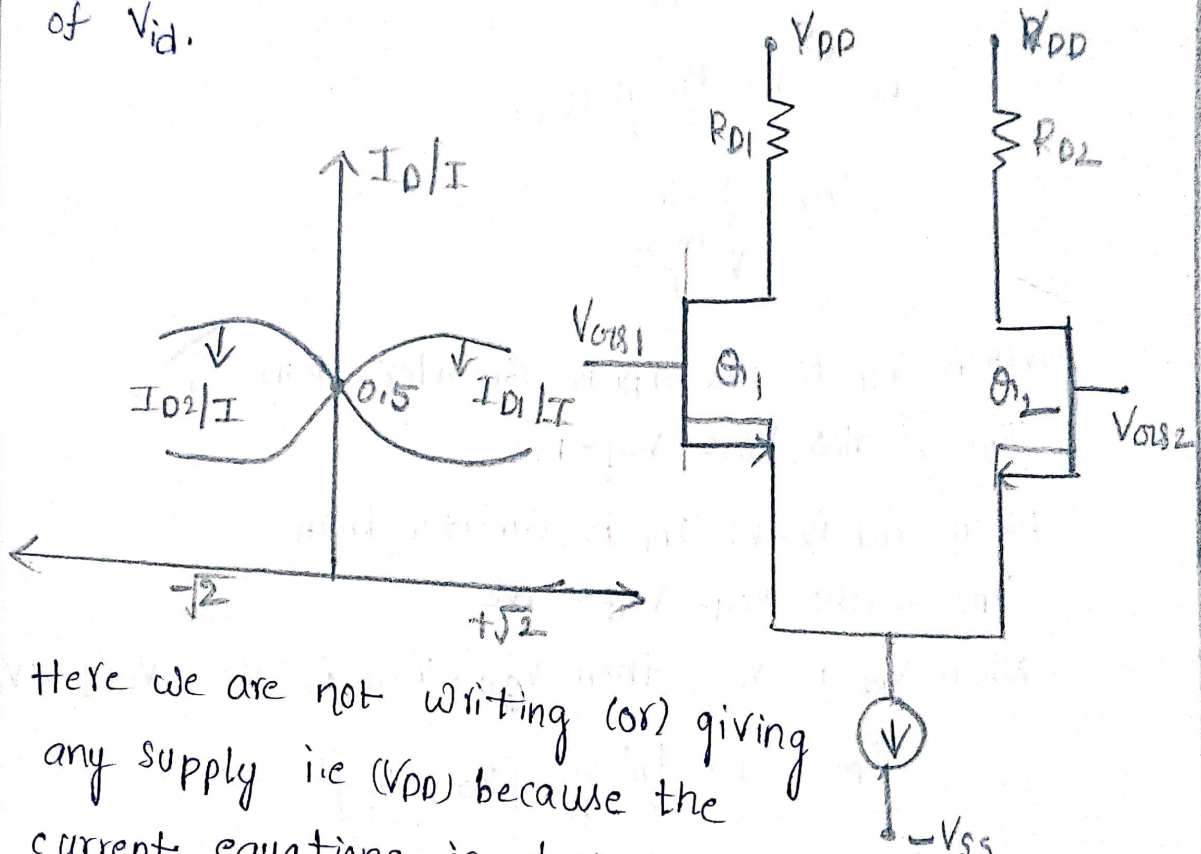3) Large signal i/p Mode:-

In large signal mode the current equations are derived in terms of V_{ov1} & V_{ov2} (or) in terms of V_{id} .



Here we are not writing (or) giving any supply i.e. (V_{DD}) because the current equations are derived from V_{s1} & V_{s2}

$$I_{D1} = \frac{I}{2} = \frac{K_n' \frac{W}{L}}{2} (V_{ov1} - V_{T})^2 \rightarrow \textcircled{1}$$

$$I_{D2} = \frac{I}{2} = \frac{1}{2} K_n' \frac{W}{L} (V_{ov2} - V_{T})^2 \rightarrow \textcircled{2}$$

Apply square root on both sides for eq ②, eq ①

$$\sqrt{I_{D1}} = \sqrt{K_n' \frac{W}{L}} (V_{ov1} - V_{T}) \rightarrow \textcircled{3}$$

$$\sqrt{I_{D2}} = \sqrt{K_n' \frac{W}{L}} (V_{ov2} - V_{T}) \rightarrow \textcircled{4}$$

Subtracting (3) & (4) equations

$$\sqrt{I_{D1}} - \sqrt{I_{D2}} = \sqrt{\frac{k_n' \omega}{L}} (V_{O11} - V_L) - \sqrt{\frac{k_n' \omega}{L}} (V_{O12} - V_L)$$

$$\sqrt{I_{D1}} - \sqrt{I_{D2}} = \sqrt{\frac{k_n' \omega}{L}} (V_{O11} - V_L - V_{O12} + V_L)$$

$$\sqrt{I_{D1}} - \sqrt{I_{D2}} = \sqrt{\frac{k_n' \omega}{L}} (V_{O11} - V_{O12})$$

squaring on both sides

$$(\sqrt{I_{D1}} - \sqrt{I_{D2}})^2 = \frac{k_n' \omega}{L} (V_{O11} - V_{O12})^2$$

$$(\sqrt{I_{D1}})^2 + (\sqrt{I_{D2}})^2 - 2\sqrt{I_{D1}}\sqrt{I_{D2}} = \frac{k_n' \omega}{L} (V_{O11} - V_{O12})^2$$

$$I_{D1} + I_{D2} - 2\sqrt{I_{D1}I_{D2}} = \frac{k_n' \omega}{L} (V_{O11} - V_{O12})^2$$

$$I_{D1} + I_{D2} - 2\sqrt{I_{D1}I_{D2}} = \frac{k_n' \omega}{L} (V_{id})^2$$

$$I - 2\sqrt{I_{D1}I_{D2}} = \frac{k_n' \omega}{L} (V_{id})^2 \quad \left[\because I_{D1} + I_{D2} = I \right]$$

$$I - \frac{k_n' \omega}{L} (V_{id})^2 = 2\sqrt{I_{D1}I_{D2}} \rightarrow (6)$$

substitute $I_{D2} = I - I_{D1}$ & apply squares on b/s we get

$$I_{D1} = I/2 + I/V_{OV} \left(\frac{V_{id}}{2} \right) \sqrt{1 - \frac{V_{id2}}{V_{OV}}}$$

$$I_{D2} = I/2 - I/V_{OV} \left(\frac{V_{id}}{2} \right) \sqrt{1 - \frac{V_{id2}}{V_{OV}}}$$

if $V_{id} = \sqrt{2}V_{OV}$

$$\frac{I}{2} + \frac{I}{V_{OV}} \cdot \frac{\sqrt{2}V_{OV}}{2} \sqrt{1 - \left(\frac{\sqrt{2}V_{OV}}{2} \right)^2}$$

$$\frac{I}{2} + \frac{I\sqrt{2}}{2} \sqrt{1 - 2/4}$$

$$\frac{I}{2} + \frac{I\sqrt{2}}{2} \sqrt{1 - 1/2}$$

$$\frac{I}{2} + \frac{I\sqrt{2}}{2} \sqrt{1/2}$$

$$I/2 + I/2 = I$$


$$I_{D1} = I, I_{D2} = 0$$

$$\text{Range: } -\sqrt{2} V_{ov} < V_{id} < \sqrt{2} V_{ov}$$

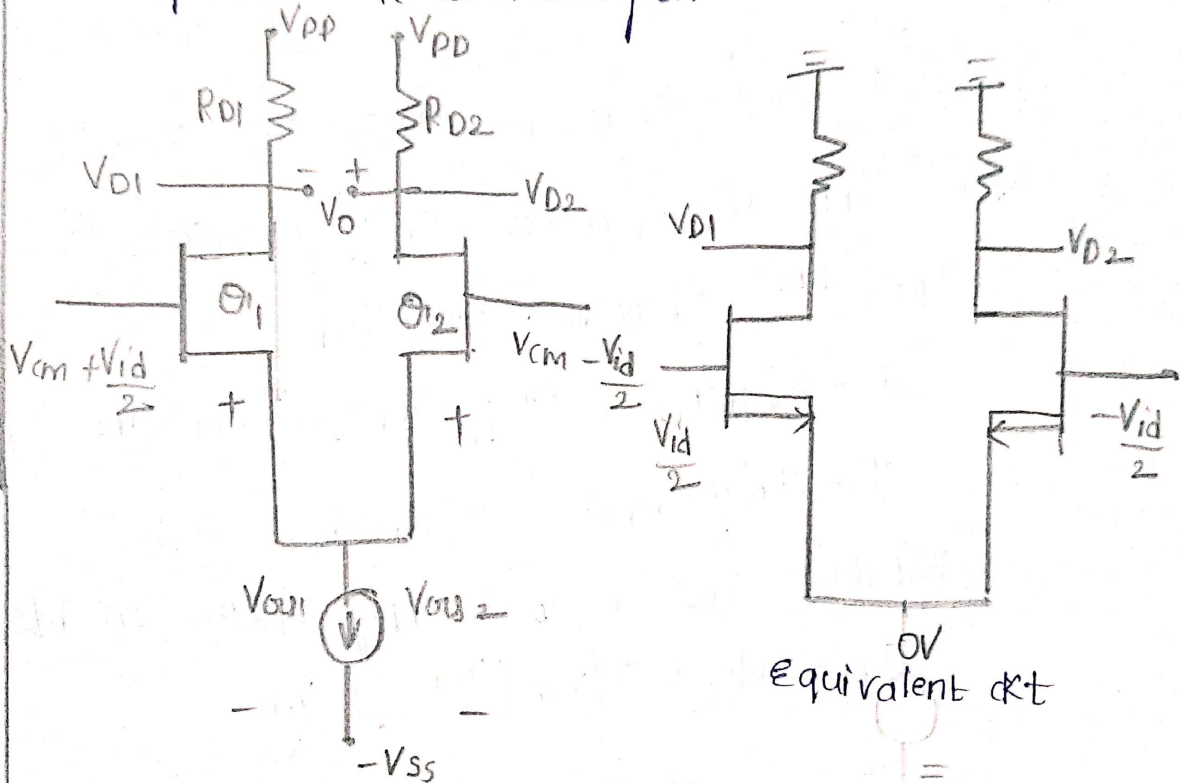4) Small signal i/p mode:-


In this small signal mode we are applying $V_{cm} \pm \frac{V_{id}}{2}$ (Θ_1) $V_{cm} - \frac{V_{id}}{2}$ (Θ_2)

* In this mode the mos transistors Θ_1 & Θ_2 are operated in active region.



Equivalent circuit

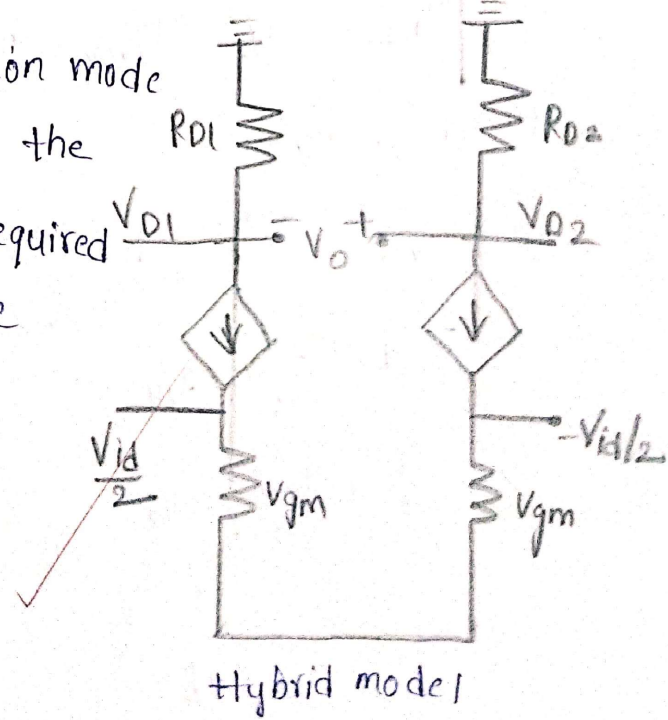V_{cm} is the common mode dc voltage within the mosfet V_{cm} is required to set dc voltage of MOSFET by considering the dc circuit.



Hybrid model

$$V_{D1} = -g_m \frac{V_{id}}{2} R_D$$

$$V_{D2} = g_m \frac{V_{id}}{2} R_D$$

$$V_o = V_{D2} - V_{D1}$$

$$V_o = g_m \frac{V_{id}}{2} R_D + g_m \frac{V_{id}}{2} R_D$$

$$V_o = g_m V_{id} R_D$$

$$\frac{V_o}{V_{id}} = g_m R_D$$

A_d - differential gain

$$A_d = g_m R_D \Rightarrow \text{without } r_d$$

With r_d

$$A_d = g_m (r_d \parallel R_D)$$

$$g_m = \frac{2I_D}{V_{ov}}$$

$$r_d = \frac{2V_A}{I}$$


5) Explain about high frequency model of BJT?

* At low frequencies we analyse the transistor using h parameters. But for high frequencies analysis the h-parameter model is not suitable for the following reasons.

1) The values of h-parameters are not constant at high frequencies.

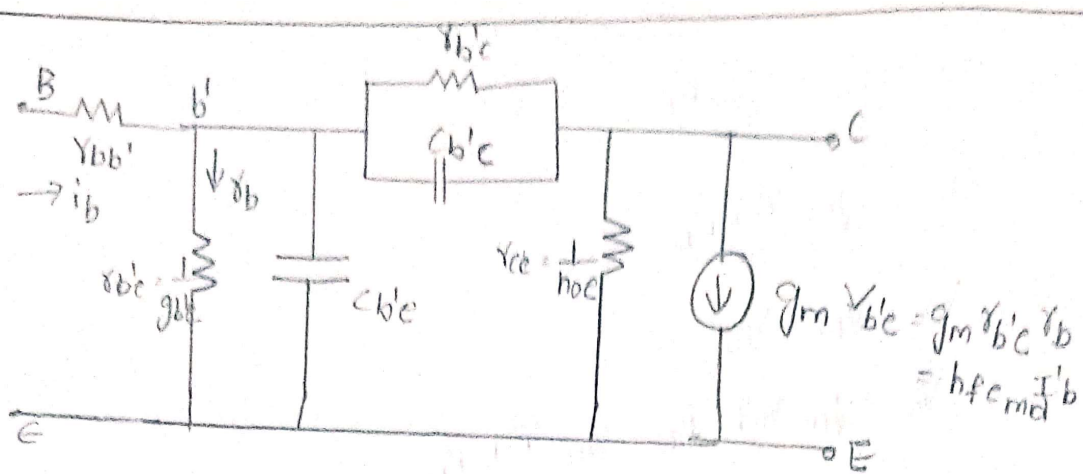2) The h-parameter model is simple & inaccurate because it neglects the early effect.

* Due to above reasons hybrid- π model is used for the analysis of transistors at high frequencies.



- 1) C_{be} :- The capacitive effect of normally forward biased base emitter junction of the transistor is represented by C_{be} or C_e in the hybrid π model. It is due to the diffusion capacitance of forward bias emitter diode. Its typical value is 100 pF.
- 2) C_{bc} :- The capacitive effect of normally reverse biased base collector junction of the transistor is represented by C_{bc} or C_c in the hybrid π model. It is due to the transition capacitance of reverse bias collector diode. Its typical value is 3 pF.
- 3) r_{be} :- The resistive effect of normally forward biased base emitter junction of the transistor is represented by r_{be} in the hybrid π model. The resistance is the portion of the base emitter which may be thought of as being "in series with" the collector junction.
- 4) r_{bc} :- The resistive effect of normally reverse biased base collector junction of the transistor is represented by r_{bc} in the hybrid π model. The resistance is due to early effect which is the varying voltage across the collector to emitter junction results in base width modulation.

A change in the effective base width causes the emitter current to change. The feedback effect btw o/p & i/p is taken by connecting $V_{b'e}$.

5) r_{bb} :- The resistance effect of bulk of resistances btw the external node B & internal base node b' . This resistance is called the base spreading resistance. Its typical value is 100Ω .

6) r_{ce} :- The resistance effect of o/p terminal is represented by r_{ce} in hybrid π model. It is also due to early effect.

7) $\partial I_{c'e} / \partial V_{b'e}$:- Due to small changes in voltage $V_{b'e}$ across the emitter junction, there is excess minority carrier concentration injected into the base which is proportional to the $V_{b'e}$. Therefore resulting small signal current is proportional to $V_{b'e}$.

Assignment - II

Name :- S. Raheem Basha

Branch :- ECE-C

10

Reg No :- 21091A04E2

Subject :- ECA4A

2

1. The loudspeaker of 8Ω is connected to the secondary of the o/p transformer of class A power amplifier. The Q-point collector current is 140mA . The turns ratio of transformer is $3:1$. The collector supply voltage is 10V if AC power delivered to the loud speaker is 0.48watt calculate DC power i/p, Efficiency, and power dissipation.

$$\text{Given } I_{CEQ} = 140\text{mA}$$

$$V_c = 10\text{V}$$

$$P_{ac} = 0.48\text{watt}$$

$$N_1/N_2 = 3:1$$

$$R_L = 8\Omega$$

$$\begin{aligned} \text{DC i/p power} &= V_{cc} \times I_{CEQ} \\ &= 10 \times 140 \times 10^{-3} \end{aligned}$$

$$P(DC) = 14 \times 10^{-1}$$

$$P(DC) = 1.4 \text{ watts}$$

$$\text{Efficiency } \eta\% = \frac{\text{AC power o/p}}{\text{DC power i/p}} \times 100$$

$$\eta\% = \frac{0.48}{1.4} \times 100$$

$$\eta\% = 34.28\%$$

$$\text{power dissipation :- } P_{dc} - P_{ac} = 1.4 - 0.48$$

$$P(D) = 0.92 \text{ watts}$$

2. A class B push pull amplifier supplies power to a resistive load of 12Ω . The o/p transformer has a turns ratio $3:1$ and efficiency of 78.5% . calculate (i) max o/p (P_{ac}) power (ii) max power dissipation in each transistor

Given $N_1:N_2 = 3:1$

$$P_{ac} = \frac{V_m I_m}{2}$$

$$\eta\% = 78.5\%$$

Let us assume $V_m = V_{cc} = 20V$, $I_m = I_m$

$$P_{ac} = \frac{V_m^2}{2R_L'}$$

$$R_L' = \left(\frac{N_1}{N_2}\right)^2 \times R_L = (3/1)^2 \times 12 = 108\Omega$$

$$\text{Max power dissipation } (P_{ac}) = \frac{V_m^2}{2R_L'} = \frac{(20)^2}{2 \times 108} = 1.85 \text{ watts}$$

we know that

$$\eta\% = \frac{P_{ac}}{P_{dc}} \times 100$$

$$P_{dc} = \frac{P_{ac}}{\eta\%} \times 100 = \frac{1.85}{78.5\%} = \frac{1.85}{0.785}$$

$$P_{dc} = 2.356 \text{ watts}$$

\therefore power dissipation = $P_{dc} - P_{ac}$

$$P(d) = 2.356 - 1.85$$

$$= 0.506 \text{ watts}$$

$$\therefore \text{ for each transistor } = P_{d/2} = 0.506/2$$

$$= 0.253 \text{ watts}$$

3. class-B push pull delivers ac load of 16Ω , connected to the secondary of an ideal transformer ($N_1:N_2 = 1:1$). supply voltage is $25V$, if the no. of turns on secondary is 50. calculate efficiency

Given $R_L = 16\Omega$

$$V_{cc} = 25V$$

$$N_2 = 50$$

$$R_L' = 16\Omega$$

$$V_m = V_{cc}$$

$$I_m = \frac{V_{cc}}{R_L'}$$

$$P_{ac} = \frac{V_m I_m}{2}$$

$$P_{dc} = \frac{2V_m(I_m)}{\pi} = \frac{2 \times 25(I_m)}{\pi}$$

$$P_{dc} = \frac{2 \times 25(V_m)}{\pi R_L'} = \frac{2 \times 25 \times 25}{\pi \times 16}$$

$$P_{dc} = 24.88 \text{ watts}$$

$$P_{ac} = \frac{V_m I_m}{2} = \frac{V_m(V_{cc})}{2R_L'} = \frac{25 \times 25}{2 \times 16} = 19.53 \text{ watts}$$

$$\begin{aligned} \text{Efficiency } \eta\% &= \frac{P_{ac}}{P_{dc}} \times 100 \\ &= \frac{19.53}{24.88} \times 100 \end{aligned}$$

$$\boxed{\eta\% = 78.296}$$

4. A class-B push pull amplifier supplies power to a load speaker of 10Ω , The o/p transformer turn ratio of $N_1:N_2 = 4:1$ and efficiency of 95%. calculate the (i) max power o/p P_{ac} (ii) Max power dissipation (iii) Max Base current of each transistor.

$$\text{Given } N_1:N_2 = 4:1$$

$$\eta\% = 95\%$$

$$R_L = R_L' = 10\Omega$$

$$P_{ac} = \frac{V_m I_m}{2}$$

$$\text{Let us assume } V_m = V_{cc} = 20V \left(\because I_m = \frac{V_m}{R_L'} \quad V_m = V_{cc} \right)$$

$$P_{ac} = \frac{V_m^2}{2R_L'}$$

$$(i) P_{ac} = \frac{400}{2 \times 16} = 40/32$$

$$\boxed{P_{ac} = 1.25 \text{ watts}}$$

$$R_k' = (N_1/N_2)^2 \times R_k = (4/1)^2 \times 10 = 160 \Omega$$

$$P_{dc} = \frac{P_{ac}}{\eta\%}$$

$$= \frac{1.25}{0.95} \times 100$$

$$P_{dc} = 1.315 \text{ watts}$$

ii) power dissipation (P_d) = $P_{dc} - P_{ac}$

$$= 1.315 - 1.25$$

$$= 0.065 \text{ watt}$$

For each transistor

$$P_{d/2} = 0.065/2$$

$$= 0.0325 \text{ watts}$$

(iii) for max Base current

$$P_{dc} = \frac{2V_{cc} I_{m}}{\pi}$$

$$I_{m} = \frac{\pi \times P_{dc}}{2V_{cc}} = \frac{\pi \times 1.315}{2 \times 20}$$

$$I_{m} = 0.1032$$

Assume $h_{fe} = 25$

$$\text{for } I_{m \max} = I_{m} / h_{fe} = \frac{0.1032}{25} = 4.128 \times 10^{-3}$$

$$I_{m \max} = 4.12 \text{ mA}$$

5. For the RC phase shift oscillator, the feedback Network uses $R = 6k\Omega$, $C = 1500\text{pf}$, The transistorized amplifier uses a collector resistance of $18k\Omega$ calculate the frequency of oscillations & minimum value of h_{fe} of transistor.

we know that in RC phase shift oscillator,

$$f = \frac{1}{2\pi RC \sqrt{10}}$$

Given that $R = 6k\Omega$, $C = 1500\text{pf}$, $R_c = 18k\Omega$

$$f = \frac{1}{2\pi RC \sqrt{6+4k}}$$

$$k = R_c/R = \frac{18 \times 10^3}{6 \times 10^3} = 3$$

$$f = \frac{1}{2 \times 3.14 \times 6 \times 10^{-3} \times 1500 \times 10^{-12} \sqrt{6+4(3)}}$$

$$f = 4.17 \text{ kHz}$$

$$h_{fe} = 23 + 4k + 29/k = 4(3) + 23 + 29/3$$

$$= 44.66$$

$$h_{fe} \geq 45$$

6. The frequency sensitive arms of Wein bridge oscillator uses $C_1 = C_2 = 0.001 \mu\text{F}$ & $R_1 = 10 \text{ k}\Omega$, R_2 is kept variable and the frequency is varied from 10 kHz to 50 kHz . Find min and max value of R_2 ?

Given that

$$C_1 = C_2 = 0.001 \mu\text{F} \quad \text{we know that } f = \frac{1}{2\pi \sqrt{R_1 R_2} C_1 C_2}$$

At $f = 10 \text{ kHz}$

$$10 \times 10^3 = \frac{1}{2\pi \sqrt{10 \times 10^3 \times 0.001 \times 10^{-6} \times 0.001 \times 10^{-6} \times R_2}}$$

$$10 \times 10^3 = \frac{1}{2\pi \sqrt{10^7 \times R_2}} \quad \text{S.O.B.S}$$

$$(10^4)^2 = \frac{1}{4\pi^2 \times 10^7 \times R_2}$$

$$R_2 = \frac{1}{4\pi^2 \times 10^7 \times 10^8}$$

$$R_2 = 2.533 \times 10^{-17}$$

At $f = 50 \text{ kHz}$

$$50 \times 10^3 = \frac{1}{2\pi \sqrt{10 \times 10^3 \times 0.001 \times 10^{-6} \times 0.001 \times 10^{-6} \times R_2}}$$

S.O.B.S

$$50 \times 10^3 = \frac{1}{2\pi \sqrt{10^7 \times R_2}}$$

$$(50 \times 10^3)^2 = \frac{1}{4\pi^2 \times 10^7 \times R_2}$$

$$R_2 = \frac{1}{4\pi^2 \times 10^7 \times (50 \times 10^3)^2}$$

$$R_2 = 1.0132 \times 10^{-18}$$

7. Find the frequency of a transistor Hartley oscillator if $L_1 = 100 \mu\text{H}$, $L_2 = 1 \text{ mH}$, mutual inductance (M) = $20 \mu\text{H}$ and $C = 20 \text{ pF}$. Find the frequency

we know that

$$L_{eq} = L_1 + L_2 + 2M$$

$$L_{eq} = 100 \times 10^{-6} + 1 \times 10^{-3} + 2(20 \times 10^{-6})$$

$$C = 20 \times 10^{-12}$$

$$f = \frac{1}{2\pi \sqrt{L_{eq} C}} = \frac{1}{2\pi \sqrt{100 \times 10^{-6} + 1 \times 10^{-3} + 40 \times 10^{-6} \times 20 \times 10^{-12}}}$$

$$f = 1054029.36 \text{ Hz}$$

$$f = 1054.02 \times 10^6 \text{ Hz}$$

$$\boxed{f = 1054.02 \text{ MHz}}$$

8. Find the frequencies of transistor Colpitts oscillator $C_1 = 0.001 \mu\text{F}$

$$C_2 = 0.01 \mu\text{F}, L = 15 \mu\text{H}$$

Given that

$$C_1 = 0.001 \mu\text{F}, C_2 = 0.01 \mu\text{F}, L = 15 \mu\text{H}$$

$$f = \frac{1}{2\pi \sqrt{L \left(\frac{1}{C_1} + \frac{1}{C_2} \right)}}$$

$$f = \frac{1}{2\pi \sqrt{15 \times 10^{-6} \times \left(\frac{1}{0.001 \times 10^{-6}} + \frac{1}{0.01 \times 10^{-6}} \right)}}$$

$$f = 1362921.05$$

$$\boxed{f = 1362.92 \text{ kHz}}$$

9. In a transistorized Hartley oscillator, two inductances are 2 mH & $20 \mu\text{H}$, while frequency is to be varied from 950 kHz to 2050 kHz . Calculate the range over which the capacitor is to be varied

Given that

$$M = 0$$

$$L_{eq} = L_1 + L_2 = 2 \times 10^{-3} + 20 \times 10^{-6}$$

$$L_{eq} = 0.00202.$$

$$f = \frac{1}{2\pi \sqrt{L_{eq} C}}$$

$$950 \text{ kHz} = \frac{1}{2\pi \sqrt{L_{eq} C}}$$

$$\sqrt{L_{eq} C} = \frac{1}{2\pi (950 \text{ K})}$$

$$C = \frac{1}{4\pi^2 (950 \text{ K})^2 \times 0.00202}$$

$$C_1 = 13.894 \text{ pF}$$

$$2050 \text{ kHz} = \frac{1}{2\pi \sqrt{L_{eq} C_2}}$$

$$C_2 = \frac{1}{4\pi^2 \times L_{eq} (2050 \text{ K})^2}$$

$$C_2 = 2.98 \times 10^{-12} \text{ F}$$

$$C_2 = 2.98 \text{ pF}$$

* capacitor range is 2.98 pF to 13.8 pF

10. In a colpitts oscillator $C_1 = 0.001 \mu\text{F}$, $C_2 = 0.01 \mu\text{F}$, $L = 10 \mu\text{H}$. Find the frequency of oscillations, (β), voltage gain (A_v)?

$$f = \frac{1}{2\pi \sqrt{\frac{1}{LC_1} + \frac{1}{LC_2}}}$$

$$= \frac{1}{2\pi \sqrt{\frac{1}{10 \times 10^{-6} \times 0.001 \times 10^{-6}} + \frac{1}{10 \times 10^{-6} \times 0.01 \times 10^{-6}}}}$$

$$f = 1670.07 \text{ kHz}$$

$$A_v = \text{Gain}(h_{fe}) = \frac{C_2}{C_1} = \frac{0.01}{0.001} = 10$$

we know that $A\beta = 1$

$$\beta = \frac{1}{A} = \frac{1}{10}$$

$$= 0.1$$

$$\boxed{\beta = 0.1}$$

11. A FET RC phase shift oscillator has $g_m = 5 \text{ mS}$, $r_d = 50 \text{ k}\Omega$, Feedback resistance is $(R) = 100 \text{ k}\Omega$, and capacitance value is 64.79 pF . Calculate the frequency of oscillations & $R_D = ?$

we know that $f = \frac{1}{2\pi RC\sqrt{10}}$

$$f = \frac{1}{2\pi \times 100 \times 10^3 \times 64.79 \times 10^{-12} \sqrt{10}}$$

$$f = 7.779 \text{ kHz}$$

$$R_D = ?$$

$$|A| \geq 29 \quad A = g_m R_L$$

$$R_L = r_d \parallel R_D$$

$$g_m R_L \geq 29 \Rightarrow R_L \geq 29/g_m$$

$$R_L > \frac{29}{5 \times 10^{-3}}$$

$$R_L > 5.8 \text{ k}\Omega$$

Let $R_L = 6 \text{ k}\Omega$

$$R_L = r_d \parallel R_D$$

$$R_L = \frac{r_d \times R_D}{r_d + R_D}$$

$$(r_d + R_D) R_L = r_d \times R_D$$

$$50 \times 10^3 \times 6 \times 10^3 + R_D \times 6 \times 10^3 = 50 \times 10^3 \times R_D$$

$$50 \times 10^3 \times R_D - R_D \times 6 \times 10^3 = 300 \times 10^6$$

$$44 \times 10^3 R_D = 300 \times 10^6$$

$$R_D = \frac{300 \times 10^6}{44 \times 10^3}$$

$$R_D = 6.818 \text{ k}\Omega$$

12. A crystal has $L = 0.4 \mu\text{H}$, $C = 0.085 \text{ pF}$, $C_m = 1 \text{ pF}$ with series resistance (R_s) = 5Ω . Calculate series resonant frequency (f_s) and parallel resonant frequency (f_p), Quality factor (Q) and By what percent that the parallel resonant frequency exceeds the series resonant frequency

$$\begin{aligned} \text{i) } f_s &= \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.4 \times 10^{-6} \times 0.085 \times 10^{-12}}} \\ &= 863516 \text{ Hz} \\ &= 863.51 \text{ kHz} \end{aligned}$$

$$\begin{aligned} \text{ii) } f_p &= \frac{1}{2\pi\sqrt{L \times C_{\text{eq}}}} = \frac{1}{2\pi\sqrt{L \times \frac{C_m \times C}{C + C_m}}} = \frac{1}{2\pi\sqrt{\frac{0.4 \times 10^{-6} \times 0.085 \times 10^{-12} \times 1 \times 10^{-12}}{0.085 \times 10^{-12} + 1 \times 10^{-12}}}} \times 0.4 \\ &= 899530 \text{ Hz} \\ &= 899.53 \text{ kHz} \end{aligned}$$

$$\begin{aligned} \text{iii) } Q &= \frac{\omega_s L}{R_s} = \frac{2\pi f_s L}{R_s} \\ &= \frac{2\pi \times 863.51 \times 10^3 \times 0.4}{5 \times 10^{-3}} = 434.07 \end{aligned}$$

$$\begin{aligned} \text{iv) } \% \text{ change} &= \frac{f_p - f_s}{f_p} \times 100 \\ &= \frac{899.53 \times 10^3 - 863.51 \times 10^3}{899.53 \times 10^3} \times 100 \end{aligned}$$

$$\% \text{ change} = 3.99\%$$

ECAD Assignment - II10
2

1. For an RC phase shift oscillator the feedback network uses $R = 6k\Omega$ & $C = 1500pF$. The transistorized amplifier uses a collector resistance of $18k\Omega$. Calculate the frequency of oscillation & minimum value of h_{fe} of transistor?

Sol: We know that in RC phase shift oscillator

$$f = \frac{1}{2\pi RC \sqrt{10}}$$

Given that,

$$R = 6k\Omega ; C = 1500pF ; R_c = 18k\Omega$$

$$f = \frac{1}{2\pi RC \sqrt{6+4k}} \quad \because k = \frac{R_c}{R} = \frac{18 \times 10^3}{6 \times 10^3} = 3$$

$$f = \frac{1}{2 \times 3.14 \times 6 \times 10^3 \times 1500 \times 10^{-12} \times \sqrt{6+4(3)}}$$

$$f = 4.17 \text{ kHz}$$

$$h_{fe} = 23 + 4k + \frac{29}{k} = 4(3) + 23 + \frac{29}{3} = 44.66$$

$$h_{fe} \geq 45$$

2. The frequency sensitive arms of the Wein bridge oscillator $C_1 = C_2 = 0.001\mu F$ & $R_1 = 10k\Omega$. While R_2 is kept variable. The frequency is to be varied from $10kHz$ to $50kHz$ by varying the R_2 . Find the min & max values of R_2 .

Sol: $f = \frac{1}{2\pi \sqrt{R_1 R_2} C_1 C_2} \Rightarrow 10 \text{ kHz} = \frac{1}{2\pi \sqrt{10k \times R_2} \times 0.001 \times 10^6 \times 0.001 \times 10^6}$

$$10 \times 10^3 = \frac{1}{50329212 \sqrt{R_2}}$$

$$10 \times 10^3 = \frac{15.91 \times 10^6}{\sqrt{R_2}} \Rightarrow \sqrt{R_2} = \frac{15.91}{10} \times 10^3$$

$$\sqrt{R_2} = 15.91 \times 10^2$$

3. Find the frequency of transistor colpits oscillator and condition for oscillation if $C_1 = 0.001 \mu\text{F}$, $C_2 = 0.01 \mu\text{F}$, $L = 15 \mu\text{H}$ also calculate gain & feedback factor.

Sol: $f = \frac{1}{2\pi\sqrt{C_{eq}L}}$

$$C_{eq} = 9.99 \times 10^{-15}$$

$$f = \frac{1}{2\pi\sqrt{9.9 \times 10^{-15} \times 15 \times 10^{-6}}} = 1361 \text{ kHz} = f$$

$$A = h_{fe} = \frac{C_2}{C_1} = \frac{0.01 \times 10^{-6}}{0.001 \times 10^{-6}} = 10$$

feedback factor (β)

$$A = \frac{C_2}{C_1} = 10$$

we know that

$$A\beta = 1 \Rightarrow \beta = \frac{1}{A} = \beta = \frac{1}{10} \Rightarrow \boxed{\beta = 0.1}$$

4. In a transistorised hartley oscillator the two inductors are 2 mH and $20 \mu\text{H}$, while frequency is to be varied from 950 kHz to 2050 kHz . calculate the range over which the capacitor is to be varied?

Sol: $M=0$

$$f = \frac{1}{2\pi\sqrt{L_{eq}C}} \quad ; \quad L_{eq} = L_1 + L_2 + 2M \rightarrow 0$$

$$L_{eq} = 0.00202$$

$$f = 950 \text{ kHz}$$

$$950 \text{ k} = \frac{1}{2\pi\sqrt{L_{eq}C}} \Rightarrow \sqrt{L_{eq}C} = \frac{1}{2\pi(950\text{k})}$$

$$C = \frac{1}{4\pi^2(950\text{k})^2 \times 0.00202} = 13.894 \text{ pF}$$

$$f = 2050 \text{ kHz}$$

$$f = \frac{1}{2\pi\sqrt{L_{eq}C}}$$

$$C = \frac{1}{4\pi^2(2050\text{k})^2 \times 0.00202} = 2.96 \times 10^{-12} \text{ F} = 2.98 \text{ pF}$$

\therefore Capacitor range is (2.98 pF to 13.89 pF)

5. Find the frequency of a transistor Hartley oscillator if $L_1 = 100 \mu\text{H}$, $L_2 = 2 \text{ mH}$, mutual inductance (M) = $50 \mu\text{H}$ and $C = 10 \text{ pF}$. Find the freq.

Sol: $L_{eq} = L_1 + L_2 + 2M = 100 \times 10^{-6} + 2 \times 10^{-3} + 2(20 \times 10^{-6})$

$C = 20 \times 10^{-12}$

$f = \frac{1}{2\pi\sqrt{L_{eq}C}} = \frac{1}{2\pi\sqrt{(100 \times 10^{-6} + 2 \times 10^{-3} + 40 \times 10^{-6}) \times 20 \times 10^{-12}}}$

$f = 1054.029 \text{ kHz}$

6. Find the frequency of transistor colpits oscillators, $C_1 = 20.001 \mu\text{F}$, $C_2 = 0.01 \mu\text{F}$, $L = 15 \mu\text{H}$

Sol: $f = \frac{1}{2\pi\sqrt{L\left(\frac{1}{C_1} + \frac{1}{C_2}\right)}} = \frac{1}{2\pi\sqrt{15 \times 10^{-6} \left(\frac{1}{20.001 \times 10^{-6}} + \frac{1}{0.01 \times 10^{-6}}\right)}}$

$f = 1363.612 \text{ kHz}$

7. A FET RC phase shift oscillator has $g_m = 5 \text{ mS}$, $r_d = 50 \text{ k}\Omega$ feedback resistance is (R) = $100 \text{ k}\Omega$ and capacitance value is 64.79 pF . Calculate the frequency of oscillations & $R_D = ?$

Sol: $f = \frac{1}{2\pi RC\sqrt{10}} = \frac{1}{2\pi \times 64.79 \times 10^{-12} \times 100 \times 10^3 \sqrt{10}} = 7.779 \text{ kHz}$

$|A| \geq 29$ $A = g_m R_L$

$R_L = r_d // R_D$

$g_m R_L \geq 29 \Rightarrow R_L > \frac{29}{g_m}$

$R_L > 5.8 \text{ k}\Omega$

let $R_L = 6 \text{ k}\Omega$

$R_L = r_d // R_D = \frac{r_d \times R_D}{r_d + R_D} = (r_d + R_D) 6 \text{ k}\Omega = r_d * R_D$

$50 \times 10^3 \times 6 \times 10^3 + R_D \times 6 \text{ k}\Omega = 50 \times 10^3 \times R_D$

$300 \times 10^3 + 6 \times 10^3 R_D = 50 \times 10^3 R_D$

$44 \times 10^3 R_D = 300 \times 10^3$

$R_D = \frac{300}{44}$

$R_D = 6.818 \text{ k}\Omega$

8. A crystal, as $L=0.4\text{H}$, $C=0.085\text{PF}$ and $C_m=2\text{PF}$ $R_s=5\text{k}\Omega$ find

i. Series resonance freqⁿ (f_s)

ii. Parallel resonance freqⁿ (f_p)

iii. quality factor of a crystal.

iv. By what % does the parallel resonance freqⁿ with series resonance freq.

Sol: i. $f_s = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.4 \times 0.085 \times 10^{-12}}}$
 $= 0.863\text{MHz}$

ii. $f_p = \frac{1}{2\pi\sqrt{LC_{eq}}}$ $\therefore C_{eq} = \frac{CC_m}{C+C_m}$
 $= \frac{1}{2\pi\sqrt{0.4 \times 0.765 \times 10^{-12}}}$
 $f_p = 0.952\text{MHz}$

iii. Quality factor $= \frac{\omega_s L}{R} = \frac{2\pi f_s L}{R} = \frac{2\pi \times 0.863 \times 10^6 \times 0.4}{5 \times 10^3}$

$= 430$

iv. % change $= \frac{f_p - f_s}{f_p} \times 100$
 $= \frac{0.952 \times 10^6 - 0.863 \times 10^6}{0.952 \times 10^6} \times 100$
 $= 9.25\%$

9. The loudspeaker of 8Ω is connected to the secondary of the opt transformer of class A power amplifier the a point collector current is 140mA . The turns ratio of the transistor is 3:1. The collector supply voltage is 10V . If AC power delivered to the loudspeaker the 0.48 watt . Calculate DC power i/p efficiency, power description.

Sol: Given $P_{dc} = V_{cc} I_{c0}$ $P_{ac} = 0.48\text{W}$
 $= 10\text{V} \times 140\text{mA} = 1.4\text{W}$

$\% \eta = \frac{P_{ac}}{P_{dc}} \times 100 = \frac{0.48}{1.4} \times 100 = 34.28\%$

$P_d = P_{dc} - P_{ac} = 1.4\text{W} - 0.48\text{W}$

$P_d = 0.92\text{W}$

10. A class B pushpull amplifier supply power to a R_L of 12Ω . The x/p transform-er as a trans ratio of 3:1 and efficiency of 78.5%. calculate (a) max. power out (b) max power distipation in each transistor.

Sol: $R_L = 12\Omega$
 $N_1:N_2 = 3:1$

$$R_L' = \left(\frac{N_1}{N_2}\right)^2 R_L = \left(\frac{3}{1}\right)^2 \times 12\Omega = 108\Omega$$

$$P_{ac\ max} = \frac{V_m I_m}{2} = \frac{V_m}{2} \cdot \frac{V_m}{R_L'} = \frac{V_m^2}{2R_L'} = \frac{(20)^2}{2 \times 108}$$

$$P_{ac\ max} = 1.85\text{W}$$

$$P_d = P_{dc} - P_{ac} \Rightarrow P_d = 2.35\text{W} - 1.85\text{W} = 0.5\text{W}$$

$$\% \eta = \frac{P_{ac}}{P_{dc}} \times 100$$

$$78.5\% = \frac{1.85}{P_{dc}} \times 100 \Rightarrow P_{dc} = \frac{1.85}{78.5} \times 100$$

$$P_{dc} = 2.35\text{W}$$

$$(P_d)_{\text{per transistor}} = \frac{P_d}{2} = \frac{0.5\text{W}}{2} = 0.25\text{W}$$

11. A class B push pull amplifier drives a load of 16Ω connected to the secondary of the ideal transformer. The power supply voltage is 25V. The no. of turns on secondary is 50. calculate the efficiency.

Sol: $R_L = 16\Omega$
 $N_1:N_2 = 50:50 = 1:1$

$$R_L' = \left(\frac{N_1}{N_2}\right)^2 R_L = \left(\frac{1}{1}\right)^2 \times 16 \Rightarrow R_L' = 16\Omega$$

$$P_{ac} = \frac{V_m I_m}{2} = \frac{V_m}{2} \cdot \frac{V_m}{R_L} = \frac{V_m^2}{2R_L}$$

$$V_m = V_{cc} = 20\text{V}$$

$$P_{ac} = \frac{(20)^2}{2 \times 16} = 19.53\text{W}$$

$$P_{dc} = \frac{2V_{cc} I_m}{\pi} = \frac{2V_{cc}^2}{\pi R_L} = \frac{2 \times (25)^2}{\pi (16)} = 24.88\text{W}$$

$$\% \eta = \frac{P_{ac}}{P_{dc}} \times 100 = \frac{19.53}{24.88} \times 100 = 78.49\%$$

12. A class B pushpull amplifier supplies power to a load speaker of 10Ω . The op transformer has a turn ratio of $n_1:n_2 = 4:1$ and $\eta = 95\%$. Assume $V_{cc} = 20V$. Calculate the following
 (a) max power op (b) max power dissipation in each transistor. (c) max base current for each transistor.

Sol:

$$R_L = 10\Omega$$

$$N_1:N_2 = 4:1$$

$$R_L' = \left(\frac{N_1}{N_2}\right)^2 R_L = \left(\frac{4}{1}\right)^2 \times 10 = 16 \times 10 = 160\Omega$$

$$P_{ac} = \frac{V_m I_m}{2} = \frac{V_m^2}{2R_L'} = \frac{(20)^2}{2 \times 160} = 1.25W$$

$$\% \eta = \frac{P_{ac}}{P_{dc}} \times 100$$

$$95\% = \frac{1.25}{P_{dc}} \times 100$$

$$P_{dc} = 1.31W$$

$$P_d = P_{dc} - P_{ac}$$

$$= 1.31 - 1.25$$

$$P_d = 0.06W$$

$$(c) \text{ per transistor} = \frac{0.06}{2} = 0.03$$

$$P_{ac} = \frac{V_m I_m}{2}$$

$$I_m = \frac{2P_{ac}}{V_m}$$

$$= \frac{2 \times 1.25}{20}$$

$$I_m = 0.125A$$

$$\therefore I_{cQ} = I_m = 0.125A$$

$$\text{Then } I_{BQ} = \frac{I_{cQ}}{\beta} = \frac{0.125}{25} \quad \left[\text{assume } \beta = h_{fe} = 25 \right]$$

$$I_{BQ} = 5mA$$

RGM COLLEGE OF ENGINEERING & TECHNOLOGY (AUTONOMOUS)
16th May 2023
II B.Tech. II Sem. (R20) Mid-I Examinations
ELECTRONIC CIRCUITS – ANALYSIS AND DESIGN
ECE

Time: 2 Hrs

Total Marks: 20

Note 1: Answer first question compulsorily. (5 x 1 : 5 Marks)

2: Answer Any THREE from 2 to 5 questions. (3 x 5 : 15 Marks)

- 1a Draw the high-frequency hybrid- Π model of BJT.
 - b Give the typical h-parameter values for a transistor at $I_E = 1.3$ mA.
 - c Define common mode rejection ratio (CMRR) of BJT differential Amplifier.
 - d Compare the three BJT configurations interms of A_i , A_v , R_i and R_o .
 - e What is differential amplifier?
- 2
 - a) Draw the block diagram of the basic amplifier circuit [Two-port active network (BJT)] and draw its h-parameter model.
 - b) Explain the analysis of above BJT amplifier circuit to derive the equations for A_i , Z_i , A_v , Y_o in terms of h-parameters.
 - 3
 - a) Draw and explain the small-signal model of the differential amplifier.
 - b) Draw the differential form of the cascode amplifier.
 - 4 For a two stage CE-CC amplifier with $R_s = 1K\Omega$, $R_{C1} = 10K\Omega$ and $R_{E2} = 5K\Omega$. Assume the typical values of h-parameters. Calculate
 - a) Overall Current Gain
 - b) Overall Input Impedance
 - c) Overall Voltage Gain
 - d) Overall Output Impedance.
 - 5
 - a) How to select the values for coupling capacitor C_{c1} and C_{c2} and bypass capacitor C_E for the common-emitter amplifier
 - b) Select the values for coupling capacitors C_{c1} , C_{c2} and bypass capacitor C_E for the common-emitter amplifier, which has $R_s = 100K\Omega$, $R_c = 8K\Omega$, $R_L = 5K\Omega$, $R_{sig} = 5K\Omega$, $\beta = 100$ and $g_m = 40mA/V$, and $r_{\pi} = 2.5K\Omega$. It is frequency to have $f_i = 100Hz$

- xxx -

S.No. 86865

RAJEEV GANDHI MEMORIAL COLLEGE OF ENGINEERING & TECHNOLOGY AUTONOMOUS



Accredited by NAAC of UGC, New Delhi with 'A' Grade:: Accredited by NBA
Affiliated to JNT University Anantapur
Nandyal - 518 501, Kurnool Dist, A.P.

INTERNAL EXAMINATIONS ANSWER BOOKLET

NAME OF THE STUDENT: P. MuniTeja Reg. No. 22095A0422

	1	2	3	4	5
A	2	2	2	5	-
B	1	3	1		
C	1				
D	1				
E	1				
Total	4	5	3	5	
Grand Total :(In Figures)					17
(in Words):					one seven

NAME OF THE SUBJECT: Electronic Circuits ^{Analysis & Design}

INTERNAL EXAM : I / II

Date of Exam: 16/05/23 (FN/AN)

Course : B.Tech. / M.Tech. / MBA / MCA

Year : IInd Sem.: IInd

Branch: Electronic Communication engineering

Signature of the Invigilator

(Start Writing From Here)

C. Common mode Rejection ratio:-

CMRR means Common mode rejection ratio.

It is the ratio of A_d to A_{cm}

$$CMRR = \frac{A_d}{A_{cm}}$$

$$CMRR = \frac{-2g_m R_{SS}}{\frac{\Delta r_d}{r_d}}$$

$$CMRR = \frac{-2g_m R_{SS}}{g_m}$$

CMRR in dB is,

$$CMRR_{dB} = 20 \log \left(\frac{A_d}{A_{cm}} \right)$$

$$CMRR \text{ in dB} = 20 \log (CMRR)$$

d. Compare the three BJT Configurations in terms of A_i , A_v , R_i , and R_o .

Parameters	CB	CE	CC
Voltage gain (A_v)	High	medium	low
Current gain (A_i)	low	High	High
input resistance	low	high	high
output resistance	high	high	high


e. Differential Amplifier:

It is defined as the output is difference between the two i/p signals.


$$V_o = V_{in1} - V_{in2}$$

(or)

$$V_{in2} - V_{in1}$$

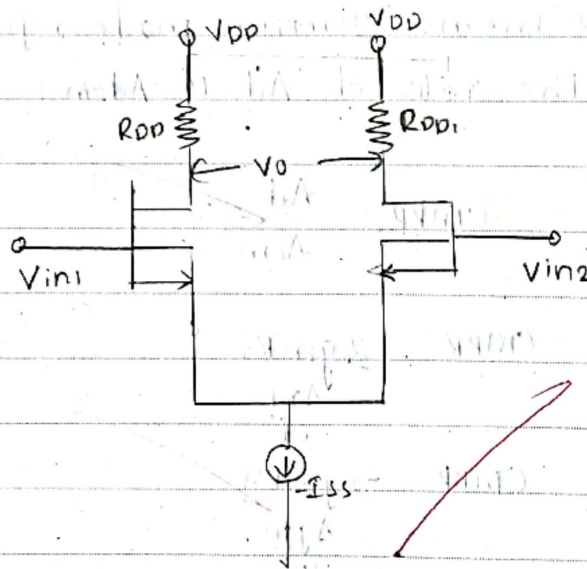

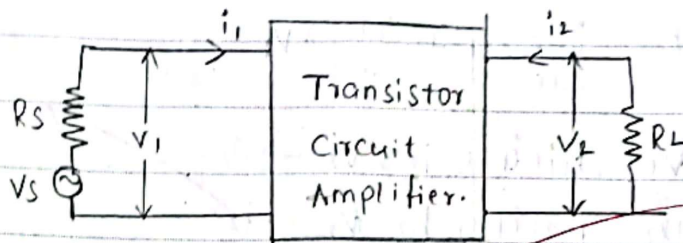2.a) Block diagram of basic amplifier ckt:-




Amplifier means to give the strength to the weak signal is called amplifier

h-parameter model:-

$$V_1 = h_{11}i_1 + h_{12}V_2$$

$$I_2 = h_{21}i_1 + h_{22}V_2$$

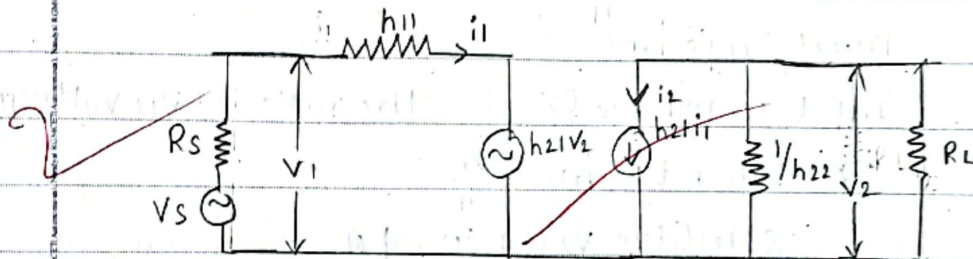

b) The Analysis of above BJT Amplifier, is here, the current passing through npn transistor is positive and pnp transistor is Negative, The voltages are currents i_1, V_1, I_2, V_2 some of them are independent. Here by this voltages and currents the h parameters are derived.

2 parameters - Both are dependent

Here V_1 voltage is function of i_1, V_2

I_2 voltage current is function of i_1, V_2

$$V_1 = f(i_1, V_2)$$

$$I_2 = f(i_1, V_2)$$

By differentiating this equations we get:

$$V_1 = \frac{\partial V_1}{\partial I_1} dI_1 + \frac{\partial V_1}{\partial V_2} dV_2$$

$$I_2 = \frac{\partial I_2}{\partial I_1} dI_1 + \frac{\partial I_2}{\partial V_2} dV_2$$

$$V_1 = h_{11} i_1 + h_{12} V_2 \rightarrow \textcircled{1}$$

$$i_2 = h_{21} i_1 + h_{22} V_2 \rightarrow \textcircled{2}$$

Here, from the above H-parameter diagram we

Short circuit then, $V_2 = 0$

Substitute $V_2 = 0$ in eq ①

$$V_1 = h_{11} i_1 + h_{12}(0)$$

$$h_{11} = \frac{V_1}{i_1}$$

Input impedance:-

Input impedance (Z_i) is the ratio of i/p voltage to

i/p current $h_{11} = \frac{V_1}{i_1}$

Substitute $V_2 = 0$ in eq ②

$$i_2 = h_{21} i_1 + h_{22}(0)$$

$$h_{21} = \frac{i_2}{i_1}$$

Current gain:-

The ratio of input output current to input current it is called ^{forward} current gain (A_i)

$$h_{21} = \frac{i_2}{i_1}$$

Voltage gain:-

We open circuit the above H-parameter diagram

then, $i_1 = 0$

Substitute $i_1 = 0$ in eq ①

$$V_1 = h_{11}(0) + h_{12} V_2$$

$$h_{12} = \frac{V_1}{V_2}$$

It is ratio of i/p voltage to the output current

it is called reverse voltage gain.

Output admittance (Y_o):


Put $i_1 = 0$ in eq (2)

$$i_2 = h_{21}(0) + h_{22}V_2$$

$$h_{22} = \frac{i_2}{V_2}$$

It is the ratio of output current to output voltage it is called output admittance.

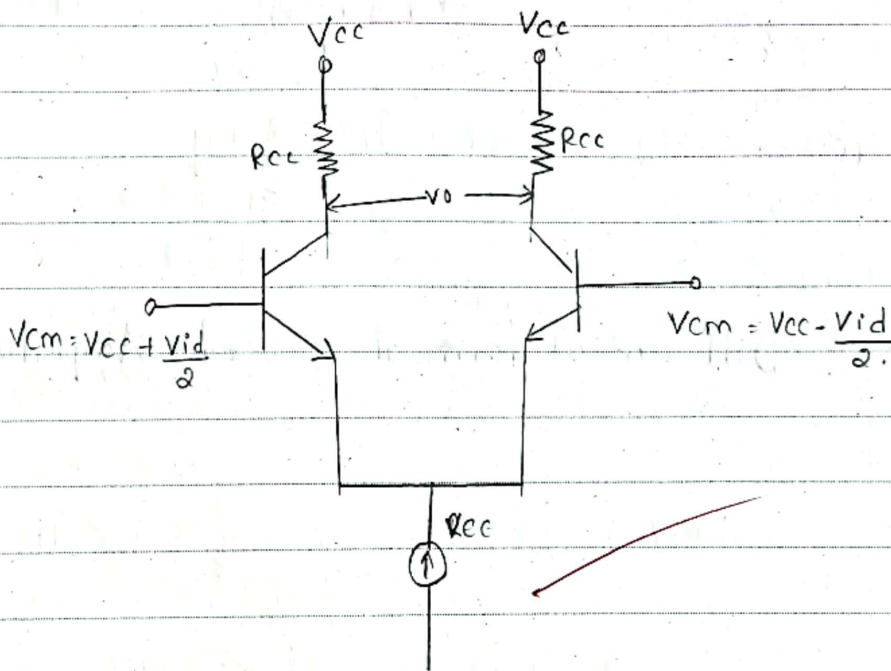3.a. Small signal model of the differential amplifier:-



$$V_i = V_{cm} = V_{cc} + \frac{v_{id}}{2} \quad \& \quad V_{cm} = V_{cc} - \frac{v_{id}}{2}$$


In BJT small signal model A

$$A_d = g_m$$


$$A_d = R_c$$

$$A_d = R_c \beta$$

$$A_d = R_c \beta$$

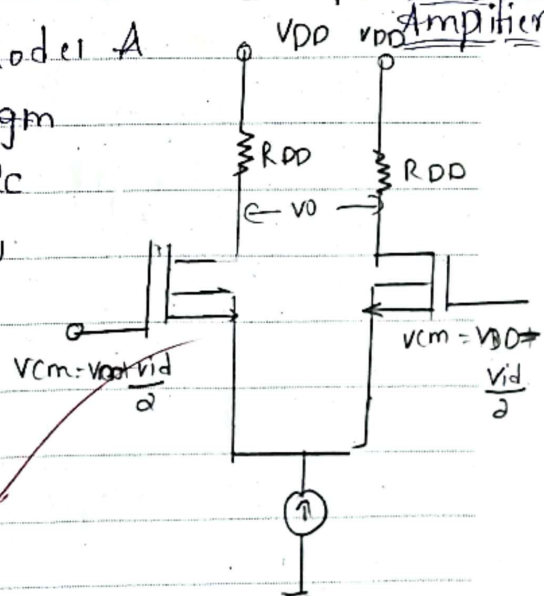

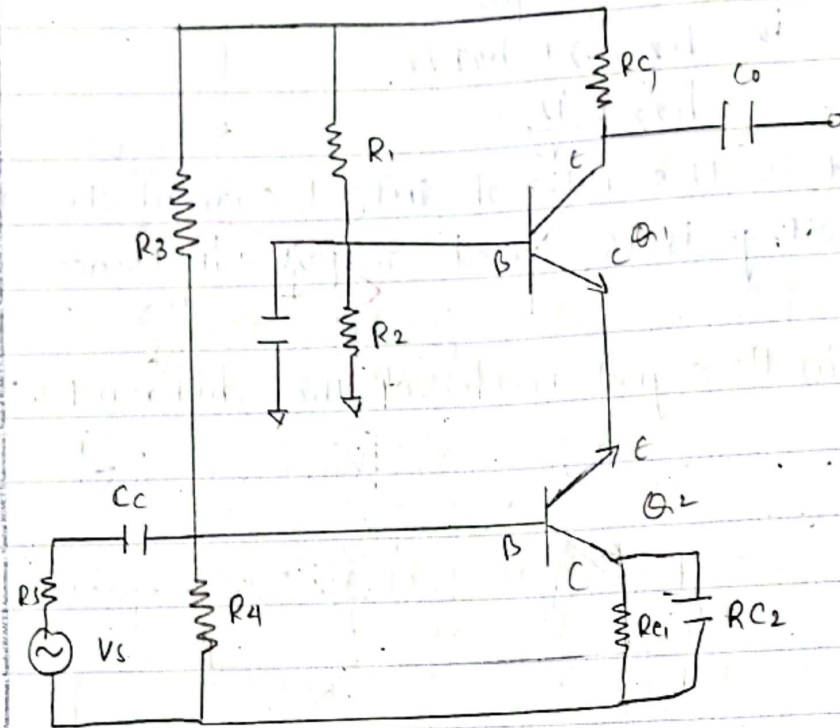b. Draw the differential form of cascode Amplifier.




Differential form of Cascode Amplifier

4.

Given that,

CE-CC amplifier

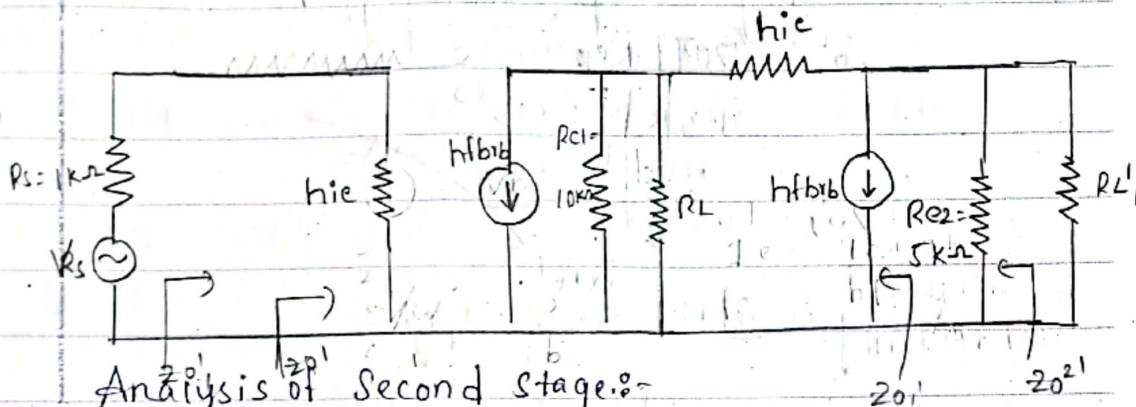$R_s = 1k\Omega, R_{C1} = 10k\Omega, R_{E2} = 5k\Omega$



Analysis of Second Stage:-

$R_L' = R_{E2} = 5k\Omega$

$h_{oe} \cdot R_L' = 20 \times 10^{-6} \times 5 \times 10^3$ here take $h_{oe} = 20 \mu A/V$
 $= 0.1$

Hence we use simplified model.

$A_{\beta 2} = 1 + h_{fe}$

$A_{\beta 2} = 1 + 50$

$A_{\beta 2} = 51$

$A_V = Z_{in}' = h_i e + h_{fe} R_L$
 $= 1.3 \times 10^3 + 50 (5 \times 10^3)$

$Z_{in} = 251.3k\Omega$

$A_{V2} = \frac{-A_{\beta} R_L'}{Z_{in}}$

$= \frac{-51 \times 5 \times 10^3}{251.3 \times 10^3}$

$A_{V2} = -1.014$

$$Z_{02} = \frac{h_{ie2}(1+h_{fe})}{1+h_{fe}}$$

$$Z_{02} = \frac{1.3 \times 10^3 (1+50)}{1+50}$$

$$Z_{01} = 1300 \Omega = 1.3 \text{ K}$$

$$Z_{01}' = Z_{01} \parallel R_{e2} \\ = 1.3 \text{ K} \parallel 5 \times 10^3$$

$$Z_{02}' = 1031.7$$

first
Analysis of second stage:-

$$Z_{in2} = h_{ie}$$

$$Z_{in2} = 1.3 \text{ K}$$

$$A_{\beta} = h_{fe}$$

$$A_{\beta 1} = 50$$

$$A_{V1} = -\frac{A_{\beta} R_L'}{Z_{in}}$$

$$= -\frac{50 \times 10 \times 10^3}{1.3 \text{ K}}$$

$$A_{V1} = -384.61$$

$$Z_0 = \infty$$

$$Z_0' = \infty \parallel R_{c1}'$$

$$Z_0' = \infty \parallel 10 \text{ K}$$

$$Z_{01}' = 10 \text{ K}$$

$$Z_{in1}' = Z_{in} \parallel R_S$$

$$= 1.3 \text{ K} \parallel 1 \text{ K}$$

$$Z_{in1}' = 565.2 \Omega$$

$$\text{Here } R_L' = R_{c1} = 10 \text{ K}$$

$$\text{hence } R_L' = 25 \times 10^{-6} \times 10 \times 10^3$$

a) Overall current gain $A_I = A_{I1} \times A_{I2}$

$= 51 \times 50$

$= 2550$

b) Overall voltage gain $A_V = A_{V1} \times A_{V2}$

$= -1.014 \times 384.61$


$= -389.99$

✓
2

c) Overall input impedance $Z_{in1} = 565.2 \Omega$


d) Overall output impedance $Z_{o2} = 1031.7 \Omega$

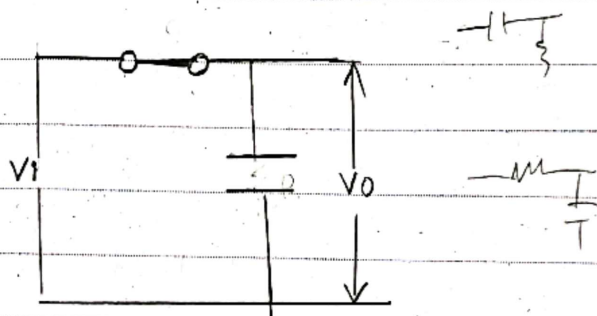1. a. High frequency hybrid- π model of BJT.



High frequency hybrid- π model

⊙

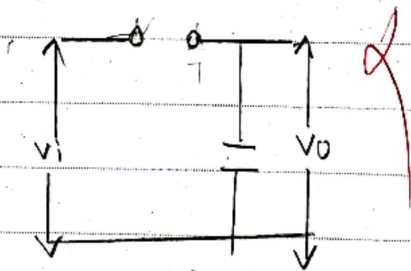

Low frequency hybrid- π model

b) Typical h-parameter values for a transistor

$$I_E = 1.3 \text{ mA}$$

$$h_{ie} = 1.3 \times 10^3 = 1.3 \text{ K}$$

$$h_{oe} = 25 \text{ } \mu\text{A/V}$$

$$h_{re} = 2.3 \times 10^{-4}$$

$$h_{fe} = 50$$

$$h_{oc} = -2.5 \times 10^{-6} \text{ } \mu\text{A/V}$$

$$h_{fc} = 51$$

$$h_{rc} = 1$$

$$h_{ic} = 1.1 \text{ K}$$

RGM COLLEGE OF ENGINEERING & TECHNOLOGY (AUTONOMOUS)

11th July 2023

II B.Tech. II Sem. (R20) Mid-II Examinations

ELECTRONIC CIRCUITS – ANALYSIS AND DESIGN

ECE

Time: 2 Hrs

Total Marks: 20

Note 1: Answer first question compulsorily. (5 x 1 : 5 Marks)

2: Answer Any THREE from 2 to 5 questions. (3 x 5 : 15 Marks)

- 1a List the applications of LC oscillators.
- b In a wein-bridge oscillator, if the value of $R=100k\Omega$ and the frequency of oscillation is 10KHz. Find the value of capacitance.
- c Classify the basic amplifiers based on the comparison between R_s and R_i and between R_o and R_L .
- d Draw the circuit diagram of class A output stage.
- e What is feedback process?
- 2 a) Draw the circuit diagram of transistorized wein-bridge oscillator.
b) Explain the operation of above circuit and derive the expression for frequency of oscillations.
- 3 a) With the help of neat sketches explain the different topologies of a negative feedback amplifier.
b) Prove that change in transfer gain with feedback is less than the change in gain without feedback by a factor $1+A\beta$. Also define sensitivity and desensitivity of transfer gain.
- 4 a) Draw the circuit diagram of Wien bridge oscillator using FET and explain its operation.
b) Mention the comparison between RC phase shift and Wien bridge oscillators.
c) The frequency sensitive arms of the Wien bridge oscillator use $C_1=C_2=0.001\mu F$ and $R_1=10K\Omega$ while R_2 is kept variable. The frequency is to be varied from 10KHz to 50KHz by varying R_2 . Find the minimum and maximum values of R_2 .
- 5 a) Show that the maximum efficiency of push pull class B power amplifier is 78.5%.
b) A loud speaker of 8Ω is connected to the secondary of the output transformer of a class A amplifier circuit. The quiescent collector current is 140mA. The turns ratio of the transformer is 3:1. The collector supply voltage is 10V. If the A.C power delivered to the loud speaker is 0.48W. Calculate
i) DC power input.
ii) Maximum Efficiency
iii) Maximum power dissipation.

- xxx -

S.No. 55745

RAJEEV GANDHI MEMORIAL COLLEGE OF ENGINEERING & TECHNOLOGY AUTONOMOUS



Accredited by NAAC of UGC, New Delhi with 'A' Grade:: Accredited by NBA
Affiliated to JNT University Anantapur
Nandyal - 518 501, Kurnool Dist, A.P.

INTERNAL EXAMINATIONS ANSWER BOOKLET

NAME OF THE STUDENT: B. Jahnvi

Reg. No.

21091A0461

	1	2	3	4	5
A	1	12	12	12	12
B	1	3	3	12	2
C	2			1	
D	1				
E	1				
Total	42	42	42	4	32
Grand Total : (In Figures)					18
(in Words):					one Eight

NAME OF THE SUBJECT: ECA&D

INTERNAL EXAM : I / II

Date of Exam: 11/07/23 (FN/AN)

Course : B.Tech. / M.Tech. / MBA / MCA

Year : II Sem.: II

Branch: ECE

Signature of the Invigilator

(Start Writing From Here)

Q 1) Applications of LC oscillators.

- a) 1) LC oscillators are used to get the sustained frequency oscillations.
- 2) If we use two inductor and one capacitor it is called Hartly oscillator. Two capacitor and one inductor used then it is called colpits oscillation.
- 3) These LC oscillators are used in feedback Amplifier with +ve feedback.

1 b) Given, $R=100k\Omega$, $f=10kHz$.

$$\omega = 2\pi f$$

$$\omega = 2 \times \pi \times 10 \times 10^3 = 62831.8 \text{ rad}$$

For wein bridge oscillation

$$f = \frac{1}{2\pi RC}$$

$$f = \frac{1}{2\pi RC}$$

$$10 \times 10^3 = \frac{1}{2\pi \times 100 \times 10^3 \times C}$$

$$\therefore C = \frac{1}{2\pi \times 100 \times 10^3 \times 10 \times 10^3}$$

$$= \frac{1}{2\pi \times 10^7}$$

$$C = 1.59 \times 10^{-10} \text{ F}$$

1c) Based on basic amplifiers, these can be classified into 4 types.

- 1) Voltage Series Feedback Amplifier
- 2) Current Series Feedback Amplifier
- 3) Voltage Shunt Feedback Amplifier
- 4) Current Shunt Feedback Amplifier

1d)

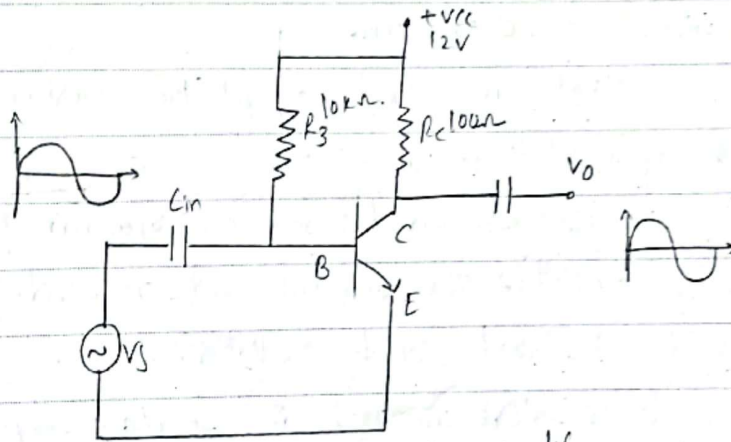


Figure: class A Power Amplifier

1e)

The process of magnitude of o/p signal increases or decreases with respect to i/p signal is called feedback process.

These are of two types

- 1) Positive feedback.
- 2) Negative feedback.

Q. 2a)
A)

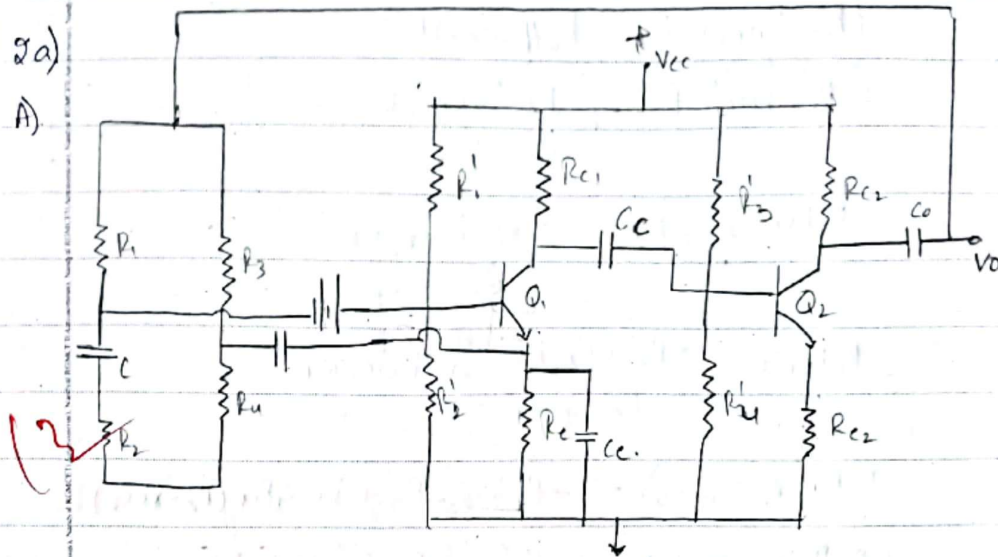


Fig. Wein bridge oscillator.

- 2b) 1) The above fig shows the Wein bridge oscillator. R_1, R_2, R_3, R_4 are the bridge resistors.
- 2) R_1, R_4 are opposite arms to the bridge. R_2 contains one capacitor C to it.
- 3) These Wein bridge oscillator consist of two Transistors with R_e resistor followed by it.
- 4) R'_1, R'_2, R'_3, R'_4 are the opposite resistive term arms to the circuit.
- 5) The output followed to the bridge network.
- 6) Wein bridge oscillators contain two CE amplifiers Transistor.
- 7) R_3, R_4 are opposite to each other. The impedances of product of opposite is equal to the other side opposite Resistor.

$$\frac{Z_1}{Z_2} = \frac{Z_3}{Z_4}$$

Here. $Z_1 = R_1 - j\omega C$

$$Z_2 = R_2 = R_2 // j\omega C$$

$$Z_3 = R_3 = R_3$$

$$Z_4 = R_4 = R_4$$

$$\frac{Z_1}{Z_2} \cdot Z_1 Z_4 = Z_3 Z_2$$

$$(R_1 - j\omega C_1) R_u = (R_2 + j\omega C_1) R_3$$

$$(R_1 - j\omega C_1) R_u = \left(\frac{-R_2 j\omega C_1}{R_2 - j\omega C_1} \right) R_3$$

$$R_1 R_u - j\omega C_1 R_u = \frac{-R_2 j\omega C_1 R_3}{R_2 - j\omega C_1}$$

$$R_1 R_u = \frac{-R_2 j\omega C_1 R_3}{R_2 - j\omega C_1} + j\omega C_1 R_u$$

$$R_1 R_u (R_2 - j\omega C_1) = -R_2 j\omega C_1 R_3 + j\omega C_1 R_u (R_2 - j\omega C_1)$$

$$R_1 R_u R_2 - j\omega C_1 R_1 R_u = -R_2 j\omega C_1 R_3 + j\omega C_1 R_u R_2 + j^2 \omega^2 C_1 C_2 R_u$$

$$R_1 R_u R_2 - j\omega C_1 R_1 R_u = -R_2 j\omega C_1 R_3 + j\omega C_1 R_u R_2 + \omega^2 C_1 C_2 R_u$$

$$R_1 R_u R_2 - \omega^2 C_1 C_2 R_u = -R_2 j\omega C_1 R_3 + j\omega C_1 R_u R_2$$

$$R_u [R_1 R_2 - \omega^2 C_1 C_2] = j\omega C_1 R_u R_2 - R_2 j\omega C_1 R_3$$

$$j\omega C_1 R_u R_2 - R_2 j\omega C_1 R_3$$

$$\Rightarrow R_u [R_1 R_2 - \omega^2 C_1 C_2] - j [R_2 \omega C_1 R_3 + \omega C_1 R_u R_2] = 0 \quad \text{--- (1)}$$

From eq (1), Imaginary part = 0

$$-R_2 \omega C_1 R_3 + \omega C_1 R_u R_2 = 0$$

If imaginary part = 0

$$R_u (R_1 R_2 - \omega^2 C_1 C_2) = 0$$

$$R_1 R_2 = \omega^2 C_1 C_2$$

$$\text{if } R_1 = R_2 = R$$

$$\omega^2 = R_1 R_2 C_1 C_2 \Rightarrow$$

$$C_1 = C_2 = C$$

$$\omega^2 = R^2 C^2$$

$$2\pi f = \frac{1}{R C}$$

$$f = \frac{1}{2\pi R C}$$

$$f = \frac{1}{2\pi R C}$$

$$\left[\begin{aligned} \because \frac{1}{2\pi f} &= R C \\ f^2 &= \frac{1}{2\pi^2 R^2 C^2} \\ f &= \frac{1}{2\pi R C} \end{aligned} \right]$$

which is frequency of oscillations.

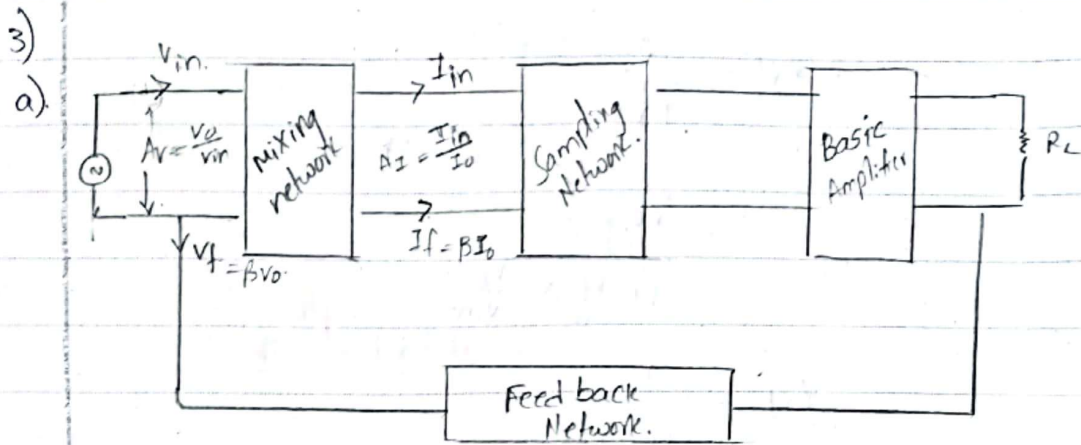


Figure: Topologies of a negative Amplifier

1) The above figure shows the Topologies of a negative feedback Amplifier.

2) To become an feedback amplifier the circuit is mixing with o/p signal and i/p signal. If any sampling voltage and current of to the a circuit we use voltage and current sampling.

3) For the basic Amplifiers the mixing and sampling network give it.

4) By these 3 types of Networks called feedback Amplifier.

5) If the magnitude of o/p signal of voltage (or) current reduces is called -ve feedback Amplifier.

3b) Transfer Gain:- It is between the i/p and output Impedances. $A_v = \frac{V_o}{V_{in}} = z_i$

for the -ve

feedback Amplifier; $V_f = \beta V_o$

$$\therefore A_v = \frac{V_o}{V_s - V_f}, \text{ for } A_{vf} = \frac{V_o}{V_s} = \frac{V_o}{V_{in} + V_f} \quad \text{--- (1)}$$

For eq (1) divide numerator and denominator with V_{in}

$$A_{vf} = \frac{V_o/V_{in}}{V_{in} + V_f/V_{in}}$$

$$A_{vf} = \frac{v_o}{v_{in}}$$

$$= \frac{v_o}{v_{in} + v_f}$$

$$= \frac{v_o}{v_{in} + \frac{v_o}{A_{vf}}}$$

$$A_{vf} = \frac{A}{1 + BA}$$

for o/p impedance $z_{of} = A_{vf} \cdot \frac{A}{1 + AB}$

$$z_{of} = \frac{A}{1 + AB}$$

From the above equation, that change in transfer gain with feedback is less than the change in gain without f_b by a factor $1 + AB$.

Sensitivity, $S = \frac{1}{1 + AB}$

$$D = \frac{1}{1 + AB}$$

Densitivity, $S \cdot D = 1 + AB$ $\left[\frac{1}{S} = D \right]$

open loop gain is A .

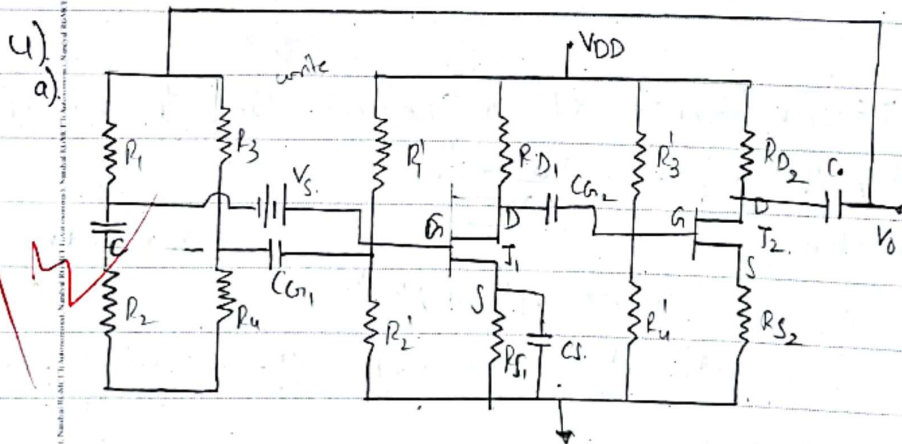


Figure: Wein bridge oscillator using JFET

4 b)

RC Phase shift	Wein bridge oscillator
1) circuit is simple	1) circuit is complex due to bridge network.
2) It is degenerative	2) It is a generative
3) Frequency of oscillations $f = \frac{1}{2\pi RC}$ $f = \frac{1}{2\pi RC}$	3) Frequency of oscillations $f = \frac{1}{2\pi RC}$
4) It is a variable oscillator	4) It is not variable oscillator.
5) Bandwidth Audio (or) Low frequency Range. (20Hz - 20kHz).	5) Radio (or) High frequency Range (20kHz - 20MHz)

4c) Given, $C_1 = C_2 = 0.001 \mu F$

$R_1 = 10k\Omega$ i $f_1 = 10Hz$, $f_2 = 50kHz$.

For RC phase shift oscillator, frequency is

$$f = \frac{1}{2\pi RC}$$

$$\therefore f_1^2 = \frac{1}{4\pi^2 R_1 R_2 C_1 C_2} \Rightarrow (10 \times 10^3)^2 = \frac{1}{4\pi^2 \times 10 \times 10^3 \times R_2 \times 0.001 \times 10^{-6}}$$

$$\therefore R_2 = \frac{1}{(10 \times 10^3)^2 \times 4\pi^2 \times 10 \times 10^3 \times 0.001 \times 10^{-6} \times 0.001 \times 10^{-6}}$$

$$R_2 = \frac{1}{4\pi^2 \times 100 \times 10^6 \times 10^3 \times 10 \times 0.001 \times 10^{-6} \times 0.001 \times 10^{-6}}$$

$$R_2 = 25.33k\Omega$$

$$f_p f_o = 50 \text{ kHz}$$

$$(50 \times 10^3)^2 = \frac{1}{\mu\pi^2 \times 10 \times 10^3 \times R_2 \times 2 \times 10^{-6} \times 10^{-6}}$$


$$R_2 = \frac{1}{\mu\pi^2 \times 2500 \times 10^6 \times 2 \times 10^{-6} \times 10^{-6}}$$

$$R_2 = 10.13 \text{ M}\Omega$$

$\therefore R_2$ value varies from $2.53 \text{ k}\Omega$ to $10.13 \text{ M}\Omega$

5a) 1) Push Pull (class B) Power Amplifier.

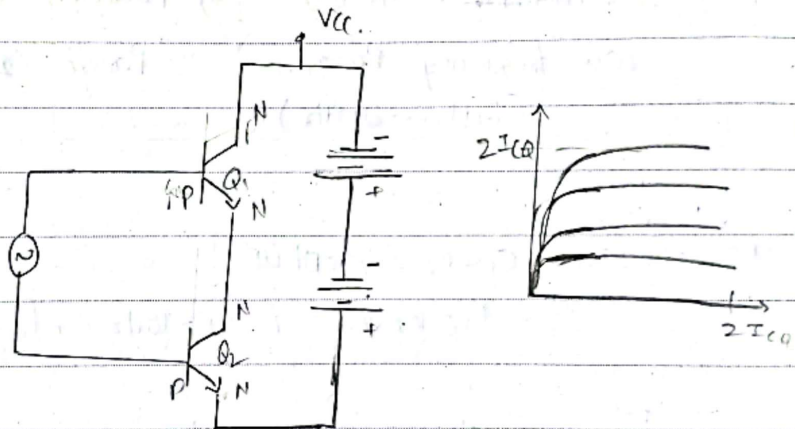2) Push pull class B Power Amplifier consists of two NPN transistors.



DC operation

Apply KVL $V_{CC} = V_{CEQ}$ for Q/P/P voltage is zero.

$$V_m = \frac{2V_m}{2} \quad \text{[For rectified]}$$

for peak to peak voltage.

AC operation

Apply KVL for input $-V_{BE} + V_s - I_B R_B = 0$

$$I_m = \frac{2I_m}{\pi} \quad \text{[For rectified]} \quad \boxed{V_s = V_{CE} - 0.7}$$

$$\text{For } (\%) \text{ efficiency} = \frac{P_{ac}}{P_{dc}} \times 100$$

$$\text{For } P_{dc} = V_{ce_{max}} I_{m_{min}}$$

$$P_{dc} = 2 V_{ceQ} - 0$$

$$P_{dc} = 2 \frac{V_m}{\pi}$$

$$\text{For, } P_{ac} = I_{m_{max}} - I_{m_{min}}$$

$$= 2 I_{m_{max}} - 0$$

$$= 2 \frac{I_m}{\pi}$$

$$\therefore \eta = \frac{P_{ac}}{P_{dc}} \times 100 = \frac{2 \frac{I_m}{\pi}}{2 \frac{V_m}{\pi}} \times 100$$

$$\eta = \frac{2 \frac{\pi}{4} I_m V_m}{(V_{ceQ} - 0)(I_m - 0)} \times 100$$

$$\eta = \frac{\pi}{4} \times \frac{V_{ceQ} I_m}{(V_{ceQ} - I_m - 0)} \times 100$$

$$\therefore \eta = 78.5\%$$

\therefore Maximum efficiency of push pull class B is 78.5%.

5b)

Sol

Given $R_L = 8\Omega$, $I_c = 100\text{mA}$, $\frac{N_1}{N_2} = \frac{3}{8.1}$

$$V_s = 10\text{V}$$


$$P_{ac} = 10\text{W}$$

(i) Dc power input $P_{dc} = V_{ceQ} I_{cQ}$.

$$R_L' = \left(\frac{N_1}{N_2}\right)^2 \times R_L$$

$$= \left(\frac{3}{1}\right)^2 \times 8$$

$$R_L' = 72\Omega$$

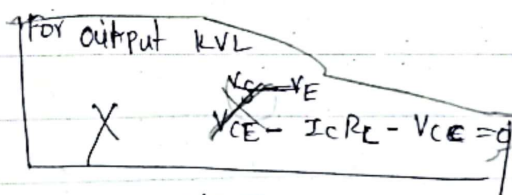

10 -

$$V_{CE} = I_C R_L + V_{CC}$$

$$= 1.4 \times 10^{-3} \times 8 + 10$$

$$V_{CC} = 11.12 \text{ V}$$

$$\text{DC input Power} = 11.12 \text{ V} \times 140 \text{ mA}$$

$$= 1.538 \text{ W}$$

$$(ii) \text{ DC input Power} = \frac{P_{dc}}{P_{ac}} \times 100$$

$$\text{Maximum efficiency } \eta = 0.48 = \frac{11.12 \times 1.4 \times 10^{-3}}{P_{ac}} \times 100$$

$$\eta P_{ac} = \frac{11.12 \times 1.55}{0.48} \times 100$$

$$\eta P_{ac} = \frac{P_{ac}}{P_{dc}} \times 100$$

$$\eta = \frac{0.48}{11.12 \times 1.4 \times 10^{-3}} \times 100$$

$$(ii) \eta = 30\%$$

$$(iii) \text{ Maximum Power dissipation} = P_{dc} - P_{ac}$$

$$= 1.538 - 0.48$$

$$= 1.058 \text{ watts}$$

5b) Given $R_L = 8\Omega$

5b) $\frac{N_1}{N_2} = \frac{3}{1} \quad \therefore R_L' = \left(\frac{N_1}{N_2}\right)^2 \times R_L$
 $= (3)^2 \times 8$
 $R_L' = 72\Omega$

(ii) Dc input power (P_{dc}) = $V_{CEQ} \times I_{CQ}$

Apply KVL

$$V_{CE} - I_C R_L - V_{CE} = 0$$

$$V_{CE} = 140 \times 10^{-3} \times 8 + 10$$

$$= 11.2V$$

$$\therefore P_{dc} = 11.2 \times 140 \times 10^{-3} = 1.56 \text{ watts}$$

(ii) $\therefore \eta = \frac{P_{dc}}{P_{dc}} \times 100 = \frac{0.48}{1.56} \times 100$ $\frac{10.08 - 10}{0.08}$
 V_{CE}
 $= 30.7\%$

(ii) Maximum power dissipation = $P_{dc} - P_{ac}$

$$= 1.56 - 0.48$$

$$= \underline{1.08 \text{ watts}}$$

RGM COLLEGE OF ENGINEERING & TECHNOLOGY (AUTONOMOUS)

20th July 2023

II B.Tech. II Sem. (R20) End Examinations (Regular)
ELECTRONIC CIRCUITS – ANALYSIS AND DESIGN
ECE

Time: 3 Hrs

Total Marks: 70

Note 1: Answer Question No.1 (Compulsory) and 4 from the remaining

2: All Questions Carry Equal Marks

- 1a Define current-shunt negative feedback.
- b Draw the high-frequency hybrid- Π model of BJT.
- c Draw the circuit diagram of class A output stage.
- d When the differential pair can be used as a linear amplifier?
- e Define h_{ic} and h_{re}
- f Define growing oscillations.
- g Define voltage-series negative feedback.
- 2 a) Draw the circuit diagram of RC-phase shift oscillator and explain its operation. (7)
b) Draw the approximate hybrid model of RC phase shift oscillator and derive the output frequency of RC phase shift oscillator. (7)
- 3 a) Draw the circuit diagram of two-stage CE-CB cascode amplifier and its approximate hybrid model. (6)
b) Explain the h-parameter analysis of the above circuit. (8)
- 4 a) Draw the topology of Current Series feedback amplifier. Derive the expressions for input and output impedances with feedback. (8)
b) For a current series feedback amplifier with $R_S=1K\Omega$, $R_E=1.2K\Omega$ and $R_L=2.2K\Omega$. The transistors with parameters are $h_{ic}=1.1K\Omega$ and $h_{fe}=50$. Calculate G_M , β , D , A_{vf} , R_{if} and R_{of} . (6)
- 5 a) Draw a common-source amplifier using the classical biasing arrangement (voltage divider biasing) and draw its equivalent circuit. (6)
b) Analyse the above circuit to find R_{in} , R_o , and Voltage Gain (8)
- 6 A common source amplifier has $C_{C1}=C_{C2}=C_S=1\mu F$, $R_G=10M\Omega$, $R_{Sig}=100K\Omega$, $g_m=2mA/V$, $R_D=R_L=R_S=10K\Omega$. Find
 - a) Mid band gain A_M (3)
 - b) f_{p1} (2)
 - c) f_{p2} (2)
 - d) f_{p3} (2)
 - e) f_z and f_l (5)

- 7 a) Show that the maximum efficiency of series fed class A power amplifier is 25%.
(7)
- b) A class B push pull amplifier supplies power to a resistive load of 12Ω . The output transformer has a turns ratio of 3:1 and efficiency of 78.5%. Assume $V_{cc} = 20V$ and $h_{fe} = 25$. Calculate (7)
- Maximum power output
 - Maximum power dissipation in each transistor.
 - Maximum base and collector currents for each transistor.

- xxx -

20th July 2023

II B.Tech II-Sem (R20) End Examinations (Regular)

ELECTRONIC CIRCUITS - ANALYSIS AND DESIGN


ECE

Code: A0409204R0723

Total Marks: 70


①

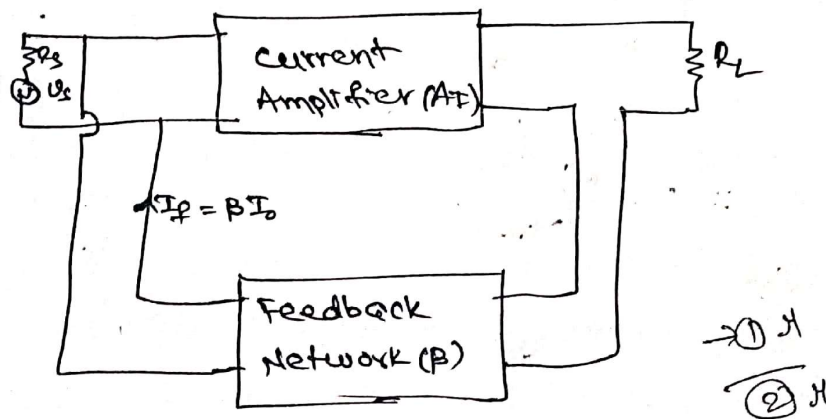② Current shunt feedback amplifier means output current is sampled and the feedback signal is mixed in shunt with input signal. In this the basic amplifier is current amplifier. The below figure shows the topology of the current shunt feedback amplifier.



①

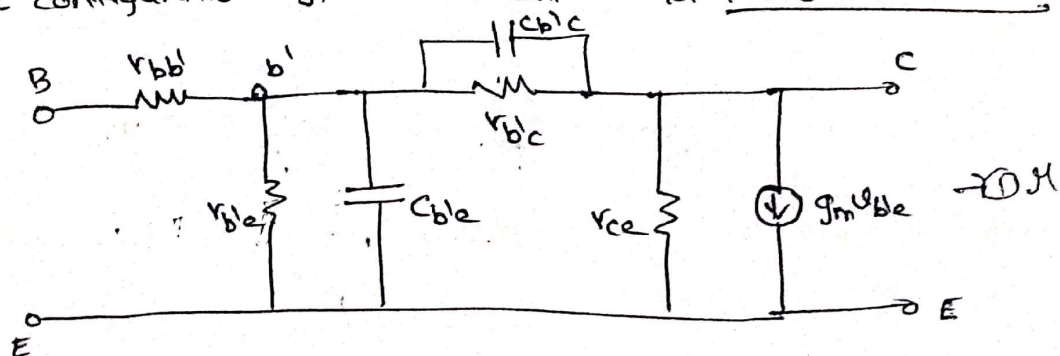② The below figure shows the hybrid- π model for a transistor in CE configuration. It is also called as "Giacobetto model".



Here r_{bb} - Base spreading resistance - 100Ω (2/13)

r_{be} - Resistance between B and E - $1k\Omega$

r_{bc} - Resistance between B and C - $4M\Omega$

r_{ce} - output resistance between C and E - $80k\Omega$

C_{be} - Junction capacitance between B and E - $100pF$

C_{bc} - Junction capacitance between B and C - $3pF$


g_m - Mutual conductance of transistor - $50mA/V$

→ (1) H
 (2) H


(1)

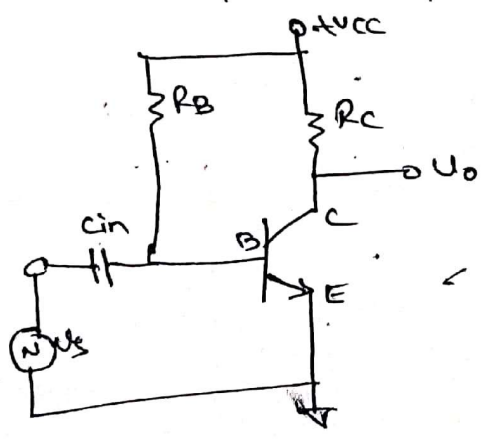(C) The power amplifier is said to be class A amplifier if the Q-point and the input signal are selected such that the output signal is obtained for a full input cycle.

→ A simple fixed bias circuit can be used as large signal class A power amplifier.




(or)

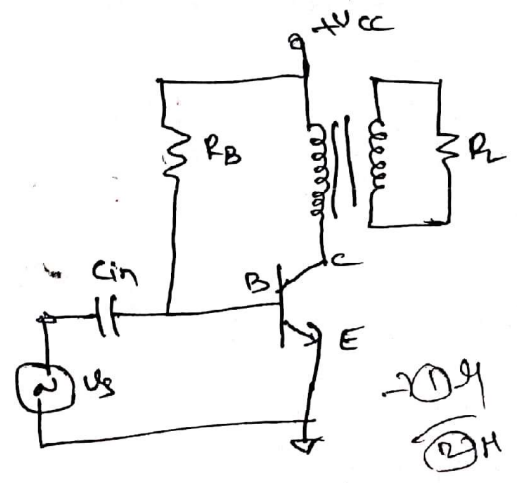

→ (1) H
 (2) H

(1)
 (d)

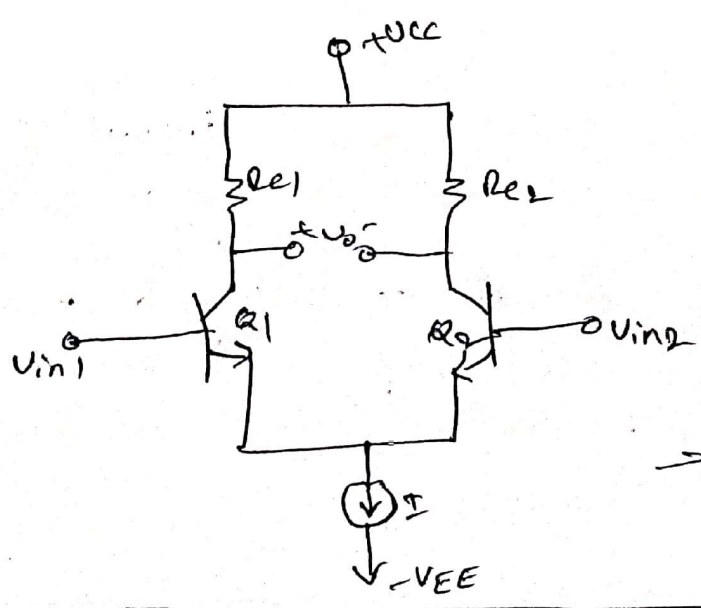

→ (1) H

→ Under BJT differential amplifier, the output voltage is

given by $v_o = (v_{in1} - v_{in2})$

→ If any one of the input voltages is zero and another input varies linearly then the differential amplifier will act as a linear amplifier.

$v_o = v_{in1}$ (or) $v_o = -v_{in2}$ $\frac{-\textcircled{1}}{\textcircled{2}}$

- ①
- ②

hie :- It is called input resistance (or) input impedance of CE transistor. It is the ratio of change in base to emitter voltage (V_{BE}) to change in base current (I_B) for a constant collector voltage. It is also defined as the ratio of input voltage to input current of a CE transistor.

i.e. $h_{ie} = \frac{V_{BE}}{I_B}$ $\rightarrow \textcircled{1}$

Its typical value is 1.1kΩ.

h_{re} :- It is called reverse voltage gain of a CE transistor. It is the ratio of change in base to emitter voltage (V_{BE}) to change in collector to emitter voltage (V_{CE}) at a constant base current.

→ It is also defined as the ratio of input voltage to output voltage of a CE transistor.

i.e. $h_{re} = \frac{V_{BE}}{V_{CE}}$ $\rightarrow \textcircled{1}$


→ It is unitless and its typical value is 2.5×10^{-4} .

$\frac{\textcircled{2}}{\textcircled{2}}$ =

①

②


When the total phase shift around a loop is 0° or 360° and $|A\beta| > 1$, then the output oscillates but the oscillations are of growing type. The amplitude of oscillations goes on increasing as shown in fig.

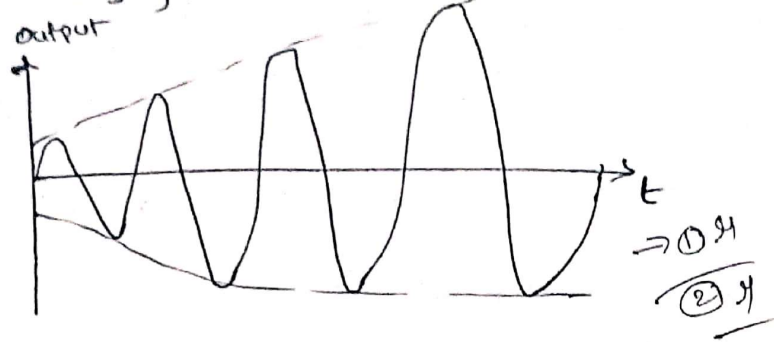

①

②

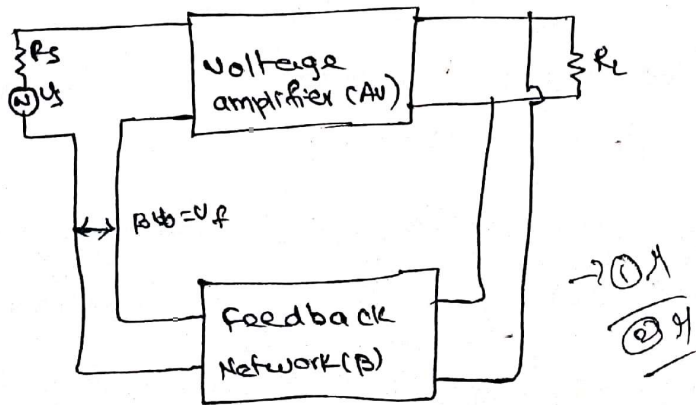In voltage series feedback amplifier, the output voltage is sampled and the feedback signal is mixed in series with the input signal. In this the basic amplifier should be voltage amplifier. The below fig shows the topology of voltage series feedback amplifier.




②

③

RC phase shift oscillator is commonly used sinusoidal low frequency oscillator. It basically consists of an amplifier and a feedback network consisting of resistors and capacitors

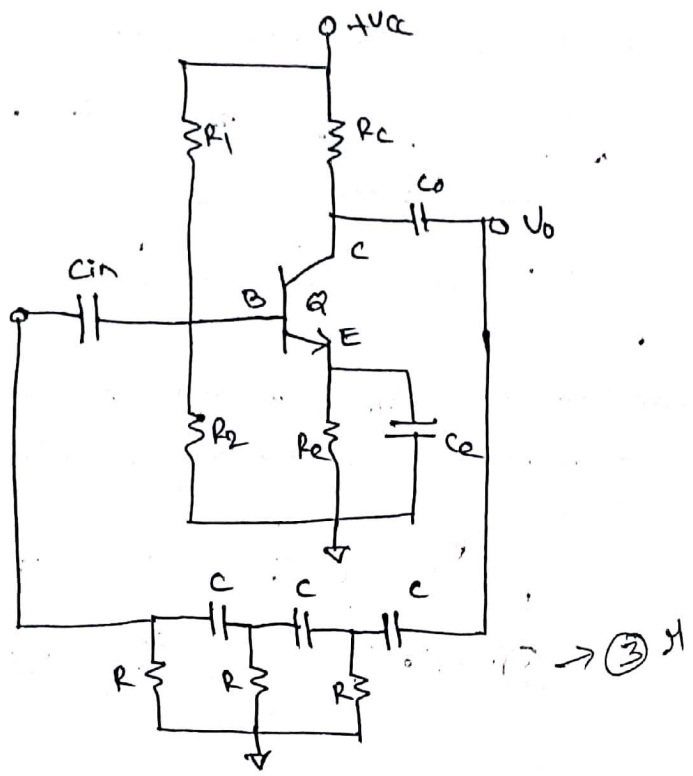arranged in ladder fashion. Hence such an oscillator is also called ladder type RC phase shift oscillator.



- The above circuit shows a practical transistorised RC phase shift oscillator which uses a common emitter single stage amplifier and a phase shifting network consisting of three identical RC sections.
- The output of the feedback network gets loaded due to the low input impedance of a transistor.
- In the above circuit, CE amplifier provides 180° of phase shift and the feedback network provides another 180° of phase shift. So the total phase shift is 0° or 360°.
- In feedback network, we can choose a suitable values of R and C to get the phase shift as 60°.

i.e $\theta = \tan^{-1} \left(\frac{X_c}{R} \right)$


where $X_c = \frac{1}{2\pi f C}$

R is resistance.


→ ⊕
⊕

- ②
- ⑥

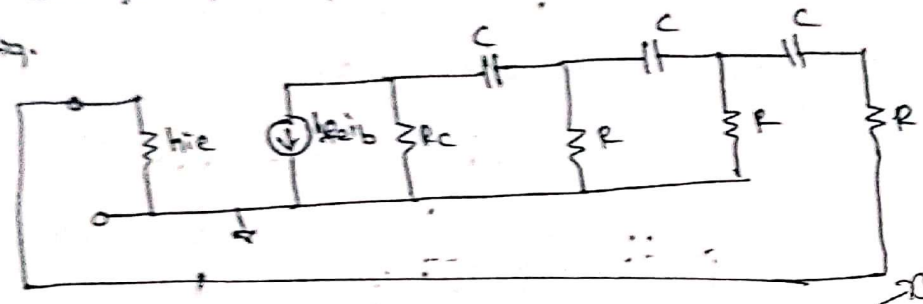By replacing the transistor by its approximate h-parameter model, we get the equivalent oscillator circuit as shown in below fig.



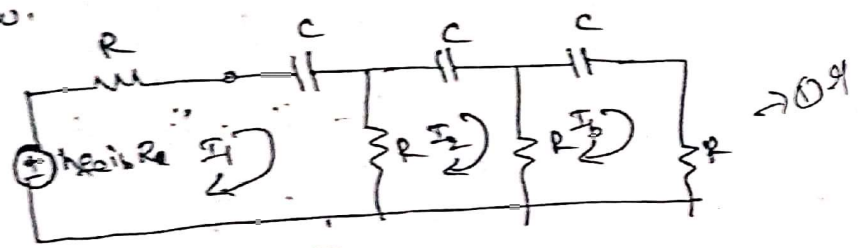By neglecting h_{re} & $1/h_{oe}$, make $R_c = R$ and replace current source by voltage source then the modified equivalent circuit is shown below.



By applying KVL to three loops, we get

For loop ①, $h_{fe} i_b R + R I_1 + \frac{1}{j\omega C} I_1 + R (I_1 - I_2) = 0$

$$(2R + \frac{1}{j\omega C}) I_1 - R I_2 + h_{fe} i_b = 0 \rightarrow ①$$

for loop ② $(I_2 - I_1) R + \frac{1}{j\omega C} I_2 + (I_2 - I_3) R = 0$

$$-R I_1 + (2R + \frac{1}{j\omega C}) I_2 - R I_3 = 0 \rightarrow ②$$

for loop ③, $(I_3 - I_2) R + \frac{1}{j\omega C} I_3 + R I_3 = 0$

$$0 I_1 - R I_2 + (R + \frac{1}{j\omega C}) I_3 = 0 \rightarrow ③$$

From eq. ①, ② & ③, the current I_1, I_2 & I_3 are non vanishing mean those does not becomes zero. So the determinant of coefficients of I_1, I_2 & I_3 must be zero.

$$\begin{vmatrix} 2R - jX_c & -R & h_{fe} R \\ -R & 2R - jX_c & -R \\ 0 & -R & 2R - jX_c \end{vmatrix} = 0 \rightarrow ④$$

$$\Rightarrow (2R - jX_c) [(2R - jX_c)^2 - R^2] + R [-R(2R - jX_c) - 0] + h_{fe} R [R^2 - 0] = 0$$

$$\Rightarrow (2R - jX_c) [4R^2 - j4RX_c - X_c^2] - R^2(2R - jX_c) + h_{fe} R^2 = 0$$

$$\Rightarrow 8R^3 - j8R^2 X_c - 2R X_c^2 - 4R^3 - j4R^2 X_c + 4R X_c^2 + j X_c^3 - j R^2 X_c - 2R^3 - j R^2 X_c + h_{fe} R^3 = 0$$

$$\Rightarrow 4R^3 - 6R X_c^2 + h_{fe} R^3 + j(X_c^3 - 10R^2 X_c) = 0$$

By equating imaginary part to zero.

$$X_c^3 - 10R^2 X_c = 0$$

$$X_c^3 = 10R^2 X_c$$

$$X_c^2 = 10R^2$$

$$X_c = \sqrt{10} R$$

$$\frac{1}{2\pi f_c} = \sqrt{10} R$$


$$f_c = \frac{1}{2\pi \sqrt{10} RC}$$

$$\begin{aligned} &\rightarrow \textcircled{3} \text{ H} \\ &\frac{\textcircled{7} \text{ H}}{7 \times 7} = \textcircled{14} \text{ H} \end{aligned}$$

③


①

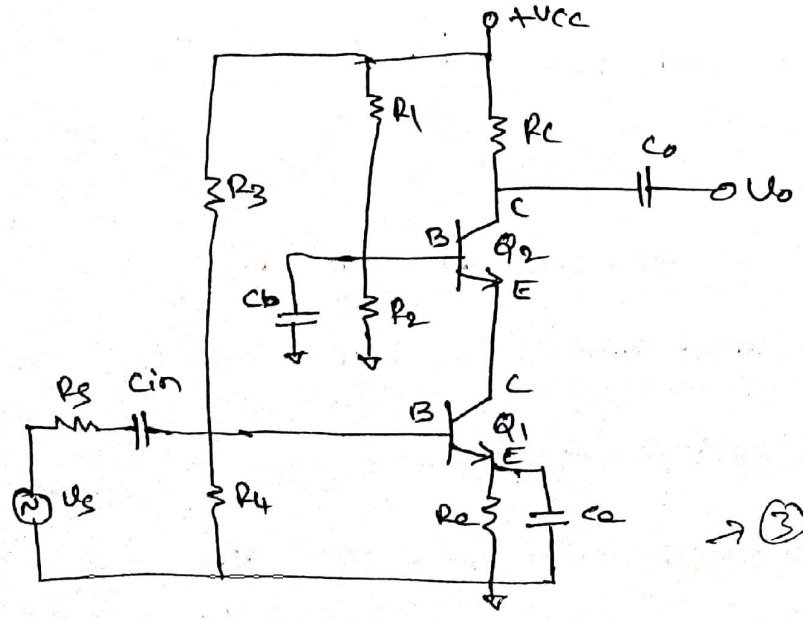The cascode amplifier consists of a common emitter amplifier in series with a common base amplifier. It is one approach to solve the low impedance problem of a common base circuit.



→ ③ H

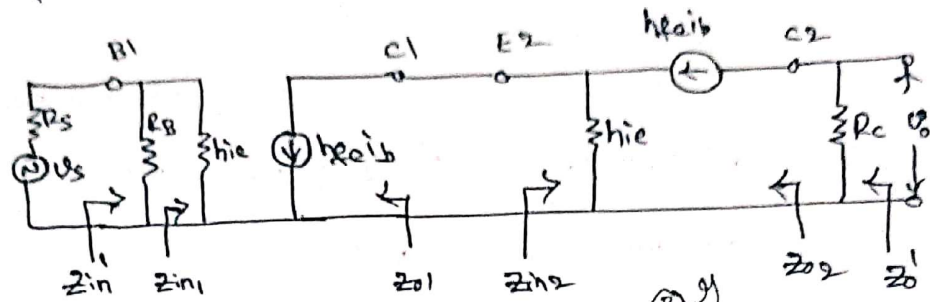The simplified h-parameter equivalent circuit for cascode amplifier is drawn by replacing transistors with their simplified equivalent circuits as shown below.



where $R_B = R_3 \parallel R_4$

③

⑥

Analysis of second stage (CCB amplifier).

① current gain, $A_{I2} = \frac{h_{fe}}{1+h_{fe}}$

② input impedance, $z_{in2} = \frac{h_{ie}}{1+h_{fe}}$

③ voltage gain, $A_{V2} = \frac{A_{I2} R_L}{z_{in2}}$

Analysis of first stage (CE amplifier)

① current gain, $A_{I1} = -h_{fe}$

② input impedance, $z_{in1} = h_{ie}$

③ voltage gain, $A_{V1} = \frac{A_{I1} R_{L1}}{z_{in1}}$

where $R_{L1} = z_{in2}$

overall voltage gain, $A_V = A_{V1} \times A_{V2}$

overall input impedance, $z_{in} = z_{in1} \parallel R_B = z_{in1} \parallel R_3 \parallel R_4$

overall voltage gain, $A_{VS} = \frac{V_o}{V_s} = A_V \times \frac{z_{in}}{z_{in} + R_s}$

overall current gain, $A_{IS} = A_{I1} \times A_{I2}$

$A_{IS} = A_{IS} \times \frac{R_B}{R_B + z_{in1}}$

output impedance, (Z_o):-

$$Z_{o1} = \infty$$

$$Z_{o2} = \infty$$


$$Z_o = Z_{o2} \parallel R_c$$

$$\boxed{Z_o = R_c}$$

$$\frac{-20 \times 1}{7+7} = -1.4 \text{ M}$$


4

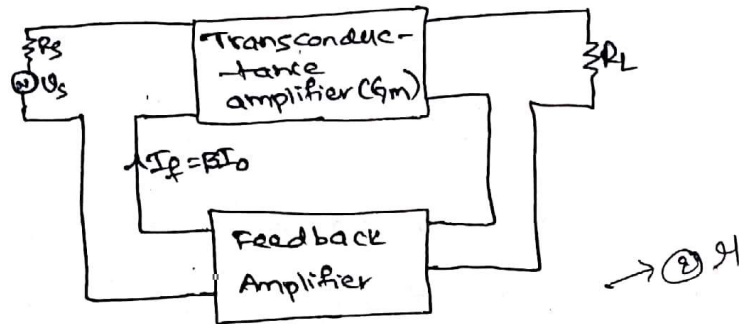(a) Current series feedback amplifier, the output current is sampled and the feedback signal is mixed in series with input. In this, the basic amplifier is transconductance amplifier with gain G_m . The below figure shows the topology of current series feedback amplifier.



Input Impedance (Z_{in}):-

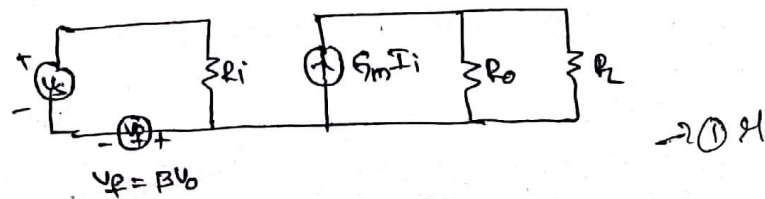The current series feedback topology with amplifier input circuit is represented by Thevenin's equivalent circuit and output circuit by Norton's equivalent circuit.



Let $Z_{in} = \frac{V_{in}}{I_{in}}$ and $Z_{if} = \frac{V_s}{I_{in}}$.

From topology, $V_{in} = V_s - V_f \Rightarrow V_s = V_{in} + V_f$

here $V_f = \beta V_o$ and $I_o = G_m V_{in}$

$$V_s = V_{in} + \beta G_m V_{in}$$

$$\frac{V_s}{I_{in}} = V_{in} (1 + G_m \beta)$$

$$z_{if} = \frac{V_s}{I_{in}} = \frac{V_{in}}{I_{in}} (1 + G_m R)$$

10/12

$$z_{if} = z_{in} (1 + G_m \beta) \rightarrow \textcircled{2} \text{H}$$

Output Impedance (z_o) :- Let z_o & z_{of} are the output impedances of without and with feedback.

$$z_{of} = \frac{V_o}{I_o} \Big|_{V_s=0 \text{ \& } R_L \rightarrow \infty}$$

By using KCL at output circuit

$$I_o = G_m V_{in} + \frac{V_o}{z_o}$$

$$\frac{V_o}{z_o} = I_o - G_m V_{in}$$

$$\text{with } V_s = 0, V_{in} = -V_f = -\beta I_o$$

$$\begin{aligned} \frac{V_o}{z_o} &= I_o - G_m (-\beta I_o) \\ &= I_o + I_o G_m \beta \end{aligned}$$

$$\frac{V_o}{I_o} = z_o (1 + G_m \beta)$$

$$z_{of} = z_o (1 + G_m \beta) \rightarrow \textcircled{3} \text{H}$$

$$\frac{\textcircled{3} \text{H}}{\textcircled{3} \text{H}}$$

(F)

(b)

Given that $R_S = 1 \text{ k}\Omega$, $R_E = 1.2 \text{ k}\Omega$ & $R_L = 2.2 \text{ k}\Omega$.

The transistors with parameters are $h_{ie} = 1.1 \text{ k}\Omega$

$$h_{fe} = 50.$$

$$\text{Open loop gain, } G_m = \frac{I_o}{V_s} = \frac{-h_{fe} i_b}{V_s}$$

$$= \frac{-h_{fe} i_b}{I_b (R_S + h_{ie} + R_E)}$$

$$= \frac{-h_{fe}}{R_S + h_{ie} + R_E} = \frac{-50}{1 \text{ k} + 1.1 \text{ k} + 1.2 \text{ k}}$$

$$G_m = -0.015 \rightarrow \textcircled{2} \text{H}$$

11/17

$$\beta = \frac{V_f}{V_o} = \frac{I_{e} R_e}{I_o} = - \frac{V_o R_e}{V_o} = - R_e = -1.2K$$

$$D = 1 + \beta g_m$$

$$= 1 + (-1.2K)(-0.015)$$

$$= 19.18 \quad \rightarrow \text{D}$$

$$g_{mf} = \frac{g_m}{D} = \frac{-0.15}{19.18} = -0.782 \times 10^{-3}$$

$$A_{uf} = \frac{V_o}{V_s} = \frac{I_o R_L}{V_s} = g_{mf} R_L$$

$$= -0.782 \times 10^{-3} \times 2.2 \times 10^3$$

$$= -1.72 \quad \rightarrow \text{D}$$

$$z_{in} = R_B + h_{ie} + R_e$$

$$= 1K\Omega + 1.1K\Omega + 1.2K\Omega$$

$$= 3.3K\Omega \quad \rightarrow \text{D}$$

$$z_{if} = R z_{in} D = 3.3K(19.18)$$

$$= 63.294K\Omega$$

$$z_o = \infty$$

$$z_{of} = R_o D = \infty$$


$$z_{of}' = R_{of} || R_L = R_L = 2.2K\Omega \quad \rightarrow \text{D}$$

$$\frac{8+6 = 14 \text{ D}}$$


5

a

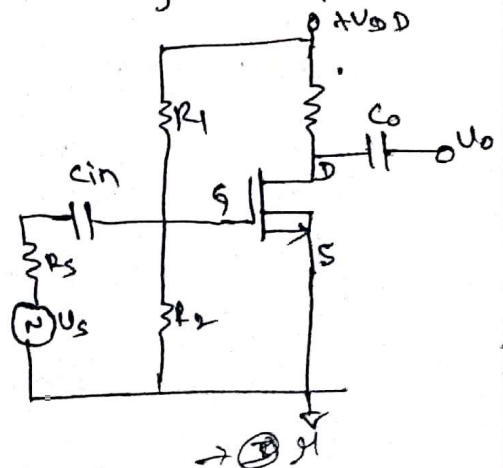In common source amplifier, the input voltage is applied between gate to source terminal and output is taken across drain to source terminal. The figure shows the CS amplifier with voltage divider bias.



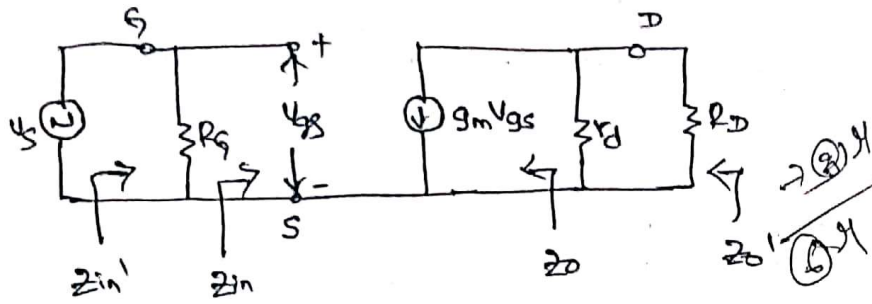→ The AC equivalent circuit of common source amplifier is shown below.



where $R_g = R_1 || R_2$.

(b) Input Impedance (R_{in}):- It is the ratio of input voltage V_{gs} to input current I_g in CS amplifier.

$$\therefore R_{in} = \frac{V_{gs}}{I_g}$$

From input circuit, input terminals are open circuited. i.e. which indicates $i_g = 0$

$$\therefore R_{in} = \frac{V_{gs}}{0}$$

$$R_{in} = \infty$$

Overall input impedance, $R_{in}' = R_{in} || R_s$

$$= \infty || R_s$$

$$R_{in}' = R_1 || R_2$$

Output Impedance (R_o):- It is the ratio of output voltage V_d to output current I_o in CS amplifier with $V_s = 0$.

$$\therefore Z_o = \frac{V_d}{I_o} \Big|_{V_s=0}$$

From output circuit, as $V_{gs} = 0 \Rightarrow g_m V_{gs} = 0$

$$\therefore Z_o = r_d$$

overall output impedance, $z_i' = z_i || R_D$

(3/17)

$$z_i' = r_d || R_D \rightarrow \text{① H}$$

Voltage Gain (A_v) :- It is the ratio of output voltage V_{ds} to input voltage V_{gs} in CS amplifier.

$$A_v = \frac{V_{ds}}{V_{gs}}$$

from output circuit, $V_{ds} = -g_m V_{gs} (r_d || R_D)$

$$A_v = \frac{-g_m V_{gs} (r_d || R_D)}{V_{gs}}$$

$$A_v = -g_m (r_d || R_D)$$

$$\begin{aligned} &\rightarrow \text{② H} \\ &\frac{\text{⑧ H}}{6+8} = \text{⑭ H} \end{aligned}$$

⑥ Given that, a common source amplifier has

$$C_{c1} = C_{c2} = C_s = 1 \mu\text{F}$$

$$R_g = 10 \text{ M}\Omega$$

$$R_D = R_L = R_s = 10 \text{ k}\Omega$$

$$R_{sig} = 100 \text{ k}\Omega$$

$$g_m = 2 \text{ mA/V}$$

① Mid band gain, $A_m = \frac{-R_s}{R_g + R_{sig}} \cdot g_m (R_D || R_L)$

$$= \frac{10 \text{ M}\Omega}{10 \text{ M}\Omega + 100 \text{ k}\Omega} \times 2 \times 10^{-3} (10 \text{ k}\Omega || 10 \text{ k}\Omega)$$

$$= 0.99 \times 2 \times 10^{-3} \times 5 \text{ k}\Omega$$

$$A_m = 9.9 \rightarrow \text{③ H}$$

b

$$f_{p1} = \frac{1}{2\pi (C_{c1} (R_{sig} + R_G))}$$

$$= \frac{1}{2\pi \times 1 \times 10^{-6} (100k + 10M)}$$

$$f_{p1} = 0.0157 \text{ Hz} \rightarrow \text{Ⓜ}$$

c

$$f_{p2} = \frac{g_m + \frac{1}{R_S}}{2\pi C_S}$$

$$= \frac{2 \times 10^{-3} + \frac{1}{10k}}{2\pi \times 1 \times 10^{-6}}$$

$$f_{p2} = 334.22 \text{ Hz} \rightarrow \text{Ⓜ}$$

d

$$f_{p3} = \frac{1}{2\pi C_{c2} (R_D + R_L)}$$

$$= \frac{1}{2\pi \times 1 \times 10^{-6} (10k\Omega + 10k\Omega)}$$

$$= \frac{1}{2\pi \times 10^{-6} \times 20k}$$

$$= 7.95 \text{ Hz} \rightarrow \text{Ⓜ}$$

e

$$f_2 = \frac{1}{2\pi C_S R_S}$$

$$= \frac{1}{2\pi \times 1 \times 10^{-6} \times 10 \times 10^3}$$

$$f_2 = 15.915 \text{ Hz} \rightarrow \text{Ⓜ}$$

$$f_L = \sqrt{f_A^2 + f_{P2}^2 + f_B^2 - 2f_2^2}$$

$$= \sqrt{(0.0157)^2 + (334.22)^2 + (7.95)^2 - 2 \times (15.915)^2}$$

$$f_L = 333.55 \text{ Hz.} \rightarrow \textcircled{3} \text{ M}$$

$$= \textcircled{14} \text{ M}$$

7
a


The circuit represents the directly coupled class A power amplifier as the load resistance is directly connected in the collector circuit.

For d.c operation, the collector supply voltage, V_{CC} and resistance R_B decides the d.c base bias current I_{BQ} .

$$\therefore I_{BQ} = \frac{V_{CC} - 0.7V}{R_B}$$

$$I_{CQ} = \beta I_{BQ}$$

$$V_{CEQ} = V_{CC} - I_{CQ} R_L$$

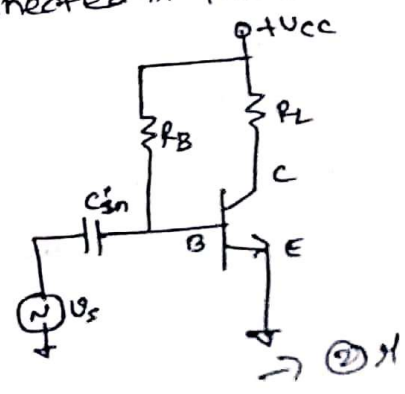

→ The d.c power input is provided by the supply. With no a.c input signal, the d.c current drawn is the collector bias current I_{CQ} . Hence d.c power input is

$$P_{dc} = V_{CC} I_{CQ} \rightarrow \textcircled{1} \text{ M}$$

→ When an input a.c signal is applied, the base current varies sinusoidally. The output current i.e I_c varies around its quiescent value while the output voltage i.e V_{ce} varies around its Q value. The varying output voltage and output current deliver an a.c power to the load.

→ The a.c power delivered to the load is

$$P_{ac} = V_{rms} I_{rms}$$

$$= \frac{V_m}{\sqrt{2}} \times \frac{I_m}{\sqrt{2}}$$

$$= \frac{V_m I_m}{2}$$

$$P_{ac} = \frac{\left(\frac{V_{PP}}{2}\right) \left(\frac{I_{PP}}{2}\right)}{2}$$

$$= \frac{V_{PP} I_{PP}}{8}$$

$$= \frac{(V_{max} - V_{min})(I_{max} - I_{min})}{8} \rightarrow \textcircled{2} \text{H}$$

Efficiency (η) :- It represents the amount of a.c power delivered or transferred to the load from the d.c power input.


$$\% \eta = \frac{P_{ac}}{P_{dc}} \times 100$$

$$\% \eta = \frac{(V_{max} - V_{min})(I_{max} - I_{min})}{8 V_{CC} I_{CQ}} \times 100$$

For maximum efficiency, assume

$$V_{max} = V_{CC} \text{ and } V_{min} = 0$$
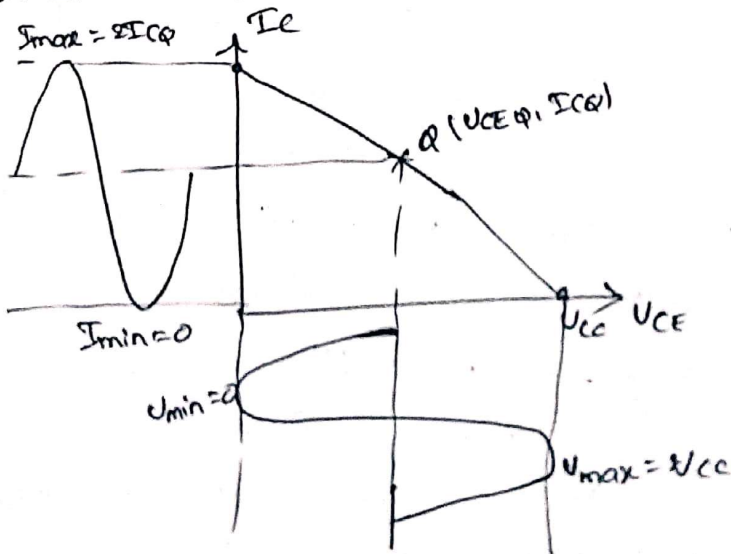
$$I_{max} = 2 I_{CQ} \text{ and } I_{min} = 0$$



$$\% \eta_{max} = \frac{(V_{CC} - 0)(2 I_{CQ} - 0)}{8 V_{CC} I_{CQ}} \times 100$$

$$= \frac{V_{CC} \cdot 2 I_{CQ}}{4 \cdot 8 V_{CC} I_{CQ}} \times 100$$

$$= \frac{1}{4} \times 100$$

$$\% \eta_{max} = 25\%$$

$\rightarrow \textcircled{2} \text{H}$
 $\textcircled{3} \text{H}$

7

5

Given that, $R_L = 12\Omega$, $n = \frac{N_2}{N_1} = \frac{1}{3} = 0.333$

$\% \eta = 78.5\%$ $h_{fe} = 25$, $V_{CC} = 20$.

$$R_L' = \frac{R_L}{(n)^2} = \frac{12\Omega}{0.333^2}$$

$$= 108\Omega \rightarrow \text{①}$$

① $(P_{ac})_{max} = \frac{1}{2} \frac{(V_{CC})^2}{R_L'}$

$$= \frac{1}{2} \frac{(20)^2}{108}$$

$$= 1.8518W$$

But $\% \eta = 78.5\%$

$$P_L = \% \eta \times (P_{ac})_{max}$$

$$= 0.785 \times 1.8518$$

$$P_L = 1.4537W \rightarrow \text{②}$$

② $(P_d)_{max} = \frac{2}{\pi^2} \frac{(V_{CC})^2}{R_L'}$

$$= \frac{2}{\pi^2} \times \frac{(20)^2}{108}$$

$$= 0.7505W$$

$(P_d)_{max}$ per transistor = $\frac{0.7505}{2} = 0.3752W \rightarrow \text{③}$

③ $(P_{ac})_{max} = \frac{V_m I_m}{2}$

$$1.8518 = \frac{20 I_m}{2} \Rightarrow I_m = 0.1851A = I_{e,max}$$

and $(I_b)_{max} = \frac{(I_e)_{max}}{h_{fe}}$

$$= \frac{0.1851}{25}$$

$$(I_b)_{max} = 7.407mA \rightarrow \text{④}$$

Prepared by
 Dr. Y. Madhu Sudhana Reddy,
 Dept. of ECE
 RGRCET.

RGM COLLEGE OF ENGINEERING & TECHNOLOGY (AUTONOMOUS)

20th July 2023

II B.Tech. II Sem. (R19) End Examinations (Supplementary)

ELECTRONICS CIRCUITS-ANALYSIS AND DESIGN

ECE

Time: 3 Hrs

Total Marks: 70

Note 1: Answer Question No.1 (Compulsory) and 4 from the remaining

2: All Questions Carry Equal Marks

- 1a Draw the CB approximated hybrid model.
- b Define voltage amplifier.
- c Draw the circuit diagram of class A output stage.
- d List the demerits of LC oscillators.
- e Define input common mode range of a differential amplifier.
- f Draw the simplified high-frequency T-model of MOSFET.
- g Give the typical h-parameter values for a transistor at $I_E = 1.3 \text{ mA}$.
- 2 a) Draw the circuit of BJT differential amplifier with an active load (4)
b) Explain the operation of above circuit (10)
- 3 a) Write a short on characteristics of power MOSFETs. (10)
b) List the advantages of power MOSFETs and power BJTs. (4)
- 4 For a CB transistor amplifier driven by a voltage source of internal resistance $R_s = 1200 \Omega$, the load $Z_L = 1000 \Omega$. The h- parameters of the transistor are $h_{ib} = 22 \Omega$, $h_{rb} = 3 \times 10^{-4}$, $h_{fb} = -0.98$ and $h_{ob} = 0.5 \mu\text{A/V}$. Compute
a) The current gain A_i (4)
b) The input impedance Z_i (3)
c) Voltage gain A_v and (3)
d) The output impedance Z_o (4)
- 5 a) Explain the effect of negative feedback on frequency response and bandwidth. (6)
b) Explain the analysis of voltage series negative feedback amplifier to find its voltage gain, input resistance and output resistance. (8)
- 6 a) Draw the circuit of BJT cascode amplifier and its high-frequency equivalent circuit. (7)
b) Explain the analysis of high-frequency response of BJT cascode amplifier to derive the equation for midband voltage gain. (7)
- 7 a) Draw the circuit diagram of tuned base oscillator. (4)
b) Explain the operation of above circuit. (10)

- xxx -

20th July 2023

II B-Tech II-Sem. (R19) End Examinations (Supplementary)

ELECTRONIC CIRCUITS - ANALYSIS AND DESIGN

ECE


Code: A040719450723

Total Marks: 70

1

a

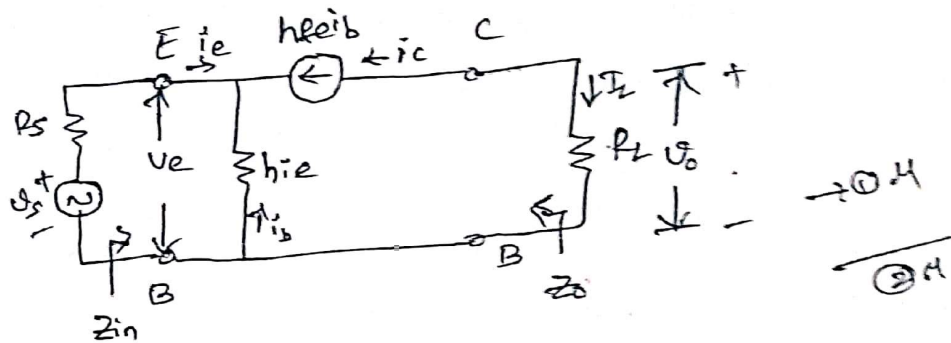The approximate CB model can be drawn by giving input to emitter, taking output at collector and making base common. The below figure shows the approximate CB model. → 1M



1


b

If the amplifier input resistance R_i is large compared to the source resistance R_s then $V_i \approx V_s$. If the external load resistance R_L is large compared to the output resistance R_o of the amplifier, then $V_o \approx A_v V_i \approx A_v V_s$. Such amplifier circuit provides a voltage output proportional to the voltage input and the proportionality factor does not depend on the magnitudes of the R_s and R_L . Hence this amplifier is called voltage amplifier. → 1M

→ An ideal voltage amplifier must have infinite input resistance R_i and zero output resistance R_o .

→ For practical voltage amplifier, we must have

$R_i \gg R_s$ and $R_L \gg R_o$.

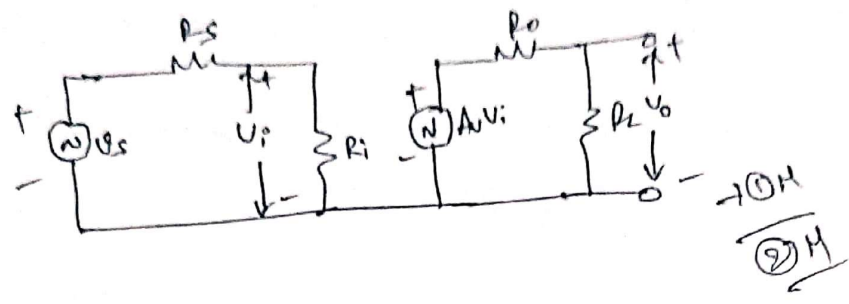

①

②

A simple fixed bias circuit can be used as a large signal class A power amplifier as shown below. The circuit represents the directly coupled class A amplifier as the load resistance is directly connected in the collector circuit.

The circuit is transformer coupled as the load resistance R_L is connected to transformer secondary at collector.

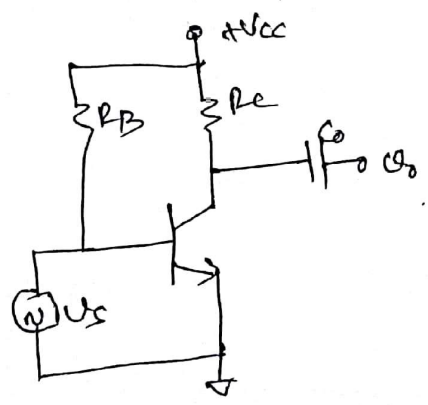


Fig: Direct coupled class A power amplifier

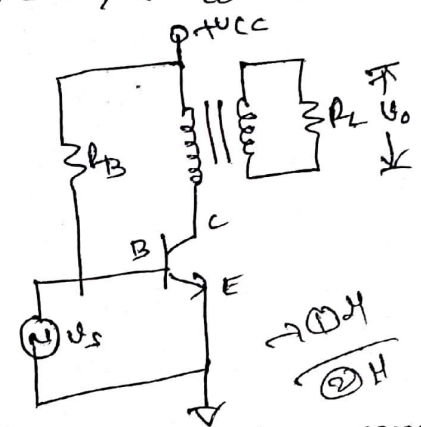


Fig:- Transformer coupled class A power amplifier

①

②

Demerits of LC oscillators:-

- ① The circuits becomes bulky and costly due to inductors.
- ② It provides poor frequency stability.
- ③ These are not able to generate microwave frequencies in the range of 5×10^2 (GHz).

④ These are not able to generate constant amplitude due to inductor losses. → ② H

①
②

An important specification of a differential amplifier is its input common mode range. This is the range of V_{cm} over which the differential pair operates properly. The highest value of V_{cm} is limited by the requirement that Q_1 and Q_2 remaining in saturation, then

$$V_{cmmax} = V_i + V_{DD} - \frac{I}{2} R_D \rightarrow ① H$$


→ The lowest value of V_{cm} is determined by the need to allow for a sufficient voltage across the current source I for it to operate properly. If a voltage V_{CS} is needed across the current source. Then

$$V_{cmmin} = -V_{SS} + V_{GS} + V_E + V_{OV} \rightarrow ① H$$

② H

①
②

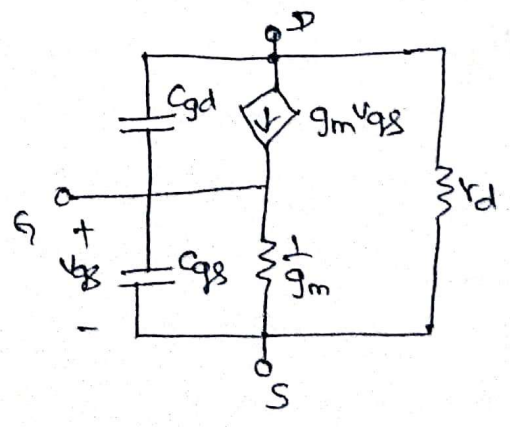The small signal model of MOSFET, including the four capacitances C_{gs} , C_{gd} , C_{sb} and C_{db} is called high-frequency MOSFET model. It is, however, quite complex for manual analysis and its use is limited to computer simulation. So by neglecting C_{sb} and C_{db} then it is called simplified T model shown below.



① H
② H

①
②

The typical h-parameters values for a transistor at $f_c = 1.3 \text{ MHz}$

	CB	CE	CC
h_i	20Ω	$1.1 \text{ k}\Omega$	$1.2 \text{ k}\Omega$
h_f	-0.98	50	-51
h_r	2.9×10^{-4}	2.5×10^{-4}	≈ 1
h_o	$0.49 \mu\text{A/V}$	$25 \mu\text{A/V}$	$25 \mu\text{A/V}$

②
a

The BJT differential amplifier with an active load is shown below. It is formed by transistors Q_1 and Q_2 , loaded by a current mirror formed by transistors Q_3 and Q_4 .

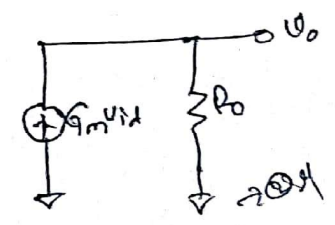
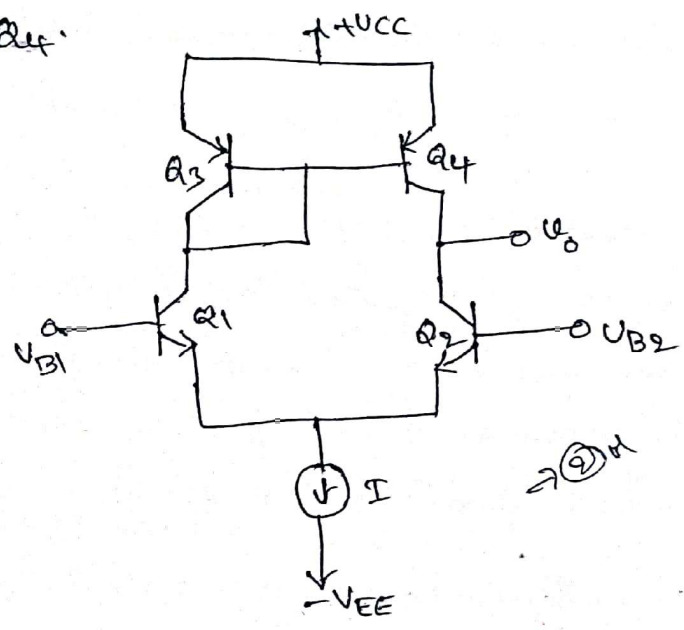


Fig. - Small signal equivalent circuit.

②
b

A simple active load circuit for a differential amplifier is the current mirror active load as shown in fig. The active load comprises of transistors Q_3 and Q_4 with the transistor connected as a diode with its base and collector shorted. The circuit is shown to drive a load R_L .

→ When an a.c input voltage is applied to the differential amplifier, the various currents of the circuit are given by

$$I_{C4} = I_{C3} = I_{E1} = g_m \frac{V_{id}}{2} \quad \rightarrow \textcircled{1}$$

where $I_{C4} = I_{C3}$, due to current mirror action.

$$I_{E2} = -g_m \frac{V_{id}}{2} \quad \rightarrow \textcircled{2}$$

→ We know that the load current I_L entering the next stage is

$$I_L = I_{E2} - I_{C4} = -g_m \frac{V_{id}}{2} - g_m \frac{V_{id}}{2} = -g_m V_{id}$$

Then the output voltage from the differential amplifier is given by

$$V_o = -I_L R_L = g_m V_{id} R_L \quad \rightarrow \textcircled{3}$$

The amplifier can amplify the differential input signals and it provides single ended output with a ground reference since the load R_L is connected to only one output terminal.

This is made possible by the use of the current mirror active load.

→ The output resistance R_o of the circuit is that offered by the parallel combinations of transistors Q_2 and Q_4 . It is given

$$R_o = r_{o2} || r_{o4} \quad \rightarrow \textcircled{4}$$

→ The differential amplifier using active load provides high voltage gain to the differential input signal and a single ended output that is referred to the ground is obtained.

→ The differential amplifier which provides conversion for a differential signal to a single ended signal is necessary in differential input signal ended output amplifiers. The changes in the common-mode signal of the bias current source. This includes a change in I_{E2} and an identical change in I_{C4} . The change in I_{E1} will then produce a change in the pnp load devices and thereby a change in I_{C4} , which is the collector current Q_4 . The current I_{C4} is in such a direction as to cancel the change in I_{E2} . As a result, any common mode input does not cause a change in output.

$$\begin{aligned} &\rightarrow \textcircled{4} \\ &\textcircled{10} \rightarrow 4 + 10 = \textcircled{14} \end{aligned}$$

3

a

Power MOSFETs have in the past number of years gained popularity in the design of power electronic circuits. This is a result of the following properties.

① Unlike ^{power} BJTs, MOSFETs have threshold voltages in the range of 1V to 4V. In saturation, the drain current is related to V_{GS} by the square law characteristics given by

$$I_D = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{GS} - V_t)^2 \quad \rightarrow \text{②}$$

where I_D is the drain current


W is the width of the channel

L is the length of the channel

V_t is threshold voltage

V_{GS} is gate to source voltage $\rightarrow \text{③}$

\rightarrow However, the $I_D - V_{GS}$ characteristics becomes linear for larger values of V_{GS} . The linear portion of the characteristics occurs as a result of the high electric field along the short channel, causing the velocity of charge carriers to reach an upper limit, a phenomenon known as velocity saturation. The linear $I_D - V_{GS}$ relationship implies a constant g_m in the velocity saturation region.

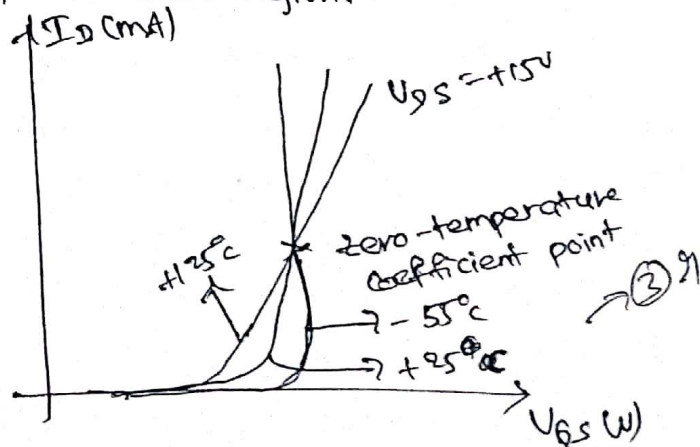

→ of considerable interest in the design of MOS power circuits is the variation of the MOSFET characteristics with temperature. Observe that there is a value of V_{GS} (in the range of 4V to 6V for most power MOSFET) at which the temperature coefficient of I_D is zero. At higher values of V_{GS} , I_D exhibits a negative temperature coefficient.

→ This is a significant property. It implies that a MOSFET operating beyond the zero-temperature-coefficient point does not risk the possibility of thermal runaway. This is not the case, however, at low currents. In that region, the temperature coefficient of I_D is positive and the power MOSFET can easily suffer thermal runaway.

→ (4) 4
(15) 4

③

⑥ Advantages of power MOSFETs and Power BJTs!:-

- ① Power MOSFETs do not require dc gate drive current. This greatly simplifies the design of the driving circuitry.
- ② MOSFETs can operate at much higher switching speeds than BJTs, a definite advantage of for power circuits employing switching
- ③ MOSFETs do not suffer from secondary breakdown, thus benefiting from an extension of SOA.
- ④ The thermal characteristics of the MOSFET as well we shall see shortly, are superior to those of the BJT.
- ⑤ To support higher voltages without device breakdown, the base is made wider and the collector is made thicker and its doping lighter.


→ (4) 4
10 + 4 = (14) 4

4

For CB transistor amplifier, given that

$R_s = 1200 \Omega$, $Z_L = 1000 \Omega$. The h-parameters of the transistor are $h_{ib} = 22 \Omega$, $h_{rb} = 3 \times 10^{-4}$, $h_{fb} = -0.98$ and $h_{ob} = 0.5 \mu A/V$.

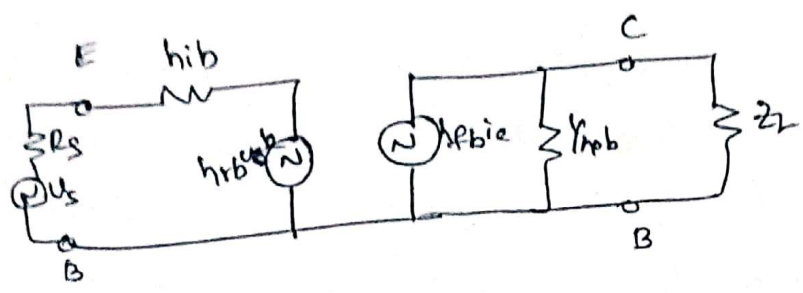From given data the h-parameter model of the amplifier is



a) Current Gain, $A_I = \frac{-h_{fe}}{1 + h_{ob} R_L}$

$$= \frac{-(-0.98)}{1 + 0.49 \times 10^{-6} \times 1 \times 10^3}$$

$$= \frac{0.98}{1 + 0.49 \times 10^{-3}}$$

$A_I = 0.98$

→ 4) 21

b) Input Impedance, $Z_{in} = h_{ib} - \frac{h_{fb} h_{rb}}{\frac{1}{R_L} + h_{ob}}$

$$= 22 \Omega - \frac{(-0.98)(3 \times 10^{-4})}{\frac{1}{1k} + 0.49 \times 10^{-6}}$$

$$= 22 \Omega + \frac{0.98 \times 3 \times 10^{-4}}{10^{-3} + 0.49 \times 10^{-6}}$$

$Z_{in} = 22.294 \Omega$


→ 3) 21

4

For CB transistor amplifier, given that

$R_s = 1200 \Omega$, $Z_L = 1000 \Omega$. The h-parameters of the transistor are $h_{ib} = 22 \Omega$, $h_{rb} = 3 \times 10^{-4}$, $h_{fb} = -0.98$ and $h_{ob} = 0.5 \mu A/V$.

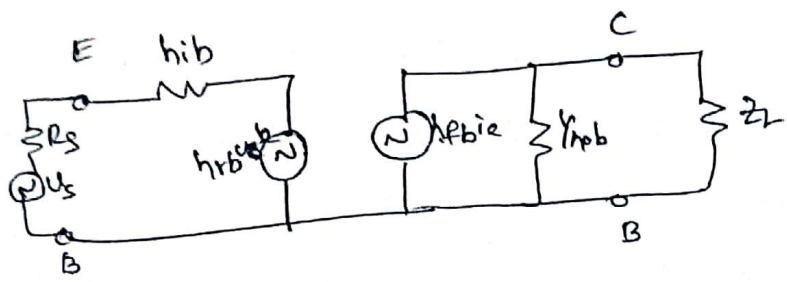From given data the h-parameter model of the amplifier is



a) Current Gain, $A_I = \frac{-h_{fe}}{1 + h_{ob} R_L}$

$$= \frac{-(-0.98)}{1 + 0.49 \times 10^{-6} \times 1 \times 10^3}$$

$$= \frac{0.98}{1 + 0.49 \times 10^{-3}}$$

$A_I = 0.98$ → 4.24

b) Input Impedance, $Z_{in} = h_{ib} - \frac{h_{fb} h_{rb}}{\frac{1}{R_L} + h_{ob}}$

$$= 22 \Omega - \frac{(-0.98)(3 \times 10^{-4})}{\frac{1}{1k} + 0.49 \times 10^{-6}}$$

$$= 22 \Omega + \frac{0.98 \times 3 \times 10^{-4}}{10^{-3} + 0.49 \times 10^{-6}}$$

$Z_{in} = 22.294 \Omega$ → 4.24

c

Voltage gain, $A_v = \frac{+A_{\beta} P_L}{Z_{in}}$

$$= \frac{0.98 \times 1 \times 10^3}{22.294}$$

$$A_v = 44$$

→ 3) 1

d

Output Impedance, $Z_o = \frac{1}{h_{ob} - \frac{h_{fb} h_{rb}}{h_{ib} + R_s}}$

$$= \frac{1}{0.49 \times 10^{-6} - \frac{(-0.98)(3 \times 10^4)}{22 + 1200}}$$

$$= \frac{1}{0.49 \times 10^{-6} + 0.0023 \times 10^{-4}}$$

$$Z_o = 1.388 \text{ M}\Omega$$

→ 4) 1

14) 1

5

a

Effect of Negative feedback on frequency response and Bandwidth:-

we know that $A_f = \frac{A}{1+AB}$

using this equation, we can write

$$A_{fmid} = \frac{A_{mid}}{1+A_{mid}B}, \quad A_{flow} = \frac{A_{low}}{1+A_{low}B}, \quad A_{fhigh} = \frac{A_{high}}{1+A_{high}B}$$

Lower cut off frequency:- we know that, the relation between gain at low frequency and gain at mid frequency is given as

$$A_{low} = \frac{A_{mid}}{1-j\left(\frac{f_L}{f}\right)} \quad \text{then} \quad A_{flow} = \frac{\frac{A_{mid}}{1-j\left(\frac{f_L}{f}\right)}}{1 + \frac{A_{mid}}{1-j\left(\frac{f_L}{f}\right)} \cdot B}$$

→ 1) 1

$$= \frac{A_{mid}}{1 - j\left(\frac{f_L}{f}\right) + A_{mid}B} = \frac{A_{mid}}{(1 + A_{mid}B) - j\left(\frac{f_L}{f}\right)}$$

Dividing numerator and denominator by $(1 + A_{mid}B)$

$$A_{f_{low}} = \frac{\frac{A_{mid}}{1 + A_{mid}B}}{1 - j\left(\frac{\frac{f_L}{1 + A_{mid}B}}{f}\right)} = \frac{A_{f_{mid}}}{1 - j\left(\frac{f_{LF}}{f}\right)}$$

where $f_{LF} = \frac{f_L}{1 + A_{mid}B}$ $\rightarrow \text{②}$

Upper cutoff frequency! — we know that, the relation between gain at high frequency and gain at mid frequency is given as

$$A_{high} = \frac{A_{mid}}{1 - j\left(\frac{f}{f_H}\right)} \quad \text{then}$$

$$A_{f_{high}} = \frac{\frac{A_{mid}}{1 - j\left(\frac{f}{f_H}\right)}}{1 + \frac{A_{mid}B}{1 - j\left(\frac{f}{f_H}\right)}} = \frac{A_{mid}}{(1 + A_{mid}B) - j\left(\frac{f}{f_H}\right)}$$

Dividing numerator and denominator by $(1 + A_{mid}B)$,

$$A_{f_{high}} = \frac{\frac{A_{mid}}{1 + A_{mid}B}}{1 - j\frac{f}{(1 + A_{mid}B)f_H}} = \frac{A_{f_{mid}}}{1 - j\frac{f}{f_{HF}}}$$

where $f_{HF} = (1 + A_{mid}B)f_H$.

The bandwidth of the amplifier is given as


$$BW = f_H - f_L$$

The bandwidth with feedback is given as

$$(BW)_f = f_{HF} - f_{LF} = (1 + A_{mid}B)f_H - \frac{f_L}{1 + A_{mid}B}$$

$\rightarrow \text{③}$

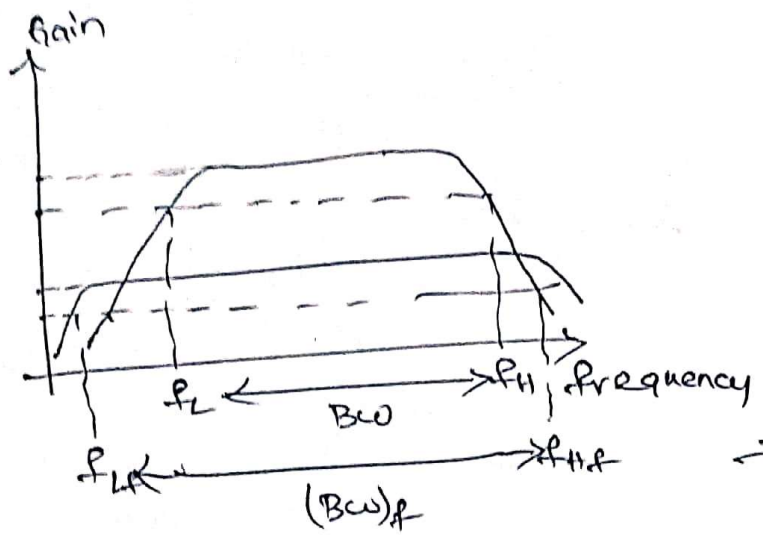→ It is clear that $(f_{Hf} - f_{Lf}) > (f_H - f_L)$ and hence bandwidth of amplifier with feedback is greater than bandwidth of amplifier without feedback.




→ 10%
 (6) 91

5
 b

The practical example of voltage series feedback amplifier is the emitter follower (or) cc amplifier.

→ In this figure, R_e resistor is the feedback resistor because it is common to both i/p & o/p equations.

$V_o = I_e R_e$ and $V_{be} = I_b R_e$

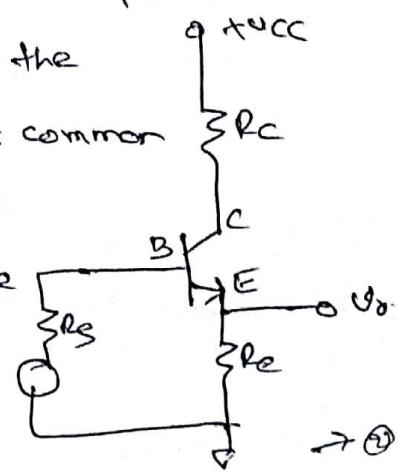

From this, $V_f = V_o$,

$B = \frac{V_f}{V_o} = 1$

Voltage gain, $A_v = \frac{V_o}{V_{in}}$

$= \frac{h_{fe} i_b R_e}{(R_s + h_{ie}) i_b}$

$A_v = \frac{h_{fe} R_e}{R_s + h_{ie}}$

→ 10% 91

$$D = 1 + A_{vB}$$

$$= 1 + \frac{h_{fe} R_e}{R_s + h_{ie}}$$

$$= \frac{R_s + h_{ie} + h_{fe} R_e}{R_s + h_{ie}}$$

$$A_{vF} = \frac{A_v}{D} = \frac{\frac{h_{fe} R_e}{R_s + h_{ie}}}{\frac{R_s + h_{ie} + h_{fe} R_e}{R_s + h_{ie}}}$$

$$A_{vF} = \frac{h_{fe} R_e}{R_s + h_{ie} + h_{fe} R_e} \rightarrow \text{② M}$$

Input Impedance, $Z_{in} = R_s + h_{ie}$.

$$Z_{iF} = Z_{in} (1 + A_{vB}) = Z_{in} D.$$

$$= (R_s + h_{ie}) \cdot \frac{R_s + h_{ie} + h_{fe} R_e}{R_s + h_{ie}}$$

$$Z_{iF} = R_s + h_{ie} + h_{fe} R_e \rightarrow \text{① M}$$

Output impedance, $Z_o = \infty$

$$Z_{oF} = \frac{Z_o}{D} = \frac{\infty}{D} = \text{undetermined.}$$

To determine Z_{oF} , make $R_e \rightarrow \infty$


$$Z_{oF} = \lim_{R_e \rightarrow \infty} \left(\frac{(R_s + h_{ie}) R_e}{R_s + h_{ie} + h_{fe} R_e} \right)$$

$$= \frac{R_e (R_s + h_{ie})}{R_e (h_{fe} + \frac{R_s + h_{ie}}{R_e})}$$

$$Z_{oF}' = \frac{R_s + h_{ie}}{h_{fe}} \rightarrow \text{① M}$$


$$\frac{\text{① M}}{\text{② M}} \times B = \text{② M}$$

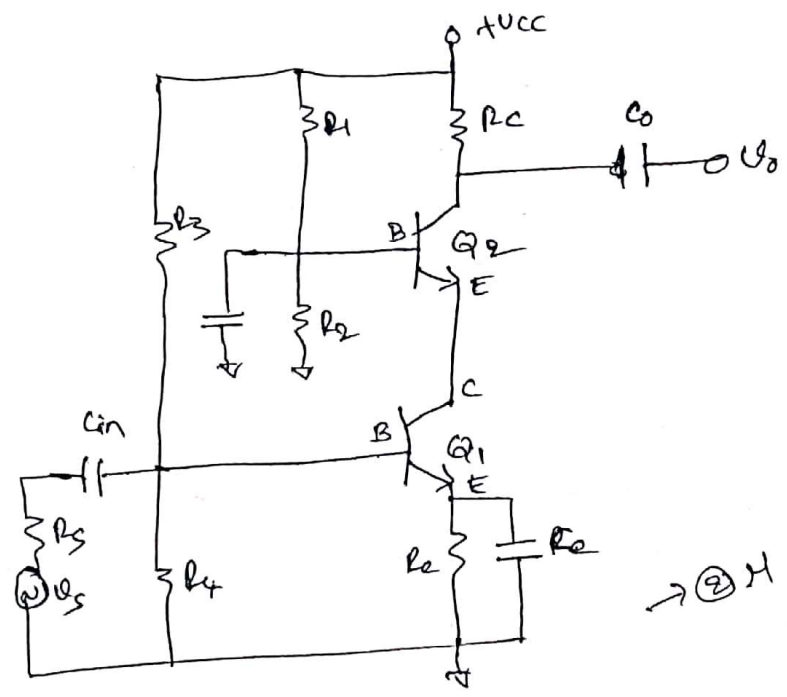- ⑥ The cascode amplifier consists of a common emitter amplifier stage in series with a common base amplifier. It is one approach to solve the low impedance problem of a common base circuit,
- ①



→ Transistor Q_1 and its associated components operate as a common emitter amplifier stage, while the circuit of Q_2 functions as a common base output stage.

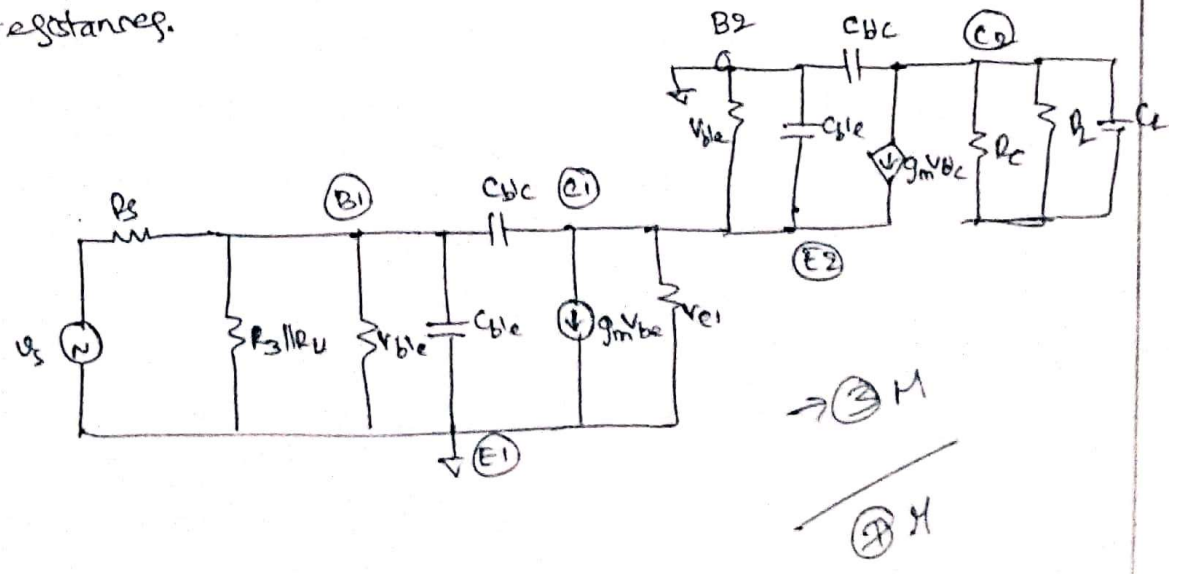
High frequency equivalent circuit consists of hybrid- π model of transistor by considering the junction capacitances and resistances.



(a)

The BJT cascode amplifier is shown below.

(b)

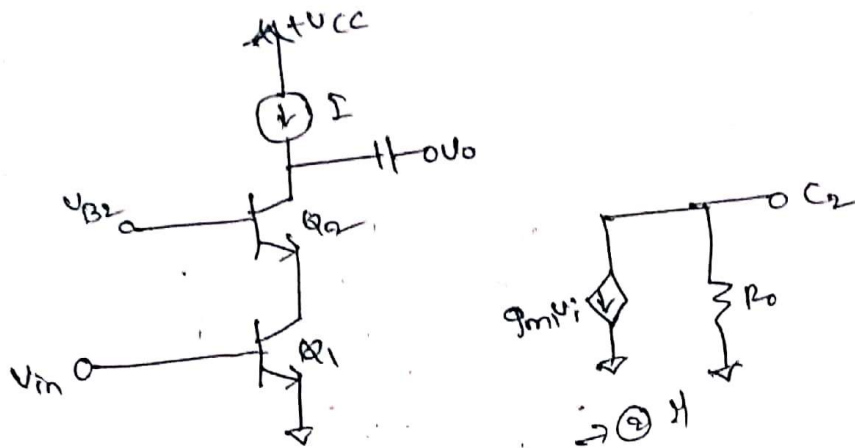

→ Voltage V_{BE} is a dc bias voltage for the CB cascode transistor Q_2 . The circuit is very similar to the MOS cascode and the small signal analysis will follow in a parallel fashion. First, note that the input resistance of the bipolar cascode amplifier is finite.

$$R_{in} = r_{\pi 1} \quad \rightarrow \text{① H}$$

→ Second, recall that the current signal in the collector of Q_2 will be approximately equal to $g_{m1} v_i$. Thus, the equivalent circuit of the cascode amplifier will be that shown in fig. To obtain R_o we use

$$R_o \approx r_{o2} + (g_{m2} r_{o2})(r_{o1} || r_{\pi 2})$$

Since $g_{m2}(r_{o1} || r_{\pi 2}) \gg 1$,

$$R_o \approx (g_{m2} r_{o2})(r_{o1} || r_{\pi 2}) \quad \rightarrow \text{① H}$$

→ The open circuit voltage gain of the ~~bip~~ bipolar cascode can be found using the equivalent circuit as shown above.

$$A_v = \frac{v_o}{v_i}$$

$$= -g_{m1} R_o$$


$$\text{Thus } A_{vo} = -g_{m1} (g_{m2} r_{o2})(r_{o1} || r_{\pi 2})$$

$$= -g_{m1} g_{m2} r_{o2} (r_{o1} || r_{\pi 2})$$

(6)

The BJT cascode amplifier is shown below.

(b)

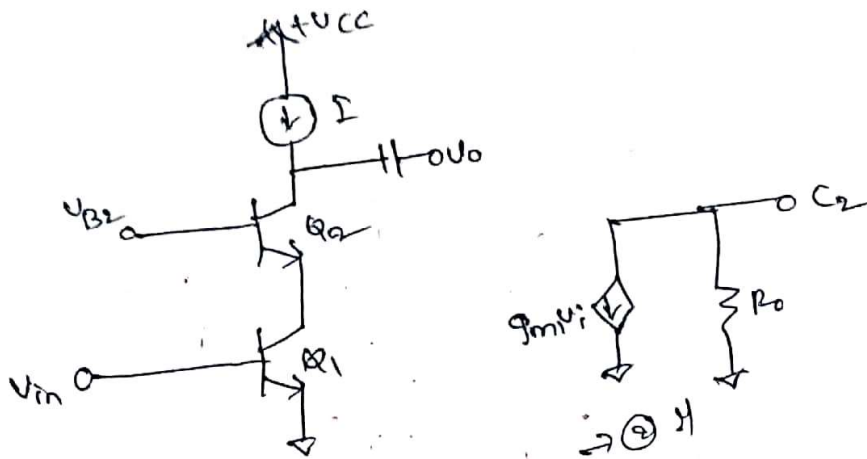

→ Voltage V_{B2} is a dc bias voltage for the CB cascode transistor Q_2 . The circuit is very similar to the MOS cascode and the small signal analysis will follow in a parallel fashion. First, note that the input resistance of the bipolar cascode amplifier is finite.

$$R_{in} = r_{\pi 1} \quad \rightarrow \text{① H}$$

→ Second, recall that the current signal in the collector of Q_2 will be approximately equal to $g_{m1} v_i$. Thus, the equivalent circuit of the cascode amplifier will be that shown in fig. To obtain R_o we use

$$R_o \cong r_{o2} + (g_{m2} r_{o2}) (r_{o1} \parallel r_{\pi 2}),$$

Since $g_{m2} (r_{o1} \parallel r_{\pi 2}) \gg 1$,

$$R_o \cong (g_{m2} r_{o2}) (r_{o1} \parallel r_{\pi 2}), \quad \rightarrow \text{① H}$$

→ The open circuit voltage gain of the ~~bip~~ bipolar cascode can be found using the equivalent circuit as shown above

$$A_v = \frac{v_o}{v_i}$$

$$= -g_{m1} R_o$$

$$\text{Thus } A_{vo} = -g_{m1} (g_{m2} r_{o2}) (r_{o1} \parallel r_{\pi 2})$$

$$= -g_{m1} g_{m2} v_{B2} (r_{o1} \parallel r_{\pi 2})$$

For the case $g_{m1} = g_{m2}$; $r_{o1} = r_{o2}$

$$A_{vo} = -g_m r_o g_m (r_o || r_{\pi})$$

which will be less than $(g_m r_o)^2$ in magnitude.

In fact, the maximum possible gain magnitude is obtained when $r_o \gg r_{\pi}$ and is given by

$$|A_{vo}|_{max} = \beta g_m r_o$$

$$= \beta A_o \rightarrow \textcircled{3} \text{ H}$$


→ Finally, we note that to be able to realize gain approaching this level, the current source load must also be cascoded.

$$\frac{\textcircled{3} \text{ H}}{2+2} = \textcircled{14} \text{ M}$$

7

a

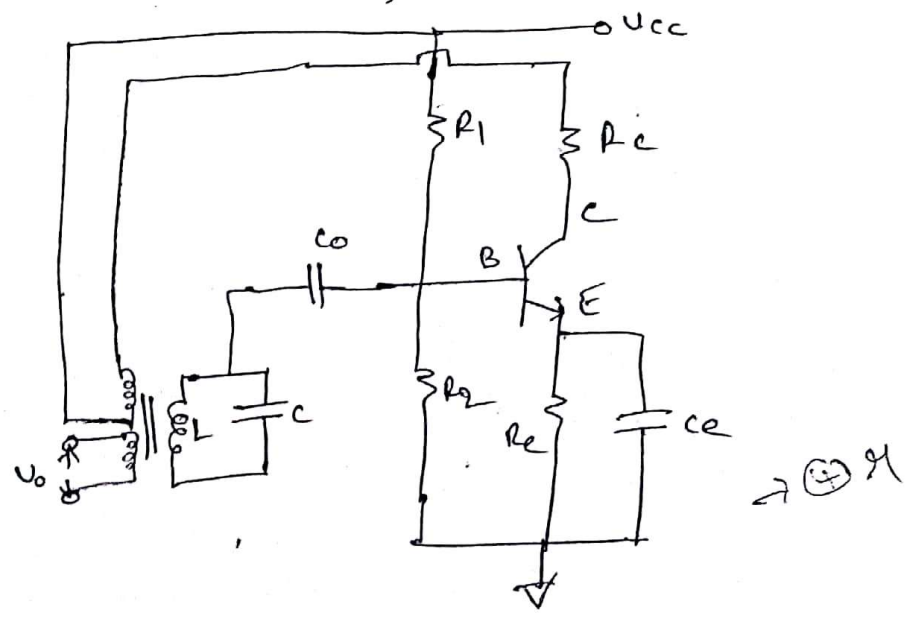Tuned base oscillators are called so because the tuned circuit is placed in the base of the transistor amplifier. The combination of L and C form the tuned circuit or frequency determining circuit. The below figure shows the tuned base oscillator.



7
b

Operation:— The resistors R_1 , R_2 and R_E are used to provide d.c bias to the transistor. The parallel combination of R_E and C_E in the emitter circuit is the stabilizing circuit. C_C is the $\rightarrow \textcircled{1} \text{ H}$

For the case $g_{m1} = g_{m2}$; $r_{o1} = r_{o2}$

$$A_{vo} = -g_m r_o g_m (r_o || r_{\pi})$$

which will be less than $(g_m r_o)^2$ in magnitude.

In fact, the maximum possible gain magnitude is obtained when $r_o \gg r_{\pi}$ and is given by

$$|A_{vo}|_{max} = \beta g_m r_o = \beta A_o \rightarrow \textcircled{3} \text{ H}$$


→ Finally, we note that to be able to realize gain approaching this level, the current source load must also be cascode.

$$\frac{\textcircled{2} \text{ H}}{2+2} = \textcircled{14} \text{ M}$$

7

a

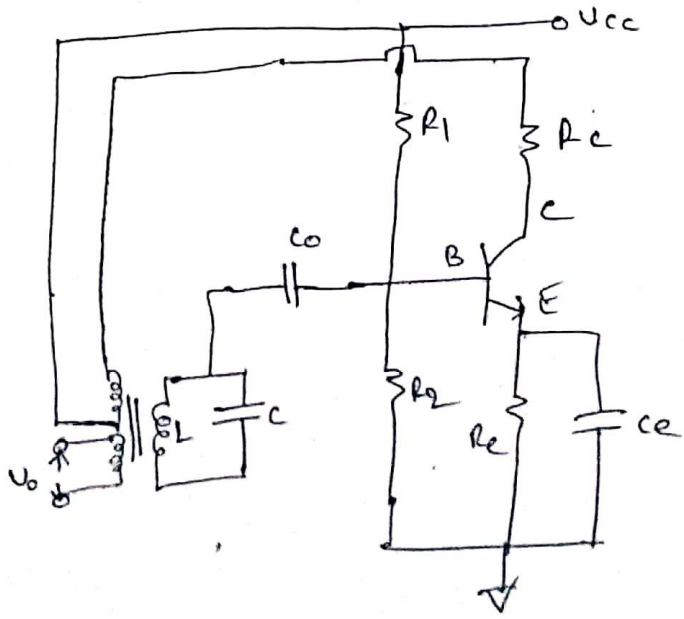Tuned base oscillators are called so because the tuned circuit is placed in the base of the transistor amplifier. The combination of L and C form the tuned circuit or frequency determining circuit. The below figure shows the tuned base oscillator.



→ ⑤ H

7

Operation: - The resistors R_1 , R_2 and R_E are used to provide d.c bias to the transistor. The parallel combination of R_E and C_E in the emitter circuit is the stabilizing circuit. C_C is the

→ ⑥ H

(16/16)

the blocking capacitor. The capacitors C_e and C_c are the bypass capacitors. The primary coil L_1 and the secondary coil L_2 of PT transformer provides the required feedback to collector and base circuits.

→ As the CE amplifier provides 180° phase shift and another 180° phase shift is provided by the transformer which makes 360° phase shift between the input and output voltages.

→ When the circuit is switched on, the collector current starts rising. As the collector is connected to the coil L_1 , that current creates some magnetic field around it. This induces a voltage in the tuned circuit coil L_2 .

→ The feedback voltage produces an increase in V_{BE} and I_B . A further increase in I_C is thus achieved and the cycle continues until the I_C becomes saturated. In the meanwhile, the capacitor is fully charged.

→ When the I_C reaches saturation level, there is no feedback voltage in L_2 . As the C has been charged fully, it starts discharging through L_2 . This decreases the V_{BE} and hence I_B and I_C also decreases. By this time the I_C reaches cutoff, the C is full charged with opposite polarity.

→ As the transistor now gets off, the condenser C begins to discharge through L_2 . This increases the emitter-base bias. As a result I_C increases.

→ The cycle repeats so long as enough energy is supplied to meet the losses in L.C circuit. The frequency of oscillations is equal to the resonant frequency of LC circuit and give by

$$f = \frac{1}{2\pi\sqrt{LC}}$$

→ ⑨ 21
⑩ 21 = $4 \times 10 = 14$ M

prepared by
Dr. Y. Radhusudhana
Reddy.

Dept of E CE
RGM CET

24/7/23

RGM COLLEGE OF ENGINEERING & TECHNOLOGY (AUTONOMOUS)

07th July 2022

II B.Tech. II Sem. (R20) End Examinations (Regular)
ELECTRONIC CIRCUITS – ANALYSIS AND DESIGN
ECE

Time: 3 Hrs

Total Marks: 70

Note 1: Answer Question No.1 (Compulsory) and 4 from the remaining

2: All Questions Carry Equal Marks

- 1a Define h_{fc} and h_{oc} .
- b Define lower 3-DB frequency.
- c Define the common mode gain of BJT differential amplifier if the output is single ended output.
- d Define positive feedback.
- e Define sustained oscillations.
- f Why power amplifier is called large signal amplifier?
- g Define h_{fb} and h_{ob} .
- 2 a) A MOS differential amplifier is operated at a total current of 0.8 mA, using transistors with a W/L ratio of 100, $\mu_n \cdot C_{ox} = 0.2 \text{ mA/V}^2$, $V_A = 20 \text{ V}$, and $R_D = 5 \text{ K}\Omega$. Find V_{OV} , g_m , r_o , and A_d . (7)
- b) Define and explain the input common-mode resistance of BJT differential amplifier (7)
- 3 a) With the help of neat diagrams explain in details the basic amplifiers. (6)
- b) Draw the block diagram of a single loop feedback connection and explain the function of each block. (8)
- 4 a) Draw the simplified h-parameter model of a CB amplifier. Derive the expressions for current gain, input impedance, voltage gain and output impedance. (10)
- b) Give the comparison between CE, CB and CC amplifiers. (4)
- 5 a) Draw the capacitive-coupled MOSFET amplifier and its high-frequency equivalent circuit model? (4)
- b) Explain the analysis of high-frequency response of common-source amplifier to find its equivalent gain and f_H . (10)
- 6 a) List the differences between class A and class B power amplifiers. (7)
- b) Draw the circuit diagram of series fed class A power amplifier using BJT and explain its operation (7)
- 7 a) Draw the circuit diagram of transistorized wein-bridge oscillator. (4)
- b) Explain the operation of above circuit and derive the expression for frequency of oscillations. (10)

- xxx -

07th July 2022

II B.Tech. II -sem (R20) End Examinations (Regular)

ELECTRONIC CIRCUITS - ANALYSIS AND DESIGN.

(ECE)


Code: A0409204R0722

Total Marks: 70

①
a

h_{fc} : Forward Current Gain with output short circuited.

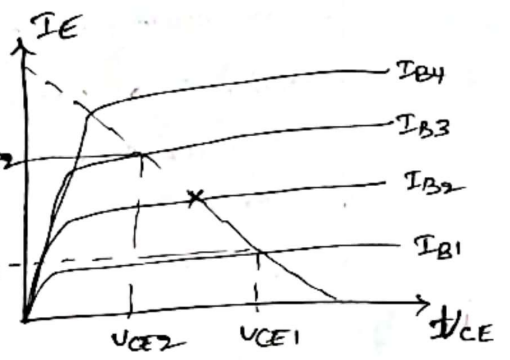From the output characteristics of common collector configuration, it is defined as the ratio of change in emitter current I_E taken around the quiescent point Q to the corresponding change in the base current I_B for constant value of output voltage V_{CE} at the Q -point.



$$\therefore \text{i.e. } h_{fc} = \frac{\Delta I_E}{\Delta I_B} \Big|_{V_{CE} \text{ constant}} = \frac{I_{E2} - I_{E1}}{I_{B3} - I_{B1}} \rightarrow \text{① M}$$

→ It's typical value is -51 if $\beta = 50$ or -101 if $\beta = 100$.

h_{oc} : Output admittance with input open circuited.

→ It can be obtained as the change in the emitter current $i_e I_E$ divided by the change in collector to emitter voltage $i.e. V_{CE}$ for a constant base current at the quiescent point Q .


$$\text{i.e. } h_{oc} = \frac{\Delta I_E}{\Delta V_{CE}} \Big|_{I_B \text{ constant}} = \frac{I_{E2} - I_{E1}}{V_{CE2} - V_{CE1}}$$

→ It's typical value is 25 $\mu A/V$ → ① M
→ ② M

29/9/23

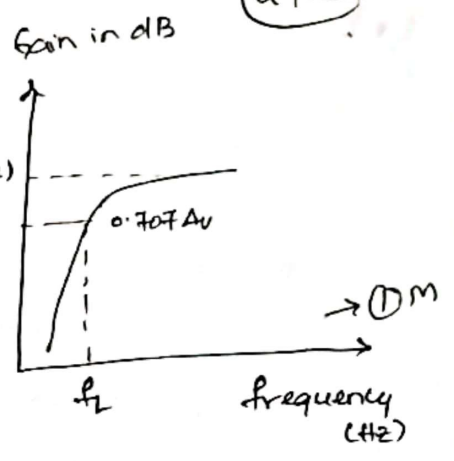(1)
(b)


Lower 3-dB frequency, it is the frequency at which the maximum gain of the amplifier falls or decreases to $\frac{1}{\sqrt{2}}$ times (or) 0.707 times of maximum gain of the amplifier at low frequency. It is denoted by f_L (or) f_{cL} .
 → It is also called half power frequency since gain or output voltage drops to 70.7% of maximum value and this represents a power level of one-half the power at the reference frequency in mid frequency range (or) region.



(2) M

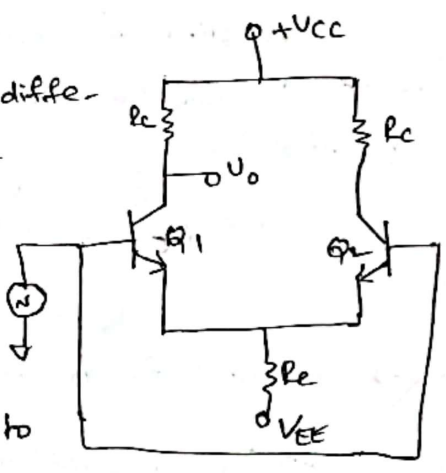(1)
(c)

The common mode gain of BJT differential amplifier if the output is single ended output is the ratio of output voltage to the common mode input signal i.e. common input signal is applied to both inputs of the transistors Q_1 and Q_2 and the output is taken either at Q_1 or Q_2 then it is called single ended output.




(1) M

$$A_c = \frac{V_o}{V_{in}} = \frac{V_o}{V_{cm}} \text{ and it is given by}$$

$$A_c = \frac{\beta R_c}{r_i + 2(\beta + 1) R_e} \quad \text{(or)} \quad \frac{h_{fe} R_c}{h_{ie} + 2(h_{fe} + 1) R_e}$$

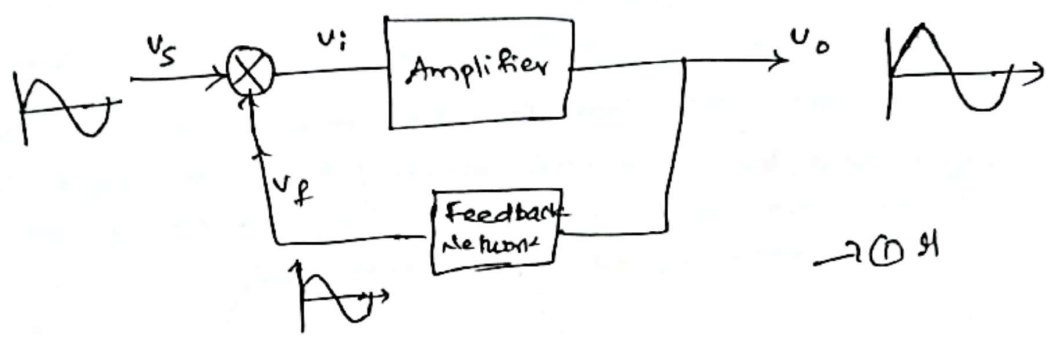(2) M


① The feedback is a property which allows to feedback the part of the output to the same circuit as its input. Such a feedback is said to be positive ~~when~~ whenever the part of the output that is feedback to the amplifier as its input is in phase with the original input signal applied to the amplifier.



→ If the magnitude of input signal increases due to the feedback signal then it is also called positive feedback.

i.e. $v_i = v_s + v_f$

①
② As stated by Barkhausen criterion, when total phase shift around a loop is 0° or 360° ensuring positive feedback and the magnitude of the product of the open loop gain of the amplifier (A) and feedback factor (B) is unity i.e. $|AB| = 1$ then the oscillations are with constant frequency and amplitude called Sustained oscillations.

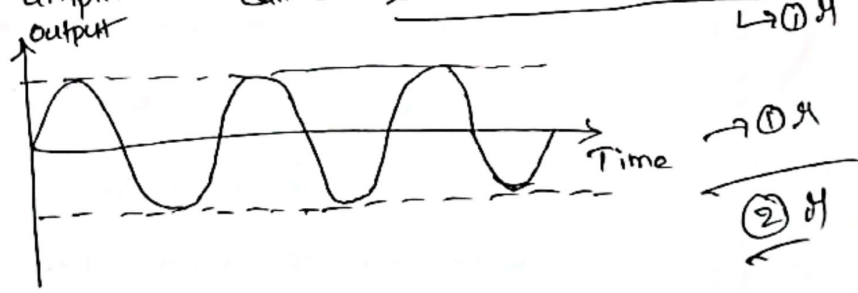

(i)

(f) Power amplifiers are basically used to increase the power level of the input signal. Power amplifier is also called large signal amplifiers, as in order to get large power at the output, input signal voltage required must also be large.

→ Power amplifiers takes the d.c power supply connected to the output circuit and converts it into a.c signal power. Output power is controlled by input signal. → (1) H

→ The power amplifiers develop an a.c power of the order of few watts. Similarly large power gets dissipated in the form of heat, at the junctions of the transistors used in it. Hence the transistor used in it are of large size, having large power dissipating rate called power transistors. → (1) H


(2) H

(1)

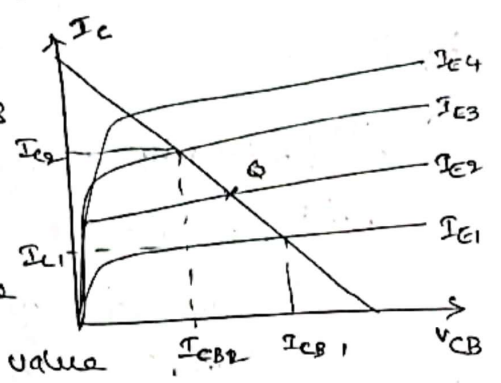(9)

h_{fb} : Forward current gain with output short circuited.

From the output characteristics of CB configuration, it is defined as the ratio of change in collector current I_c taken around Q-point to the corresponding change in the emitter current I_e for constant value of output voltage V_{CB} at the Q-point.



$$h_{fb} = \frac{\Delta I_c}{\Delta I_e} \Big|_{V_{CB} \text{ constant}}$$

$$= \frac{I_{c1} - I_{c2}}{I_{e1} - I_{e2}}$$

→ (1) H

h_{fb} 's typical value is -0.98 to -0.99.

h_{ob} : Output admittance with input open circuited.
 → It can be obtained as the change in the collector current, i.e. I_c divided by the change in collector to base voltage i.e. V_{CB} for a constant emitter current at the Q-point.

$$i.e. h_{ob} = \frac{\Delta I_c}{\Delta V_{CB}} = \frac{I_{c2} - I_{c1}}{V_{CB2} - V_{CB1}}$$

→ It's typical value is 0.49 $\mu A/V$ → ① M
② M

②
 a

Given that, Total current, $I = 0.8 mA$
 Transistors with $\frac{W}{L} = 100$
 $\mu_n C_{ox} = 0.2 mA/V^2$
 $V_A = 20V$ and $R_D = 5K\Omega$.

We know that, the total current through MOS differential amplifier is

$$I = \mu_n C_{ox} \left(\frac{W}{L}\right) \frac{(V_{ov})^2}{2} \rightarrow ① M$$

$$\rightarrow 0.8 mA = 0.2 mA/V^2 \times 100 \times \frac{(V_{ov})^2}{2}$$

$$(V_{ov})^2 = \frac{0.8}{10} = 0.08$$

$$\boxed{V_{ov} = 0.2V} \rightarrow ② M$$

$$g_m = \frac{I}{V_{ov}} = \frac{0.8 mA}{0.2V} = 4 mA/V \rightarrow ① M$$

$$r_o = \frac{V_A}{I/2} = \frac{20V}{0.4 mA} = 50 K\Omega \rightarrow ① M$$

$$A_d = g_m (R_o \parallel r_o)$$

$$= 4 \text{ mA/V} (5 \text{ k}\Omega \parallel 50 \text{ k}\Omega)$$

$$A_d = 18.2 \rightarrow \frac{2 \text{ M}}{7 \text{ M}}$$

29
b

The input common-mode resistance of BJT differential amplifier is the resistance measured between the two interconnected inputs and ground. It is denoted by R_{icm} .

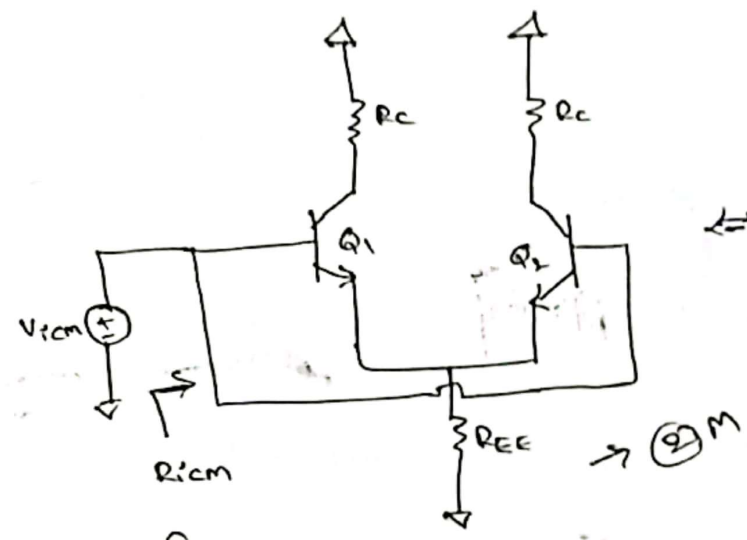


Fig. (a) Definition of the input common-mode resistance


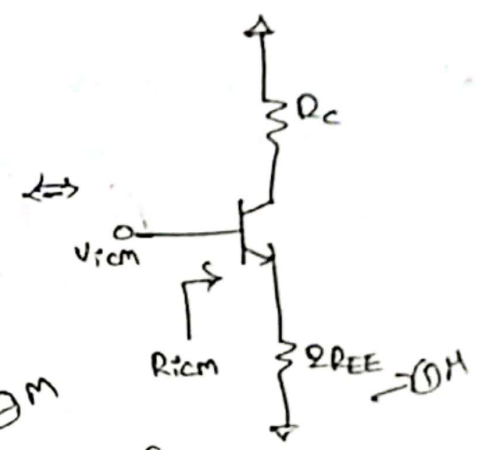


Fig. (b) The equivalent common mode half-circuit.

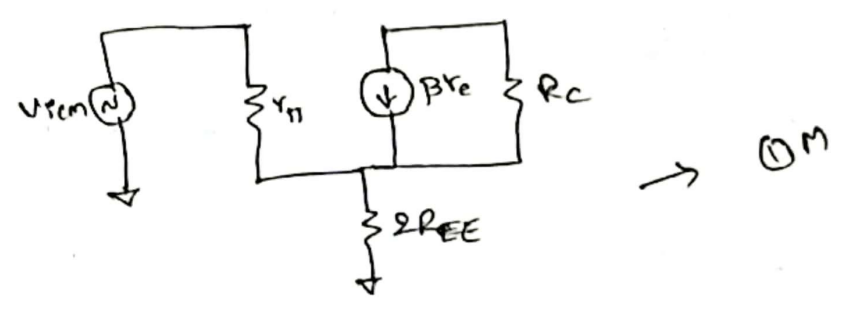The equivalent circuit of the half circuit of differential amplifier is shown in fig.



→ By applying KVL to the input loop,

$$I_b = \frac{V_{icm}}{r_{\pi} + 2(\beta + 1)R_{EE}}$$

The common mode input resistance is given by

$$R_{icm} = \frac{V_{icm}}{I_b}$$

$$\frac{V_{icm}}{I_b} = r_{\pi} + 2(\beta + 1)R_{EE}$$

$$\therefore R_{icm} = r_{\pi} + 2(\beta + 1)R_{EE}$$

→ ② M

⑦ M

7 + 7 = 14 M

③


②

The amplifiers can be classified into four categories based on the magnitudes of the input impedance and output impedance of an amplifier relative to the source and load impedances. They are

- ① Voltage Amplifier
- ② Current Amplifier
- ③ Trans conductance Amplifier and → ② M
- ④ Trans resistance Amplifier.

Voltage Amplifier:- If the amplifier input resistance R_i is large compared with the source resistance R_s , then $V_i \approx V_s$. If the external load resistance R_L is large compared with output resistance R_o of the amplifier, then $V_o = A_v V_i = A_v V_s$. Such

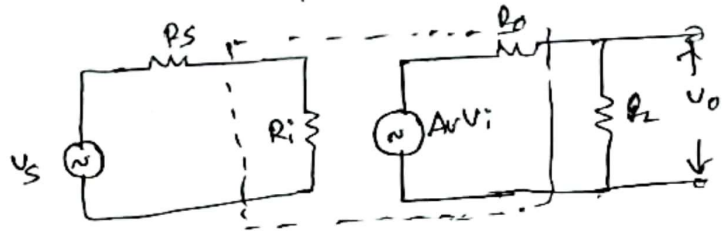
amplifier provides a voltage output proportional to the voltage input. Hence this amplifier is called voltage amplifier.



For ideal cases, $R_i \rightarrow \infty$ and $R_o \rightarrow 0$
 For practical cases, $R_i \gg R_s$ and $R_L \gg R_o$

→ ① H

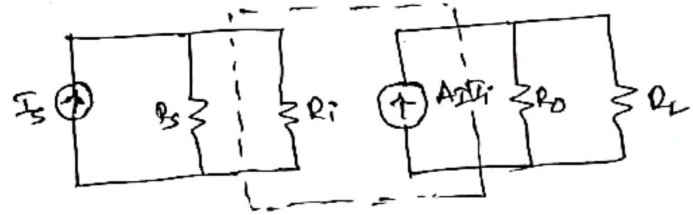
Current Amplifier :- If the amplifier R_i is small than $R_s \approx I_s$ and the amplifier R_o large compared with R_L than $I_L \approx A_i I_i$. Such amplifier provides a current output proportional to the signal current. Hence this amplifier is called current amplifier.



For ideal cases, $R_i \rightarrow 0$ and $R_o \rightarrow \infty$
 For practical cases, $R_i \ll R_s$ and $R_L \ll R_o$

→ ① H

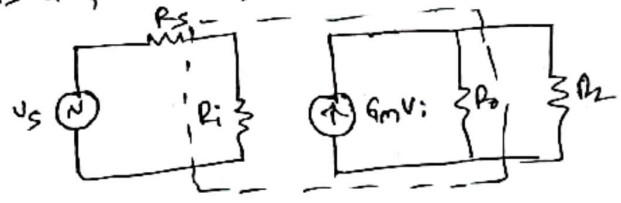
Transconductance Amplifier :- If the amplifier R_i is large compared with R_s then $V_i \approx V_s$ and if the amplifier R_o is large compared with R_L then $I_L \approx G_m V_i$. Such an amplifier provides a current output is proportional to the input voltage. Hence this amplifier is called transconductance amplifier.



For ideal cases, $R_i \rightarrow \infty$ and $R_o \rightarrow \infty$
 For practical cases, $R_i \gg R_s$ and $R_o \gg R_L$ ($R_L \ll R_o$)

→ ① H

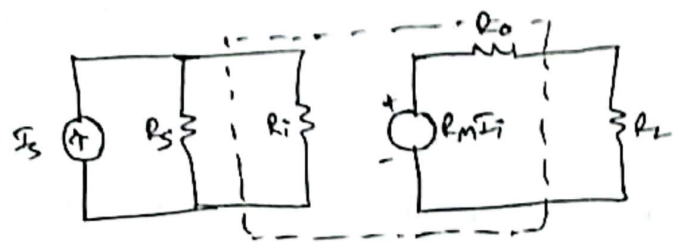
Transresistance Amplifier :- If the amplifier R_i is small compared to R_s then $I_i \cong I_s$ and if the amplifier R_o is large compared to R_L then $V_o \cong R_m I_i$. Such amplifier circuit provides a voltage output is proportional to the source current. Hence this amplifier is called transresistance amplifier.



For ideal cases, $R_i \rightarrow 0$ and $R_o \rightarrow \infty$
 For practical cases, $R_i \ll R_s$ and $R_L \gg R_o$

→ 1M
6M

3
 b

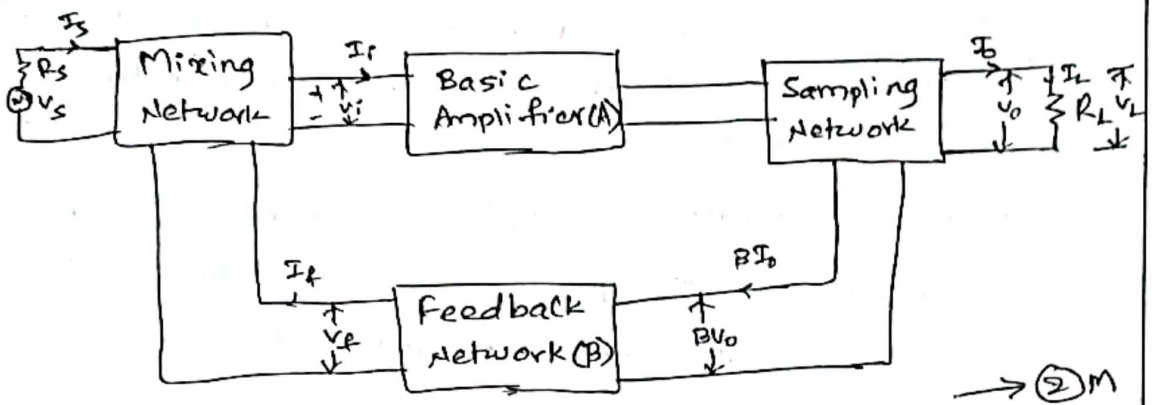

→ 2M

Fig:- Block diagram of single loop feedback connection.

Sampling Network :- There are two ways to sample the output according to the sampling parameter, either voltage or current. The output voltage is sampled by connecting the feedback network in shunt across the output as shown in fig. 1. This type of connection is referred to as voltage or node sampling. The output current is sampled by connecting the feedback network in series with the output as shown in fig. 2. This type of connection is referred to as current or loop sampling.

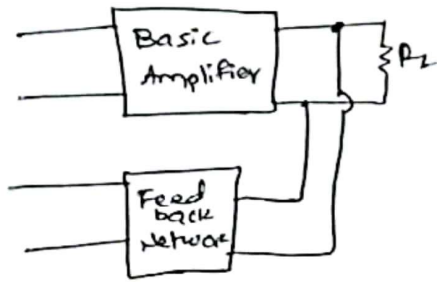


Fig. ① Voltage or node sampling

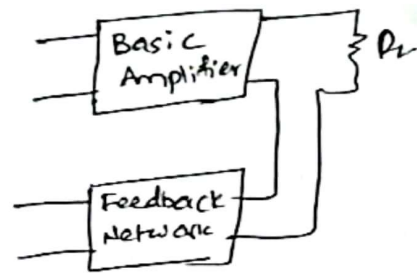


Fig. ② Current or loop sampling. → ② H


Feedback Network :- It may consists of resistors, capacitors or inductors. Most often it is simply a resistive configuration. It provides reduced portion of the output as feedback signal to the input mixer network. It is given as

$$V_f = \beta V_o$$


where β is a feedback factor or feedback ratio, which lies between 0 and 1. It is totally different from β symbol used to represent current gain in CE amplifier which is greater than 1. → ① H

Mixer Network :- Like sampling, there are two ways of mixing feedback signal with the input signal. These are

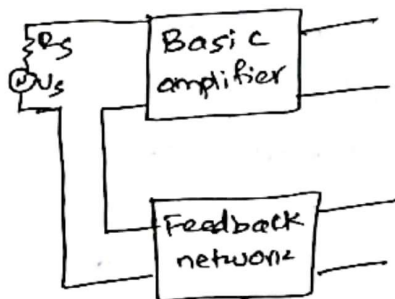- ① Series input connection and
- ② Shunt input connection.



① Series Mixing

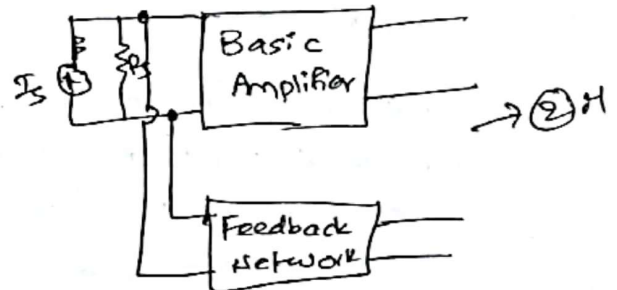

② Shunt Mixing → ② H

11/23

Basic Amplifier :- Here the basic amplifier may be either voltage or current or transconductance or transresistance amplifier based on the way of sampling and the way of mixing the feedback signal with input with transfer gains of A_v , A_I , G_M and R_M without feedback. It can also be represented as A_{vf} , A_{If} , G_{Mf} and R_{Mf} with feedback. These can be defined as

$$A_v = \frac{V_o}{V_i} = \text{Voltage gain}, \quad A_{vf} = \frac{V_o}{V_s} = \text{Voltage gain with feedback}$$

$$A_I = \frac{I_o}{I_i} = \text{Current gain}, \quad A_{If} = \frac{I_o}{I_s} = \text{Current gain with feedback}$$


$$G_M = \frac{I_o}{V_i} = \text{Transconductance}, \quad G_{Mf} = \frac{I_o}{V_s} = \text{Transconductance with feedback}$$

$$R_M = \frac{V_o}{I_i} = \text{Transresistance}, \quad R_{Mf} = \frac{V_o}{I_s} = \text{Transresistance with feedback}$$

\rightarrow (1) M
 \rightarrow (8) M
 \rightarrow 6+8 = (14) M

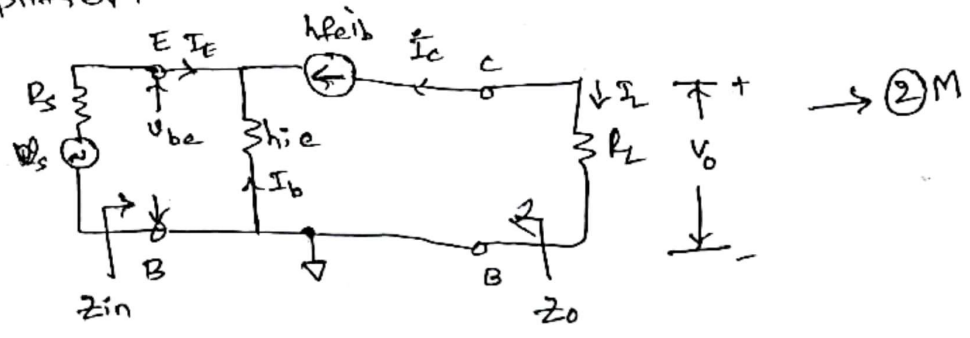(4)
(a)

The simplified h-parameter model of a CB amplifier can be drawn by giving input to emitter, taking output from collector and making base common. The below figure shows the simplified h-parameter model of a CB amplifier.



Current Gain, (A_I) :- It is defined as a ratio of output current to input current. In CB amplifier, input current is emitter current, I_E and output current is collector current I_C .

$$A_I = \frac{I_O}{I_E} = -\frac{I_C}{I_E}$$

From circuit, $I_C = h_{fe} i_b$ and

$$I_E = -(1+h_{fe}) i_b$$

$$A_I = \frac{h_{fe} i_b}{-(1+h_{fe}) i_b}$$

$$\therefore A_I = \frac{h_{fe}}{1+h_{fe}} \rightarrow \textcircled{2} M$$

Input Impedance, (Z_{in}) :- It is defined as a ratio of input voltage to input current. In CB amplifier, input voltage is emitter to base voltage V_{be} and input current is emitter current, I_E .

$$\therefore Z_{in} = \frac{V_{be}}{I_E}$$

From circuit, $V_{be} = -h_{ie} i_b$ and

$$I_E = -(1+h_{fe}) i_b$$

$$Z_{in} = \frac{-h_{ie} i_b}{-(1+h_{fe}) i_b}$$

$$\therefore Z_{in} = \frac{h_{ie}}{1+h_{fe}} \rightarrow \textcircled{2} M$$

(13/19/23)

Voltage Gain, (A_v) :- It is defined as a ratio of output voltage to input voltage. In CB amplifier, input voltage is v_b emitter to base voltage, v_{be} and output voltage is collector to base voltage v_{bc} .

$$\therefore A_v = \frac{V_o}{V_{in}} = \frac{I_o R_L}{I_b R_{in}} = \frac{A_I R_L}{Z_{in}}$$

$$A_v = \frac{\frac{h_{fe}}{1+h_{fe}}}{\frac{h_{ie}}{1+h_{fe}}} \cdot R_L$$

$$\therefore \boxed{A_v = \frac{h_{fe} R_L}{h_{ie}}} \rightarrow \text{(2) M.}$$

Output Impedance, (Z_o) :- It is defined as a ratio of output voltage to output current by making $R_S = 0$ and $R_L \rightarrow \infty$. In CB amplifier, output voltage is v_{bc} and output current is I_c .

$$Z_o = \left. \frac{V_o}{I_o} \right|_{V_s=0}$$

When $V_s = 0$, the current through input loop is zero.

i.e. $I_b = 0$ hence $I_c = 0$

$$\therefore Z_o = \frac{V_o}{0} = \infty.$$

By considering the load resistance into account then output impedance becomes

$$Z_o' = Z_o \parallel R_L = \infty \parallel R_L$$

$$\boxed{Z_o' = R_L}$$

$$\rightarrow \text{(2) M}$$

$$\text{(10) M}$$

4

14/23

b

Comparison of CE, CB and CC amplifiers:-

S.No	Characteristic	Common Base	Common Emitter	Common Collector
1.	Input Resistance	Very low (20Ω)	Low ($1K\Omega$)	High (> $100K\Omega$)
2.	Output Resistance	Very high ($1M\Omega$)	High ($40K\Omega$)	Low (50Ω)
3.	Current Gain	Less than unity	High (20 to few hundreds)	High (20 to few hundreds)
4.	Voltage gain	Medium (>100)	Medium (>100)	Low (<1)
5.	Current amplification factor	$\alpha = \frac{I_c}{I_E}$ (0.96 to 0.99)	$\beta = \frac{I_c}{I_B}$ (20 to 500)	$\beta = \frac{I_E}{I_B}$ (20 to 500).
6.	Applications	As a input stage of multistage Amplifier.	For audio signal amplification	For impedance matching.


$$\rightarrow 4M$$

$$\underline{10+4=14M}$$


5

a

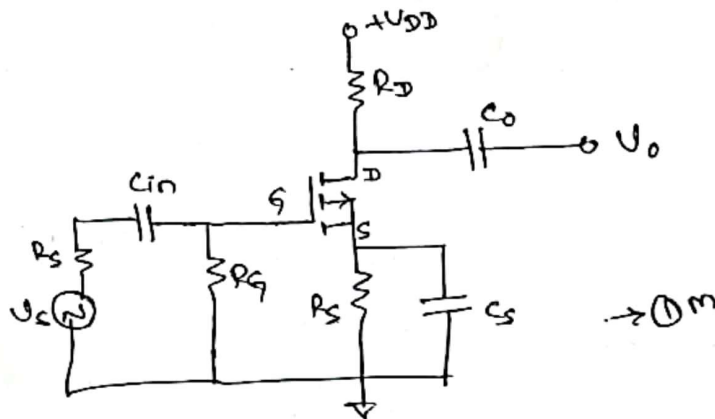
Circuit diagram of capacitive coupled MOSFET Amplifier:-



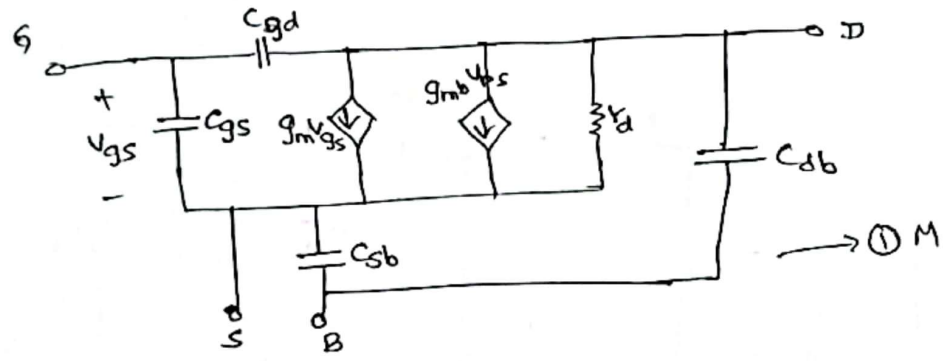High frequency equivalent model of MOSFET:- The below figure shows the small signal model of the MOSFET, including the four capacitances C_{gs} , C_{gd} , C_{sb} and C_{db} . This model can be used to predict the high frequency response of MOSFET amplifiers. → ① M




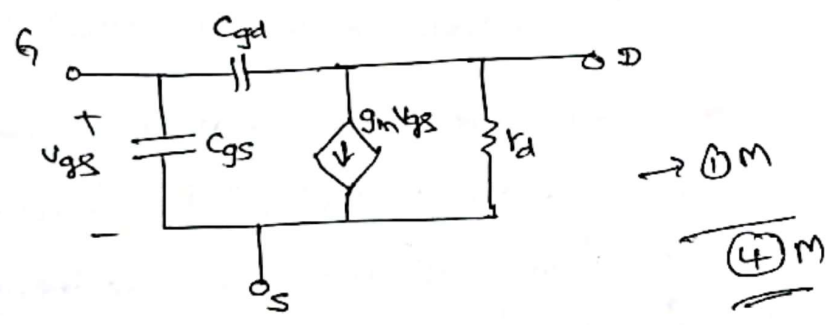The above model can be simplified by neglecting C_{sb} and C_{db} .





⑤

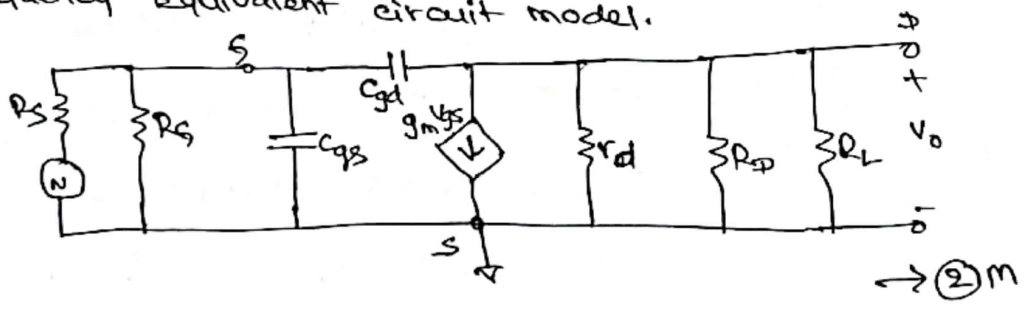⑥ The below figure shows the high frequency equivalent circuit model of a CS amplifier. It is obtained by replacing the MOSFET in an amplifier circuit such that as shown in above figure by its high frequency equivalent circuit model.



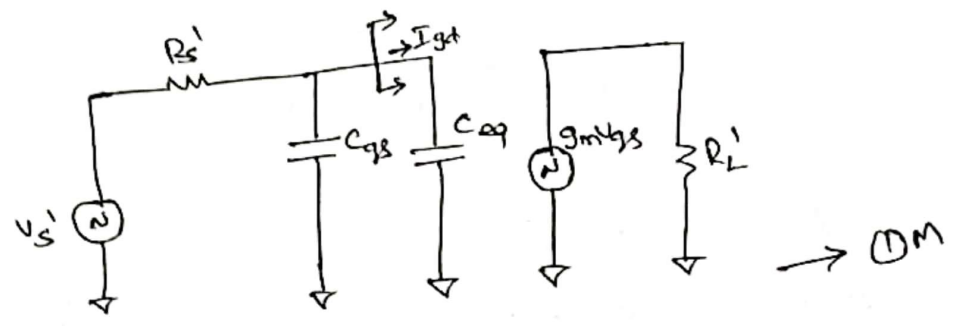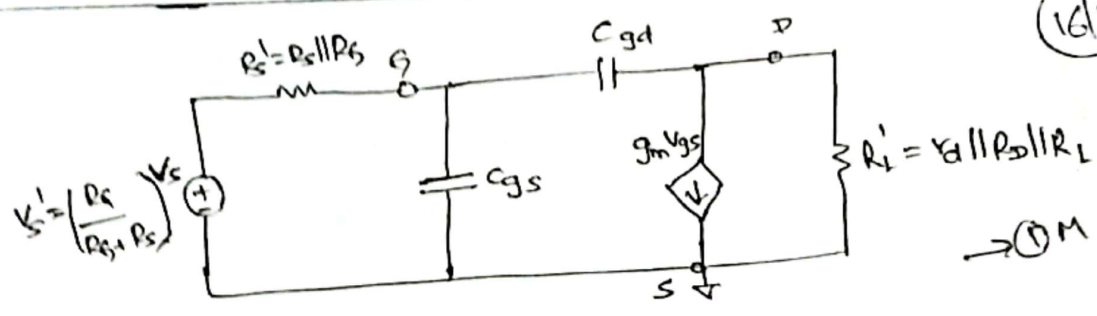The above equivalent circuit can be simplified by utilizing Thevenin's theorem at the input side and by combining the three parallel resistances at the output side. The resulting simplified circuit is shown in figure.



where $C_{eq} = C_{gd} (1 + g_m R_L')$

From above circuit, the output voltage is given by

$$V_o = -(g_m V_{gs}) R_L' \quad \text{where } R_L' = R_D || R_L$$

Since $V_o = V_{ds}$ indicates that the gain from gate to drain is $-g_m R_L'$, the same value as in the midband. The current I_{gd} can now be found as

$$\begin{aligned} I_{gd} &= s C_{gd} (V_{gs} - V_o) \\ &= s C_{gd} (V_{gs} - (-g_m R_L' V_{gs})) \\ &= s C_{gd} V_{gs} (1 + g_m R_L') \end{aligned}$$

From circuit, the value of $I_{gd} = s C_{eq} V_{gs}$

$$\begin{aligned} \therefore s C_{eq} V_{gs} &= s C_{gd} V_{gs} (1 + g_m R_L') \\ \Rightarrow \boxed{C_{eq} = C_{gd} (1 + g_m R_L')} \end{aligned}$$

The expression for the high frequency gain of the CS amplifier

$$A_v = \frac{V_o}{V_s} = \left(\frac{R_g}{R_g + R_s} \right) g_m R_L' \cdot \frac{1}{1 + \frac{s}{\omega_0}}$$

which can be expressed in the form

$$\frac{V_o}{V_s} = \frac{A_m}{1 + \frac{s}{\omega_H}}$$

where the midband gain $A_m = \frac{R_G}{R_G + R_s} (g_m R_L')$ and

ω_H is the upper 3-dB frequency,

$$\omega_H = \omega_0 = \frac{1}{C_{in} R_s'}$$
 and



$$f_H = \frac{\omega_H}{2\pi} = \frac{1}{2\pi C_{in} R_s'} \rightarrow \textcircled{2} M$$

where $C_{in} = C_{gs} + C_{gd}(1 + g_m R_L')$

$$R_s' = R_s \parallel R_G$$

$$\frac{10M}{4 + 10} = \textcircled{14} M$$

⑥
a

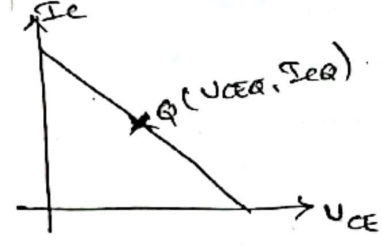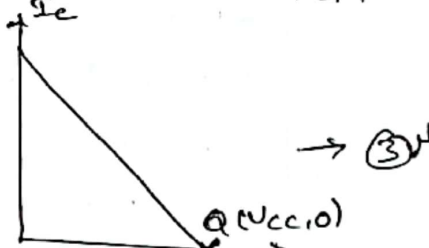
Class A Power Amplifier	Class B Power Amplifier
<p>① - the power amplifier is said to be class A amplifier if the Q-point and the input signal are selected such that the output signal is obtained for a full input cycle.</p>	<p>① The power amplifier is said to be class B amplifier if the Q-point and the input signal are selected such that the output signal is obtained only for one half cycle for a full cycle input.</p>
<p>② For this class, position of the Q-point is approximately at the mid point of the load line.</p>	<p>② For this class, the Q-point is shifted on x-axis i.e. the transistor is biased to cut-off.</p>
 <p>A graph showing the load line for a Class A amplifier. The vertical axis is labeled I_c and the horizontal axis is labeled V_{CE}. A straight line (load line) connects the two axes. A point labeled $Q(V_{CEQ}, I_{CQ})$ is marked on the load line, positioned approximately at its midpoint.</p>	 <p>A graph showing the load line for a Class B amplifier. The vertical axis is labeled I_c and the horizontal axis is labeled V_{CE}. A straight line (load line) connects the two axes. A point labeled $Q(V_{CE0}, 0)$ is marked on the x-axis, representing the Q-point where the transistor is biased to cut-off.</p>
<p>③ For all values of input signal, the transistor remains in the active region.</p>	<p>③ The transistor remains in active region only for positive half cycle of input.</p>

Class A power Amplifier	Class B power Amplifier
<p>④ Here signal is faithfully reproduced at the output without any distortion.</p> <p>⑤ It uses only one transistor.</p> <p>⑥ It requires one transformer at the output.</p> <p>⑦ There are of two types.</p> <p>① Series fed class A amp.</p> <p>② Transformer coupled class A amplifier</p> <p>⑧ It's efficiency is low range from 25% to 50%.</p> <p>⑨ Power dissipation is more</p> <p>⑩ The output impedance is high hence can not be used for low low impedances.</p>	<p>④ There only a half cycle is obtained at the output for full cycle of input so the output signal is distorted.</p> <p>⑤ It uses two transistors.</p> <p>⑥ It requires two transformer.</p> <p>⑦ There are also two types</p> <p>① Push pull class B</p> <p>② Symmetry Complementary-symmetry class B</p> <p>⑧ It's efficiency is high i.e. 78.5%.</p> <p>⑨ Power dissipation is less.</p> <p>⑩ Low impedance matching is possible due to transformers → ④H</p>

⑥
⑥

Series Fed class A Amplifier :- A simple fixed bias circuit can be used as a large signal class A amplifier.

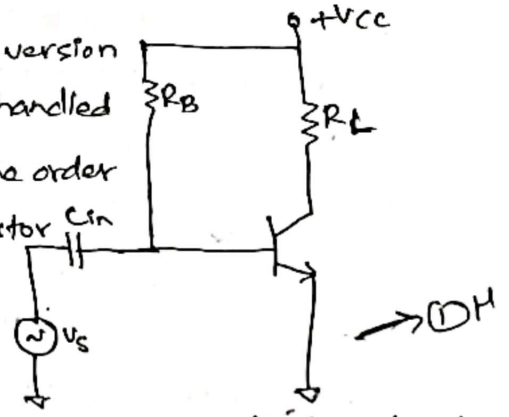The difference between small signal version of this circuit is that the signals handled by this large signal circuit are of the order of few volts. Similarly the transistor used is a power transistor.




→ The value of R_B is selected in such a way that the Q point lies at the center of the d.c load line.

→ The circuit represents the directly coupled class A amplifier as the load resistance is directly connected in the collector circuit. Most of the times the load is a loud speaker, the impedance of which varies from 3 to 4 ohms to 16 ohms.

The β value of the transistor is less than 100.

→ The overall circuit handles large power in the range of a few to tens of watts without providing much voltage gain.

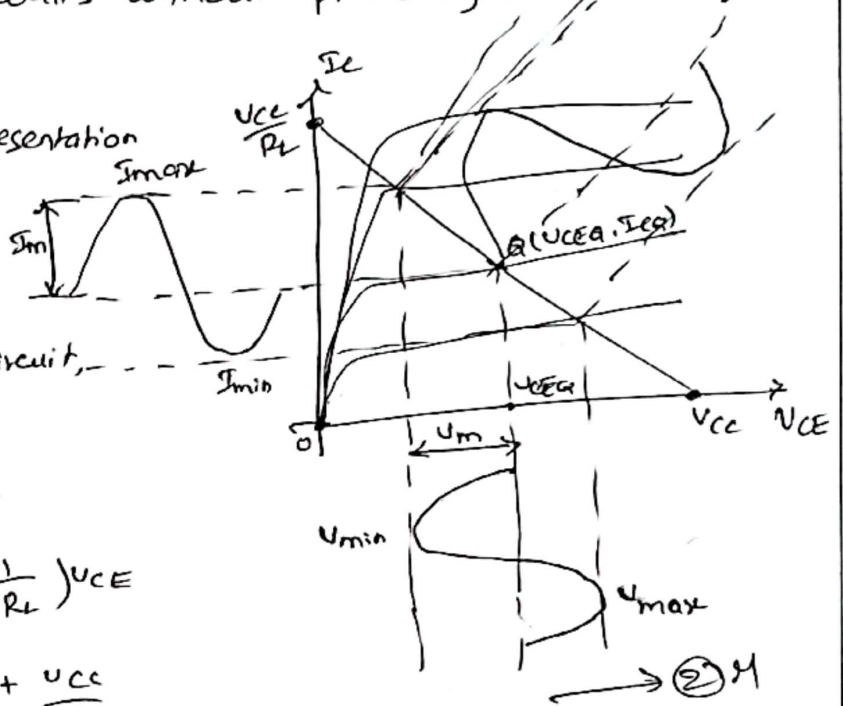→ The graphical representation of a class A amplifier is shown in fig.



→ Applying KVL to the circuit, -

$$V_{CC} = I_c R_L + V_{CE}$$

$$I_c R_L = V_{CC} - V_{CE}$$

$$I_c = \frac{V_{CC}}{R_L} + \left(-\frac{1}{R_L}\right) V_{CE}$$

$$I_c = -\left(\frac{1}{R_L}\right) V_{CE} + \frac{V_{CC}}{R_L}$$

The above equation is similar to $y = mx + c$ and thus the slope of the load line is $-\frac{1}{R_L}$ while the y -intercept is $\frac{V_{CC}}{R_L}$.

D.C operation:- The collector supply voltage V_{CC} and R_B decides the d.c base bias current I_{BQ} .

$$I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B} = \frac{V_{CC} - 0.7V}{R_B}$$

The corresponding collector current is

$$I_{CQ} = \beta I_{BQ}$$

The corresponding collector to emitter voltage is

$$V_{CEQ} = V_{CC} - I_{CQ} R_L \quad \rightarrow \textcircled{1}$$

Hence the Q point can be defined as $Q(U_{CEQ}, I_{CQ})$.

D.c power input:— The d.c power input is provided by the supply. With no a.c input signal, the d.c current drawn is the collector bias current I_{CQ} . Hence d.c power input is

$$P_{dc} = U_{cc} \cdot I_{CQ} \rightarrow \textcircled{1} M$$

A.c Power output:— when an input a.c signal is applied, the base current varies sinusoidally. Then the output voltage and output current also varies sinusoidally around its Q-point which delivers an a.c power output to the load. It is given by

$$P_{ac} = \frac{(U_{max} - U_{min})(I_{max} - I_{min})}{8} \rightarrow \textcircled{1} M$$

Efficiency:— It represents the amount of a.c power delivered to the load from the d.c source i.e. accepting the d.c power input.

$$\% \eta = \frac{P_{ac}}{P_{dc}} \times 100 = \frac{(U_{max} - U_{min})(I_{max} - I_{min})}{8 U_{cc} I_{CQ}} \times 100$$

For maximum efficiency, $U_{max} = U_{cc}$ and $U_{min} = 0$

$$I_{max} = 2 I_{CQ} \text{ and } I_{min} = 0$$

$$\% \eta_{max} = \frac{(U_{cc} - 0)(2 I_{CQ} - 0)}{8 U_{cc} I_{CQ}} \times 100$$

$$= \frac{2 U_{cc} I_{CQ}}{8 U_{cc} I_{CQ}} \times 100$$

$$\% \eta_{max} = 25\% \rightarrow \textcircled{1} M$$


Power dissipation:— The amount of power that must be dissipated by the transistor is the difference between the d.c power input and the a.c power delivered to the load.

$$P_d = P_{dc} - P_{ac} \Rightarrow (P_d)_{max} = U_{cc} I_{CQ}$$

$$\begin{aligned} & \textcircled{7} M \\ & \frac{7+7}{2} = \textcircled{14} M \end{aligned}$$

→ In this circuit, two stage common emitter transistor amplifier is used. Each stage contributes 180° phase shift hence the total phase shift due to the amplifier stage becomes 360° (or) 0° which is necessary as per the oscillator conditions.

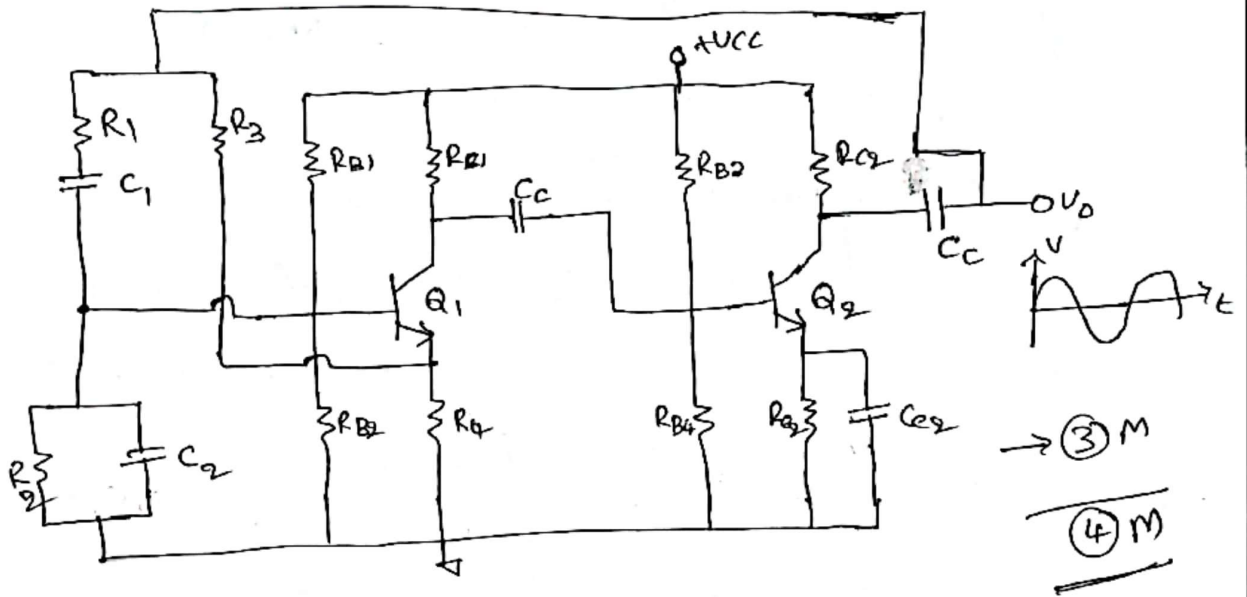→ The bridge circuit consists of R and C in series, R and C in parallel, R_3 and R_4 in arm bridges. The feedback is applied from the collector of Q_2 through the coupling capacitor to the bridge circuit. The resistance R_4 serves the dual purpose of emitter resistance of the transistor Q_1 and also the element of the Wien bridge. → ① M



A basic Wien bridge used in this oscillator and an amplifier stage is shown in above figure. The output of the amplifier is applied between the terminals 1 and 3 which is the input to the feedback network. while the amplifier input is supplied from the diagonal terminals 2 and 4 which is the output from the feedback network. Thus amplifier

supplied its own input through the Wien bridge as a feedback network.

→ The two arms of the bridge namely R,C in series and R,C in parallel are called frequency sensitive arms. This is because the components of these two arms decide the frequency of the oscillator. → (2)^M

Derivation for frequency of oscillations:-

→ If the bridge is balanced, product of opposite arms of impedances are equal (or) the ratio of adjacent arms are equal.

$$\text{i.e. } \frac{Z_1}{Z_2} = \frac{Z_3}{Z_4} \quad \rightarrow \text{DM}$$

$$\Rightarrow Z_2 Z_3 = Z_1 Z_4$$

From Wien bridge, $Z_1 = R_1 = jX_{C1}$

$$Z_2 = R_2 \parallel X_{C2} = \frac{-jR_2 X_{C2}}{R_2 - jX_{C2}}$$

$$Z_3 = R_3$$

$$Z_4 = R_4$$

→ DM

$$\Rightarrow \frac{-jR_2 X_{C2}}{R_2 - jX_{C2}} \times R_3 = (R_1 - jX_{C1}) R_4$$

$$\Rightarrow R_2 R_3 (-jX_{C2}) = (R_1 - jX_{C1})(R_2 - jX_{C2}) R_4$$

$$\Rightarrow -jX_{C2} R_2 R_3 = (R_1 R_2 - jX_{C2} R_1 - jX_{C1} R_2 - X_{C1} X_{C2}) R_4$$

$$\Rightarrow -jX_{C2} R_2 R_3 = R_1 R_2 R_4 - jX_{C2} R_1 R_4 - jX_{C1} R_2 R_4 - X_{C1} X_{C2} R_4$$

⇒ R₁R₂R₄ - X_{C1}X_{C2}R₄ + j(R₂R₃X_{C2} - R₁R₄X_{C2} - R₂R₄X_{C1}) = 0

Equating real part to zero, we can get the frequency of oscillations. → 2M

i.e R₁R₂R₄ - X_{C1}X_{C2}R₄ = 0

⇒ R₁R₂ = X_{C1}X_{C2}

⇒ R₁R₂ = 1/ω_{C1} 1/ω_{C2}

⇒ ω² = 1 / (R₁R₂C₁C₂)

⇒ ω = 1 / √(R₁R₂C₁C₂)

⇒ f = 1 / (2π √(R₁R₂C₁C₂)) → 2M

if R₁ = R₂ = R
C₁ = C₂ = C then

f = 1 / (2π RC)

→ 1M

10M

4 + 10 = 14M

7/14/7/22

Prepared by
Y. Madhu Sudhana Reddy,
Dept. of E.C.E
RGKCET, Nandyal.
Call No. - 9440486567

CO- PO Attainment Process (Model Calculations)

Academic Year 2022-23

Regulations R20

Year II Sem II

Batch 21

Branch ECE

Subject (Code) ECA&D&A0409204

Name of the Faculty Dr.Y MADHU SUDHANA REDDY

External Question Paper Marks --> Cos							
Q.No.	CO 1	CO 2	CO 3	CO 4	CO 5	CO 6	Total
1 a)				2			2
b)			2				2
c)						2	2
d)		2					2
e)	2						2
f)					2		2
g)				2			2
2 a)					7		7
b)					7		7
c)							0
3 a)		6					6
b)		8					8
c)							0
4 a)				8			8
b)				6			6
c)							0
5 a)	6						6
b)	8						8
c)							0
6 a)			5				5
b)			4				4
c)			5				5
7 a)						7	7
b)						7	7
c)							0
Total	16	16	16	18	16	16	98

Mid I Marks --> Cos							
Q.No.	CO 1	CO 2	CO 3	CO 4	CO 5	CO 6	Total
1 a)	1						1
b)			1				1
c)		1					1
d)	1						1
e)			1				1
2 a)	3						3
b)				2			2
3 a)			3				3
b)					2		2
4 a)					3		3
b)		2					2
5 a)						3	3
b)						2	2
Total	5	3	5	2	5	5	25

Mid II Marks --> Cos							
Q.No.	CO 1	CO 2	CO 3	CO 4	CO 5	CO 6	Total
1 a)	1						1
b)		1					1
c)			1				1
d)						1	1
e)					1		1
2 a)	2						2
b)				3			3
3 a)		3					3
b)					2		2
4 a)			3				3
b)				2			2
5 a)						3	3
b)	2						2
Total	5	4	4	5	3	4	25

Assignment 1 Marks --> Cos							
----------------------------	--	--	--	--	--	--	--

	CO 1	CO2	CO3	CO4	CO5	CO6	Total
	2	2	2	2	1	1	10

Total	2	2	2	2	1	1	10
--------------	---	---	---	---	---	---	----

Assignment 2 Marks --> Cos

	CO1	CO2	CO3	CO4	CO5	CO6	Total
	2	2	2	2	1	1	10

Total	2	2	2	2	1	1	10
--------------	---	---	---	---	---	---	----

Total	4	4	4	4	2	2	20
-------	---	---	---	---	---	---	----

Total	4	4	4	4	2	2	20
--------------	---	---	---	---	---	---	----

Regulation Weightage of Marks		
R20		
Final exam	Internal tests	Ass/Quiz
70	20	10
0.7	0.2	0.1

Weightage marks for each CO							
	CO 1	CO 2	CO 3	CO 4	CO 5	CO 6	Total
EM	16	16	16	18	16	16	98
IM	10	7	9	7	8	9	50
AM	4	4	4	4	2	2	20

% Weightage of each CO							
	CO 1	CO 2	CO 3	CO 4	CO 5	CO 6	Total
EM (%)	16.3265	16.3265	16.3265	18.3673	16.3265	16.3265	100
IM (%)	20	14	18	14	16	18	100
AM (%)	20	20	20	20	10	10	100
Avg	17.4286	16.2286	17.0286	17.6571	15.6286	16.0286	100

S.No	Reg.No.	Internal marks	Assignment marks	Final Internal marks	Total Final Marks	External Marks
1	21091A0401	-10	10	0	0	0
2	21091A0402	12	10	22	49	27
3	21091A0403	11	10	21	21	0
4	21091A0404	13	10	23	41	18
5	21091A0405	10	10	20	40	20
6	21091A0406	13	10	23	56	33

7	21091A0407	18	10	28	76		48
8	21091A0408	16	10	26	51		25
9	21091A0409	16	10	26	66		40
10	21091A0410	9	10	19	50		31
11	21091A0411	18	10	28	79		51
12	21091A0412	11	10	21	35		14
13	21091A0413	5	10	15	20		5
14	21091A0414	9	10	19	19		0
15	21091A0415	10	10	20	31		11
16	21091A0416	12	10	22	56		34
17	21091A0417	13	10	23	50		27
18	21091A0418	15	10	25	62		37
19	21091A0419	11	10	21	39		18
20	21091A0420	17	10	27	55		28
21	21091A0421	16	10	26	66		40
22	21091A0422	12	10	22	51		29
23	21091A0423	16	10	26	61		35
24	21091A0424	16	10	26	61		35
25	21091A0426	12	10	22	47		25
26	21091A0427	14	10	24	60		36
27	21091A0428	10	10	20	50		30
28	21091A0429	16	10	26	57		31
29	21091A0430	14	10	24	50		26
30	21091A0431	12	10	22	48		26
31	21091A0432	5	10	15	24		9
32	21091A0433	9	10	19	28		9
33	21091A0434	16	10	26	69		43
34	21091A0435	14	10	24	59		35
35	21091A0436	8	10	18	43		25
36	21091A0437	7	10	17	30		13
37	21091A0438	5	10	15	30		15
38	21091A0439	13	10	23	33		10
39	21091A0440	15	10	25	58		33
40	21091A0441	11	10	21	46		25
41	21091A0442	17	10	27	76		49
42	21091A0443	7	10	17	36		19
43	21091A0444	5	10	15	24		9
44	21091A0445	10	10	20	31		11
45	21091A0446	13	10	23	53		30
46	21091A0447	18	10	28	65		37
47	21091A0448	19	10	29	67		38
48	21091A0449	18	10	28	74		46
49	21091A0450	5	10	15	22		7
50	21091A0451	13	10	23	52		29
51	21091A0452	12	10	22	60		38
52	21091A0453	14	10	24	50		26

53	21091A0454	18	10	28	73		45
54	21091A0455	11	10	21	47		26
55	21091A0456	11	10	21	50		29
56	21091A0457	5	10	15	26		11
57	21091A0458	10	10	20	56		36
58	21091A0459	13	10	23	49		26
59	21091A0460	17	10	27	77		50
60	21091A0461	18	10	28	78		50
61	21091A0462	17	10	27	64		37
62	21091A0463	18	10	28	80		52
63	21091A0464	5	10	15	18		3
64	22095A0402	15	10	25	57		32
65	22095A0403	13	10	23	55		32
66	22095A0404	19	10	29	60		31
67	22095A0406	19	10	29	76		47
68	22095A0410	16	10	26	54		28
69	22095A0416	13	10	23	50		27
70	22095A0420	13	10	23	64		41
71	22095A0424	12	10	22	30		8
72	22095A0427	9	10	19	44		25
73	22095A0433	15	10	25	50		25
74	21091A0465	14	10	24	52		28
75	21091A0466	12	10	22	52		30
76	21091A0467	11	10	21	55		34
77	21091A0468	5	10	15	23		8
78	21091A0469	13	10	23	49		26
79	21091A0470	18	10	28	77		49
80	21091A0471	11	10	21	36		15
81	21091A0472	10	10	20	48		28
82	21091A0473	18	10	28	77		49
83	21091A0474	7	10	17	34		17
84	21091A0475	18	10	28	64		36
85	21091A0476	10	10	20	52		32
86	21091A0477	10	10	20	46		26
87	21091A0478	9	10	19	26		7
88	21091A0479	9	10	19	38		19
89	21091A0480	5	10	15	23		8
90	21091A0481	16	10	26	81		55
91	21091A0482	18	10	28	81		53
92	21091A0483	10	10	20	45		25
93	21091A0484	8	10	18	31		13
94	21091A0485	11	10	21	36		15
95	21091A0486	17	10	27	55		28
96	21091A0487	15	10	25	50		25
97	21091A0488	15	10	25	50		25
98	21091A0489	9	10	19	32		13

99	21091A0490	12	10	22	63		41
100	21091A0491	16	10	26	65		39
101	21091A0493	18	10	28	78		50
102	21091A0494	15	10	25	55		30
103	21091A0495	16	10	26	61		35
104	21091A0496	18	10	28	67		39
105	21091A0497	18	10	28	66		38
106	21091A0498	8	10	18	25		7
107	21091A0499	18	10	28	75		47
108	21091A04A0	9	10	19	44		25
109	21091A04A1	13	10	23	48		25
110	21091A04A2	13	10	23	52		29
111	21091A04A3	14	10	24	54		30
112	21091A04A4	18	10	28	60		32
113	21091A04A5	13	10	23	48		25
114	21091A04A6	12	10	22	35		13
115	21091A04A7	14	10	24	51		27
116	21091A04A8	18	10	28	78		50
117	21091A04A9	14	10	24	53		29
118	21091A04B0	14	10	24	64		40
119	21091A04B1	8	10	18	43		25
120	21091A04B2	8	10	18	34		16
121	21091A04B3	16	10	26	73		47
122	21091A04B4	5	10	15	40		25
123	21091A04B5	11	10	21	46		25
124	21091A04B6	7	10	17	28		11
125	21091A04B7	11	10	21	46		25
126	21091A04B9	13	10	23	49		26
127	21091A04C0	19	10	29	80		51
128	21091A04C1	10	10	20	45		25
129	21091A04C2	5	10	15	32		17
130	21091A04C3	17	10	27	60		33
131	21091A04C4	17	10	27	53		26
132	21091A04C5	17	10	27	81		54
133	21091A04C6	19	10	29	87		58
134	21091A04C7	11	10	21	46		25
135	22095A0407	18	10	28	77		49
136	22095A0408	13	10	23	62		39
137	22095A0409	15	10	25	53		28
138	22095A0411	18	10	28	73		45
139	22095A0413	18	10	28	69		41
140	22095A0415	15	10	25	65		40
141	22095A0417	18	10	28	75		47
142	22095A0422	19	10	29	85		56
143	22095A0428	14	10	24	24		
144	22095A0429	18	10	28	71		43

145	22095A0435	17	10	27	55		28
146	22095A0436	16	10	26	61		35
147	21091A04C8	14	10	24	47		23
148	21091A04C9	17	10	27	48		21
149	21091A04D0	7	10	17	41		24
150	21091A04D1	16	10	26	51		25
151	21091A04D2	11	10	21	48		27
152	21091A04D3	17	10	27	40		13
153	21091A04D4	17	10	27	44		17
154	21091A04D5	17	10	27	45		18
155	21091A04D6	17	10	27	49		22
156	21091A04D7	18	10	28	51		23
157	21091A04D8	18	10	28	55		27
158	21091A04D9	13	10	23	49		26
159	21091A04E0	19	10	29	56		27
160	21091A04E1	11	10	21	47		26
161	21091A04E2	18	10	28	52		24
162	21091A04E3	15	10	25	45		20
163	21091A04E4	19	10	29	46		17
164	21091A04E5	12	10	22	39		17
165	21091A04E6	9	10	19	41		22
166	21091A04E7	19	10	29	52		23
167	21091A04E8	17	10	27	54		27
168	21091A04E9	19	10	29	56		27
169	21091A04F0	17	10	27	54		27
170	21091A04F1	17	10	27	52		25
171	21091A04F2	18	10	28	53		25
172	21091A04F3	17	10	27	46		19
173	21091A04F4	14	10	24	49		25
174	21091A04F5	12	10	22	47		25
175	21091A04F6	13	10	23	45		22
176	21091A04F7	19	10	29	48		19
177	21091A04F8	11	10	21	46		25
178	21091A04F9	17	10	27	45		18
179	21091A04G0	14	10	24	42		18
180	21091A04G1	15	10	25	50		25
181	21091A04G2	12	10	22	44		22
182	21091A04G3	13	10	23	50		27
183	21091A04G4	13	10	23	48		25
184	21091A04G5	17	10	27	48		21
185	21091A04G6	10	10	20	37		17
186	21091A04G7	13	10	23	48		25
187	21091A04G8	12	10	22	47		25
188	21091A04G9	17	10	27	47		20
189	21091A04H0	17	10	27	45		18
190	21091A04H1	14	10	24	52		28

191	21091A04H2	12	10	22	48		26
192	21091A04H3	13	10	23	47		24
193	21091A04H5	13	10	23	48		25
194	21091A04H6	15	10	25	53		28
195	21091A04H7	15	10	25	53		28
196	21091A04H8	11	10	21	46		25
197	21091A04H9	19	10	29	54		25
198	21091A04J0	19	10	29	56		27
199	21091A04J1	19	10	29	55		26
200	21091A04J2	17	10	27	52		25
201	21091A04J3	18	10	28	49		21
202	21091A04J4	19	10	29	52		23
203	21091A04J5	15	10	25	48		23
204	21091A04J6	10	10	20	46		26
205	21091A04J7	19	10	29	43		14
206	21091A04J8	18	10	28	52		24
207	21091A04J9	19	10	29	46		17
208	22095A0401	15	10	25	42		17
209	22095A0405	14	10	24	48		24
210	22095A0412	17	10	27	52		25
211	22095A0414	19	10	29	56		27
212	22095A0418	16	10	26	45		19
213	22095A0419	19	10	29	51		22
214	22095A0421	19	10	29	54		25
215	22095A0425	19	10	29	47		18
216	22095A0426	18	10	28	57		29
217	22095A0430	16	10	26	52		26
218	22095A0432	19	10	29	54		25
219	22095A0437	13	10	23	51		28
220	19091A04N9	15	10	25	26		1
221	20091A0482	13	10	23	23		
222	20091A0498	13	10	23	23		
223	20091A04A1	8	10	18	29		11
224	20091A04F0	10	10	20	45		25
225	20091A04M4	14	10	24	53		29
226	21091A04K0	16	10	26	61		35
227	21091A04K1	11	10	21	35		14
228	21091A04K2	18	10	28	57		29
229	21091A04K3	15	10	25	63		38
230	21091A04K4	13	10	23	25		2
231	21091A04K5	7	10	17	24		7
232	21091A04K6	8	10	18	24		6
233	21091A04K7	10	10	20	33		13
234	21091A04K8	15	10	25	62		37
235	21091A04K9	12	10	22	26		4
236	21091A04M0	17	10	27	61		34

237	21091A04M1	18	10	28	59		31
238	21091A04M2	14	10	24	54		30
239	21091A04M3	18	10	28	71		43
240	21091A04M4	7	10	17	42		25
241	21091A04M5	5	10	15	19		4
242	21091A04M6	19	10	29	73		44
243	21091A04M7	18	10	28	59		31
244	21091A04M8	14	10	24	53		29
245	21091A04M9	9	10	19	35		16
246	21091A04N0	12	10	22	30		8
247	21091A04N1	8	10	18	34		16
248	21091A04N2	7	10	17	42		25
249	21091A04N3	12	10	22	50		28
250	21091A04N4	16	10	26	67		41
251	21091A04N5	12	10	22	53		31
252	21091A04N7	13	10	23	54		31
253	21091A04N8	18	10	28	69		41
254	21091A04N9	17	10	27	73		46
255	21091A04P0	11	10	21	36		15
256	21091A04P1	18	10	28	83		55
257	21091A04P2	16	10	26	64		38
258	21091A04P3	19	10	29	82		53
259	21091A04P4	15	10	25	53		28
260	21091A04P5	7	10	17	42		25
261	21091A04P6	16	10	26	54		28
262	21091A04P7	8	10	18	18		0
263	21091A04P8	15	10	25	65		40
264	21091A04P9	16	10	26	59		33
265	21091A04Q0	12	10	22	52		30
266	21091A04Q1	17	10	27	60		33
267	21091A04Q2	7	10	17	46		29
268	21091A04Q3	11	10	21	35		14
269	21091A04Q4	11	10	21	49		28
270	21091A04Q5	11	10	21	34		13
271	21091A04Q6	8	10	18	22		4
272	21091A04Q7	13	10	23	48		25
273	21091A04Q8	12	10	22	38		16
274	21091A04Q9	10	10	20	35		15
275	21091A04R0	6	10	16	41		25
276	21091A04R1	11	10	21	46		25
277	21091A04R2	16	10	26	32		6
278	21091A04R3	5	10	15	16		1
279	21091A04R4	10	10	20	45		25
280	21091A04R5	18	10	28	78		50
281	21091A04R6	11	10	21	49		28
282	21091A04R7	9	10	19	49		30

283	21091A04R8	11	10	21	38		17
284	21091A04R9	18	10	28	63		35
285	21091A04S0	12	10	22	50		28
286	21091A04S1	5	10	15	15		0
287	22095A0423	19	10	29	64		35
288	22095A0431	15	10	25	54		29
289	22095A0434	14	10	24	53		29

% of IM	% of AM	% of EM		N CO 1	N CO 2	N CO 3	N CO 4	N CO 5	N CO 6
-50	100	0		0	3.697183	1.174497	3.398058	-3.8391225	-4.99109
60	100	38.57143		50.53864	49.83903	50.3164	48.92742	46.8895273	47.2167
55	100	0		24.09836	21.81338	23.37248	20.04854	17.6599634	18.5918
65	100	25.71429		43.25527	41.64738	42.74449	40.3583	38.5113607	39.1724
50	100	28.57143		41.68618	41.07143	41.49089	40.0601	37.529381	37.84059
65	100	47.14286		57.30679	56.73793	57.12608	55.96163	54.1812484	54.45124
90	100	68.57143		77.09602	76.14185	76.79291	75.52936	74.969966	75.34505
80	100	35.71429		53.25527	51.27767	52.62704	50.01849	48.8952729	49.6715
80	100	57.14286		67.30679	66.36821	67.00863	65.62182	64.5651606	64.95034
45	100	44.28571		50.84309	51.27515	50.98035	50.70966	47.996866	47.92208
90	100	72.85714		79.90632	79.15996	79.66922	78.65002	78.1039436	78.40081
55	100	20		37.21311	35.89789	36.7953	34.61165	32.285192	32.85205
25	100	7.142857		21.89696	21.66751	21.82407	20.49237	16.7406634	16.94678
45	100	0		21.80328	20.08803	21.25839	18.46278	15.6124314	16.34581
50	100	15.71429		33.25527	32.0171	32.86194	30.6981	28.1274484	28.67329
60	100	48.57143		57.09602	56.88129	57.0278	56.20897	54.2021416	54.34683
65	100	38.57143		51.68618	50.70171	51.37344	49.7203	47.9132933	48.3397
75	100	52.85714		63.34895	62.48742	63.07526	61.70828	60.4074171	60.77158
55	100	25.71429		40.96019	39.92203	40.63039	38.77254	36.4638287	36.92641
85	100	40		57.21311	55.15845	56.5604	53.93204	53.0530165	53.85027
80	100	57.14286		67.30679	66.36821	67.00863	65.62182	64.5651606	64.95034
60	100	41.42857		52.41218	51.85111	52.23394	51.00786	48.9788457	49.25388
80	100	50		62.62295	61.33803	62.21477	60.42071	59.3418647	59.8574
80	100	50		62.62295	61.33803	62.21477	60.42071	59.3418647	59.8574
60	100	35.71429		48.66511	47.82696	48.39885	46.84697	44.8002089	45.17953
70	100	51.42857		61.26464	60.61871	61.05944	59.87517	58.3389919	58.63
50	100	42.85714		51.05386	51.13179	51.07862	50.46232	47.9759728	48.02648
80	100	44.28571		58.87588	57.31388	58.37967	56.25982	55.163228	55.78304
70	100	37.14286		51.89696	50.55835	51.47172	49.47295	47.8924001	48.4441
60	100	37.14286		49.60187	48.833	49.35762	47.88719	45.8448681	46.19812
25	100	12.85714		25.64403	25.69165	25.65916	24.65326	20.9193001	21.02114
45	100	12.85714		30.23419	29.14235	29.88734	27.82478	25.0143641	25.51311
80	100	61.42857		70.1171	69.38632	69.88495	68.74249	67.6991382	68.00611
70	100	50		60.32787	59.61268	60.10067	58.83495	57.2943327	57.61141
40	100	35.71429		44.07494	44.37626	44.17066	43.67545	40.7051449	40.68755

35	100	18.57143		31.68618	31.44115	31.60834	30.39991	27.1454688	27.34148
25	100	21.42857		31.26464	31.72787	31.41179	30.89459	27.1872552	27.13267
65	100	14.28571		35.76112	33.59909	35.0743	32.03652	30.1540872	31.02368
75	100	47.14286		59.60187	58.46328	59.24017	57.54739	56.2287804	56.69722
55	100	35.71429		47.51756	46.96429	47.3418	46.05409	43.7764429	44.05653
85	100	70		76.88525	76.28521	76.69463	75.7767	74.9908592	75.24064
35	100	27.14286		37.30679	37.47736	37.36098	36.64124	33.4134239	33.45302
25	100	12.85714		25.64403	25.69165	25.65916	24.65326	20.9193001	21.02114
50	100	15.71429		33.25527	32.0171	32.86194	30.6981	28.1274484	28.67329
65	100	42.85714		54.49649	53.71982	54.24976	52.84096	51.0472708	51.39547
90	100	52.85714		66.79157	65.07545	66.2464	64.08692	63.4787151	64.14057
95	100	54.28571		68.87588	66.94416	68.26222	65.92002	65.5471402	66.28215
90	100	65.71429		75.22248	74.12978	74.87536	73.44891	72.8806477	73.30787
25	100	10		23.77049	23.67958	23.74161	22.57282	18.8299817	18.98396
65	100	41.42857		53.55972	52.71378	53.29099	51.80074	50.0026116	50.37688
60	100	54.28571		60.84309	60.90543	60.8629	60.36986	58.3807783	58.42119
70	100	37.14286		51.89696	50.55835	51.47172	49.47295	47.8924001	48.4441
90	100	64.28571		74.28571	73.12374	73.91659	72.40869	71.8359885	72.28928
55	100	37.14286		48.45433	47.97032	48.30058	47.09431	44.8211021	45.07512
55	100	41.42857		51.26464	50.98843	51.17689	50.21498	47.9550797	48.13089
25	100	15.71429		27.51756	27.70372	27.5767	26.7337	23.0086184	23.05831
50	100	51.42857		56.67447	57.16801	56.83126	56.70365	54.2439279	54.13802
65	100	37.14286		50.74941	49.69567	50.41467	48.68007	46.8686341	47.32111
85	100	71.42857		77.82201	77.29125	77.6534	76.81692	76.0355184	76.25923
90	100	71.42857		78.96956	78.15392	78.71045	77.6098	77.0592844	77.38223
85	100	52.85714		65.64403	64.21278	65.18936	63.29404	62.4549491	63.01757
90	100	74.28571		80.84309	80.166	80.628	79.69025	79.1486028	79.4194
25	100	4.285714		20.02342	19.65543	19.90652	18.41193	14.651345	14.9096
75	100	45.71429		58.66511	57.45724	58.2814	56.50717	55.1841212	55.67864
65	100	45.71429		56.37002	55.73189	56.16731	54.92141	53.1365892	53.43265
95	100	44.28571		62.3185	59.90191	61.55081	58.63847	58.234526	59.15202
95	100	67.14286		77.30679	75.99849	76.89118	75.28202	74.9490729	75.44945
80	100	40		56.06557	54.29577	55.50336	53.13916	52.0292505	52.72727
65	100	38.57143		51.68618	50.70171	51.37344	49.7203	47.9132933	48.3397
65	100	58.57143		64.80094	64.78622	64.79626	64.2834	62.5385218	62.59995
60	100	11.42857		32.74005	30.72435	32.09971	29.1632	27.0410029	27.86351
45	100	35.71429		45.22248	45.23893	45.22771	44.46833	41.7289109	41.81054
75	100	35.71429		52.10773	50.41499	51.56999	49.22561	47.8715069	48.54851
70	100	40		53.77049	52.57042	53.38926	51.5534	49.9817185	50.48128
60	100	42.85714		53.34895	52.85714	53.19271	52.04808	50.0235048	50.27247
55	100	48.57143		55.94848	56.01861	55.97076	55.41609	53.1783756	53.22383
25	100	11.42857		24.70726	24.68561	24.70038	23.61304	19.8746409	20.00255
65	100	37.14286		50.74941	49.69567	50.41467	48.68007	46.8686341	47.32111
90	100	70		78.03279	77.14789	77.75168	76.56958	76.0146252	76.36364
55	100	21.42857		38.14988	36.90392	37.75407	35.65187	33.3298511	33.87064
50	100	40		49.18033	49.11972	49.16107	48.38188	45.8866545	45.9893

90	100	70		78.03279	77.14789	77.75168	76.56958	76.0146252	76.36364
35	100	24.28571		35.43326	35.46529	35.44343	34.5608	31.3241055	31.41584
90	100	51.42857		65.8548	64.06942	65.28763	63.04669	62.4340559	63.12198
50	100	45.71429		52.9274	53.14386	52.99616	52.54276	50.0652912	50.06366
50	100	37.14286		47.30679	47.10765	47.24353	46.30143	43.7973361	43.95213
45	100	10		28.36066	27.13028	27.9698	25.74434	22.9250457	23.47594
45	100	27.14286		39.60187	39.20272	39.47507	38.227	35.4609559	35.69901
25	100	11.42857		24.70726	24.68561	24.70038	23.61304	19.8746409	20.00255
80	100	78.57143		81.35831	81.45875	81.39022	81.22515	80.2350483	80.22918
90	100	75.71429		81.77986	81.17203	81.58677	80.73047	80.1932619	80.43799
50	100	35.71429		46.37002	46.10161	46.28476	45.26121	42.7526769	42.93354
40	100	18.57143		32.83372	32.30382	32.66539	31.19279	28.1692348	28.46448
55	100	21.42857		38.14988	36.90392	37.75407	35.65187	33.3298511	33.87064
85	100	40		57.21311	55.15845	56.5604	53.93204	53.0530165	53.85027
75	100	35.71429		52.10773	50.41499	51.56999	49.22561	47.8715069	48.54851
75	100	35.71429		52.10773	50.41499	51.56999	49.22561	47.8715069	48.54851
45	100	18.57143		33.98126	33.1665	33.72244	31.98567	29.1930008	29.58747
60	100	58.57143		63.6534	63.92354	63.73921	63.49052	61.5147558	61.47695
80	100	55.71429		66.37002	65.36217	66.04986	64.5816	63.5205014	63.93175
90	100	71.42857		78.96956	78.15392	78.71045	77.6098	77.0592844	77.38223
75	100	42.85714		56.79157	55.44517	56.36385	54.42672	53.0948028	53.64146
80	100	50		62.62295	61.33803	62.21477	60.42071	59.3418647	59.8574
90	100	55.71429		68.66511	67.08753	68.16395	66.16736	65.5680334	66.17774
90	100	54.28571		67.72834	66.08149	67.20518	65.12714	64.5233742	65.15915
40	100	10		27.21311	26.26761	26.91275	24.95146	21.9012797	22.35294
90	100	67.14286		76.15925	75.13581	75.83413	74.48914	73.9253069	74.32646
45	100	35.71429		45.22248	45.23893	45.22771	44.46833	41.7289109	41.81054
65	100	35.71429		49.81265	48.68964	49.4559	47.63985	45.8239749	46.30252
65	100	41.42857		53.55972	52.71378	53.29099	51.80074	50.0026116	50.37688
70	100	42.85714		55.64403	54.58249	55.30681	53.63384	52.0710368	52.51846
90	100	45.71429		62.10773	60.04527	61.45254	58.88581	58.2554192	59.04762
65	100	35.71429		49.81265	48.68964	49.4559	47.63985	45.8239749	46.30252
60	100	18.57143		37.42389	35.75453	36.89358	34.36431	32.2642988	32.95646
70	100	38.57143		52.83372	51.56439	52.43049	50.51318	48.9370593	49.46269
90	100	71.42857		78.96956	78.15392	78.71045	77.6098	77.0592844	77.38223
70	100	41.42857		54.70726	53.57646	54.34803	52.59362	51.0263776	51.49987
70	100	57.14286		65.01171	64.64286	64.89453	64.03606	62.5176286	62.70435
40	100	35.71429		44.07494	44.37626	44.17066	43.67545	40.7051449	40.68755
40	100	22.85714		35.64403	35.32193	35.54171	34.31345	31.3032123	31.52024
80	100	67.14286		73.86417	73.41046	73.72004	72.90337	71.8777749	72.08047
25	100	35.71429		40.63232	41.78823	40.99952	41.29681	37.633847	37.31856
55	100	35.71429		47.51756	46.96429	47.3418	46.05409	43.7764429	44.05653
35	100	15.71429		29.81265	29.42907	29.6908	28.31946	25.0561504	25.3043
55	100	35.71429		47.51756	46.96429	47.3418	46.05409	43.7764429	44.05653
65	100	37.14286		50.74941	49.69567	50.41467	48.68007	46.8686341	47.32111
95	100	72.85714		81.05386	80.02264	80.72627	79.4429	79.1277096	79.52381

50	100	35.71429		46.37002	46.10161	46.28476	45.26121	42.7526769	42.93354
25	100	24.28571		33.13817	33.73994	33.32934	32.97503	29.2765735	29.16985
85	100	47.14286		61.89696	60.18863	61.35427	59.13315	58.2763124	58.94321
85	100	37.14286		55.33958	53.14638	54.64286	51.8516	50.9636981	51.81309
85	100	77.14286		81.56909	81.31539	81.48849	80.97781	80.2141551	80.33359
95	100	82.85714		87.61124	87.06489	87.43768	86.72446	86.4403238	86.65393
55	100	35.71429		47.51756	46.96429	47.3418	46.05409	43.7764429	44.05653
90	100	70		78.03279	77.14789	77.75168	76.56958	76.0146252	76.36364
65	100	55.71429		62.9274	62.77414	62.87872	62.20296	60.4492034	60.56277
75	100	40		54.91803	53.4331	54.44631	52.34628	51.0054845	51.60428
90	100	64.28571		74.28571	73.12374	73.91659	72.40869	71.8359885	72.28928
90	100	58.57143		70.53864	69.0996	70.0815	68.2478	67.6573518	68.21492
75	100	57.14286		66.15925	65.50553	65.95158	64.82894	63.5413946	63.82735
90	100	67.14286		76.15925	75.13581	75.83413	74.48914	73.9253069	74.32646
95	100	80		85.7377	85.05282	85.52013	84.64401	84.3510055	84.61676
70	100	0		27.54098	24.40141	26.54362	22.42718	20.7312614	21.96078
90	100	61.42857		72.41218	71.11167	71.99904	70.32825	69.7466701	70.2521
85	100	40		57.21311	55.15845	56.5604	53.93204	53.0530165	53.85027
80	100	50		62.62295	61.33803	62.21477	60.42071	59.3418647	59.8574
70	100	32.85714		49.08665	47.54024	48.5954	46.35229	44.7584226	45.38834
85	100	30		50.65574	48.1162	49.84899	46.65049	45.7404022	46.72014
35	100	34.28571		41.99063	42.50755	42.15484	41.84235	38.6367198	38.54596
80	100	35.71429		53.25527	51.27767	52.62704	50.01849	48.8952729	49.6715
55	100	38.57143		49.3911	48.97636	49.25935	48.13454	45.8657613	46.09371
85	100	18.57143		43.16159	40.06791	42.17881	38.32871	37.3831288	38.57143
85	100	24.28571		46.90867	44.09205	46.0139	42.4896	41.5617655	42.64579
85	100	25.71429		47.84543	45.09809	46.97267	43.52982	42.6064247	43.66437
85	100	31.42857		51.59251	49.12223	50.80777	47.69071	46.7850614	47.73873
90	100	32.85714		53.67681	50.99095	52.82359	49.52381	48.8534866	49.88032
90	100	38.57143		57.42389	55.01509	56.65868	53.6847	53.0321233	53.95467
65	100	37.14286		50.74941	49.69567	50.41467	48.68007	46.8686341	47.32111
95	100	38.57143		58.57143	55.87777	57.71572	54.47758	54.0558893	55.07767
55	100	37.14286		48.45433	47.97032	48.30058	47.09431	44.8211021	45.07512
90	100	34.28571		54.61358	51.99698	53.78236	50.56403	49.8981457	50.89891
75	100	28.57143		47.42389	45.38481	46.77613	44.0245	42.648211	43.45556
95	100	24.28571		49.20375	45.8174	48.128	44.07536	43.6092975	44.89177
60	100	24.28571		41.17096	39.77867	40.72867	38.5252	36.4429355	37.03081
45	100	31.42857		42.41218	42.22082	42.35139	41.34767	38.5949334	38.75477
95	100	32.85714		54.82436	51.85362	53.88063	50.31669	49.8772525	51.00331
85	100	38.57143		56.27635	54.15241	55.60163	52.89182	52.0083573	52.83168
95	100	38.57143		58.57143	55.87777	57.71572	54.47758	54.0558893	55.07767
85	100	38.57143		56.27635	54.15241	55.60163	52.89182	52.0083573	52.83168
85	100	35.71429		54.40281	52.14034	53.68408	50.81137	49.9190389	50.7945
90	100	35.71429		55.55035	53.00302	54.74113	51.60425	50.9428049	51.91749
85	100	27.14286		48.7822	46.10412	47.93145	44.57004	43.6510838	44.68296
70	100	35.71429		50.96019	49.55231	50.51294	48.43273	46.8477409	47.42552

60	100	35.71429		48.66511	47.82696	48.39885	46.84697	44.8002089	45.17953
65	100	31.42857		47.00234	45.67153	46.57958	44.51919	42.6899974	43.24675
95	100	27.14286		51.07728	47.82948	50.04554	46.1558	45.6986158	46.92895
55	100	35.71429		47.51756	46.96429	47.3418	46.05409	43.7764429	44.05653
85	100	25.71429		47.84543	45.09809	46.97267	43.52982	42.6064247	43.66437
70	100	25.71429		44.40281	42.51006	43.80153	41.15118	39.5351267	40.29539
75	100	35.71429		52.10773	50.41499	51.56999	49.22561	47.8715069	48.54851
60	100	31.42857		45.8548	44.80885	45.52253	43.72631	41.6662314	42.12376
65	100	38.57143		51.68618	50.70171	51.37344	49.7203	47.9132933	48.3397
65	100	35.71429		49.81265	48.68964	49.4559	47.63985	45.8239749	46.30252
85	100	30		50.65574	48.1162	49.84899	46.65049	45.7404022	46.72014
50	100	24.28571		38.87588	38.05332	38.61457	36.93944	34.3954035	34.78482
65	100	35.71429		49.81265	48.68964	49.4559	47.63985	45.8239749	46.30252
60	100	35.71429		48.66511	47.82696	48.39885	46.84697	44.8002089	45.17953
85	100	28.57143		49.71897	47.11016	48.89022	45.61026	44.695743	45.70155
85	100	25.71429		47.84543	45.09809	46.97267	43.52982	42.6064247	43.66437
70	100	40		53.77049	52.57042	53.38926	51.5534	49.9817185	50.48128
60	100	37.14286		49.60187	48.833	49.35762	47.88719	45.8448681	46.19812
65	100	34.28571		48.87588	47.6836	48.49712	46.59963	44.7793157	45.28393
65	100	35.71429		49.81265	48.68964	49.4559	47.63985	45.8239749	46.30252
75	100	40		54.91803	53.4331	54.44631	52.34628	51.0054845	51.60428
75	100	40		54.91803	53.4331	54.44631	52.34628	51.0054845	51.60428
55	100	35.71429		47.51756	46.96429	47.3418	46.05409	43.7764429	44.05653
95	100	35.71429		56.69789	53.86569	55.79818	52.39713	51.9665709	53.04049
95	100	38.57143		58.57143	55.87777	57.71572	54.47758	54.0558893	55.07767
95	100	37.14286		57.63466	54.87173	56.75695	53.43736	53.0112301	54.05908
85	100	35.71429		54.40281	52.14034	53.68408	50.81137	49.9190389	50.7945
90	100	30		51.80328	48.97887	50.90604	47.44337	46.7641682	47.84314
95	100	32.85714		54.82436	51.85362	53.88063	50.31669	49.8772525	51.00331
75	100	32.85714		50.23419	48.40292	49.65244	47.14517	45.7821886	46.51133
50	100	37.14286		47.30679	47.10765	47.24353	46.30143	43.7973361	43.95213
95	100	20		46.39344	42.7993	45.25168	40.95469	40.4753199	41.83601
90	100	34.28571		54.61358	51.99698	53.78236	50.56403	49.8981457	50.89891
95	100	24.28571		49.20375	45.8174	48.128	44.07536	43.6092975	44.89177
75	100	24.28571		44.61358	42.3667	43.89981	40.90384	39.5142335	40.3998
70	100	34.28571		50.02342	48.54628	49.55417	47.39251	45.8030817	46.40693
85	100	35.71429		54.40281	52.14034	53.68408	50.81137	49.9190389	50.7945
95	100	38.57143		58.57143	55.87777	57.71572	54.47758	54.0558893	55.07767
80	100	27.14286		47.63466	45.24145	46.8744	43.77716	42.6273178	43.55997
95	100	31.42857		53.88759	50.84759	52.92186	49.27647	48.8325934	49.98472
95	100	35.71429		56.69789	53.86569	55.79818	52.39713	51.9665709	53.04049
95	100	25.71429		50.14052	46.82344	49.08677	45.11558	44.6539566	45.91036
90	100	41.42857		59.29742	57.02716	58.57622	55.76514	55.1214416	55.99185
80	100	37.14286		54.19204	52.2837	53.58581	51.05871	49.9399321	50.69009
95	100	35.71429		56.69789	53.86569	55.79818	52.39713	51.9665709	53.04049
65	100	40		52.62295	51.70775	52.33221	50.76052	48.9579525	49.35829

75	100	1.428571		29.62529	26.27012	28.55944	24.26029	22.7996866	24.10237
65	100	0		26.39344	23.53873	25.48658	21.6343	19.7074954	20.83779
65	100	0		26.39344	23.53873	25.48658	21.6343	19.7074954	20.83779
40	100	15.71429		30.96019	30.29175	30.74784	29.11234	26.0799164	26.4273
50	100	35.71429		46.37002	46.10161	46.28476	45.26121	42.7526769	42.93354
70	100	41.42857		54.70726	53.57646	54.34803	52.59362	51.0263776	51.49987
80	100	50		62.62295	61.33803	62.21477	60.42071	59.3418647	59.8574
55	100	20		37.21311	35.89789	36.7953	34.61165	32.285192	32.85205
90	100	41.42857		59.29742	57.02716	58.57622	55.76514	55.1214416	55.99185
75	100	54.28571		64.28571	63.49346	64.03404	62.7485	61.4520763	61.79017
65	100	2.857143		28.26698	25.5508	27.40412	23.71475	21.7968138	22.87497
35	100	10		26.06557	25.40493	25.8557	24.15858	20.8775137	21.22995
40	100	8.571429		26.27635	25.26157	25.95398	23.91123	20.8566205	21.33435
50	100	18.57143		35.12881	34.02918	34.77948	32.77855	30.2167668	30.71047
75	100	52.85714		63.34895	62.48742	63.07526	61.70828	60.4074171	60.77158
60	100	5.714286		28.99297	26.7002	28.26462	25.00231	22.8623662	23.78915
85	100	48.57143		62.83372	61.19467	62.31304	60.17337	59.3209715	59.9618
90	100	44.28571		61.17096	59.03924	60.49377	57.84558	57.21076	58.02903
70	100	42.85714		55.64403	54.58249	55.30681	53.63384	52.0710368	52.51846
90	100	61.42857		72.41218	71.11167	71.99904	70.32825	69.7466701	70.2521
35	100	35.71429		42.9274	43.51358	43.11361	42.88257	39.681379	39.56455
25	100	5.714286		20.96019	20.66147	20.86529	19.45215	15.6960042	15.92819
95	100	62.85714		74.49649	72.98038	74.01486	72.16135	71.8150953	72.39368
90	100	44.28571		61.17096	59.03924	60.49377	57.84558	57.21076	58.02903
70	100	41.42857		54.70726	53.57646	54.34803	52.59362	51.0263776	51.49987
45	100	22.85714		36.79157	36.18461	36.59875	35.10633	32.3269783	32.64324
60	100	11.42857		32.74005	30.72435	32.09971	29.1632	27.0410029	27.86351
40	100	22.85714		35.64403	35.32193	35.54171	34.31345	31.3032123	31.52024
35	100	35.71429		42.9274	43.51358	43.11361	42.88257	39.681379	39.56455
60	100	40		51.47541	50.84507	51.27517	49.96764	47.9341865	48.23529
80	100	58.57143		68.24356	67.37425	67.9674	66.66204	65.6098198	65.96893
60	100	44.28571		54.28571	53.86318	54.15149	53.0883	51.068164	51.29106
65	100	44.28571		55.43326	54.72586	55.20853	53.88118	52.09193	52.41406
90	100	58.57143		70.53864	69.0996	70.0815	68.2478	67.6573518	68.21492
85	100	65.71429		74.07494	73.2671	73.81831	72.65603	71.8568817	72.18487
55	100	21.42857		38.14988	36.90392	37.75407	35.65187	33.3298511	33.87064
90	100	78.57143		83.6534	83.1841	83.50431	82.81091	82.2825803	82.47517
80	100	54.28571		65.43326	64.35614	65.09108	63.54138	62.4758423	62.91317
95	100	75.71429		82.9274	82.03471	82.64382	81.52335	81.2170279	81.56099
75	100	40		54.91803	53.4331	54.44631	52.34628	51.0054845	51.60428
35	100	35.71429		42.9274	43.51358	43.11361	42.88257	39.681379	39.56455
80	100	40		56.06557	54.29577	55.50336	53.13916	52.0292505	52.72727
40	100	0		20.65574	19.22535	20.20134	17.6699	14.5886654	15.22282
75	100	57.14286		66.15925	65.50553	65.95158	64.82894	63.5413946	63.82735
80	100	47.14286		60.74941	59.32596	60.29722	58.34027	57.2525464	57.82022
60	100	42.85714		53.34895	52.85714	53.19271	52.04808	50.0235048	50.27247

85	100	47.14286		61.89696	60.18863	61.35427	59.13315	58.2763124	58.94321
35	100	41.42857		46.67447	47.53773	46.94871	47.04346	43.8600157	43.63891
55	100	20		37.21311	35.89789	36.7953	34.61165	32.285192	32.85205
55	100	40		50.32787	49.98239	50.21812	49.17476	46.9104205	47.1123
55	100	18.57143		36.27635	34.89185	35.83653	33.57143	31.2405328	31.83346
40	100	5.714286		24.40281	23.2495	24.03643	21.83079	18.7673022	19.29717
65	100	35.71429		49.81265	48.68964	49.4559	47.63985	45.8239749	46.30252
60	100	22.85714		40.23419	38.77264	39.76989	37.48497	35.3982763	36.01222
50	100	21.42857		37.00234	36.04125	36.69703	34.85899	32.3060851	32.74764
30	100	35.71429		41.77986	42.65091	42.05657	42.08969	38.657613	38.44156
55	100	35.71429		47.51756	46.96429	47.3418	46.05409	43.7764429	44.05653
80	100	8.571429		35.45667	32.16298	34.41035	30.25428	29.0467485	30.31831
25	100	1.428571		18.14988	17.64336	17.98897	16.33148	12.5620266	12.87242
50	100	35.71429		46.37002	46.10161	46.28476	45.26121	42.7526769	42.93354
90	100	71.42857		78.96956	78.15392	78.71045	77.6098	77.0592844	77.38223
55	100	40		50.32787	49.98239	50.21812	49.17476	46.9104205	47.1123
45	100	42.85714		49.90632	50.26911	50.02157	49.66944	46.9522068	46.90349
55	100	24.28571		40.02342	38.916	39.67162	37.73232	35.4191695	35.90782
90	100	50		64.91803	63.06338	64.32886	62.00647	61.3893967	62.10339
60	100	40		51.47541	50.84507	51.27517	49.96764	47.9341865	48.23529
25	100	0		17.21311	16.63732	17.0302	15.29126	11.5173675	11.85383
95	100	50		66.06557	63.92606	65.38591	62.79935	62.4131627	63.22638
75	100	41.42857		55.8548	54.43913	55.40508	53.3865	52.0501436	52.62287
70	100	41.42857		54.70726	53.57646	54.34803	52.59362	51.0263776	51.49987

	CO 1		CO 2		CO 3		CO 4		CO 5		CO 6	
	No. of students Attained	Weightage Points	No. of students Attained	Weightage Points	No. of students Attained	Weightage Points	No. of students Attained	Weightage Points	No. of students Attained	Weightage Points	No. of students Attained	Weightage Points
>= 50%	167	3	152	3	163	3	138	3	120	3	130	3
40% to 50%	65	2	76	2	67	2	89	2	96	2	88	2
<40%	57	1	61	1	59	1	62	1	73	1	71	1
Total No. of students	289		289		289		289		289		289	
Attainment value		2.38		2.31		2.36		2.26		2.16		2.20

% of Attainment		57.79		52.60		56.40		47.75		41.52		44.98
Attained or not		YES		YES		YES		NO		NO		NO

II Year Threshold
50

CO	CO Attainment Value	PO 1	PO 2	PO 3	PO 4	PO 5	PO 6	PO 7	PO 8	PO 9	PO 10	PO 11	PO 12	PS O 1	PS O 2	PS O 3
CO 1	2.17	1	3	2	0	1	0	0	0	0	0	0	1	3	1	0
CO 2	2.10	2	2	0	0	2	0	0	0	0	0	0	2	3	2	0
CO 3	2.15	2	3	2	2	1	0	0	0	0	0	0	2	0	2	1
CO 4	2.07	1	3	2	2	0	0	0	0	0	0	0	1	1	2	1
CO 5	2.01	3	1	0	0	1	0	0	0	0	0	0	2	0	2	1
CO 6	2.03	2	1	1	2	1	0	0	0	0	0	0	0	2	1	1
ECA&D		2.08	2.11	2.11	2.08	2.10	-	-	-	-	-	-	2.10	2.10	2.09	2.07

RGM COLLEGE OF ENGINEERING & TECHNOLOGY (AUTONOMOUS)

20th July 2023

II B.Tech. II Sem. (R20) End Examinations (Regular)
ELECTRONIC CIRCUITS – ANALYSIS AND DESIGN
ECE

Time: 3 Hrs

Total Marks: 70

Note 1: Answer Question No.1 (Compulsory) and 4 from the remaining

2: All Questions Carry Equal Marks

- 1a Define current-shunt negative feedback.
- b Draw the high-frequency hybrid- Π model of BJT.
- c Draw the circuit diagram of class A output stage.
- d When the differential pair can be used as a linear amplifier?
- e Define h_{ic} and h_{re} .
- f Define growing oscillations.
- g Define voltage-series negative feedback.
- 2 a) Draw the circuit diagram of RC-phase shift oscillator and explain its operation. (7)
b) Draw the approximate hybrid model of RC phase shift oscillator and derive the output frequency of RC phase shift oscillator. (7)
- 3 a) Draw the circuit diagram of two-stage CE-CB cascode amplifier and its approximate hybrid model. (6)
b) Explain the h-parameter analysis of the above circuit. (8)
- 4 a) Draw the topology of Current Series feedback amplifier. Derive the expressions for input and output impedances with feedback. (8)
b) For a current series feedback amplifier with $R_S=1K\Omega$, $R_E=1.2K\Omega$ and $R_L=2.2K\Omega$. The transistors with parameters are $h_{ic}=1.1K\Omega$ and $h_{fc}=50$. Calculate G_M , β , D , A_{vf} , R_{if} and R_{of} . (6)
- 5 a) Draw a common-source amplifier using the classical biasing arrangement (voltage divider biasing) and draw its equivalent circuit. (6)
b) Analyse the above circuit to find R_{in} , R_o , and Voltage Gain (8)
- 6 A common source amplifier has $C_{C1}=C_{C2}=C_S=1\mu F$, $R_G=10M\Omega$, $R_{Sig}=100K\Omega$, $g_m=2mA/V$, $R_D=R_L=R_S=10K\Omega$. Find
 - a) Mid band gain A_M (3)
 - b) f_{p1} (2)
 - c) f_{p2} (2)
 - d) f_{p3} (2)
 - e) f_z and f_l (5)

- 7 a) Show that the maximum efficiency of series fed class A power amplifier is 25%. (7)
- b) A class B push pull amplifier supplies power to a resistive load of 12Ω . The output transformer has a turns ratio of 3:1 and efficiency of 78.5%. Assume $V_{CC} = 20V$ and $h_{fe} = 25$. Calculate (7)
- Maximum power output
 - Maximum power dissipation in each transistor.
 - Maximum base and collector currents for each transistor.

- xxx -



2

a) Based on the RC oscillations are classified into 3 types. They are

- i) RC phase
- ii) LC oscillations
- iii) crystal oscillators

Again RC oscillators are classified into two types

Subject: Electronic Circuits analysis and Design
 Q.P. Code: A0409204R0723

Subject: Electronic Circuits analysis and Design
 Q.P. Code: A0409204R0723

7-60

For Office Use							
12409041							
VALUATION-II							
Q.No.	1	2	3	4	5	6	7
A							
B							
C							
D							
E							
F							
G							
TOTAL							
GRAND TOTAL							
(in words)							
Signature of the Examiner							
Signature of the Scrutinizer							

For Office Use							
12409041							
VALUATION-I							
Q.No.	1	2	3	4	5	6	7
A	2	6		7	5		7
B	0	7		4	6		6
C	1						
D	0						
E	2						
F	0						
G	2						
TOTAL	7	13		11	11		13
GRAND TOTAL		55					
(in words) <u>fifty five</u>							
<i>CPB</i>							
Signature of the Examiner							
Signature of the Scrutinizer							

7-60

For Office Use							
12409041							

2


8) Based on the RC oscillations are classified into 3 types. they are

- 1) RC phase
- 2) LC oscillations
- 3) crystal oscillators

Again RC oscillators are classified into two types they are :-

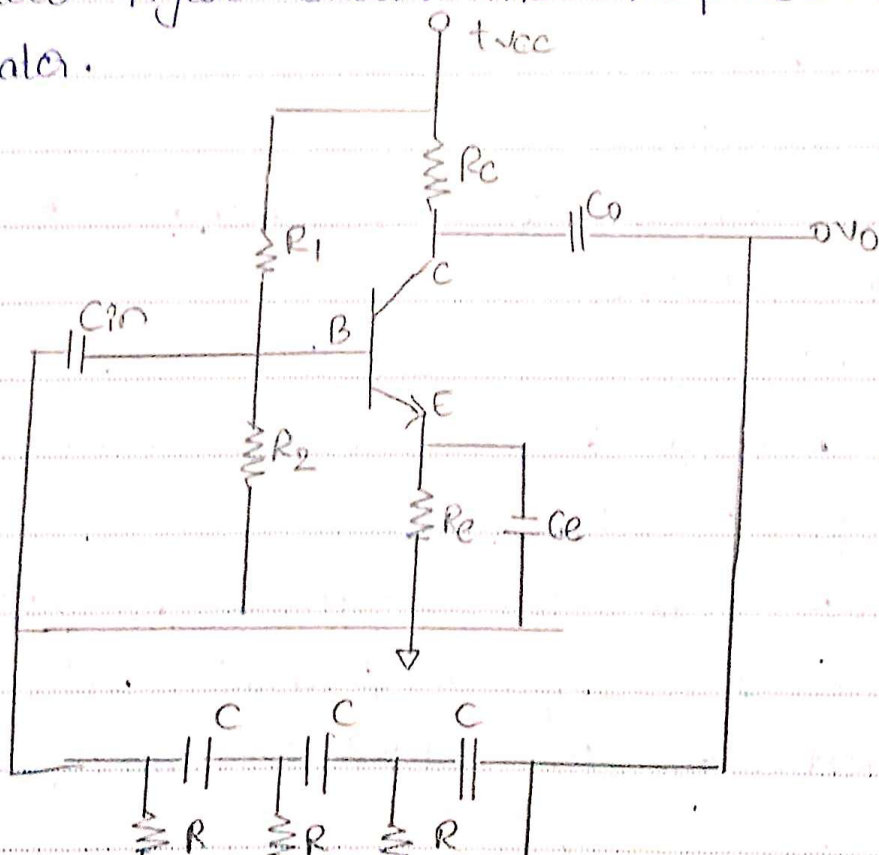- 1) RC phase shift oscillators
- 2) Wien bridge oscillations.

The below figure shows the RC phase-shift oscillator.



For the use of Evaluator Only

Q.No	Marks

Q.No	Marks

Q.No	Marks



The above figure shows the RC-phase shift oscillations and common emitter amplifier with a voltage divider biasing.

Let R_1 and R_2 are the resistors acts as a voltage divider biasing.

There are 3 capacitors are connected to in series with a resistor (R)

→ In a RC-phase shift oscillator produces 130° phase shift

→ another feedback network produces a 180° phase shift.

→ overall phase shift produces a 360° of a oscillators.

→ but general oscillations they can't produce any phase shift.

→ In these positive feedback amplifiers also used not negative feedback networks are used. due to sufficient stabilization.

Q.No	Marks


For the use of Evaluator Only

Q.No	Marks

Q.No	Marks



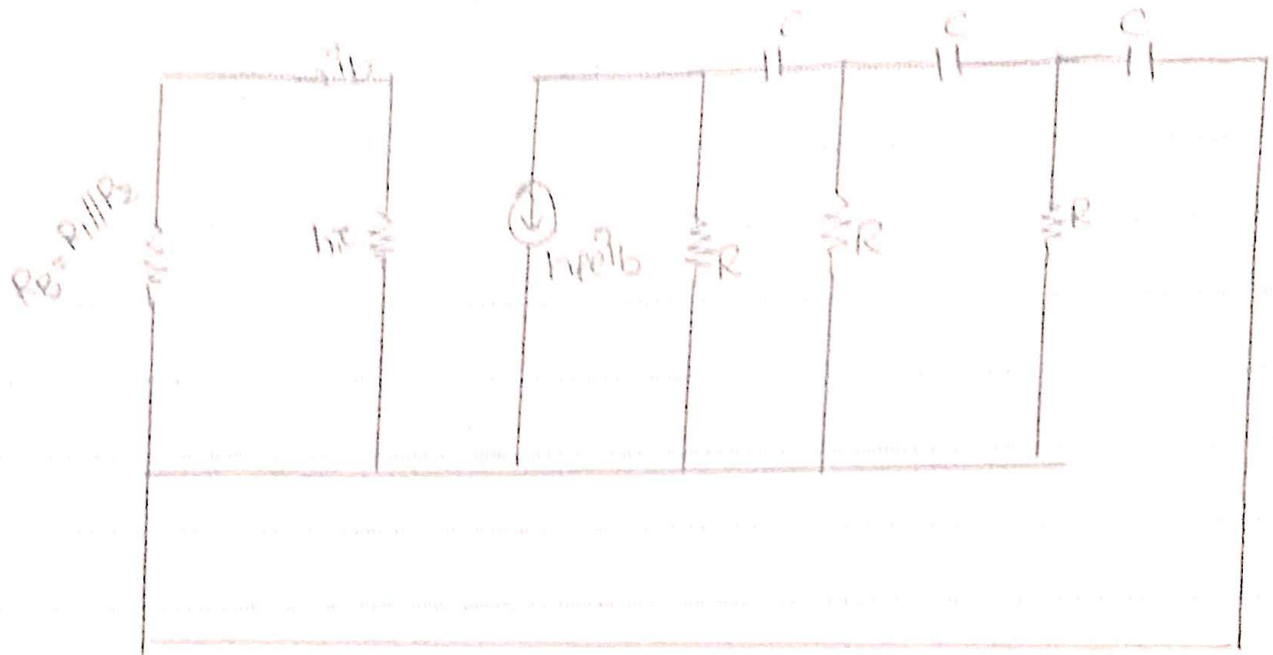Generalized RC phase shift oscillations are drawn below figure.



where $R_B = R_1 // R_2$

$$f = \frac{1}{2\pi RC\sqrt{10}}$$

$$f = \frac{1}{2\pi RC\sqrt{6-4k}}$$

where $k = \frac{R_C}{R}$


For the use of Evaluator Only

Q.No	Marks

Q.No	Marks
2a	6

Q.No	Marks

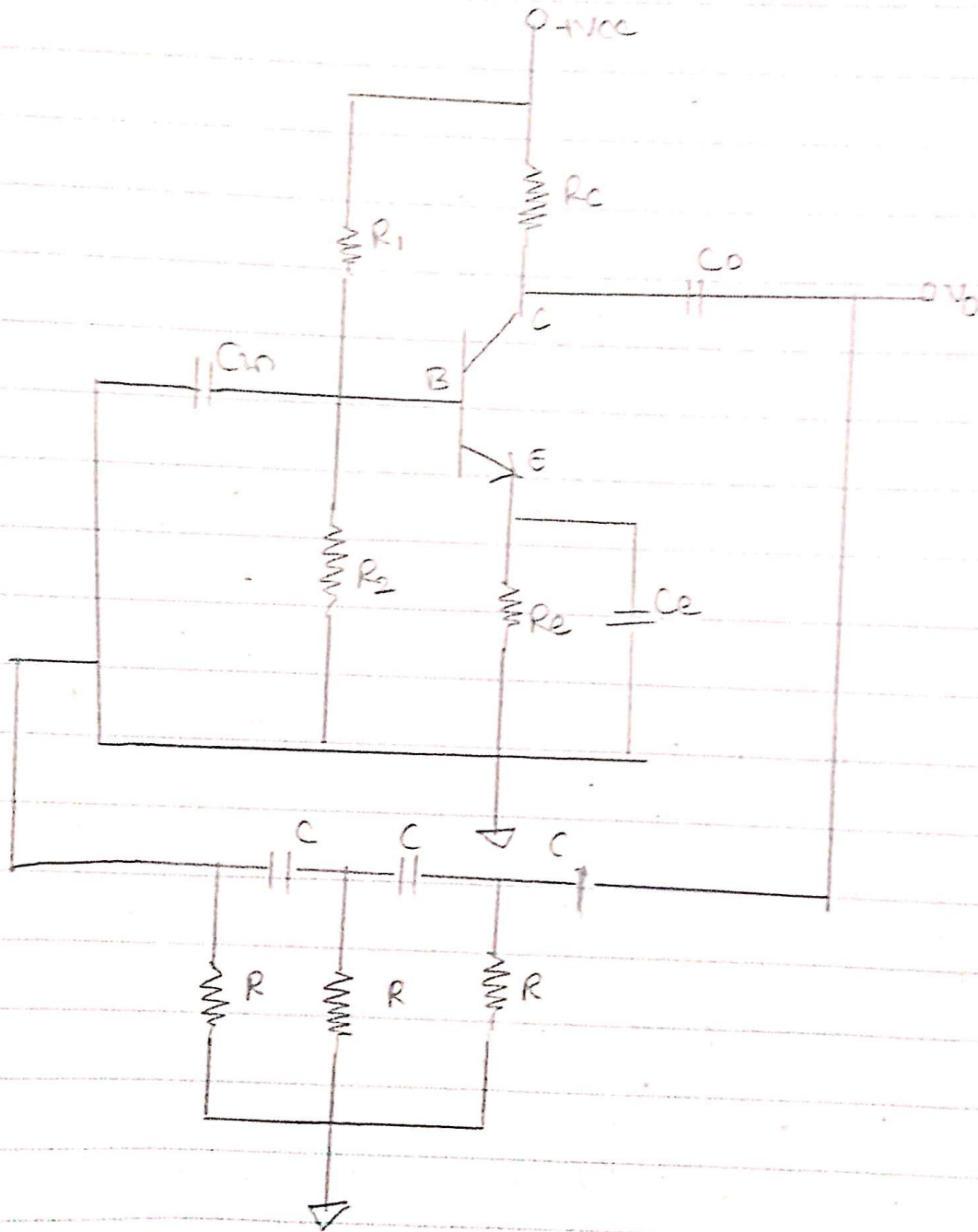b) The below figure shows the RC phase shift oscillations and voltage divider biasing circuit shown in below figure.



For the use of Evaluator Only


Q.No	Marks

Q.No	Marks


Q.No	Marks



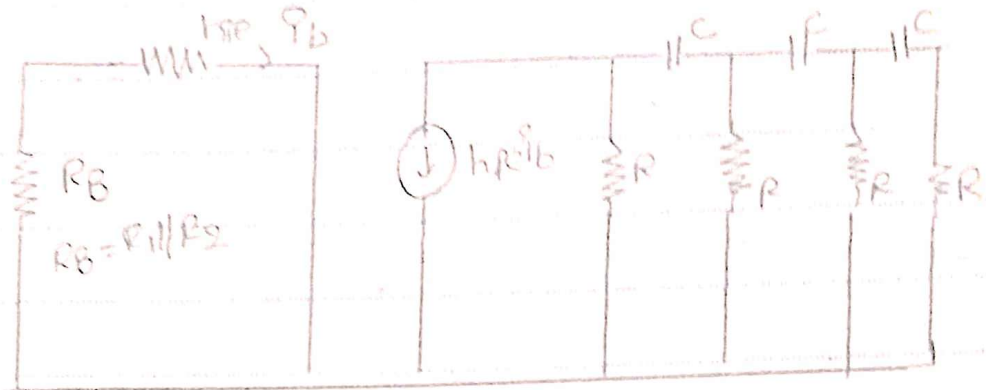The below figure shows the approximate hybrid model of a RC phase shift oscillator



Consider the below figure

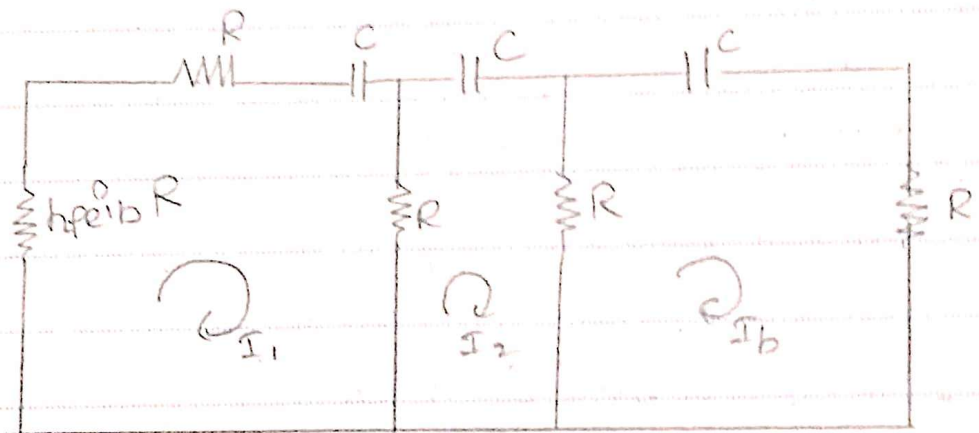

Apply the KVL to the 1st loop; we get

$$hfe ib R + R I_1 + \frac{I_1}{j\omega C} + R(I_1 - I_2) = 0$$

$$hfe ib R + R I_1 + \frac{I_1}{j\omega C} + R I_1 - R I_2 = 0$$

$$I_1 (gR + \frac{1}{j\omega C}) - R I_2 + hfe ib R = 0 \quad \text{--- (1)}$$

For the use of Evaluator Only

Q.No	Marks

Q.No	Marks

Q.No	Marks



Apply kvl to the 2nd loop

$$\rightarrow R(I_2 - I_1) + \frac{I_2}{j\omega C} + R(I_2 - I_b) = 0$$

$$R I_2 - R I_1 + \frac{I_2}{j\omega C} + R I_2 - R I_b = 0$$

$$-R I_1 - R_2 I_2 + \frac{I_2}{j\omega C} + R I_2 - R I_b = 0$$

$$-R I_1 + I_2 (2R + \frac{1}{j\omega C}) - R I_b = 0 \rightarrow (2)$$

\Rightarrow Apply kvl to the loop 3 ; we get

$$R(I_b - I_2) + \frac{I_b}{j\omega C} + R I_b = 0$$

$$R I_b - R I_2 + \frac{I_b}{j\omega C} + R I_b = 0$$

$$-R I_2 + I_b (2R + \frac{1}{j\omega C}) = 0 \rightarrow (3)$$

we can equate the eq (1) & (2) & (3) ; we get

let put

$$\frac{1}{j\omega C} = -jX_C$$

then;

For the use of Evaluator Only

Q.No	Marks

Q.No	Marks

Q.No	Marks

$$\begin{vmatrix} 2R - j\omega C & -R & h_{fe}R \\ -R & 2R - j\omega C & -R \\ 0 & -R & 2R - j\omega C \end{vmatrix} = 0$$

$$(2R - j\omega C) \left[(2R - j\omega C)(2R - j\omega C) - R^2 \right] + R \left[-R(2R - j\omega C) - 0 \right]$$

$$+ h_{fe}R \left[R^2 - 0 \right] = 0$$

$$(2R - j\omega C)^3 - (2R - j\omega C)^2 R^2 + R \left[-2R^2 + j\omega C R \right] + R^3 h_{fe} = 0$$

$$\because (a-b)^3 = a^3 - b^3 - 3ab(a-b)$$

$$(2R)^3 - (j\omega C)^3 - 3(2R)(j\omega C)(2R - j\omega C) + 2R^3 + R^2 j\omega C + R^3 h_{fe} = 0$$

$$8R^3 + j\omega^3 C^3 - 6R^2 j\omega C + 6R^2 \omega^2 C^2 - 2R^3 + R^2 j\omega C - 2R^3 + R^2 j\omega C + R^3 h_{fe} = 0$$

$$4R^3 + j\omega^3 C^3 - 12R^2 j\omega C + 6R^2 \omega^2 C^2 - 2R^3 + R^2 j\omega C - 2R^3 + R^2 j\omega C + R^3 h_{fe} = 0$$

$$4R^3 + j\omega^3 C^3 - 10R^2 j\omega C - 6R^2 \omega^2 C^2 + R^3 h_{fe} = 0$$

$$(4R^3 - 6R^2 \omega^2 C^2 + R^3 h_{fe}) + j(\omega^3 C^3 - 10R^2 \omega C) = 0$$

For the use of Evaluator Only

Q.No	Marks

Q.No	Marks

Q.No	Marks



By equating the Imaginary part

$$X_C^3 - 10XR^2 = 0$$

$$X_C^3 = 10R^2 X_C$$

$$X_C^2 = 10R^2$$

$$X_C = \sqrt{10} R //$$

By equating the Real parts we get

$$4R^3 - 6RX_C^2 + R^3 h_{fe} = 0$$

$$4R^3 - 6R(10R^2) + R^3 h_{fe} = 0$$

$$4R^3 - 60R^3 + R^3 h_{fe} = 0$$

$$R^3(4 - 60 + h_{fe}) = 0$$

$$4 - 60 + h_{fe} = 0$$

$$-56 + h_{fe} = 0$$

$$h_{fe} = 56$$

$$\therefore h_{fe} = 56$$

$$\therefore h_{fe} = 56$$

Q.No	Marks

For the use of Evaluator Only

Q.No	Marks

Q.No	Marks

$$f = \frac{1}{2\pi RC \cdot 10}$$

$$f = \frac{1}{2\pi RC \sqrt{6+4k}}$$

where $k = \frac{Rc}{C_{11}}$

where $f =$ frequency of oscillator

$R =$ resistor

$C =$ capacitor

$k =$ constant.

For the use of Evaluator Only

Q.No	Marks

Q.No	Marks
26	7


Q.No	Marks

4.

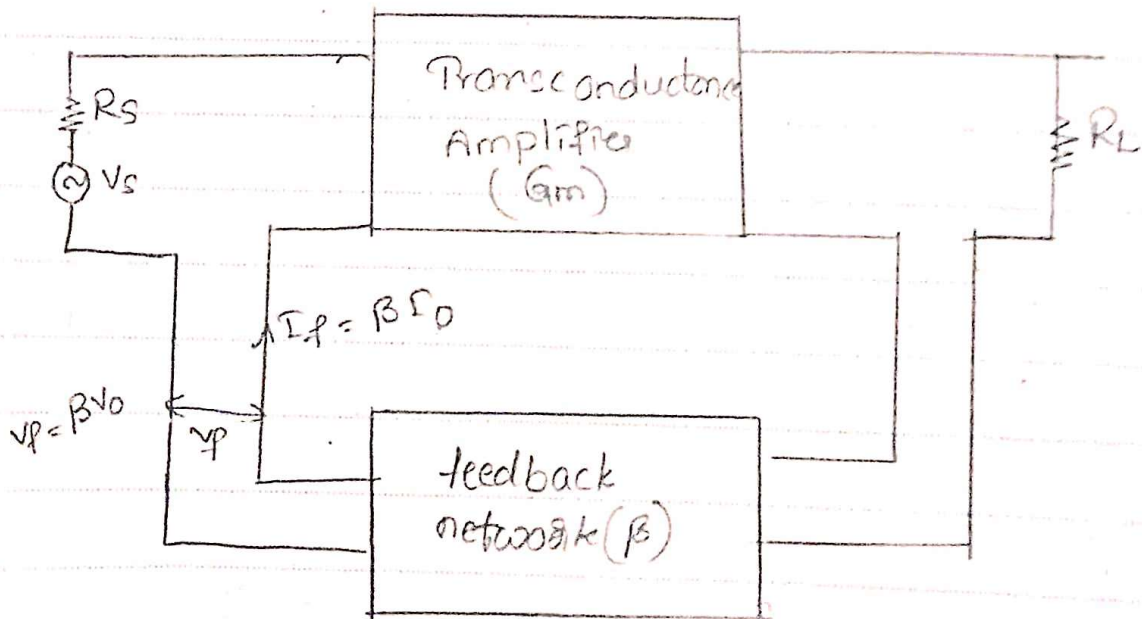a) Current series feedback amplifier is also called as a series CE amplifier.

→ the current series feedback amplifier the basic amplifier is transconductance and feedback network (β) can be sampled circuit.

the below figure shows the current series feedback amplifier.



For the use of Evaluator Only

Q.No	Marks

Q.No	Marks

Q.No	Marks



Input Impedance:

Input impedance without feedback

$$Z_{in} = \frac{V_{in}}{I_{in}}$$

Input impedance with feedback $Z_{if} = \frac{V_s}{I_{in}}$

$$V_{in} = V_s + V_f$$

$$V_s = V_{in} - V_f$$

$$\text{Let } V_f = \beta V_o$$

$$V_o = A_{v_m} V_{in}$$

$$V_{in} = (-\beta A_{v_m} V_{in}) + V_s$$

$$V_{in} + \beta A_{v_m} V_{in} = V_s$$

$$V_{in} (1 + \beta A_{v_m}) = V_s$$

$$\frac{V_{in}}{I_{in}} (1 + \beta A_{v_m}) = \frac{V_s}{I_{in}}$$

$$\frac{V_s}{I_{in}} = \frac{V_{in}}{I_{in}} (1 + \beta A_{v_m})$$

$$Z_{if} = Z_{in} (1 + G_m \beta) \quad \parallel$$

For the use of Evaluator Only

Q.No	Marks

Q.No	Marks

Q.No	Marks



in output impedance:

output sampled across it can be defined by

t.t.c. r_{o1} , where;

$$r_{o1} = \frac{v_{o1}}{i_{o1}} \quad | \quad v_{o2} = 0 ; R_L \rightarrow \infty$$

$$v_{o1} = v_{o2} = v_o$$

$$\text{where } v_o = \beta v_b$$

$$v_o = \beta i_{b1} r_{o1}$$

$$\text{where } v_{b1} = 0 ; i_{b1} = i_{o1}$$

$$v_{o1} = -\beta i_{o1} r_{o1}$$

$$v_{o1} = -\beta v_o$$

$$v_o = -r_{o1} (1 + \beta \beta)$$

$$r_{o1} = r_{o1} (1 + \beta \beta)$$

$$\therefore r_{o1} = r_{o1} (1 + \beta \beta)$$

Q.No	Marks

For the use of Evaluator Only

Q.No	Marks

Q.No	Marks



b) Given that

$$R_S = 1\text{ k}\Omega$$


$$R_E = 1.2\text{ k}\Omega$$

$$R_L = 2.2\text{ k}\Omega$$

h-parameters are $h_{ie} = 1\text{ k}\Omega$

$$h_{fe} = 50$$

In a current series feedback amplifier

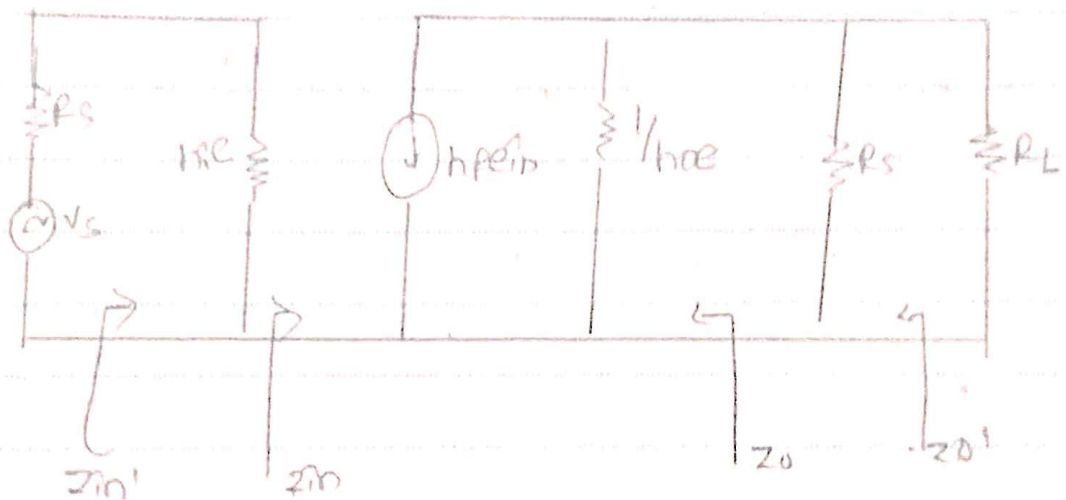

$$\beta = \frac{V_o}{V_f}$$

In common emitter $V_o = V_f$

$$\beta = \frac{V_o}{V_f}$$

$$\beta = \frac{V_f}{V_f} = 1$$

$$\therefore \beta = 1$$

For the use of Evaluator Only

Q.No	Marks
49	7

Q.No	Marks

Q.No	Marks



$$\begin{aligned}
 2) \quad Z_{in}(s) &= h_{ie} + h_{ie} R_1 \\
 &= 1k\Omega + 2.9k\Omega \\
 &= 3.9k\Omega
 \end{aligned}$$

Time: 8.00

$$3) \quad A_v = \frac{A_{\beta} \cdot R_L}{Z_{in}}$$

$$A_{\beta} = \frac{h_{fe}}{h_{ie} R_{L1}}$$

$$= \frac{50}{2.9k\Omega \cdot (2.2k\Omega + 1)}$$

$$A_{\beta} = 49.6$$

$$A_v = \frac{A_{\beta} \cdot R_L}{Z_{in}} = \frac{49.6 \times 2.2k\Omega}{3.9k\Omega}$$

$$A_v = 27.59$$

$$R_{of} = Z_o = \frac{h_{ie}}{h_{ie} h_{oe} + h_{fe} h_{fe}}$$

For the use of Evaluator Only

Q.No	Marks

Q.No	Marks

Q.No	Marks



$$\frac{1.132}{1.1 \times 10^3 (2.4 \times 10^6)} = 0.00047$$

$$R_oP = 244.61$$

$$G_m = \frac{2.70}{D}$$

$$D = (1 + A_v \beta)$$

$$= 1 + 49.6(1)$$

$$= 1 + 49.6$$

$$= 50.6$$

$$G_m = \frac{2.7}{50.6}$$

$$G_m = 0.171$$

Ans

For the use of Evaluator Only


Q.No	Marks
4b	4

Q.No	Marks

Q.No	Marks

7
 a) class A power amplifier it can be defined by the maximum common emitter configuration with moves from one wave of full cycle to another half cycles is known.

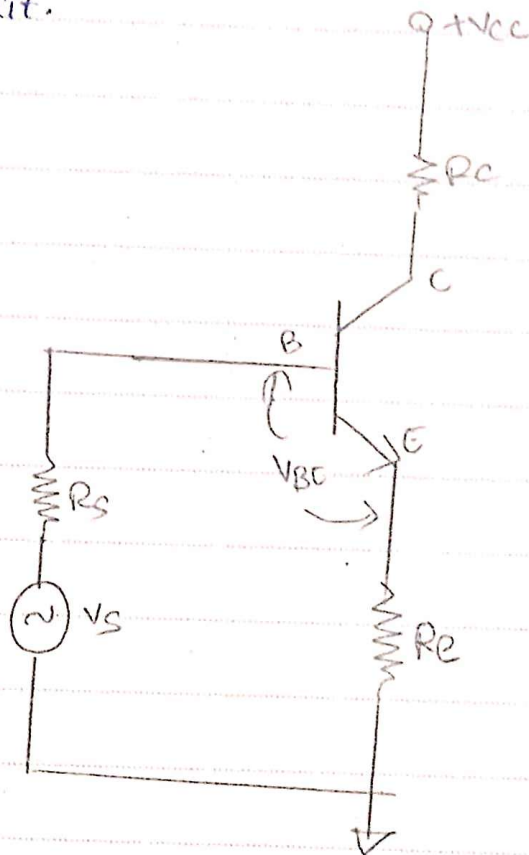The below figure shows the common collector circuit.



Apply kvl to P.P. loop

$$V_s - V_{BE} - I_E R_E = 0$$

$$V_s = I_E R_E + V_{BE} = 0$$

$$V_{BE} = I_E R_E - V_{BE} \Rightarrow V_{BE} = \frac{V_s}{2} - I_E R_E$$

For the use of Evaluator Only

Q.No	Marks

Q.No	Marks

Q.No	Marks





Apply KVL to OLP loop

$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

$$V_{CE} = -V_{CE} + I_E R_E + I_C R_C$$

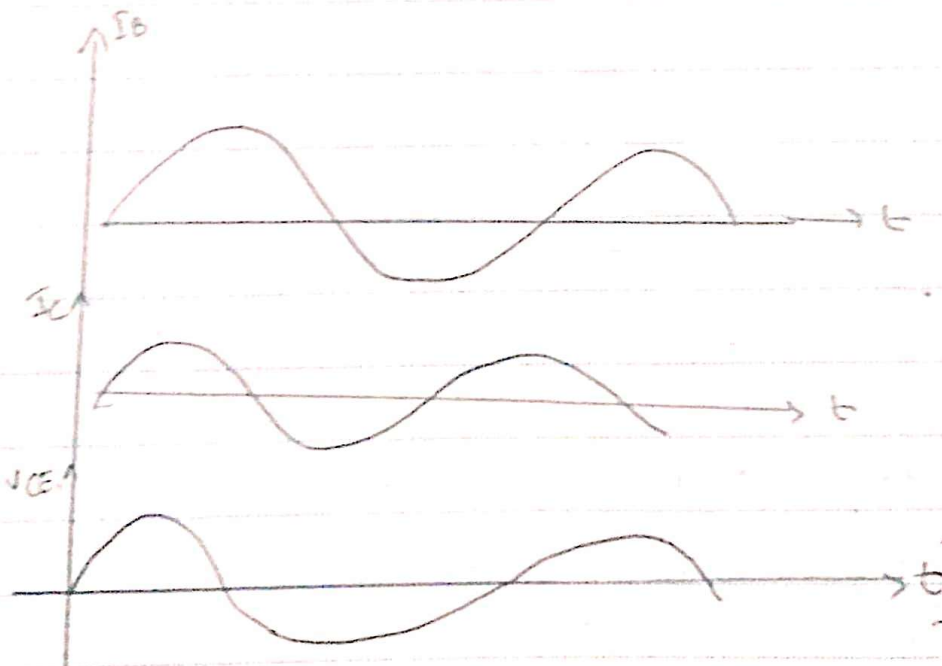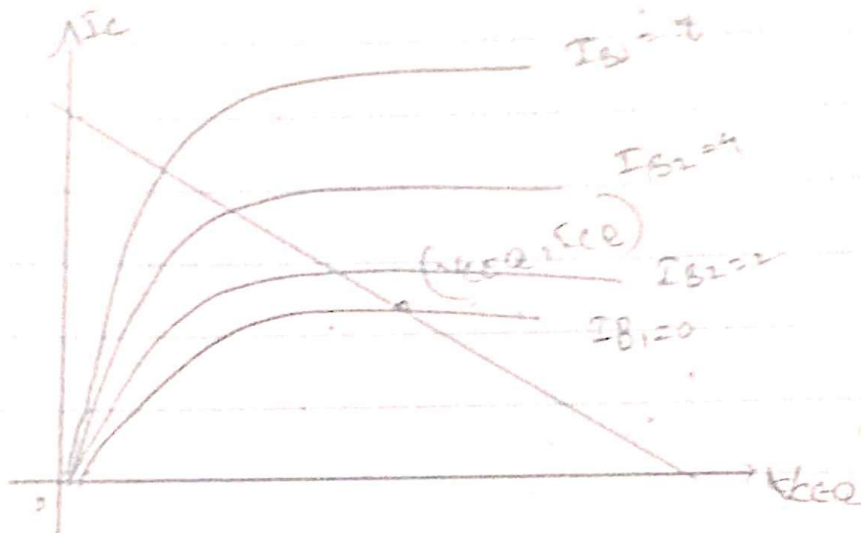The below figure shows the class A power amplifier



For the use of Evaluator Only

Q.No	Marks

Q.No	Marks



Q.No	Marks

DC Power P

In DC power amplifier

$$P_{dc} = V_{dc} \times I_{dc}$$

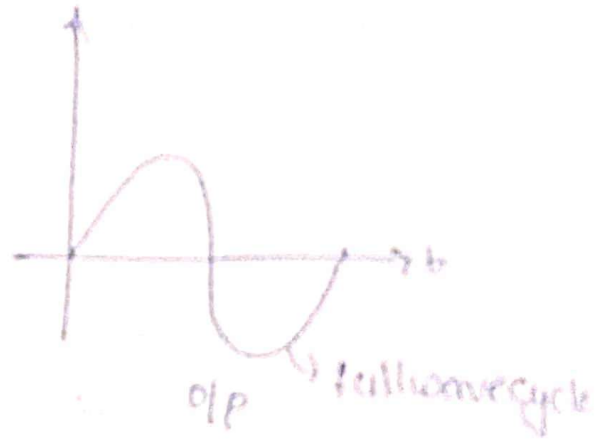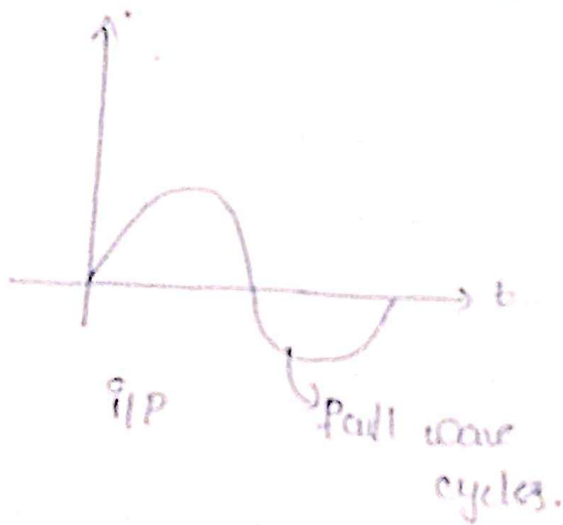The class-A power amplifier its common collector moves to 50% of full wave cycles.



AC power:

$$P_{ac} = \frac{(V_{max} - V_{min}) \times (I_{max} - I_{min})}{8}$$

where V_{max} = maximum voltage

V_{min} = minimum voltage

I_{max} = maximum current

For the use of Evaluator Only

Q No	Marks

Q No	Marks

Q No	Marks



Define minimum current

Distortion Power Amplifier:

It can be defined by the maximum power in Distortion Power Amplifier is equal to power amplifier in AC to power amplifier in DC.

$$\therefore P_D = P_{DC} - P_{AC}$$

% efficiency:

$$\eta = \frac{P_{AC}}{P_{DC}} \\ = \frac{(V_{max} - V_{min}) \times (I_{max} - I_{min})}{8 \times V_{dc} \times I_{dc}} \times 100$$

PA $V_{min} = 0$

$I_{min} = 0$

$$= \frac{(V_{max} - 0) (2I_{max} - 0)}{8 \times V_{dc} \times I_{dc}} \times 100$$

$$= \frac{2 \times V_{dc} \times I_{dc}}{8 \times V_{dc} \times I_{dc}} \times 100 \Rightarrow \frac{100}{4} = 25\%$$

$V_{ce} = V_{dc}$

$V_{dc} = V_{ce}$

$\therefore \eta = 25\%$

$\therefore \eta = 25\%$

For the use of Evaluator Only

Q.No	Marks

Q.No	Marks
7A	7

Q.No	Marks



i) maximum efficiency of series feed class
A power amplifier

$$\eta = 25\%$$

b) Given that

A class B push pull amplifier

Resistive load = $12\ \Omega$

output transformer has turns ratio
3:1

$$\text{i.e.; } \frac{n_1}{n_2} = 3/1$$

$$\eta = 78.5\%$$

Assume $V_{CC} = 20\text{V}$

$$h_{FE} = 25$$

ii) maximum power output

$$V_{rms} = \frac{2V_m}{2}$$

$$I_{rms} = \frac{2V_m}{\pi R}$$

For the use of Evaluator Only

Q.No	Marks

Q.No	Marks

Q.No	Marks

$$P_{max} = V_{rms} \times I_{rms}$$

$$\Rightarrow \frac{2V_m}{\sqrt{2}} \times \frac{2V_m}{\sqrt{2}}$$

$$= \frac{2V_m}{\sqrt{2}} \times \frac{V_m}{\sqrt{2}}$$

$$\Rightarrow \frac{2V_m}{\sqrt{2}}$$

$$P_{max} = V_{rms} \times I_{rms}$$

$$R_L' = \left(\frac{n_1}{n_2}\right) R_L$$

$$= \frac{3}{1} (12 \Omega)$$

$$= 36 \Omega$$

$$V_m = I \times R_L'$$

$$= 36 \times 0.12 = 3.6 \times 10^{-3}$$

$$= 0.12$$

$$P_{max} = \frac{2(0.12)}{\sqrt{2}}$$

$$= 0.07 \text{ watts}$$

For the use of Evaluator Only

Q.No	Marks

Q.No	Marks

Q.No	Marks



2) maximum power dissipation

$$P_D = P_{dc} - P_{ac}$$

$$P_D = 21.03 - 62.38 \times 10^{-3}$$

$$P_D = 20.9672$$

3) maximum base and collector for each transistor

$$\frac{(V_{max} - V_{min}) \times (I_{max} - I_{min})}{8 \times V_{ce} \times I_c} \times 100$$

$$\frac{(2V_{max} - 0) (2I_{max} - 0)}{8 \times V_{ce} \times I_c} \times 100$$

$$\frac{4I_{max} V_{ce} \times I_c}{8 V_{ce} \times I_c} \times 100$$

$$I_{BP} = I_{cQ}$$

$$\frac{1}{2} \times 100 = 50\%$$

$$h_{FE} = 25 \Rightarrow \frac{h_{FE}}{h_{oe}} = \frac{25}{50} = 0.5$$

For the use of Evaluator Only


Q.No	Marks
7b	6

Q.No	Marks

Q.No	Marks



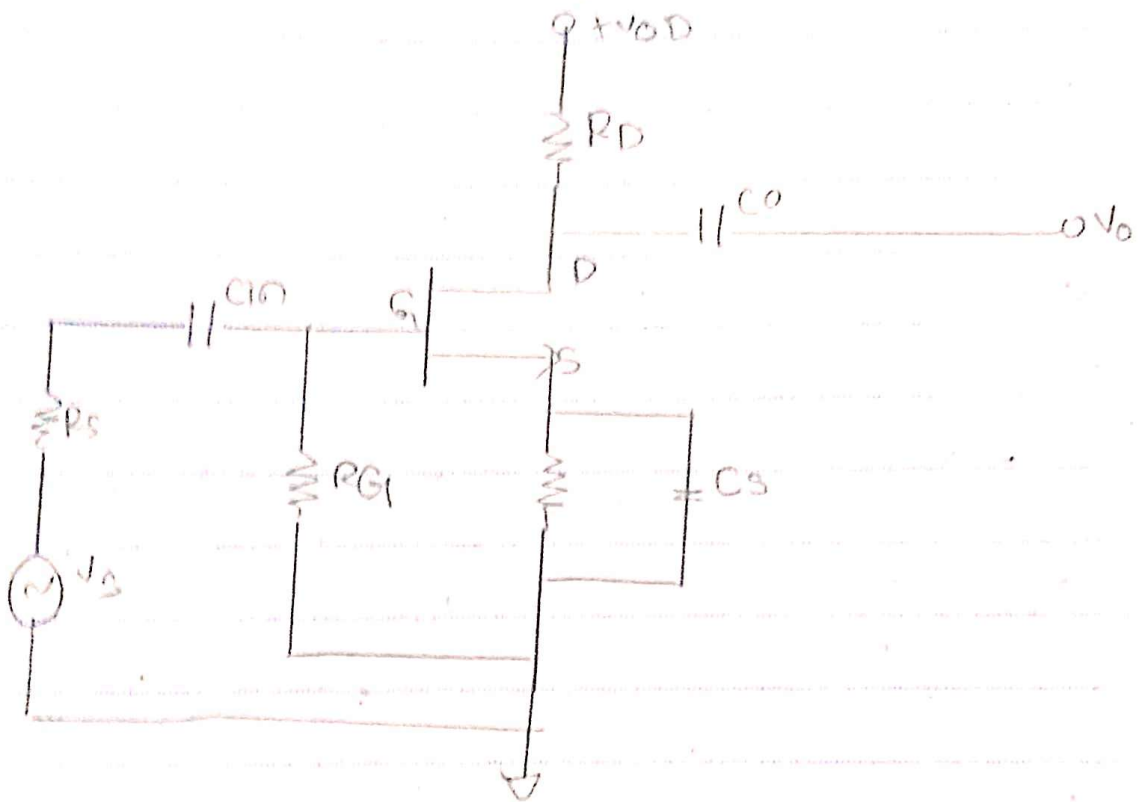2) The below figure shows the common source amplifier of FET and voltage divider biasing. R_E will act as a voltage biasing as shown in a below figure.




For the use of Evaluator Only

Q.No	Marks

Q.No	Marks

Q.No	Marks

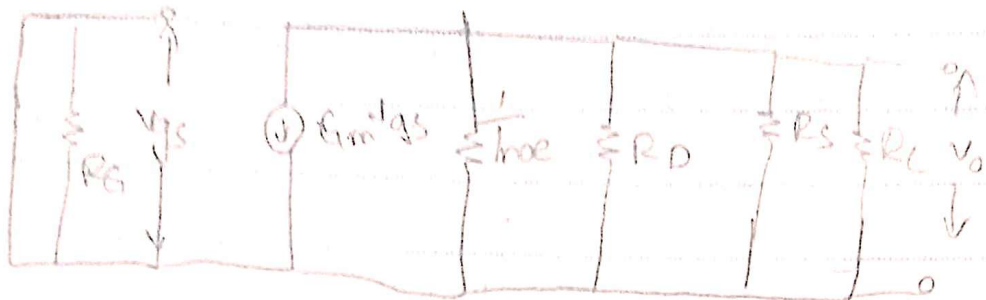Equivalent circuit of a common source amplifier is



b) For common source amplifier,
 Z_{in} (input impedance)

$$= \frac{V_{in}}{I_{in}}$$

$$Z_{in} = \frac{V_{gs}}{I_G}$$

Z_{in} = It is the ratio of input voltage to input current. It is known as an input impedance.

• For Z_o = output impedance

$$Z_o = \frac{O/P \text{ (Voltage)}}{O/P \text{ (Current)}}$$

$$= \frac{V_{gs}}{R_D + r_{ds}}$$

Z_o = It is the ratio of output voltage to output current. It is known as an output impedance.

For the use of Evaluator Only

Q.No	Marks
5a	5

Q.No	Marks

Q.No	Marks



Voltage Gain

$$V_v = \frac{A_I \cdot Z_L}{Z_{in}}$$

$$= \frac{V_{gs} \cdot I_{G1} \cdot R_L}{G_{m1} \cdot R_{L \parallel R_d}}$$


$$R_L = R_D \parallel R_L$$

Where $R_{L \parallel R_d} = \frac{R_D \cdot R_L}{R_D + R_L}$

G_m = conductance.

voltage gain A_v
 it is the ratio of output voltage to input voltage
 is known as a voltage gain (A_v)

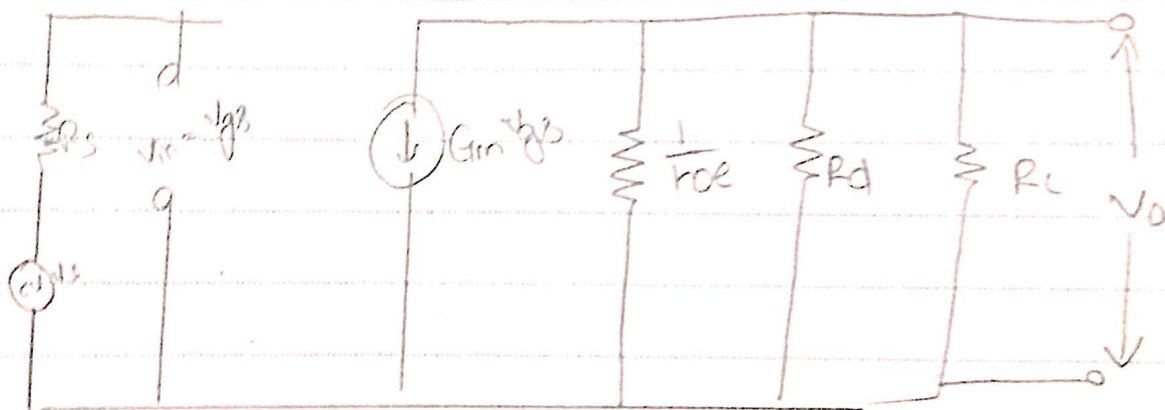Equivalent circuit of a common-source amplifier



$$Z_{in} = \frac{R_{in}}{D}$$

$$Z_o = \frac{Z_D}{A_I}$$

For the use of Evaluator Only


Q.No	Marks

Q.No	Marks
56	6

Q.No	Marks




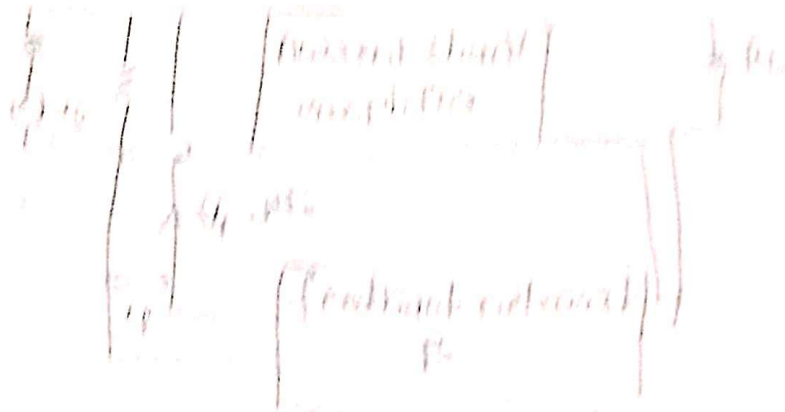3 (a) Draw a current shunt feedback amplifier



In a current shunt feedback network current enters in a basic amplifier and feedback network will be a sampled.

b)

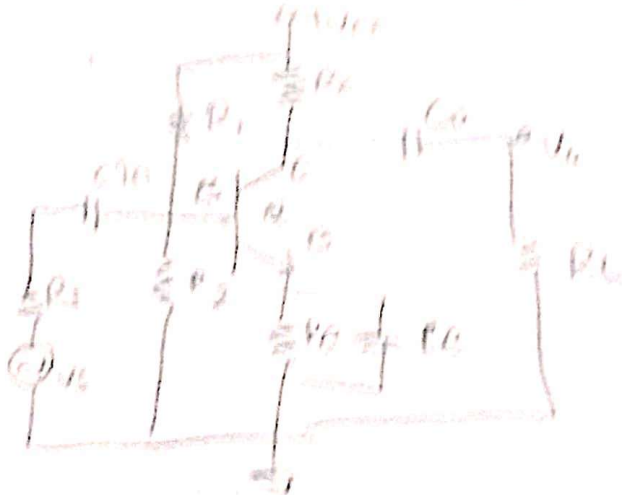



This circuit current will be the high frequency model of CE model

For the use of Evaluator Only


Q No	Marks

Q No	Marks
1a	2

Q No	Marks
1b	0

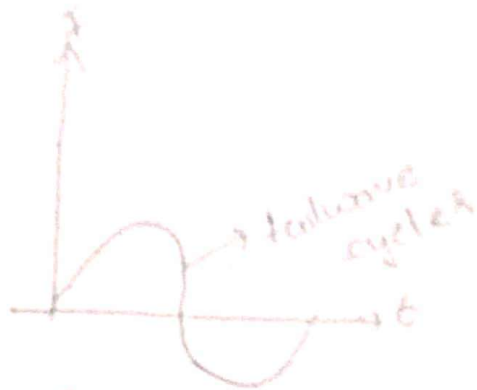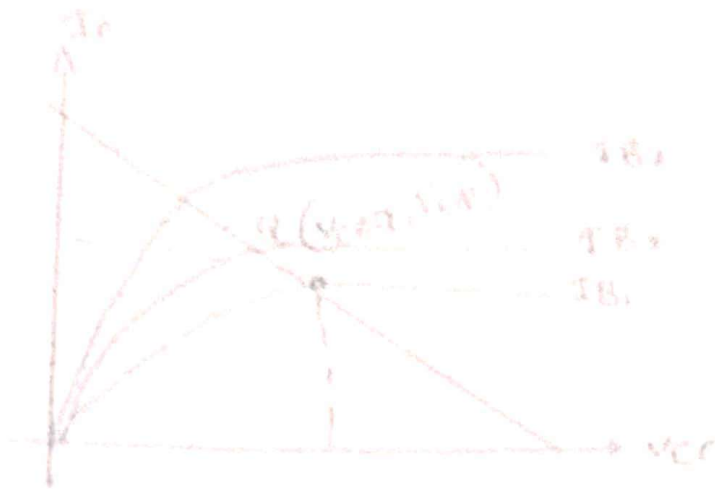

1/2 cycle class A power amplifier

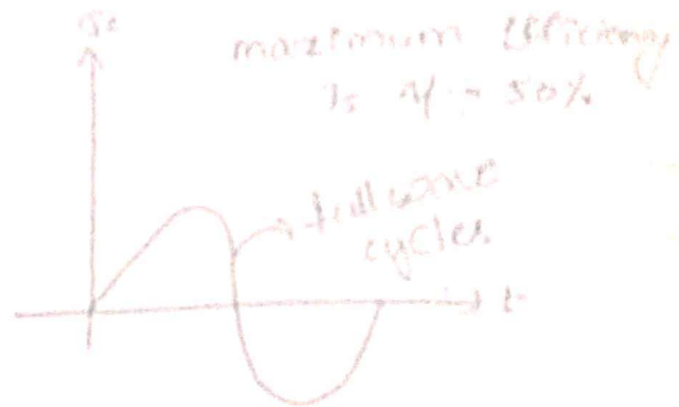

1/2 cycle class A power amplifier

maximum efficiency is $\eta = 50\%$

These class A power amplifier is maximum frequency and cost of the circuit will be less and high frequency signal.

For the use of Evaluator Only

Q No	Marks

Q No	Marks
15	1

Q.No	Marks



d) differential pairs can be used in a common emitter amplifier because of transformer coupled amplifiers and inductive coupled amplifiers are that are less stability characteristics of single stage and multistage amplifiers are not constant then we go for a differential pair of common emitter amplifier.

e) h_{ie} :

h_{ie} is defined by the r_{be} voltage to the input current of a common emitter amplifier.

$$h_{ie} = \frac{V_{be}}{I_B}$$

This is also called input impedance.

h_{re} :

h_{re} it can be defined by the output current by input current.

$$h_{re} = \frac{I_c}{I_B}$$

It is also called reverse parameter of a circuit.

For the use of Evaluator Only


Q.No	Marks
1d	0

Q.No	Marks
1e	2

Q.No	Marks

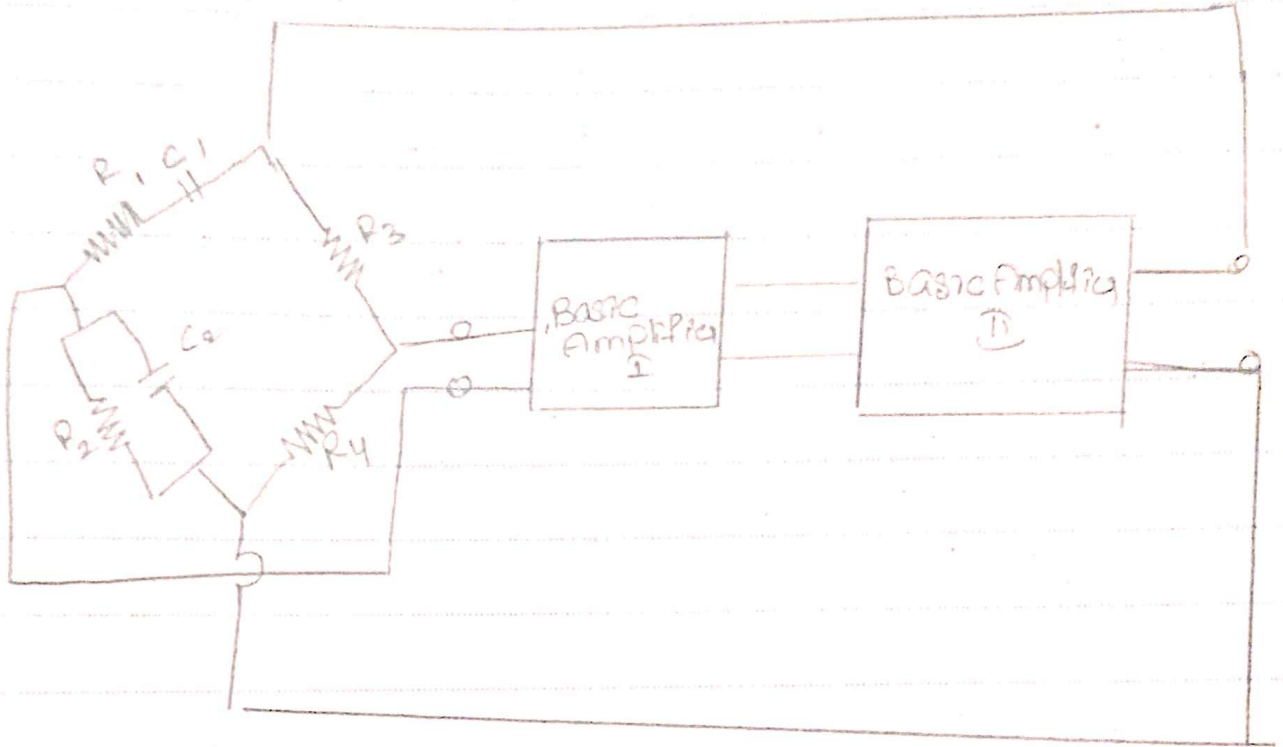f) Growing Oscillations.

Growing oscillations means Wien bridge oscillator.



For the use of Evaluator Only

Q.No	Marks
1f	0


Q.No	Marks

Q.No	Marks



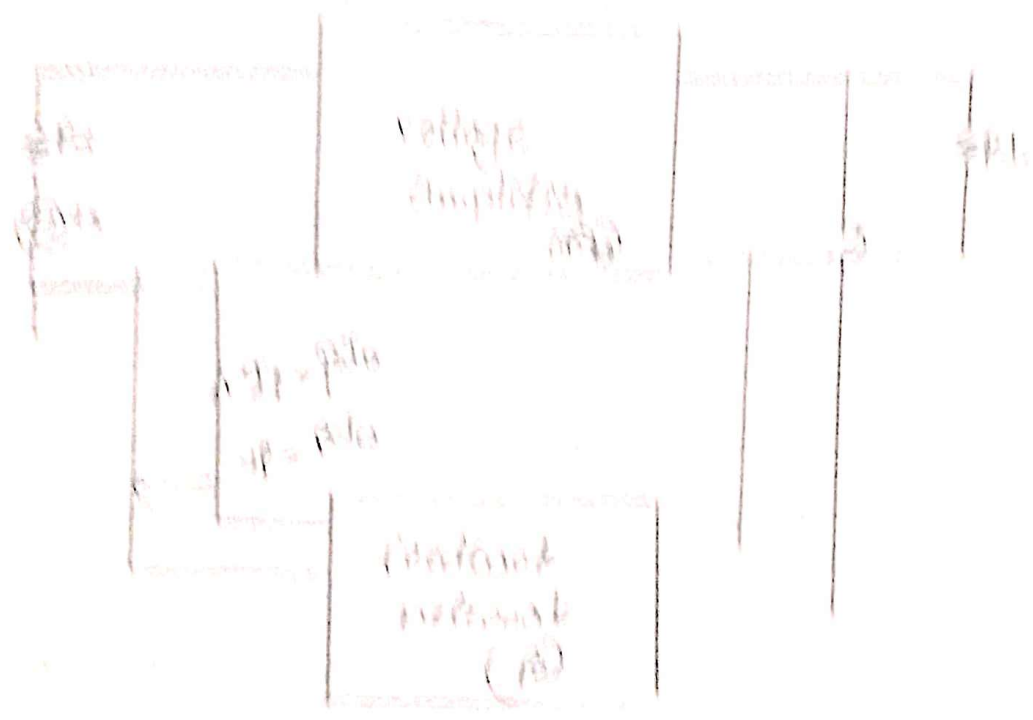Q1) Voltage divider negative feedback

Voltage divider negative feedback amplifier
The closed circuit gain is voltage divider amplifier
Resistor network is a feedback



For the use of Evaluator Only

Q No	Marks

Q No	Marks
19	2

Q No	Marks



For the use of Evaluator Only


Q.No	Marks

Q.No	Marks

Q.No	Marks

An amplifier is an electronic circuit which is used to strengthen / increase the voltage (or current or) power levels of the ^{weak} input signal without any change in input signal ~~of~~ frequency & time period.

Block Diagram of an Amplifier

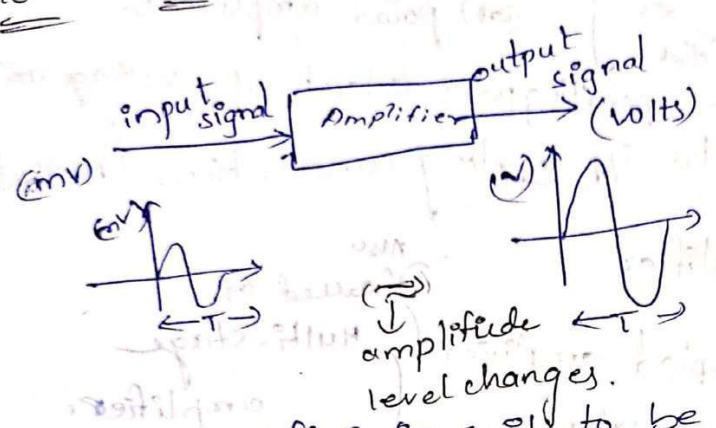

→ If the amplifier is said to be small signal amplifier when i/p voltage is in terms of (mv).

20HZ → 20KHZ → small signal

20KHZ → 20MHZ → Radio frequency.

→ If we apply input signal in the range of (mv) then it is called small signal amplifier

→ If we apply i/p signal in range of (volts) then it is called large signal amplifier.

Classification of amplifiers :- (Based on diff categories)

- 1) A/c to their frequency Range.
- 2) A/c to mode of operation.
- 3) Based on i/p coupling connection.
- 4) Based on o/p coupling connection.
- Based on application of amplifier.

① A/c to frequency Range :-

- Types
- 1) DC Amplifier (0 Frequency) (no Frequency).
 - 2) Audio Amplifier (or) low frequency amplifier [20HZ → 20KHZ]
 - 3) Radio / High Frequency Amplifier [20KHZ → 2MHZ]

2, 3, 4 amplifiers are called AC amplifiers.

classification

→ A/c to Mode of Operation =

- a) class A amplifier Transistor operation should select active region
 - b) class B amplifier op select at cut-off region
 - c) class AB amplifier below $I_B=0$ and above voltage axis
- All are called as large signal (or) power amplifiers.
- class B amplifier means operating point select at voltage axis

classification A/c to i/p coupling connection: Method of Coupling.

- ① RC coupled amplifier
 - ② Transformer coupled amplifier
 - ③ Direct coupled amplifier
- also called as multi-stage amplifier.

RC is best among three coupled circuits.

If input is given with the help of Resistor & Capacitor, it is called as RC coupled amplifier.

Similarly Transformer & direct amplifier

classification A/c to type of load: (Application)

- ① Resistive load
- ② Inductive load.


classification A/c to application of amplifier

- ① Voltage amplifier → It amplifies voltage level
- ② Current amplifier → It amplifies current level
- ③ Power amplifier → It amplifies both voltage & current
- ④ Tuned amplifier → It amplifies single frequency.

When sudden range of frequencies, but o/p is constant then it is good amplifier.



Basic CE Amplifier

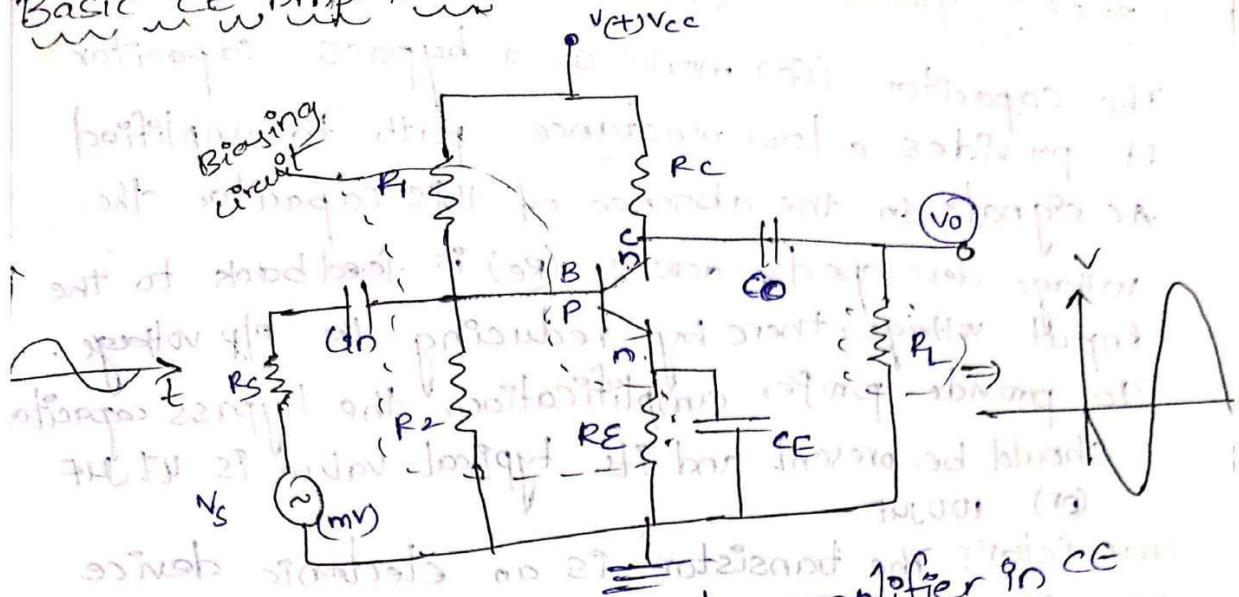

Above fig. shows basic transistor amplifier in CE configuration with voltage divider (self bias). The various circuit elements and their functions are described below:

Biasing circuit: The resistors R_1 , R_2 , R_E are the elements which forms voltage divider bias which provides stabilisation. (i.e., It sets the proper operating point which lies middle of the load line)

2) Load Resistor (R_L): The resistance (R_L) connected at o/p is known as load, when no. of stages are used, when R_L represents i/p resistance of next stage

Coupling Capacitors: Here C_{in} , C_o are called i/p & o/p coupling capacitors. These are used to pass/allow AC signal from one side to another side and blocks any dc signal. It means capacitors acts as open circuit for dc and short-circuit for AC.

and their typical values are 10μF.

4) Bypass capacitor C_E := (To attain max o/p voltage level/camp)

The capacitor (C_E) works as a bypass capacitor. It provides a low reactance path to amplified AC signal. In the absence of this capacitor the voltage developed across (R_E) is feedback to the input voltage, thereby reducing the o/p voltage. To provide proper amplification, the bypass capacitor should be present and its typical value is 47μF (or) 100μF.

Transistor := The transistor is an electronic device which acts as an amplifier when it operates in active region with proper biasing.


Load Line Analysis :=

Load line :=



Load line is the line drawn on the o/p characteristics of a transistor by intersecting voltage & current axes.


Types

- 1) DC load line
- 2) AC load line.


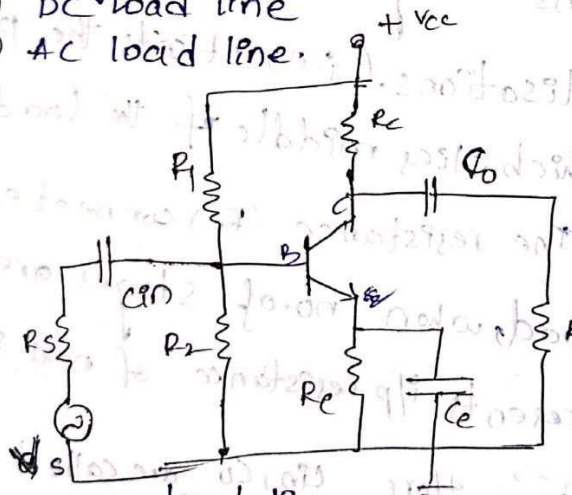


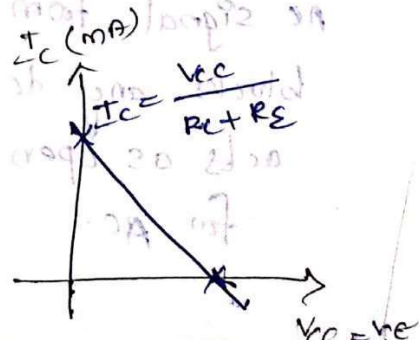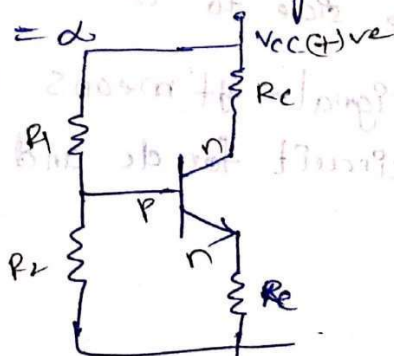For DC load line, all capacitors act as open circuit, all AC voltages are short circuit and $R_L = \infty$.



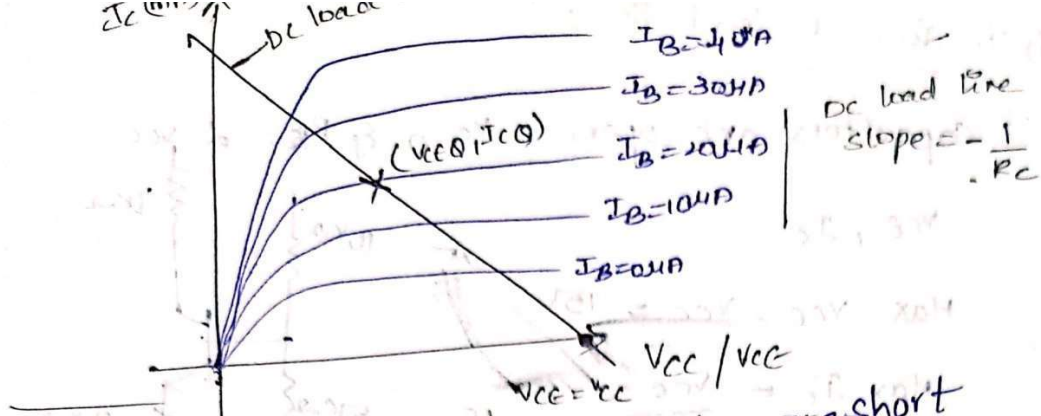


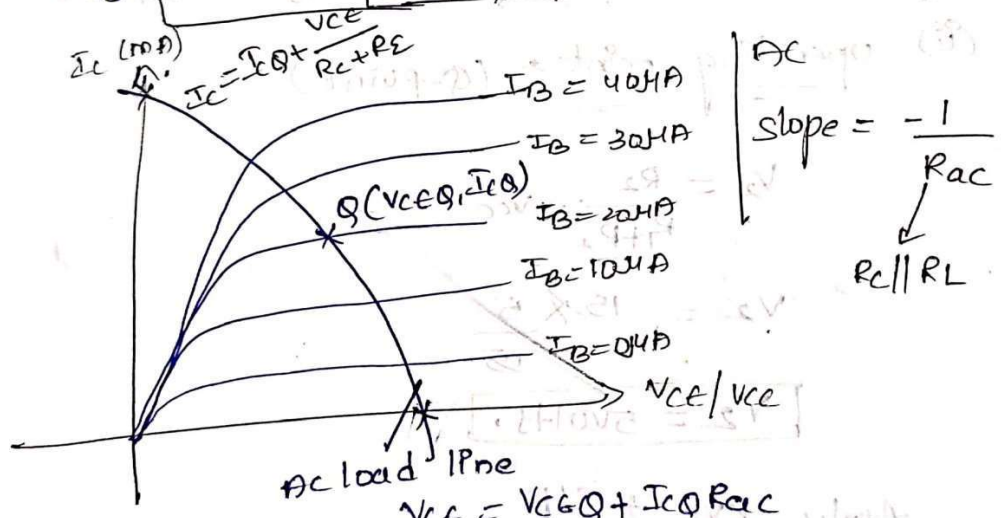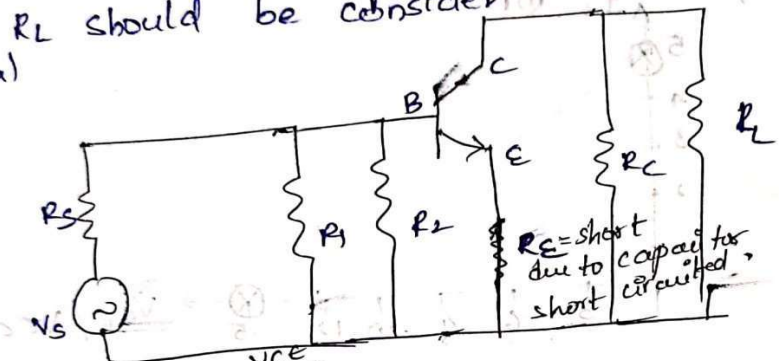To draw AC load line, all capacitors are short circuited, all DC voltages are short circuit and V_S & R_L should be considered.



An A transistor amplifier shown in fig. $R_C = 10K\Omega$, $R_E = 2K\Omega$, $R_1 = 10K\Omega$, $R_2 = 5K\Omega$ and $R_L = 1K\Omega$

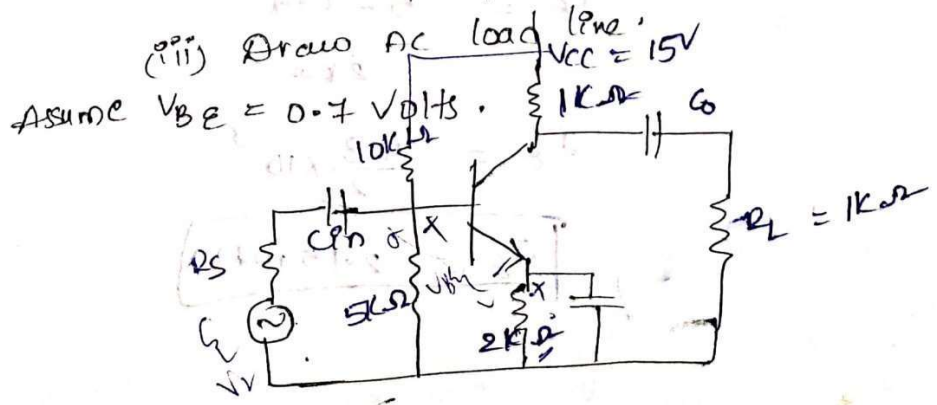- (i) Draw the DC load line
- (ii) Determine Q-point





(i) To draw dc load line:

Capacitors are open $V_S = 0$ & $R_B = 2 \text{ k}\Omega$

V_{CE}, I_C

$$\text{Max } V_{CE} = V_{CC} = 15 \text{ V}$$
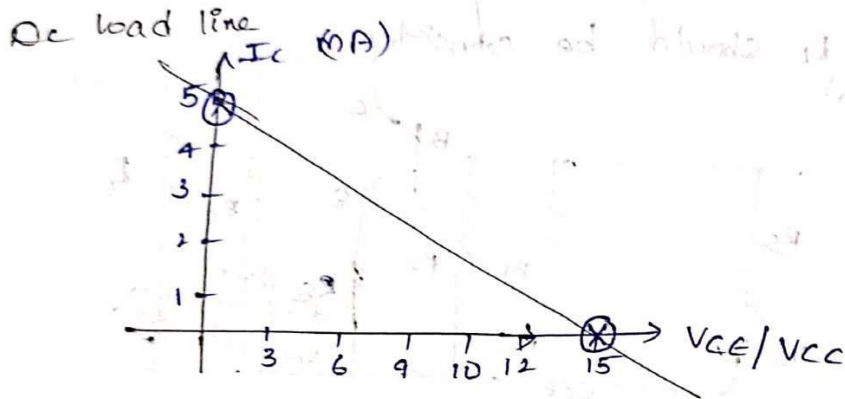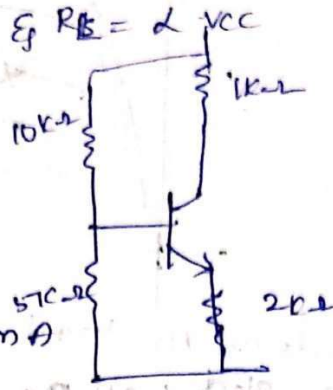
$$\text{Max } I_C = \frac{V_{CC}}{R_C + R_E} = \frac{15}{3} = 5 \text{ mA}$$



(ii) operating point \div (ϕ -point)

$$V_2 = \frac{R_2}{R_1 + R_2} \times V_{CC}$$

$$V_2 = \frac{15 \times 5}{15}$$

$$V_2 = 5 \text{ V}$$

Apply KVL to P/P

$$-V_2 + V_{BE} + I_E R_E = 0$$

$$I_E R_E = + (V_2 - V_{BE})$$

$$I_E = \frac{5 - 0.7}{2 \text{ k}\Omega}$$

$$I_E = \frac{4.3}{2} \times 10^{-3}$$

$$I_E = 2.15 \text{ mA}$$


$$V_{CEQ} = V_{CC} - I_{CQ} (R_C + R_E)$$

$$= 15 - 2.15 \times 10^{-3} [3 \times 10^3]$$

$$= 15 - 2.15 \times 3$$

$$= 15 - 6.45$$

$$\boxed{V_{CEQ} = 8.55V}$$

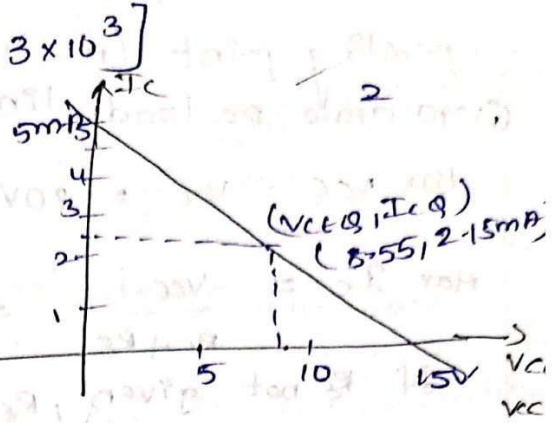

(iii) To draw AC load line:

$$\text{Max } V_{CE} = V_{CEQ} + I_{CQ} R_{ac}$$

$$R_{ac} = R_C \parallel R_E$$

$$= \frac{1 \times 1}{2} = \frac{1}{2} = 0.5 \text{ k}\Omega$$

$$\boxed{R_{ac} = 0.5 \text{ k}\Omega}$$

$$V_{CE} = V_{CEQ} + I_{CQ} R_{ac}$$

$$= 8.55 + 2.15 \times 10^{-3} \times 0.5 \times 10^3$$

$$= 8.55 + 1.075$$

$$\boxed{V_{CE} = 9.625V}$$


$$\text{Max } I_C = I_{CQ} + \frac{V_{CEQ}}{R_{ac}}$$

$$= 2.15 \text{ mA} + \frac{8.55}{0.5 \times 10^3}$$

$$= 2.15 \text{ mA} + 0.017 \text{ A}$$

$$= 2.15 \text{ mA} + 17.1 \text{ mA}$$

$$I_C = 19.25 \text{ mA}$$

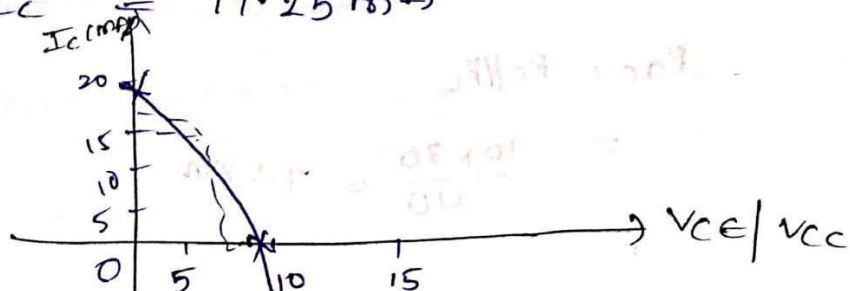


For transistor amplifier, $R_c = 10k\Omega$, $R_L = 30k\Omega$, $V_{CC} = 20V$
 The values of R_1 & R_2 such that so as to fix the
 operating point $(10V, 1mA)$, Draw DC & AC load line.

(i) To draw DC load line

$$\text{Max } V_{CE} = V_{CC} = 20V$$

$$\text{Max } I_c = \frac{V_{CC}}{R_c + R_E} = \frac{20}{10k} = 2mA$$

If R_E not given, $R_E = 0$.

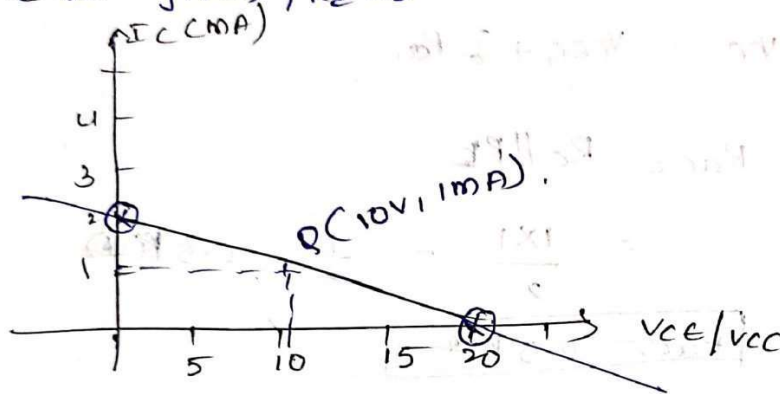

(ii) To draw AC load line.

$$\text{Max } V_{CE} = V_{CEQ} + I_{CQ} R_{AC}$$

$$R_{AC} = R_c \parallel R_L$$

$$= \frac{10 \times 30k\Omega}{(10+30)k\Omega} = \frac{300 \times 10^6}{40 \times 10^3} = 7.5k\Omega$$

$$V_{CE} = 10 + 1 \times 10^{-3} \times 7.5 \times 10^3$$

$$V_{CE} = 10 + 7.5$$

$$\boxed{V_{CE} = 17.5V}$$

$$I_c = I_{CQ} + \frac{V_{CEQ}}{R_{AC}} = 1 \times 10^{-3} + \frac{10}{7.5k\Omega} =$$


$$R_{AC} = R_c \parallel R_L$$

$$= \frac{10 \times 30}{40} = 7.5k\Omega$$

∴ For AC load line

$$V_{CE} = 17.5V$$


$$I_C = 2.33mA$$

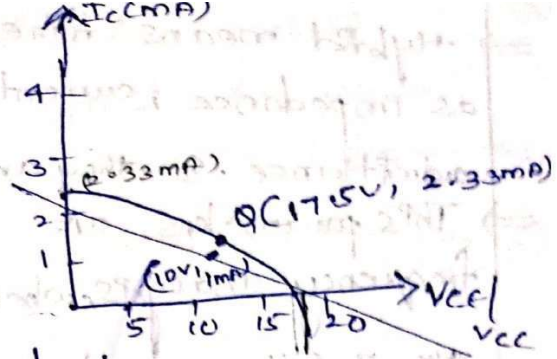

Transistor is a three terminal device, but when it connects to a circuit, it is a four pole n/w

(or) 2-port network. Perspective of its configuration.

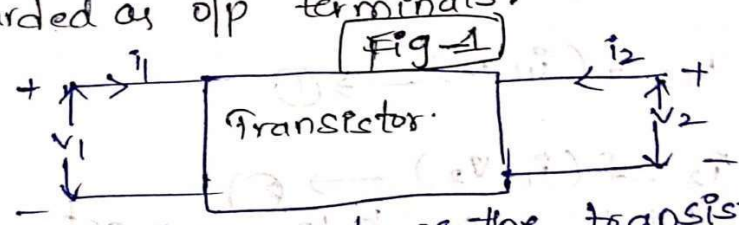ex: Considering a CB configuration, the emitter and base terminals may be regarded as i/p terminals, while the collector & base terminals regarded as o/p terminals.



The above figure shows the transistor as a four pole / two port network. The currents are taken as positive when they are enter into the transistor & (-)ve while they leave the transistor.

→ The n/w behaviour is specified by $V_1, I_1, V_2,$ and I_2 as external quantities.

→ Among these four variables, any two maybe selected as independent and the remaining two can be expressed as choosen dependent variable.

This leads to various parameters, such as.

- 1) Impedance-parameters [z-parameters]
- 2) Admittance-parameters [y-parameters]
- 3) h-parameters (hybrid).

Among three parameters, only h-parameters model is currently used for transistor circuit analysis.

⇒ hybrid means mixed parameters/dimensions as impedance, current gain, voltage gain and admittance. So they are called hybrid-parameters.

⇒ These parameters are very useful at low & high frequency analysis, whereas, at high frequencies, the z & y-parameters are complex. Hence they are not used.

In h-parameter model i_1 & v_2 are taken as independent variables while v_1 & i_2 are dependent variables.

(Consider

$$V_1 = f(i_1, V_2)$$

Based on above conditions.

$$V_1 = f(i_1, V_2) \rightarrow (1)$$

$$i_2 = f(i_1, V_2) \rightarrow (2)$$

By taking total differentiation we get

$$dV_1 = \frac{\partial V_1}{\partial i_1} di_1 + \frac{\partial V_1}{\partial V_2} dV_2 \rightarrow (3)$$

$$di_2 = \frac{\partial i_2}{\partial i_1} di_1 + \frac{\partial i_2}{\partial V_2} dV_2 \rightarrow (4)$$

For small signal AC analysis, we can operate the transistor in Active Region. (linear region) which indicates ^{change in} voltages & currents are constant [i.e. partial derivatives becomes constant].

$$V_1 = h_{11} i_1 + h_{12} V_2 \rightarrow (5)$$

$$i_2 = h_{21} i_1 + h_{22} V_2 \rightarrow (6)$$

Eqn (5) & (6) can be expressed in matrix form as

$$\begin{bmatrix} V_1 \\ i_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} i_1 \\ V_2 \end{bmatrix} \rightarrow (7)$$

By appropriate choice of (i.e. $P=0$) & short circuit ($V=0$) applied to eqn ⑤ & ⑥, we can define small signal ac values of h parameters

Case 1 \rightarrow If we short circuit the o/p terminals (i.e. $V_2=0$)

then eqn ⑤ becomes

$$V_1 = h_{11} i_1 + h_{12}(0)$$

$$V_1 = h_{11} i_1$$

$$h_{11} = \frac{V_1}{i_1} \text{ input impedance. (ohm)}$$

h_{11} is Ratio of input voltage to input current

then eqn ⑥ becomes

$$I_2 = h_{21} i_1 + h_{22}(0)$$

$$i_2 = h_{21} i_1$$

$$h_{21} = \frac{i_2}{i_1} \text{ forward current gain}$$

h_{21} is ratio of o/p current to i/p current.

Case 2 \rightarrow

If the open circuit i/p terminals (i.e. $i_1=0$)

then eqn ⑤ becomes.

$$V_1 = h_{11}(0) + h_{12}(V_2)$$

$$V_1 = h_{12}(V_2)$$

$$h_{12} = \frac{V_1}{V_2} \rightarrow \text{Reverse voltage gain.}$$

Similarly

eqn ⑥ becomes

$$i_2 = h_{21}(0) + h_{22} V_2$$

$$i_2 = h_{22} V_2$$

$$h_{22} = \frac{i_2}{V_2} \text{ o/p admittance (mho)}$$

h_{22} is Ratio of o/p current to o/p voltage.

Equivalent circuit of transistor shown in fig-1

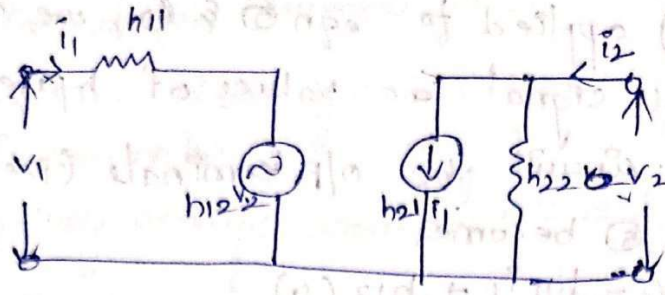


Fig-2

In the above fig, subscripts in 'h' are modified in different configurations of a transistor circuit


⇒ Here the first letter (h₁₁) indicates whether the particular parameter is input, output, forward, and 2nd letter (h₂₁) indicates transistor configuration such as CB, CE, CC.

*) For example, in case of common Base the hybrid parameters used are h_{ib}, h_{fb}, h_{sb}, h_{ob}.

*) Similarly for common emitter and common collector the h-parameters are h_{ie}, h_{fe}, h_{re}, h_{oe} and h_{ic}, h_{fc}, h_{rc}, h_{oc} respectively.

*) The transistor circuit in different configurations as shown in below.


Equivalent circuit

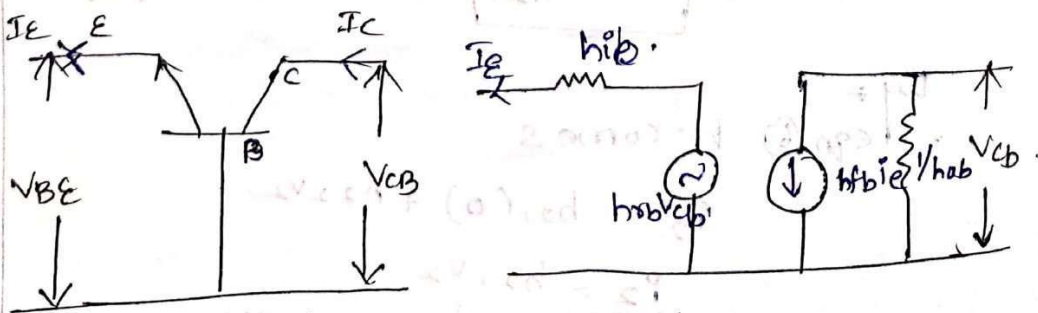

$$V_{be} = h_{ib} i_E + h_{rb} V_{cb}$$

$$i_C = h_{fb} i_E + h_{ob} V_{cb}$$

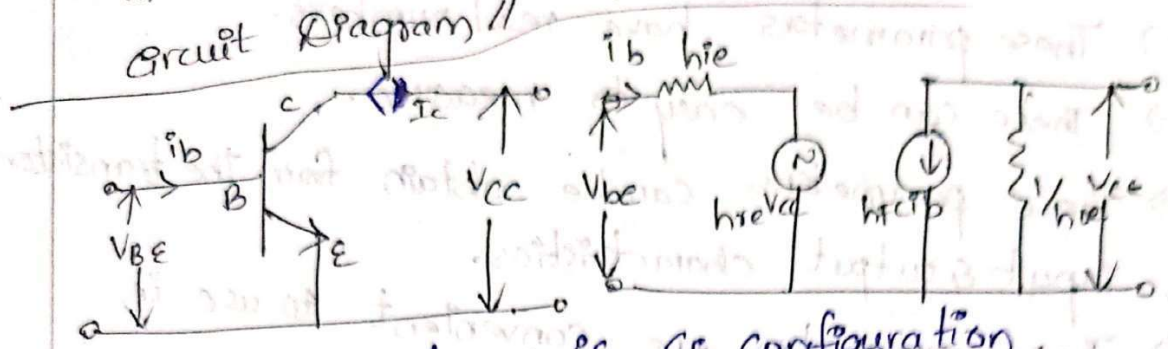
This common base configuration circuit & Equivalent circuit Diagram //



The above figure is CE configuration.

$$V_{be} = h_{ie}i_b + h_{re}V_{ce}$$

$$i_c = h_{fe}i_b + h_{oe}V_{ce}$$

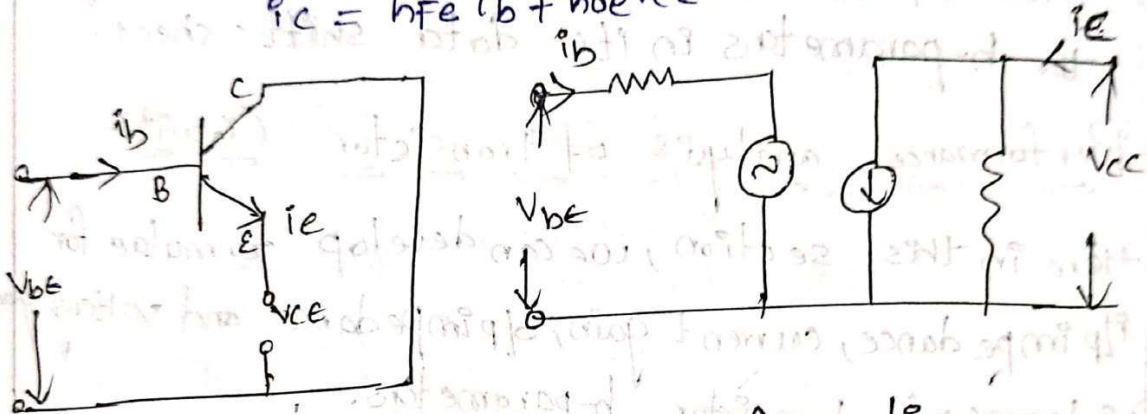

Typical values of CB configuration.

$$h_{ib} = 20\Omega \quad h_{rb} = 2.9 \times 10^{-4}$$

$$h_{fb} = -0.98 \quad h_{ob} = 0.49 \mu A/V = 0.49 \times 10^{-6} \text{ mhos}$$

Typical values of CE configuration.

$$h_{ie} = 1.1 k\Omega \quad h_{fe} = 50$$

$$h_{re} = 2.5 \times 10^{-4} \quad h_{oe} = 25 \mu A/V$$

$$= 25 \times 10^{-6} A/V$$

Typical values of CC configuration.

$$h_{ic} = 1.2 k\Omega \quad h_{fc} = -51$$


$$h_{oc} = 1 \quad h_{oe} = 25 \mu A/V$$

Advantages of h-parameters:

- ⇒ These parameters have real numbers.
- ⇒ These can be easy to measure.
- ⇒ These parameters can be obtain from the transistor input & output characteristics.
- ⇒ These parameters are convenient to use in circuit analysis & design.
- ⇒ Most of the transistor manufactures specify the h-parameters in its data sheet.

Performance analysis of Transistor Circuit

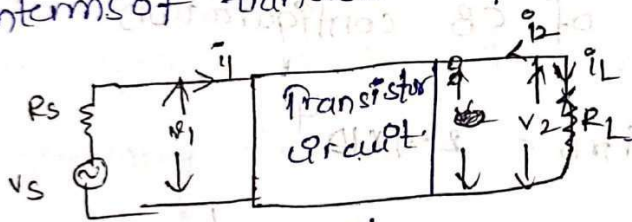Here in this section, we can develop formulae for i_L impedance, current gain, o/p impedance and voltage gain in terms of transistor h-parameters.



From above circuit

$$V_1 = h_{11} i_1 + h_{12} V_2 \rightarrow (1)$$

$$i_2 = h_{21} i_1 + h_{22} V_2 \rightarrow (2)$$

$$i_L \text{ (or) } i_2 = -\frac{V_2}{R_L} \rightarrow (3) \text{ (opposite direction)}$$

(i) Input Impedance (Z_{in}) It is the ratio of input voltage to input current.

$$Z_{in} = \frac{V_1}{i_1} \rightarrow (4)$$

Sub eqn (1) in eqn (4)

$$Z_{in} = \frac{h_{11} i_1 + h_{12} V_2}{i_1}$$

$$Z_{in} = h_{11} + h_{12} \frac{V_2}{i_1} \rightarrow (5)$$

From eqn ② & ③

$$\frac{-V_2}{R_L} = h_{21}i_1 + h_{22}V_2$$

$$h_{21}i_1 = -\frac{V_2}{R_L} - h_{22}V_2$$

$$h_{21}i_1 = -\left[\frac{V_2}{R_L} + h_{22}V_2 \right]$$

$$\frac{V_2}{i_1} = \frac{-h_{21}}{\left(h_{22} + \frac{1}{R_L} \right)} \rightarrow \textcircled{6}$$

Sub $\frac{V_2}{i_1}$ in eqn ⑤

$$Z_{in} = h_{11} + h_{12} \left[\frac{-h_{21}}{h_{22} + \frac{1}{R_L}} \right]$$

$$Z_{in} = h_{11} - \frac{h_{12}h_{21}}{h_{22} + \frac{1}{R_L}} \rightarrow \textcircled{a}$$

Current gain (A_I) : It is the ratio of output current to i/p current. It is denoted by (A_I).

$$A_I = \frac{i_2}{i_1} \rightarrow \textcircled{7}$$

From ③,

$$V_2 = -i_2 R_L$$

Substitute (V_2) in eqn ②

$$i_2 = h_{21}i_1 + h_{22}(-i_2 R_L)$$

$$i_2 = h_{21}i_1 - h_{22}i_2 R_L$$

$$i_2 [1 + h_{22}R_L] = h_{21}i_1$$

$$\frac{i_2}{i_1} = \frac{h_{21}}{(1 + h_{22}R_L)}$$

$$A_I = \frac{h_{21}}{(1 + h_{22}R_L)} \rightarrow \textcircled{b}$$

Voltage gain (A_V) : It is the ratio of o/p voltage to i/p voltage. It is denoted by (A_V).

$$A_V = \frac{V_2}{V_1} \rightarrow \textcircled{8}$$

From eqn (4)

$$z_{in} = \frac{V_1}{i_1}$$

$$V_1 = z_{in} i_1$$

sub V_1 in eqn

$$A_v = \frac{V_2}{z_{in} i_1}$$

$$A_v = \frac{V_2}{i_1} \cdot \frac{1}{z_{in}} \rightarrow (9)$$

substitute eqn (6) in eqn (9)

$$A_v = \frac{-h_{21}}{\left(h_{22} + \frac{1}{R_L}\right)} \cdot \frac{1}{z_{in}} \rightarrow (10)$$

$$A_v = \frac{-h_{21}}{\left(h_{22} + \frac{1}{R_L}\right)} \cdot \frac{1}{\left(h_{11} - h_{21} \frac{h_{12}}{h_{22} + \frac{1}{R_L}}\right)}$$

output Impedance (Z_o): It is the ratio of o/p voltage to o/p current by setting $V_s = 0$ ($R_L = \infty$)

by setting $V_s = 0$ ($R_L = \infty$)

$$Z_o = \frac{V_2}{i_2} \rightarrow (11)$$

From eqn (2)

$$i_2 = h_{21} i_1 + h_{22} V_2$$

$$\frac{i_2}{V_2} = h_{21} \frac{i_1}{V_2} + h_{22} \rightarrow (11)$$

From eqn (11) $V_1 = 0$

$$h_{11} i_1 + h_{12} V_2 = 0$$

$$\frac{i_1}{V_2} = -\frac{h_{12}}{h_{11}} \rightarrow (12)$$

sub eqn (12) in eqn (11)

$$\frac{i_2}{V_2} = h_{21} \left(-\frac{h_{12}}{h_{11}}\right) + h_{22}$$

$$\frac{i_2}{V_2} = -\frac{h_{12} h_{21}}{h_{11}} + h_{22}$$


$$\frac{i_D}{v_2} = \frac{h_{11}h_{22} - h_{12}h_{21}}{h_{11}}$$

$$Z_o = \frac{h_{11}}{h_{11}h_{22} - h_{12}h_{21}} \rightarrow (d)$$

⇒ The above a, b, c and d represents the input impedance, current gain, voltage gain and output impedance of a transistor circuit using h-parameters.

Analysis of CE Amplifier:

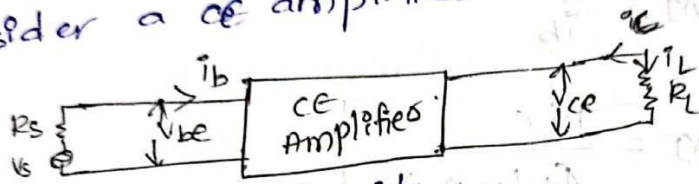Consider a CE amplifier as shown in figure.




From above circuit

$$v_{be} = h_{ie} i_b + h_{oe} v_{ce} \rightarrow (1)$$

$$i_e = h_{fe} i_b + h_{oe} v_{ce} \rightarrow (2)$$

$$i_e = i_L = \frac{-v_{ce}}{R_L} \rightarrow (3)$$

The h-parameter transistor circuit (CE)

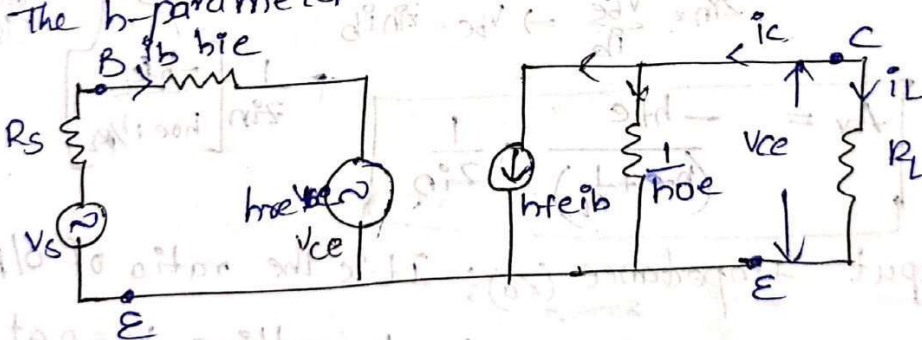

Input Impedance $(Z_{in}) = \frac{v_{be}}{i_b} \rightarrow (4)$ It is the ratio of i/p voltage (v_{be}) to input current (i_b).
Sub eqn (1) in (4)

$$Z_{in} = \frac{h_{ie} i_b + h_{oe} v_{ce}}{i_b}$$

$$Z_{in} = h_{ie} + h_{oe} \frac{v_{ce}}{i_b}$$

From eqn (2) & (3)

$$-\frac{V_{ce}}{R_L} = h_{fe} i_b + h_{oe} V_{ce}$$

$$\frac{V_{ce}}{R_L} \leq \left[h_{fe} R_L + h_{oe} \frac{V_{ce}}{R_L} \right]$$

$$z_{in} = h_{ie} + h_{re} \left[\frac{h_{fe}}{h_{oe} + 1/R_L} \right]$$

Current gain (A_I): It is the ratio of o/p current to i/p current (i_b)

$$A_I = \frac{i_c}{i_b}$$

$$A_I = \frac{h_{fe}}{(1 + h_{oe} R_L)}$$

Voltage gain (A_v): It is the ratio of o/p voltage to i/p voltage.

$$A_v = \frac{V_{ce}}{V_{be}} = \frac{V_{ce}}{z_{in} i_b} = \frac{1}{z_{in}} \left[\frac{V_{ce}}{i_b} \right] = \frac{h_{fe} i_b + h_{oe} V_{ce}}{V_{ce} [1 + h_{oe} R_L] i_b}$$

$$z_{in} = \frac{V_{be}}{i_b} \Rightarrow V_{be} = z_{in} i_b$$


$$A_v = \frac{-h_{fe}}{(h_{oe} + 1/R_L)} \cdot \frac{1}{z_{in}}$$

$$\frac{1}{z_{in}} \left[\frac{-h_{fe}}{h_{oe} + 1/R_L} \right]$$


Output Impedance (z_o): It is the ratio of o/p voltage to o/p current by setting v_s = 0 at R_L = ∞

$$z_o = \frac{V_{ce}}{I_c}$$
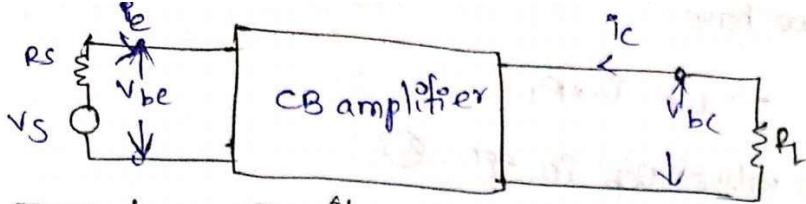
$$z_o = \frac{h_{ie}}{h_{ie} h_{oe} - h_{re} h_{fe}}$$



From above circuit

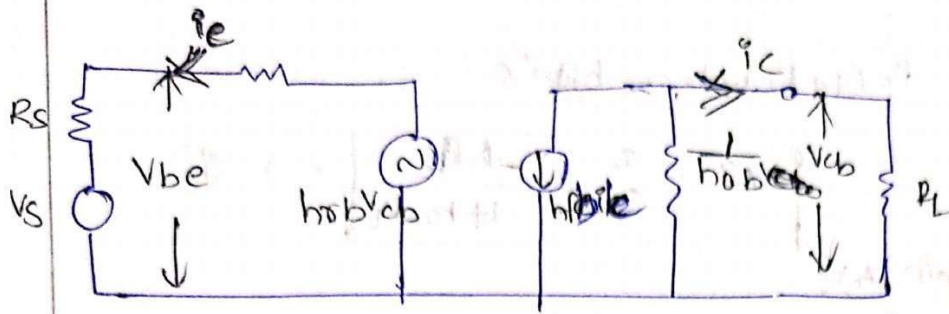

$$V_{be} = h_{ie} i_e + h_{ob} V_{cb} \rightarrow (1)$$

$$i_c = h_{fe} i_e + h_{ob} V_{cb} \rightarrow (2)$$

$$i_c = \frac{-V_{cb}}{R_L} \rightarrow (3)$$

Input Impedance $= Z_{in}$

$$Z_{in} = \frac{V_i}{I_i} = \frac{V_{be}}{i_e} \rightarrow (4)$$

from eqn (1)

$$Z_{in} = \frac{h_{ie} i_e + h_{ob} V_{cb}}{i_e} \rightarrow (5)$$

Eqn (3) in eqn (5)

$$\frac{-V_{cb}}{R_L} = h_{fe} i_e + h_{ob} V_{cb}$$

$$-h_{fe} i_e = h_{ob} V_{cb} + \frac{V_{cb}}{R_L}$$

$$i_e = - \left[\frac{h_{ob} V_{cb} + \frac{V_{cb}}{R_L}}{h_{fe}} \right]$$

$$\frac{i_e}{-V_{cb}} = \frac{h_{ob} + \frac{1}{R_L}}{h_{fe}}$$

$$\frac{-V_{cb}}{i_e} = \frac{h_{fe}}{h_{ob} + \frac{1}{R_L}} \rightarrow (6)$$

Sub eqn (6) in eqn (5)

$$Z_{in} = \frac{h_{ie} i_e}{i_e} + h_{ob} \left(\frac{-h_{fe}}{h_{ob} + \frac{1}{R_L}} \right)$$

$$Z_{in} = h_{ie} - \frac{h_{ob} h_{fe}}{h_{ob} + \frac{1}{R_L}}$$

Current gain (AI) $\div AI = \frac{i_c}{i_b} = \frac{i_c}{i_e} \rightarrow \textcircled{7}$

from eqn ③ we have

$$-v_{cb} = i_c \times R_L$$

sub value v_{cb} in eqn ②

$$i_c = h_{fe} i_e + h_{ob} (-i_c R_L)$$

$$i_c (1 + R_L h_{ob}) = h_{fe} i_e$$

$$AI = \frac{i_c}{i_e} = \frac{-h_{fb}}{1 + h_{ob} R_L} \rightarrow \textcircled{8}$$

Voltage gain (Av) \div

$$Av = \frac{V_2}{V_1} = \frac{v_{cb}}{v_{be}} \rightarrow \textcircled{9}$$

from eqn

$$Z_{in} = \frac{v_{be}}{i_c}$$

$$v_{bc} = Z_{in} i_c$$

sub v_{bc} in eqn ④

$$Av = \frac{v_{cb}}{Z_{in} i_c} = \frac{v_{cb}}{i_e} \left(\frac{1}{Z_{in}} \right) \rightarrow \textcircled{10}$$

sub eqn ⑥ in eqn ⑩

$$Av = + \left[\frac{h_{fe}}{h_{ob} + 1/R_L} \right] \left(\frac{1}{Z_{in}} \right) \rightarrow \textcircled{11}$$

output Impedance $(Z_o) \quad Z_o = \frac{V_2}{i_2} = \frac{v_{cb}}{i_c} \rightarrow \textcircled{12}$

from eqn ⑤,

$$i_c = h_{fe} i_e + h_{ob} v_{cb}$$

$$\frac{i_c}{v_{cb}} = \frac{h_{fe} i_e}{v_{cb}} + h_{ob}$$

$$\frac{i_c}{v_{cb}} = \frac{h_{fe} i_e + h_{ob} v_{cb}}{v_{cb}} \rightarrow \textcircled{12}$$

$$\frac{v_{cb}}{i_c} = \frac{v_{cb} h_{ob} + h_{fe} i_e}{i_c} = Z_o$$

from eqn ① $v_1 \Rightarrow$

$v_{be} \Rightarrow$

$v_{be} = h_{ie} i_b + h_{rb} v_{cb}$

$h_{ie} i_b = -h_{rb} v_{cb}$

$$\frac{i_e}{v_{cb}} = \frac{-h_{rb}}{h_{ie}} \rightarrow (13)$$

sub eq ⑬ in eqn ②

$$\frac{i_c}{v_{cb}} = h_{fb} \left(\frac{i_e}{v_{cb}} \right) + h_{ob}$$



$$\frac{i_c}{v_{cb}} = h_{fb} \left(\frac{-h_{rb}}{h_{ie}} \right) + h_{ob}$$

$$\frac{i_c}{v_{cb}} = \frac{-h_{rb} h_{fb} + h_{ie} h_{ob}}{h_{ie}}$$

$$z_o = \frac{v_{cb}}{i_c} = \frac{h_{ie}}{h_{ie} h_{ob} - h_{rb} h_{fb}}$$

Analysis of CC Amplifier:-

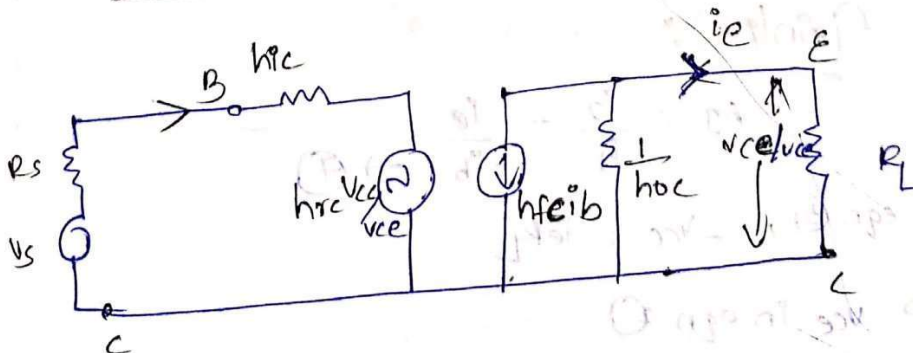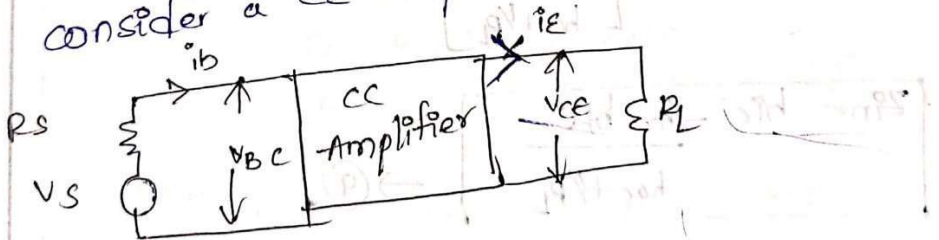consider a CC amplifier as shown in figure.



$v_{be} = h_{ie} i_b + h_{rb} v_{ce} \rightarrow (1)$

$i_e = h_{fb} i_b + h_{ob} v_{ce} \rightarrow (2)$

$$i_2 = \frac{-v_2}{R_L} \quad i_e = \frac{+V_{ce}}{R_L} \rightarrow (3)$$

Input Impedance (z_{in})

$$z_{in} = \frac{v_1}{i_1} = \frac{V_{be}}{i_b} \rightarrow (4)$$

from eqn (1)

$$z_{in} = \frac{h_{ie} i_b + h_{re} V_{ce}}{i_b} \rightarrow (5)$$

$$\text{eqn (2) = eqn (3)}$$

$$\frac{-V_{ce}}{R_L} = h_{fc} i_b + h_{oc} V_{ce}$$

$$-h_{fc} i_b = h_{oc} V_{ce} + \frac{V_{ce}}{R_L}$$

$$-i_b = \frac{h_{oc} V_{ce} + \frac{V_{ce}}{R_L}}{h_{fc}}$$

$$\frac{-i_b}{V_{ce}} = \frac{h_{oc} + \frac{1}{R_L}}{h_{fc}}$$

$$\frac{V_{ce}}{i_b} = - \left[\frac{h_{fc}}{h_{oc} + \frac{1}{R_L}} \right] \rightarrow (6)$$

sub. eqn (6) in eqn (5)

$$z_{in} = h_{ie} + h_{re} \left[\frac{-h_{fc}}{h_{oc} + \frac{1}{R_L}} \right]$$

$$\boxed{z_{in} = h_{ie} - \frac{h_{re} h_{fc}}{h_{oc} + \frac{1}{R_L}}} \rightarrow (9)$$

Current Gain (A_I)

$$A_I = \frac{i_2}{i_1} = \frac{i_e}{i_b} \rightarrow (7)$$

from eqn (3), $-V_{ce} = i_e R_L$

sub V_{ce} in eqn (1)

$$i_e = h_{fc} i_b + h_{oc} V_{ce}$$

$$i_e = h_{fc} i_b + h_{oc} (-i_e R_L)$$

$$i_e (1 + h_{oc} R_L) = h_{fc} i_b$$



$$\frac{i_e}{i_b} = \frac{h_{fc}}{1+h_{oc}R_L} \rightarrow (8)$$

$$A_{\Gamma} = \frac{-h_{fc}}{1+h_{oc}R_L} \rightarrow (9)$$

Voltage Gain: $(A_V) \Rightarrow A_V = \frac{v_2}{v_1} = \frac{V_{ce}}{V_{be}} \rightarrow (1)$

from eqn (1), $Z_{in} = \frac{V_{be}}{i_b}$

$$V_{be} = Z_{in} i_b$$

sub V_{be} in eqn (1)

$$A_V = \frac{V_{ce}}{Z_{in} i_b}$$

$$A_V = \frac{1}{Z_{in}} \left[\frac{V_{ce}}{i_b} \right] \rightarrow (10)$$

sub eqn (6) in eqn (10)

$$A_V = \frac{-h_{fc}}{h_{oc} + 1/R_L} \left(\frac{1}{Z_{in}} \right)$$

$$A_V = \frac{+h_{fc}}{Z_{in} [h_{oc} + 1/R_L]} \rightarrow (10)$$

Output Impedance: (Z_o) :

$$Z_o = \frac{v_2}{i_2} = \frac{V_{ce}}{I_c} \rightarrow (11)$$

from eqn (2)

$$i_e = h_{fc} i_b + h_{oc} V_{ce}$$

$$\frac{i_e}{V_{ce}} = h_{fc} \left(\frac{i_b}{V_{ce}} \right) + h_{oc} \rightarrow (12)$$

From eqn (1)

$$V_{bc} = h_{rc} i_b + h_{rc} V_{ce}$$

$$0 = h_{ic} i_b + h_{rc} V_{ce}$$

$$-h_{ic} i_b = h_{rc} V_{ce}$$

sub (13) in (12)

$$\frac{i_e}{V_{ce}} = h_{fc} \left[\frac{-h_{rc}}{h_{ic}} \right] + h_{oc} \rightarrow (13)$$

$$\frac{i_e}{V_{ce}} = h_{fc} \left[\frac{-h_{rc}}{h_{ic}} \right] + h_{oc}$$



$$\frac{V_{ce}}{I_c} = Z_o = \frac{h_{ic}}{h_{oc} I_c - h_{rc} h_{fc}} \rightarrow (14)$$

Guidelines of Analysis of CE Amplifier with transistor


- The analysis of transistor circuits for small signal behaviour can be made by following simple guidelines
- 1) Draw the actual circuit diagram from given specifications
 - 2) Replace coupling & bypass capacitors as short circuit
 - 3) Replace DC voltage source by a short circuit
 - 4) Make the points, C, B, E on a circuit diagram and locate this points as the start of the equivalent circuit.

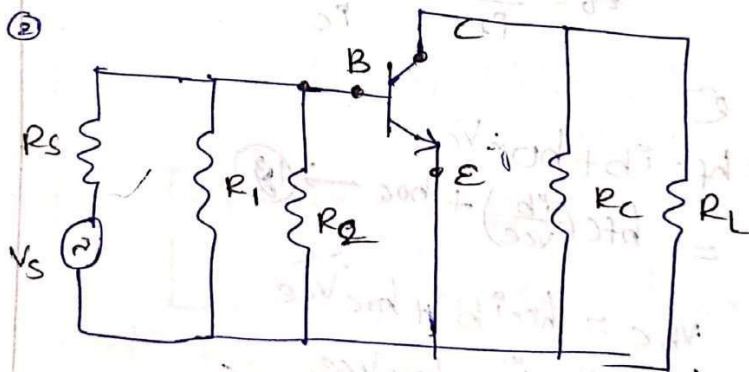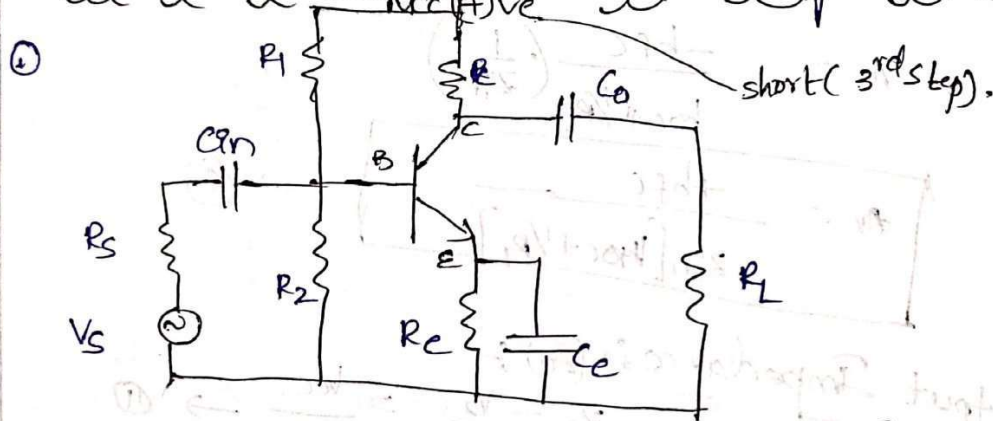5) Replace the transistor by its h-parameter model.

→ Consider a CE amplifier with voltage divider Bias



[where B = input
 $R_L = o/p$]

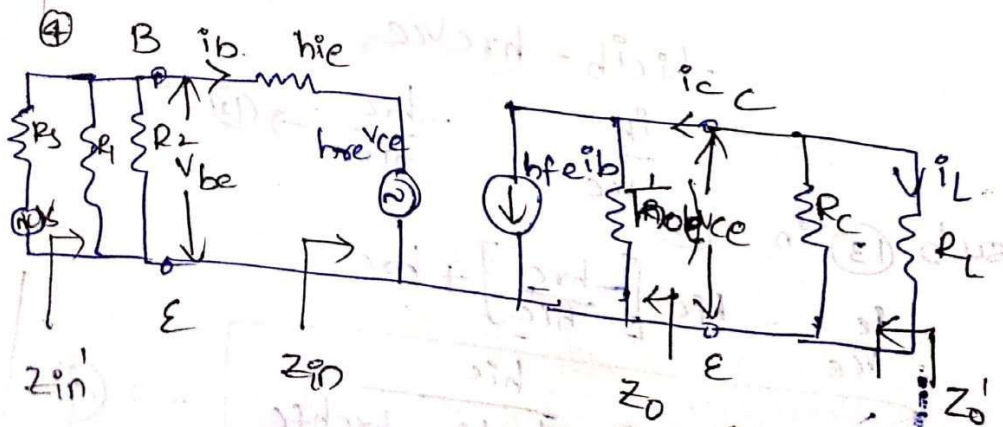


Problem: Consider a single stage CE amplifier with

$R_S = 1k\Omega$; $R_1 = 50k\Omega$; $R_2 = 2k\Omega$, $R_C = 1k\Omega$, $R_E = 1.2k\Omega$


The typical values of h-parameters $h_{ie} = 1.1k\Omega$,
 $h_{fe} = 50$ $h_{oe} = 2.5 \times 10^{-4}$ $h_{re} = 25 \mu A/V$. Calculate Z_{in} ,
 Z_{in}' , A_i , A_v , Z_o , Z_o' , $A_{OS} = \frac{V_o}{V_s}$ and $A_{IS} = \frac{I_L}{I_S}$.

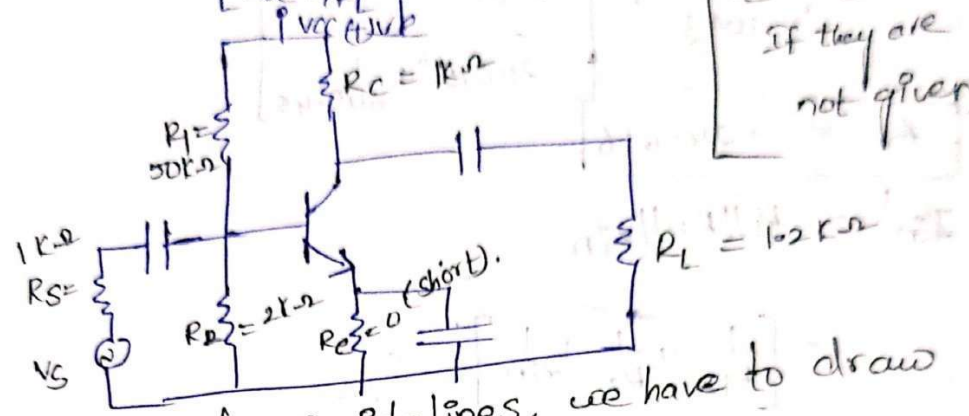$Z_{in} = h_{ie} - h_{re} \left[\frac{h_{fe}}{h_{oe} + 1/R_L} \right]$



$R_E = 0$ [short if they are not given]

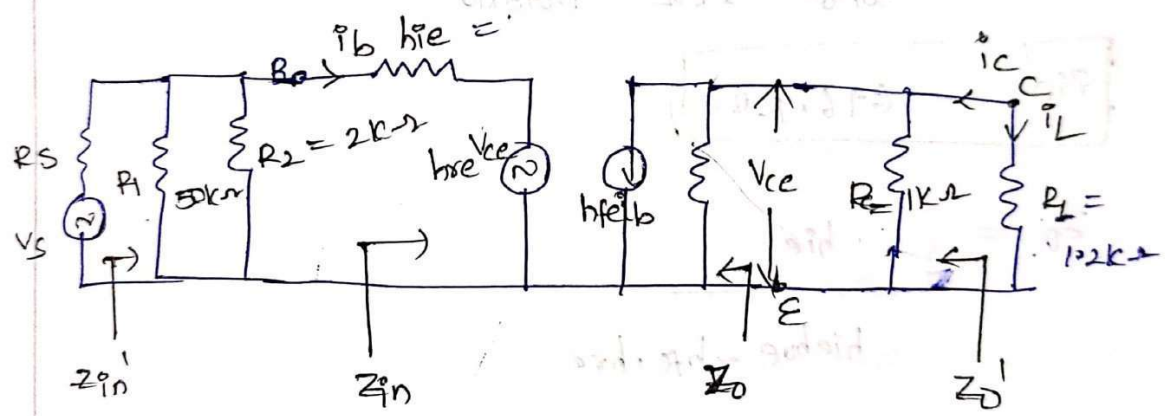with the help of Equidelines, we have to draw equivalent circuit with h-parameters. $10^6 \ 10^3$



Equivalent load $R_L = R_C || R_L$

$= 1k\Omega || 1.2k\Omega = \frac{(1 \times 1.2) \times 10^6}{(1+1.2) \times 10^3}$

$R_L = 545.45 \Omega$

$Z_{in} = h_{ie} - h_{re} \left[\frac{h_{fe}}{h_{oe} + 1/R_L} \right]$ (total Equ R_L)

$= 1.1k\Omega - 2.5 \times 10^{-4} \left[\frac{50}{2.5 \times 10^{-4} + \frac{1}{545.45}} \right]$
 $Z_{in} = 1093.2735 \Omega$

$$A_I = \frac{h_{fe}}{1 + h_{oe} R_L} \stackrel{\text{equ RL}}{=} = \frac{50}{1 + 25 \times 10^{-6} \times 545.45} = \boxed{49.327}$$

$$A_V = \frac{1}{z_{in}} \left[\frac{-h_{fe}}{h_{oe} + \frac{1}{R_L}} \right] = \boxed{-24.616}$$

$$= \frac{1}{1093} \times \left[\frac{-50}{25 \times 10^{-6} + \frac{1}{545.45}} \right]$$

$$\boxed{A_V = -24.616}$$

$$z_{in}' = R_1 \parallel R_2 \parallel z_{in}$$

$$= \left[\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{z_{in}} \right]$$

$$= \frac{1}{50 \times 10^3} + \frac{1}{2k\Omega} + \frac{1}{1.093 \times 10^3}$$

$$\boxed{z_{in}' = 696.9 \Omega}$$

$$z_o = \frac{h_{ie}}{h_{ie} h_{oe} - h_{fe} h_{re}}$$

$$= \frac{1.1k\Omega}{(1.1k\Omega)(25 \times 10^{-6}) - (50)(2.5 \times 10^{-4})}$$

$$= \frac{1.1k\Omega}{(1.1k\Omega)(25 \times 10^{-6}) - (50)(2.5 \times 10^{-4})}$$

$$= 73333.33$$

$$\boxed{z_o = 73.333k\Omega}$$

$$z_o' = R_L \parallel z_o = 545.45 \parallel 73.333k\Omega$$


$$z_o' = 541 \Omega$$

$$A_{VS} = \frac{V_o}{V_s} = \left(\frac{V_{CC}}{V_{BE}} \right) \times \frac{V_{BE}}{V_s} = A_V \times \frac{V_{BE}}{V_s}$$

$$= A_V \times \frac{Z_{in}}{Z_{in} + R_s}$$


$$= -24.69 \times \frac{696.9}{696.9 + 11 \times 10^3}$$

$$A_{VS} = -10.107$$

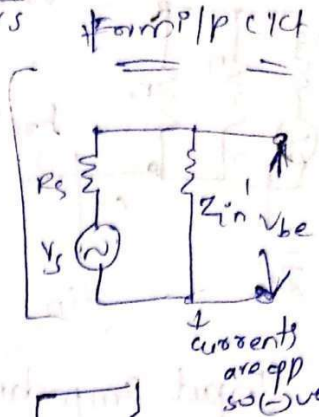


overall current gain.

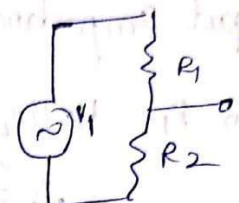
$$A_{IS} = \frac{I_L}{I_s} = \frac{I_L}{I_c} \times \frac{I_c}{I_B} \times \frac{I_B}{I_s}$$



from o/p circuit =

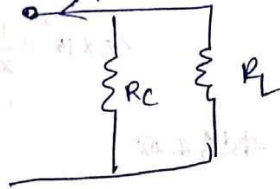

from i/p circuit =

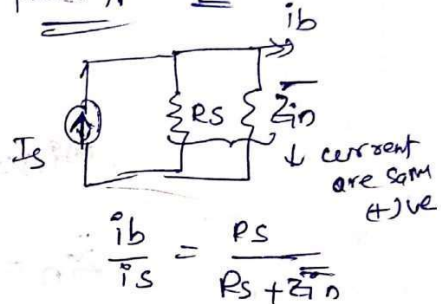


$$A_{IS} = \frac{-R_c}{R_c + R_L} \times A_V \times \frac{R_s}{R_s + Z_{in}} \Rightarrow \frac{-1 \times 10^3}{1 \times 10^3 + 1.2 \times 10^3} \times 49.3 \times \frac{1 \times 10^3}{1 \times 10^3 + 696}$$


$$A_{IS} = -13.2$$

consider CC amplifier as shown in figure
 The h-parameters of a transistor $h_{ic} = 1.2 k\Omega$ $h_{fc} = -101$
 $h_{oc} = 1$; $h_{oc} = 25 \times 10^{-6} A/V$. calculate Z_{in} , Z_{out} , A_V , A_{IS}

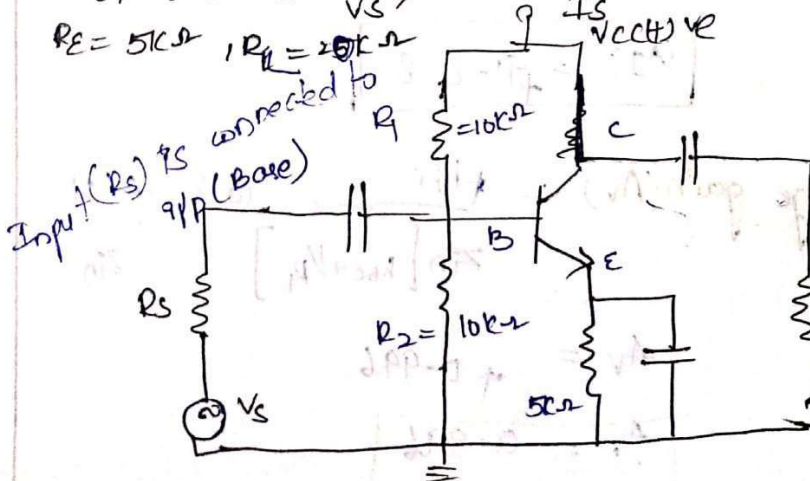Z_{B1} , Z_{B1}' , $A_{VS} = \frac{V_o}{V_s}$; $A_{IS} = \frac{I_L}{I_s}$, A_V ? $R_s = 1k\Omega$, $R_L = 10k\Omega$
 $R_E = 5k\Omega$, $R_B = 20k\Omega$



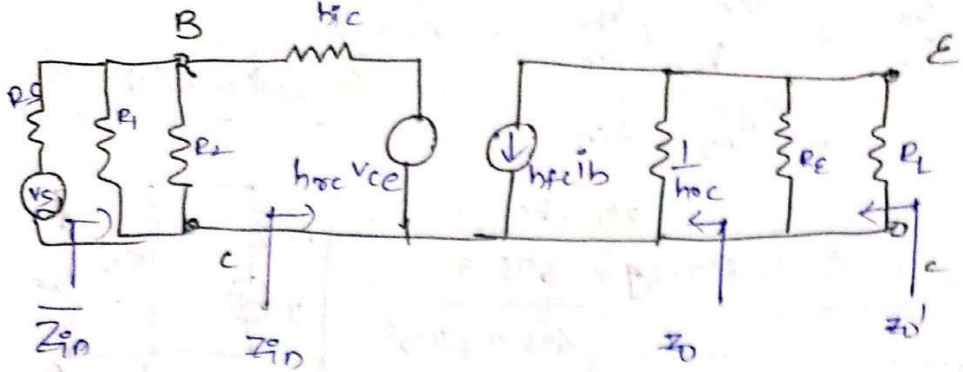load is connected across R_E so o/p is I_E
 $5k\Omega$ so it is CC amplifier



Input Impedance (Z_{in}) = $h_{ie} - \frac{h_{oc} h_{fe}}{h_{oc} + 1/R_L}$

eg) $R_L = R_C || R_E = 4K\Omega$

$\therefore Z_{in} = 1.2 \times 10^3 + \frac{1 \times 10^1}{25 \times 10^{-6} + \frac{1}{4 \times 10^3}}$

~~$Z_{in} = 1164 \Omega$~~

$Z_{in} = +368472$

$Z_{in} = 368472 - 723$

$Z_{in} = 368.472 K\Omega$

current gain (A_I) = $\frac{-h_{fe}}{h_{oc} R_L + 1}$

$(A_I) = \frac{-(-101)}{(25 \times 10^{-6})(4 \times 10^3) + 1}$

$(A_I) = +91.818$

Voltage gain (A_V) = $\frac{+h_{fe}}{Z_{in} [h_{oc} + 1/R_L]} \cdot \frac{-A_I R_L}{Z_{in}}$

$A_V = +0.996$

$A_V = 0.996$

Signs are same
 $A_I \neq A_V$
 for CC $A_V = 1$
 $A_I = \beta$
 for CE $A_V = \beta$
 $A_I = \beta + 1$

$$\bar{Z}_{in} = R_1 \parallel R_2 \parallel Z_{in}$$

$$= 10k\Omega \parallel 10k\Omega \parallel 368.472 \times 10^3$$

$$\boxed{\bar{Z}_{in} = 4.93k\Omega}$$

$$Z_o = \frac{h_{fc}}{h_{ic}h_{oc} - h_{fc}h_{rc}} = \frac{102 \times 10^3}{(1.2 \times 10^3 \times 25 \times 10^{-6}) - (-101)(1)}$$

$$Z_o = 11.87\Omega$$

$$Z_o' = R_L \parallel Z_o = 4k\Omega \parallel 11.87\Omega$$


$$\boxed{Z_o' = 11.83}$$

$$A_{VS} = \frac{V_o}{V_s} = \frac{V_{CE}}{V_{BE}} \times \frac{V_{bc}}{V_s}$$

$$= A_V \times \frac{\bar{Z}_{in}}{Z_{eqs}}$$

$$= 0.996 \times \frac{4.93k\Omega}{(4.93k\Omega) + (1 \times 10^3)}$$

$$\boxed{A_{VS} = 0.828}$$

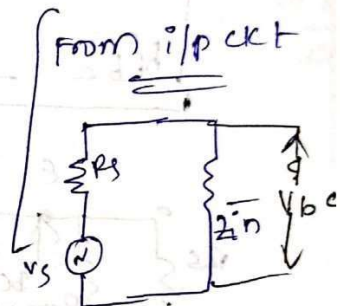


$$A_{VS} = \frac{I_L}{I_B} = \frac{I_L}{I_E} \times \frac{I_E}{I_B} \times \frac{I_B}{I_S}$$

$$= \frac{R_E}{R_E + R_L} \times A_V \times \frac{R_S}{R_S + \bar{Z}_{in}}$$

$$= \frac{5 \times 10^3}{(5 \times 10^3) + (20k\Omega)} \times 91.81 \times \frac{1 \times 10^3}{(1 \times 10^3) + 4.93}$$

$$\boxed{A_{VS} = 3.096}$$

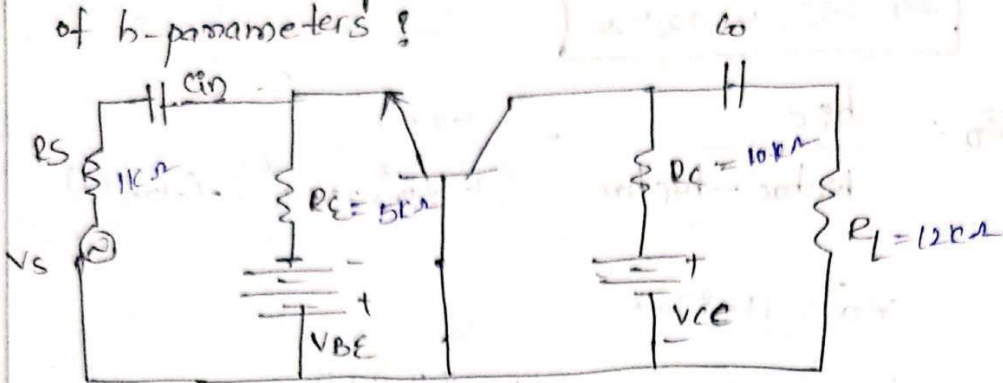
Consider CB amplifier with $R_E = 5k\Omega$, $R_C = 10k\Omega$,
 $R_S = 1k\Omega$, $R_L = 12k\Omega$. Calculate the value of Z_{in}/A_i ,
 A_v , Z_o for the given circuit. Assume typical values
of h-parameters!



Typical Values of CB configuration

$h_{ib} = 20\Omega$	$h_{rb} = 2.9 \times 10^{-4}$
$h_{fb} = -0.98$	$h_{ob} = 0.49 \mu A/V$

$b_{ce} = 2.5 \times 10^{-4}$
 h_{re}

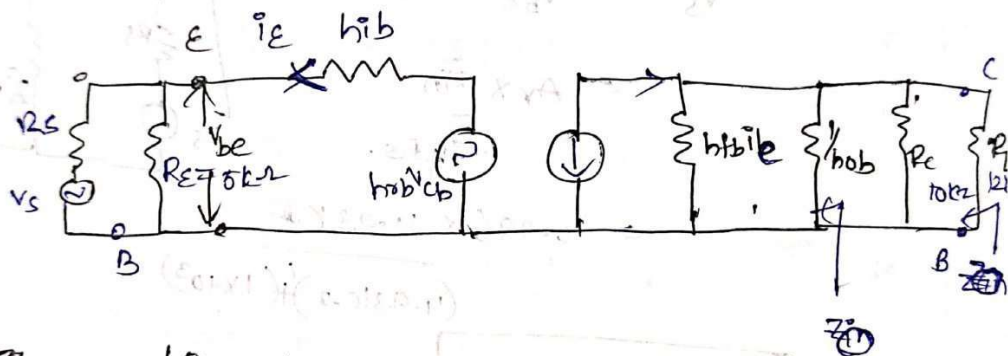

$$Z_{in} = h_{ib} - \frac{h_{rb} h_{fb}}{h_{ob} + 1/R_L}$$

$$R_{L \text{ equivalent}} = R_C \parallel R_L$$

$$= 10k\Omega \parallel 12k\Omega$$

$$= 5454\Omega$$

$$R_L = 5.454k\Omega$$

$$Z_{in} = 20 - \frac{2.9 \times 10^{-4} \times (-0.98)}{0.49 \times 10^{-6} + \frac{1}{5.454 \times 10^3}}$$

$$= 20 - \frac{2.842 \times 10^{-4}}{0.49 \times 10^{-6} + 1.834 \times 10^{-4}}$$

$h_{oe} = 2.5 \times 10^{-6}$
 $= 0.00025 \mu S$

$$Z_{in} = 21.545 \Omega$$

$$Z_{in}' = R_e \parallel Z_{in}$$

$$= 5k\Omega \parallel 21.545$$

$$Z_{in}' = 21.452$$

$$\text{current gain (A}_I\text{)} = \frac{-h_{fb}}{1 + h_{ob}R_L} = \frac{-0.98}{1 + 0.49 \times 10^{-6} \times 5 \times 10^3 \times 10^3}$$

$$A_I = +0.977$$

$$\text{voltage gain (A}_v\text{)} = \frac{+h_{fb}}{h_{ob} + \frac{1}{R_L}} \left(\frac{1}{Z_{in}} \right) \text{ or } \frac{A_I R_L}{Z_{in}}$$

$$A_v = \frac{0.977 \times 5.45 \times 10^3}{21.545}$$

$$A_v = 247.19$$

$$\text{output Impedance (Z}_o\text{)} = \frac{h_{ib}}{h_{ob}h_{ib} - h_{ob}h_{fb}}$$

$$Z_o = \frac{20}{(20 \times 0.49 \times 10^{-6}) - ((-0.98 \times 2.9 \times 10^{-4}))}$$

$$Z_o = 68027.21$$

$$Z_o = 68.027k\Omega$$

$$\text{Overall o/p Impedance } Z_o' = Z_o \parallel R_c \parallel R_L$$

$$= 68.027k\Omega \parallel 10k\Omega \parallel 12k\Omega$$

$$= 5045.7$$

$$Z_o' = 5.045k\Omega$$

$$A_{vs} = \frac{V_o}{V_s} = A_v \times \frac{Z_{in}'}{Z_{in}' + R_s}$$

$$= 247.19 \times \frac{21.45}{21.45 + 1 \times 10^3}$$

$$A_{vs} = 5.186$$

$$A_{IS} = \frac{I_L}{I_S} = \frac{I_L}{I_C} \times \frac{I_C}{I_E} \times \frac{I_E}{I_S}$$

$$A_{IS} = \frac{R_c}{R_c + R_L} \times A_I \times \frac{R_s}{R_s + Z_{in}'}$$

$$A_{IS} = 0.43476$$

Analysis of Transistor Amplifier using simplified/

Approximate Model:-

→ we have seen the exact calculations of the (Z_o, A_v) with transistor amplifier circuit.

→ In most practical cases, it is approximate to obtain the approximate values of A_v, Z_{in}, A_{vs} and Z_o rather than to carry out more lengthy exact calculations.

→ Such an approximate model is justified because h -parameters are not constant (steady) but vary considerably for the same type of transistor.

→ In h -parameters, the values of h_{re} and h_{oe} significance is negligible, because values are very very small.

→ The condition to go for the simplified model.
 When do we use h-parameter simplified model / if
 $h_{oe} R_L < 0.1$ then we can go otherwise do
 the exact analysis.

Analysis of CE amplifier using simplified h-parameter model
 → consider a CE amplifier in exact model as shown in Fig 1:

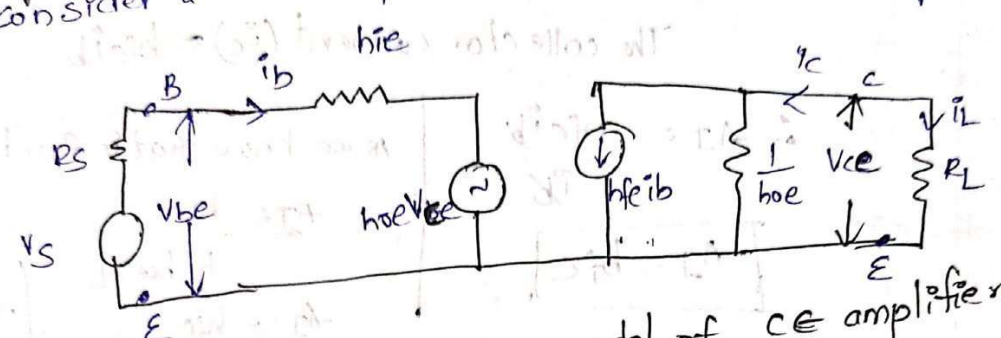


Fig 1: Exact h-parameter model of CE amplifier

→ From the input, the value $\frac{h_{oe} V_{ce}}{i_c} = h_{oe} (i_c R_L)$ $(V_{ce} = -i_c R_L)$

→ When compared to $h_{fe} i_b$ the term $h_{oe} V_{ce}$ is very small, so neglect $h_{oe} V_{ce}$

From output circuit: $\frac{1}{h_{oe}} \parallel R_L \approx R_L$

$$E_{in} \approx \frac{1}{25 \times 10^{-6}} \parallel 10k\Omega \Rightarrow 40k\Omega \parallel 10k\Omega = \frac{40 \times 10}{50} = 8k\Omega \approx 23R_L$$

Hence, neglect the term $\frac{1}{h_{oe}}$ on output side.
 With these assumptions, the circuit (in Fig 1) can be redrawn as Fig 2:

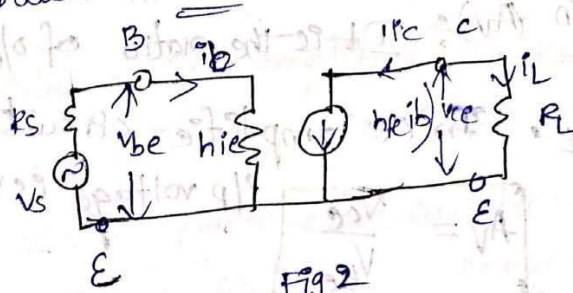


Fig 2: Simplified Model using h-parameters for CE amplifier.

Current Gain (A_I) :- It is the ratio of output current to input current.

In CE, input current is i_b , and output current is i_c

$$\therefore A_I = \frac{i_c}{i_b}$$

From output circuit,

The collector current (i_c) = $h_{fe} i_b$

$$\therefore A_I = \frac{h_{fe} i_b}{i_b}$$

$$A_I = h_{fe}$$

As we know that in exact model.

$$A_I = \frac{h_{fe}}{1 + h_{oe} R_L}$$

$$A_I = \frac{h_{fe}}{1 + 0}$$

$\because h_{oe} \ll \frac{1}{R_L} \approx 0$

$$A_I = h_{fe}$$

Input Impedance (Z_{in}) :- It is the ratio of i/p voltage to i/p current, in CE amplifier.

$$Z_{in} = \frac{V_{be}}{i_b}$$

From i/p circuit :-

$$V_{be} = h_{ie} i_b$$

$$\therefore Z_{in} = \frac{h_{ie} i_b}{i_b}$$

$$Z_{in} = h_{ie}$$

As we know that from exact model.

$$Z_{in} = h_{ie} - \frac{h_{fe} h_{re}}{h_{oe} + 1/R_L}$$

$$Z_{in} = h_{ie} - \frac{0}{0} \left[\begin{array}{l} h_{re} \approx 0 \\ h_{oe} \approx \infty \end{array} \right]$$

$$Z_{in} = h_{ie}$$

Voltage gain (A_V) :- It is the ratio of o/p voltage to

i/p voltage. In CE amplifier circuit o/p voltage is V_{ce} and i/p voltage is V_{be}

$$A_V = \frac{V_{ce}}{V_{be}}$$

From o/p circuit :-

$$V_{ce} = -i_c R_L$$



From P/p circuit $V_{ce} = -h_{fe} i_b R_L$
 $V_{be} = h_{ie} i_b$

\therefore Voltage gain $(A_v) = \frac{-h_{fe} i_b R_L}{h_{ie} i_b}$

$A_v = \frac{-h_{fe} R_L}{h_{ie}}$

From exact
 $A_v = \frac{-h_{fe}}{h_{oe} + \frac{1}{R_L}}$
 $h_{oe} \approx 0$

output Impedance (Z_o) is the ratio of o/p voltage to o/p current.

$Z_o = \frac{V_{ce}}{i_c}$

In CE amplifier, the o/p voltage is V_{ce} and o/p current is i_c

$\therefore Z_o = \frac{V_{ce}}{i_c}$ | $V_{be} = 0$
 $R_L = \infty$

From o/p circuit

$V_{ce} = -i_c R_L$

$\therefore Z_o = \frac{-i_c R_L}{i_c}$

$Z_o = -R_L$ AS $R_L \approx \infty$

$Z_o = \infty$

(or) $V_{be} = 0$
 $i_b = 0$
 AS $i_b = 0 \Rightarrow i_c = 0$

$\therefore \frac{V_{ce}}{i_c} = \infty$

Consider a CE amplifier with $R_s = 1k\Omega$,

$R_1 = 50k\Omega$; $R_2 = 2k\Omega$; $R_C = 1k\Omega$; $R_L = 1.2k\Omega$

transistor parameters are $h_{fe} = 50$, $h_{ie} = 10k\Omega$
 $h_{oe} = 25 \times 10^{-6} A/V$. $\therefore h_{re}$ is not given then it is simplified model.

From Exact Model

$Z_o = \frac{h_{ie}}{h_{ie} h_{oe} - h_{fe} h_{re}}$

$Z_o = \frac{h_{ie}}{h_{ie} h_{oe}}$ $= \frac{1}{h_{oe}}$

$Z_o = \infty$

condition is $h_{oe} R_L < 0.1$

$$R_L = R_C \parallel R_L$$

$$= 1\text{K}\Omega \parallel 10.2\text{K}\Omega$$


$$R_L = 545.45\ \Omega$$

$$\therefore \text{The condition for } h_{oe} R_L = 25 \times 10^{-6} \times 545.45$$

$$= 0.013 < 0.1$$

so as $h_{oe} R_L < 0.1$ use simplified Model

Circuit:-

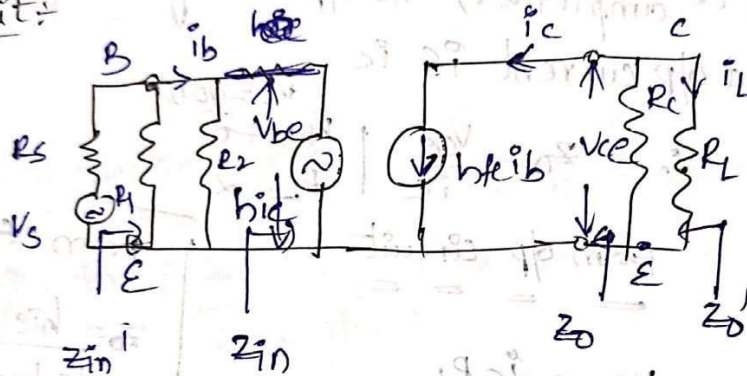

Input Impedance (z_{in}) :-

$$z_{in} = h_{ie}$$

$$z_{in} = 1.1\text{K}\Omega$$

overall i/p Impedance (z_{in}') :-

$$z_{in}' = z_{in} \parallel R_1 \parallel R_2$$

$$= 50 \parallel 2\text{K}\Omega \parallel 10.2\text{K}\Omega$$

$$z_{in}' = 699.7455\ \Omega$$

Current gain (A_I) :-

$$(A_I) = h_{fe}$$

$$A_I = 50$$

$$\text{Voltage gain } (A_v) = \frac{V_{ce}}{V_{be}}$$

$$A_v = \frac{-h_{fe} R_L}{h_{ie}} = \frac{-50 \times 515.45}{1 \times 10^3}$$

$$A_v = \frac{-24.793}{1} = -24.793$$

$$\text{output Impedance } (Z_o) = \alpha$$

$$Z_o' = Z_o \parallel R_L = R_C \parallel R_L$$

$$= \frac{1}{\alpha} \parallel 1.2 \text{ k}\Omega$$

$$= \frac{1}{\alpha} \parallel \frac{1}{1.2 \text{ k}\Omega}$$

$$= \frac{1}{\frac{1}{515.45} + 0}$$

$$= 0.00183$$

$$Z_o' = \frac{1}{0.00183} = 545.45 \Omega$$

$$A_{VS} = \frac{V_o}{V_s} = A_v \times \frac{Z_o'}{Z_o' + R_s}$$

$$= -24.793 \times \frac{545.45}{545.45 + 1 \times 10^3}$$

$$= 10.206$$

$$A_{IS} = \frac{I_L}{I_s} = \frac{-R_c}{R_c + R_L} \times A_v \times \frac{R_s}{R_s + Z_o'}$$

$$= \frac{-1 \times 10^3}{1 \times 10^3 + 1.2 \times 10^3} \times 50 \times \frac{1 \times 10^3}{1 \times 10^3 + 545.45}$$

$$A_{IS} = -13.37$$

Generalised Approximate Model of a Transistor

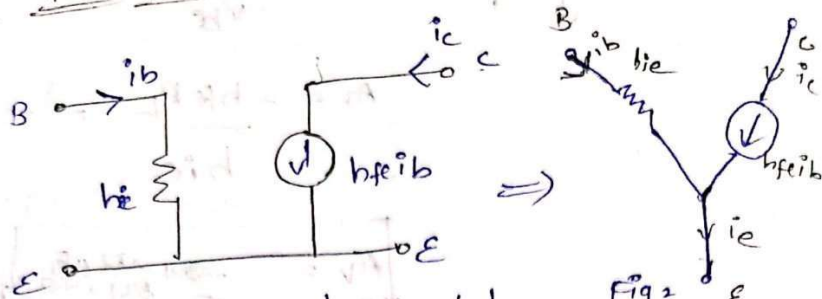


Fig 1: simplified h-parameter model of CE amplifier. & redrawn as h-parameter of a transistor

Fig 2:


→ This model can be used for any configuration by simple grounding the appropriate terminal.

→ In this model, the i/p signal is always applied b/w i/p terminal and ground while the load resistor (R_L) is connected b/w output terminal & ground.


Analysis of CE Amplifier using simplified Model:

→ As we know that in CE, the i/p voltage is connected b/w i/p signal is connected b/w base terminal to collector terminal and the load resistor (R_L) is connected b/w emitter to collector.

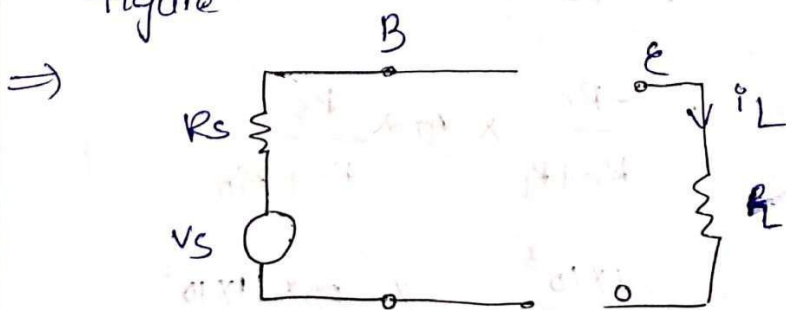→ From generalised approximate model, the equivalent circuit of CE amplifier is shown in figure.



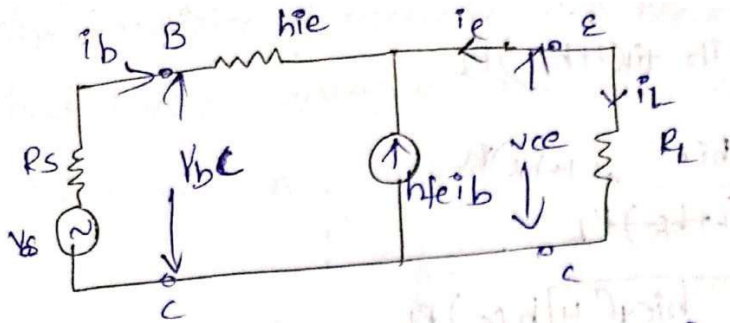From generalised model, we will connected from base terminal (h_{ie}) is connected and for collector terminal ($h_{fe} i_b$) is connected.



Current Gain (AI) :- In CC amplifier, the o/p current is i_e and i/p current is i_b

$$A_I = \frac{i_e}{i_b}$$

From o/p circuit

$$i_e = i_b + h_{fe} i_b$$

$$i_e = i_b (1 + h_{fe})$$

$$\therefore A_I = 1 + h_{fe}$$

Voltage Gain (Av) :- In CC amplifier, o/p voltage is V_{ce} and i/p voltage is V_{be} .

$$\therefore A_V = \frac{V_{ce}}{V_{be}} = \frac{A_I \times R_L}{Z_{in}}$$

$$A_V = \frac{(1 + h_{fe}) \cdot R_L}{h_{ie} + (1 + h_{fe}) R_L}$$

$$\left[\begin{array}{l} Z_{in} \gg h_{ie} \\ h_{ie} \ll Z_{in} \end{array} \right]$$

$$A_V = \frac{(1 + h_{fe}) R_L + h_{ie} - h_{ie}}{h_{ie} + (1 + h_{fe}) R_L} = 1 - \frac{h_{ie}}{(1 + h_{fe}) R_L}$$

$$A_V \approx 1$$


Input Impedance (Zin) :- In CC amplifier input voltage is V_{be} and i/p current is i_b

$$Z_{in} = \frac{V_{be}}{i_b}$$

From i/p circuit

$$V_{be} = i_b h_{ie} + V_{be}$$

$$V_{be} = h_{ie} i_b + i_e R_L$$

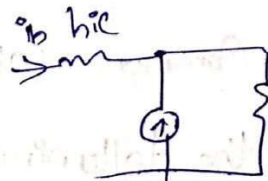

$$V_{bc} = h_{ie} i_b + (1+h_{fe}) R_L$$

$$\frac{V_{bc}}{i_b} = \frac{h_{ie} + (1+h_{fe}) R_L}{(1+h_{fe}) R_L}$$

$$Z_{in} = \frac{h_{ie} + (1+h_{fe}) R_L}{(1+h_{fe}) R_L}$$

Output Impedance (Z_o): In cc amplifier, o/p voltage is V_{ce} and o/p current is i_e

$$\therefore Z_o = \frac{V_{ce}}{i_e}$$

$$\begin{aligned} & \because V_s \infty \text{ (or) } V_{bc} = 0 \\ & R_L = \infty \end{aligned}$$

From i/p circuit:

$$V_s = R_s i_b + h_{ie} i_b + V_{ce}$$

put $V_s = 0$

$$V_{ce} = -[R_s i_b] - h_{ie} i_b$$

$$V_{ce} = -[i_b (R_s + h_{ie})]$$

From o/p circuit:

$$i_e = i_b (1+h_{fe})$$



$$Z_o = \frac{-V_{ce}}{i_e} = \frac{i_b (R_s + h_{ie})}{i_b (1+h_{fe})}$$

$$Z_o = \frac{R_s + h_{ie}}{(1+h_{fe})}$$

Common Collector Amplifier is considered as (emitter follower)


the following components $R_1 = 27k\Omega$, $R_2 = 27k\Omega$

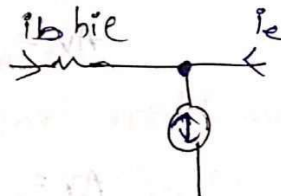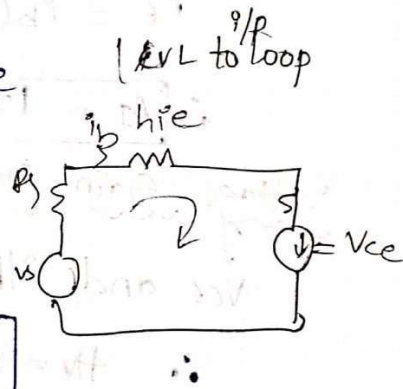$R_e = 5.6k\Omega$, $R_L = 47k\Omega$, $R_s = 400\Omega$



The transistor parameters are $h_{ie} = 1k\Omega$, $h_{fe} = 85$ and $h_{oe} = 25\mu A/V$ calculate A_V , Z_{in} , Z_{in}' , A_V ,

Z_o , Z_o' , A_{V_S} , A_{V_S}' ?

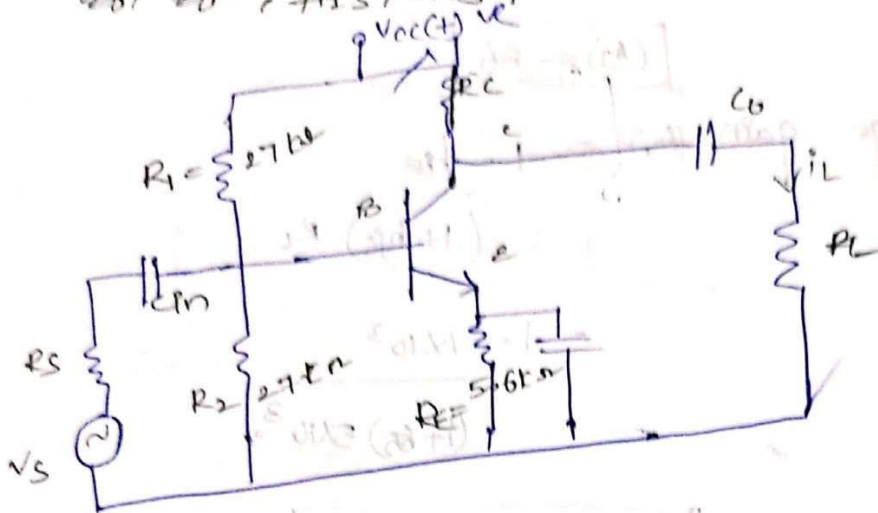

$$R_L = R_E \parallel R_L$$

$$= 5.6k\Omega \parallel 47k\Omega$$

$$= \frac{(5.6 \times 47) \times 10^6}{(5.6 + 47) \times 10^3}$$

$$R_L = 5.003k\Omega$$

The condition is $h_{oe} R_L \ll 1$

$$= 2 \times 10^{-6} \times 5.003 \times 10^3$$


$$= 10.003 \times 10^{-3}$$

$$= 0.010$$

$$h_{oe} R_L = 0.01 \ll 1$$

So simplified
if $h_{oe} R_L > 1$
then exact.

Draw Equivalent circuit:

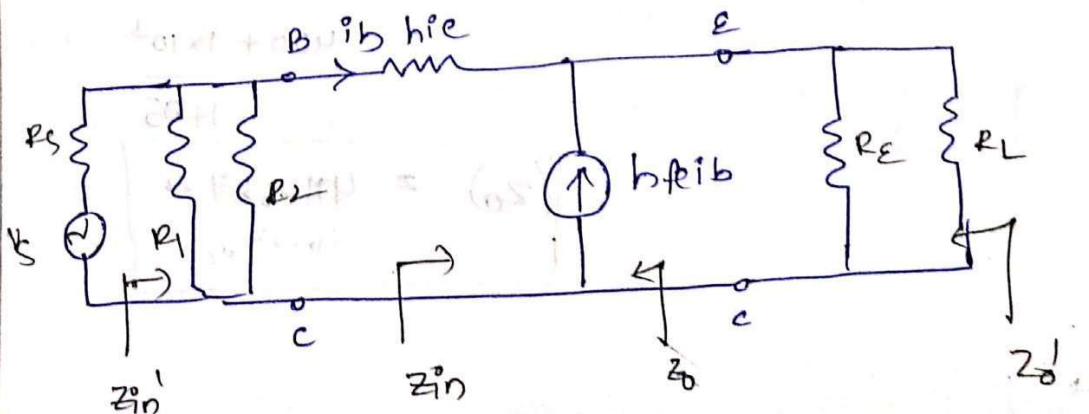

current gain $(A_I) = 1 + h_{fe}$

$= 1 + 85$

$(A_I) = 86$

voltage gain $(A_V) = 1 - \frac{h_{fe}}{(1 + h_{fe}) R_L}$

$= 1 - \frac{1 \times 10^3}{(1 + 85) 5 \times 10^3}$

$A_V = 0.9976$

Input Impedance $(Z_{in}) = h_{ie} + (1 + h_{fe}) R_L$

$= 1 \times 10^3 + (1 + 85) 5 \times 10^3$

$Z_{in} = 431 \text{ k}\Omega$

$Z_{in}^1 = R_1 \parallel R_2 \parallel Z_{in}$

$= \frac{1}{\frac{1}{27} + \frac{1}{27} + \frac{1}{431 \times 10^3}}$

$Z_{in}^1 = 13.499 \text{ k}\Omega$

output impedance $(Z_o) = \frac{R_s + h_{ie}}{1 + h_{fe}}$

$= \frac{400 + 1 \times 10^3}{1 + 85}$

$(Z_o) = 16.27 \Omega$

$$Z_0' = Z_0 \parallel R_L \parallel R_E$$

$$= Z_0 \parallel R_L$$

$$= \frac{16.27 \times 5 \times 10^3}{16.27 + 5 \times 10^3}$$

$$Z_0' = 16.217 \Omega$$

$$A_{VS} = \frac{V_{CE}}{V_S}$$

$$= \frac{V_{CE}}{V_S} \times \frac{V_{BE}}{V_S}$$

$$A_{VS} = A_V \times \frac{Z_{in}'}{Z_{in}' + R_S}$$

$$= 0.997 \times \frac{13.499 \times 10^3}{13.499 \times 10^3 + 400}$$

$$= 0.9683$$

$$A_{IS} = \frac{R_E}{R_E + R_L} \times A_V \times \frac{R_S}{R_S + Z_{in}'}$$


$$= \frac{5.6 \times 10^3}{5.6 \times 10^3 + 47 \times 10^3} \times 86 \times \frac{400}{400 + 13.499 \times 10^3}$$

$$A_{IS} = 0.26349$$

Analysis of CB using simplified Model.

→ In CB amplifier, the source voltage (V_S) is connected b/n emitter to base terminal and load resistor (R_L) is connected b/n collector to base terminal.

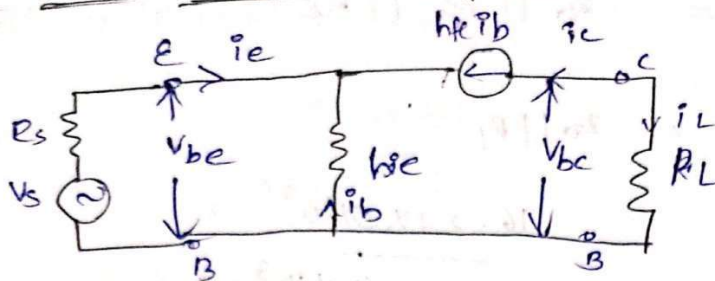From Generalised Model, Equivalent Circuit Shown below



As we know that a resistance (h_{ie}) is connected b/n Base to Emitter and a current source $h_{fe}i_b$ is connected b/n collector to emitter Terminal.

Current Gain (A_I): In CB amplifier, o/p current i_c and i/p current i_e

$$A_I = \frac{i_c}{i_e}$$

From o/p circuit

$$i_c = h_{fe}i_b$$

$$i_e = i_b(1 + h_{fe})$$

$$A_I = \frac{h_{fe}i_b}{i_b(1 + h_{fe})}$$

$$A_I = \frac{h_{fe}}{(1 + h_{fe})}$$

Voltage gain (A_V): In CB amplifier, o/p voltage is V_{bc} and i/p voltage is V_{be} .

$$\therefore A_V = \frac{V_{bc}}{V_{be}} \quad \text{or} \quad A_V = \frac{A_I \times R_L}{R_{in}}$$

$$A_V = \frac{V_{bc}}{V_{be}}$$

where $V_{be} = \frac{R_C R_L}{R_C + R_L}$

$$A_V = \frac{h_{fe}}{(1 + h_{fe})} \cdot \frac{R_L}{\frac{R_C R_L}{R_C + R_L}} \Rightarrow \frac{h_{fe} R_L}{h_{ie}}$$

Input Impedance (Z_{in}): In CB amplifier, i/p voltage is V_{be} , and i/p current is i_e .

$$\therefore Z_{in} = \frac{V_{be}}{i_e}$$

From i/p circuit

$$V_{be} = h_{ie} i_b$$

$$i_e = (1+h_{fe}) i_b$$

$$\therefore Z_{in} = \frac{h_{ie} i_b}{(1+h_{fe}) i_b}$$

$$Z_{in} = \frac{h_{ie}}{(1+h_{fe})}$$

Output Impedance (Z_o): In CB amplifier, o/p voltage V_{bc} and o/p current i_c .

$$\therefore Z_o = \frac{V_{bc}}{i_c}$$

$$V_{bc} = i_c R_L$$

$$Z_o = \frac{i_c R_L}{i_c} = R_L = \alpha$$

As $V_{be} \rightarrow 0 \Rightarrow i_e \rightarrow 0 \Rightarrow i_c \rightarrow 0$

$$\therefore Z_o = \frac{V_{bc}}{i_c} = \alpha$$

$$Z_o = \alpha$$

Consider a CB amplifier as shown in figure. as the following components $R_s = 600 \Omega$, $R_e = 5.6 k\Omega$

$R_c = 5.6 k\Omega$, $R_L = 39 k\Omega$, The transistor parameters are $h_{ie} = 1 k\Omega$, $h_{fe} = 85$; $h_{oe} = 2 \mu A/V$ calculate

A_i, Z_{in}, A_v, Z_o of given amplifier?


The effective load

$$R_L = 5.6 k\Omega \parallel 39 k\Omega$$

$$R_L = 4.89 k\Omega$$

$$h_{oe} R_L = 2 \times 10^{-6} \times 4.89 \times 10^3 = 0.00978 \ll 1$$

hence use simplified model

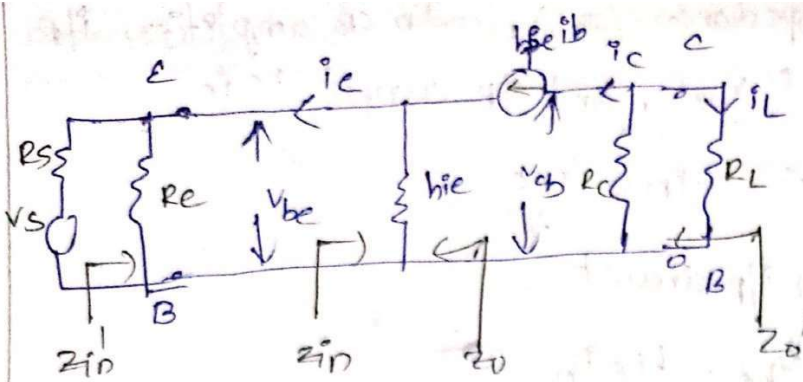

$$\text{Current gain } (A_I) = \frac{h_f}{1 + h_f} = \frac{85}{86}$$

$$(A_I) = 0.9883$$

$$\text{Input Impedance } (z_{in}) = \frac{h_{ie}}{1 + h_{fe}}$$

$$(z_{in}) = 11.627 \Omega$$

$$\text{Voltage gain } (A_V) = \frac{h_{fe} \cdot R_L}{h_{ie}}$$

$$= \frac{85 \times 24.84 \text{ K}\Omega}{1 \times 10^3}$$

$$(A_V) = 415.65$$

$$\text{Output Impedance } (z_o) = \frac{r_c / R_L}{r_c} \quad \left| \begin{array}{l} V_s = V_{be} \Rightarrow \\ R_L = \infty \end{array} \right.$$

$$z_o = r_c$$

$$z_{in}' = R_E \parallel z_{in}$$

$$= \frac{5.6 \times 10^3 \times 11.627 \Omega}{5.6 \times 10^3 + 11.627}$$

$$= 11.602 \Omega$$

$$z_{in}' = 11.602 \Omega$$

overall o/p impedance (Z_o) = $R_c \parallel R_L \parallel Z_o$

= $4.89k \Omega \parallel \frac{1}{2}$

= $\left(\frac{1}{4.89k \Omega}\right)^{-1}$

$Z_o = 4.89 \times 10^{-3} \Omega$

$A_{VS} = \frac{R_E}{R_E + R_L} \times \beta \times \frac{R_s}{R_s + Z_{in}}$

$A_{VS} = 0.1217$



$A_{VS} = \frac{A_V \times Z_{in}'}{Z_{in}' + R_s} \Rightarrow \frac{V_{cc}}{V_s} = \frac{V_{cc}}{V_s} \times \frac{V_{be}}{V_s}$

= $\frac{415.65 \times 11.602}{11.602 + 600}$

$A_{VS} = 4.8848$

Analysis of CE Amplifier with R_E Resistor (or)

unbypassed Resistor (or) reactive

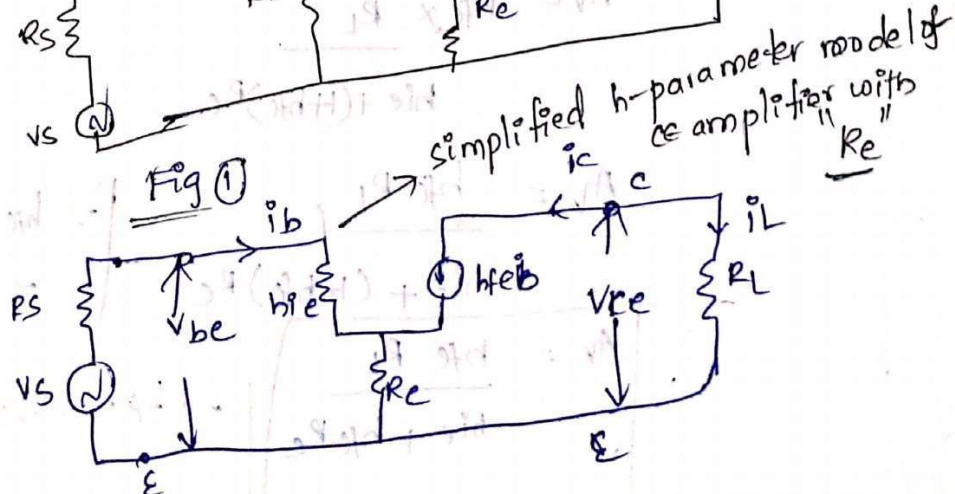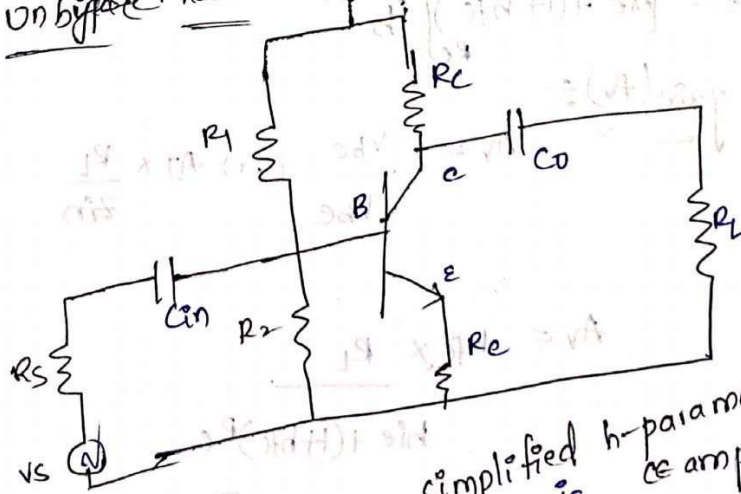

Current gain \div (A_I) In CE amplifier, o/p current is i_c

and i/p current is i_b

$$\therefore A_I = \frac{i_c}{i_b} \\ = \frac{h_{fe} i_b}{i_b}$$

Input Impedance (Z_{in}) \div

$$(Z_{in}) = \frac{V_{be}}{i_b}$$

From i/p circuit \div

$$V_{be} = h_{ie} i_b + R_e i_e \Rightarrow Z_{in} = \frac{(1+h_{fe}) i_b + h_{ie} i_b}{i_b}$$

$$V_{be} = h_{ie} i_b +$$

$$i_e = i_b + i_c$$

$$= i_b + h_{fe} i_b$$

$$V_{be} = i_b (1+h_{fe})$$

$$V_{be} = h_{ie} i_b + i_b (1+h_{fe}) R_e$$

$$V_{be} = [h_{ie} + (1+h_{fe}) R_e] i_b$$

Voltage gain (A_V) \div

$$A_V = \frac{V_{bc}}{V_{be}} \quad (\text{or}) \quad A_I \times \frac{R_L}{Z_{in}}$$

$$A_V = \frac{h_{fe} \times R_L}{h_{ie} + (1+h_{fe}) R_e}$$

$$h_{ie} + (1+h_{fe}) R_e$$

$$A_V = \frac{h_{fe} R_L}{h_{ie} + (1+h_{fe}) R_e}$$

$$h_{ie} + (1+h_{fe}) R_e$$

$\because h_{fe} \gg 1$

$\approx h_{fe}$

$$A_V = \frac{h_{fe} R_L}{h_{ie} + h_{fe} R_e}$$

$\because h_{fe} R_e \gg h_{ie}$



$$A_V = \frac{h_{fe} R_L}{h_{fe} R_e}$$

here $\rightarrow h_{ie}$

$h_{ie} + h_{fe} R_e \approx h_{fe} R_e$

$$A_V = \frac{R_L}{R_e}$$

output Impedance (Z_o) :-

$$Z_o = \frac{V_{be}}{I_c}$$

$$V_{be} = V_{be} = 0$$

$$R_L = d$$

$$V_{be} = 0 \Rightarrow I_b = 0$$

$$I_c = 0$$

$$Z_o = \frac{V_{ce}}{0}$$

$$Z_o = d$$

SUMMARY OF BJT AMPLIFIER

Parameter	Amplifier with exact Model.			Amplifier with simplified Model (Approximate Model)			CE with Re
	CE	CC	CB	CE	CC	CB	
Current gain (A _i)	$\frac{h_{fe}}{(1+h_{oe}R_L)}$	$\frac{-h_{fc}}{(h_{oc}R_L+1)}$	$\frac{-h_{fb}}{(1+h_{ob}R_L)}$	h_{fe}	$1+h_{fe}$	$\frac{h_{fe}}{(1+h_{fe})}$	h_{fe}
Input Impedance (Z _i)	$h_{ie} - h_{fe}h_{oe} \left(h_{oe} + \frac{1}{R_L} \right)$	$\frac{h_{ic} - h_{oc}h_{fc}}{h_{oc} + \frac{1}{R_L}}$	$\frac{h_{ib} - h_{ob}h_{fb}}{h_{ob} + \frac{1}{R_L}}$	h_{ie}	$h_{ie} + (1+h_{fe})R_L$	$\frac{h_{ie}}{(1+h_{fe})}$	$h_{ie} + (1+h_{fe})R_L$
Voltage gain (A _v)	$\frac{-h_{fe}}{(h_{oe} + \frac{1}{R_L})} \cdot \frac{1}{Z_{in}}$	$\frac{h_{fc}}{(h_{oc} + \frac{1}{R_L})} \cdot \frac{1}{Z_{in}}$	$\frac{h_{fb}}{(h_{ob} + \frac{1}{R_L})} \cdot \frac{1}{Z_{in}}$	$\frac{-h_{fe}R_L}{h_{ie}}$	$\left[\frac{1-h_{ie}}{Z_{in}} \right]$	$\frac{h_{fe}R_L}{h_{ie}}$	$\frac{R_L}{R_e}$
Output Impedance (Z _o)	$\frac{h_{re}}{h_{re}h_{oe} - h_{fe}h_{oc}}$	$\frac{h_{ic}}{h_{ic}h_{oc} - h_{fe}h_{fc}}$	$\frac{h_{fb}}{h_{fb}h_{ob} - h_{fe}h_{fb}}$	α	$\frac{R_s + h_{ie}}{(1+h_{fe})}$	α	α

Comparison of BJT Amplifiers.


Parameter	CE Amplifier	CC Amplifier	CB Amplifier
Input Impedance (Z_{in})	Medium (range of $k\Omega$)	High (Range of hundreds of $k\Omega$)	Low [Range of tens of Ω s]
Current gain (A_I)	High (> 100) It depends on h_{fe} value.	High ($\times 100$) [It depends on h_{fe} value.]	Low High ($\times 100$) Low (< 1)
Voltage gain (A_V)	High (> 100)	Low (< 1)	High (> 100).
Output Impedance (Z_o)	High (Range of tens of $k\Omega$)	Low [Range of tens of Ω m]	High (Range of tens of $k\Omega$).

Consider a single stage CE amplifier with unbypassed emitter resistance as the following components,
 $R_1 = 50k\Omega$, $R_2 = 2k\Omega$, $R_C = 1k\Omega$, $R_E = 270\Omega$ and
 $R_L = 1.2k\Omega$. Find A_I , A_V , Z_{in} , Z_o ? use typical values of h-parameters, $R_S = 1k\Omega$.

For CE

$$h_{ie} = 1.1k\Omega, h_{fe} = 50$$
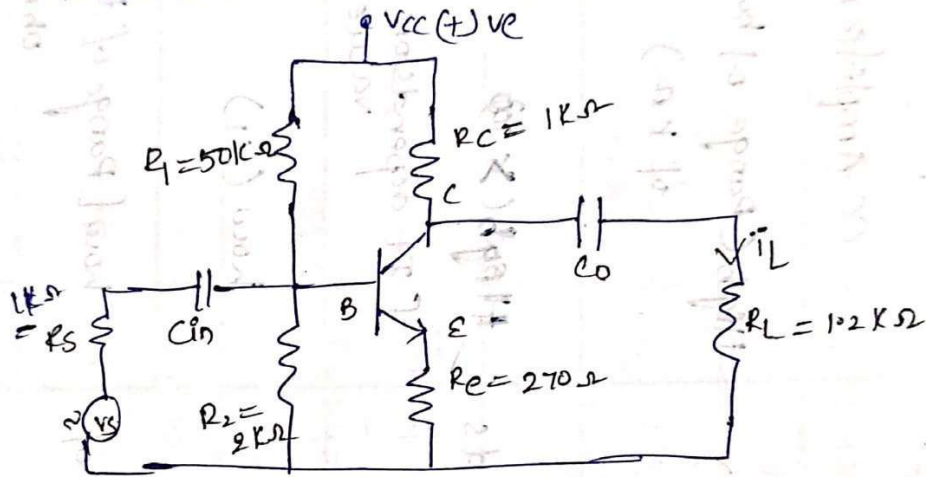
$$h_{re} = 2.5 \times 10^{-4}, h_{oe} = 25 \mu A/V$$



$$\text{Current gain } (A_I) = h_{fe}$$

$$(A_I) = h_{fe} = 50$$

$$\text{Input Impedance } (Z_{in}) = h_{ie} + (1 + h_{fe})R_E$$

$$= 1.1 \times 10^3 + (1 + 50) \times 270$$

$$(Z_{in}) = 14.877 k\Omega$$

$$R_L = R_C \parallel R_L = 14.87 k\Omega$$


$$= 1 \times 10^3 \parallel 1.2 k\Omega$$

$$R_L = 545.45 \Omega$$

$$h_{oe} R_L = 25 \times 10^{-6} \times 545.45$$

$$= 0.013 < 0.1$$

Hence use simplified model.

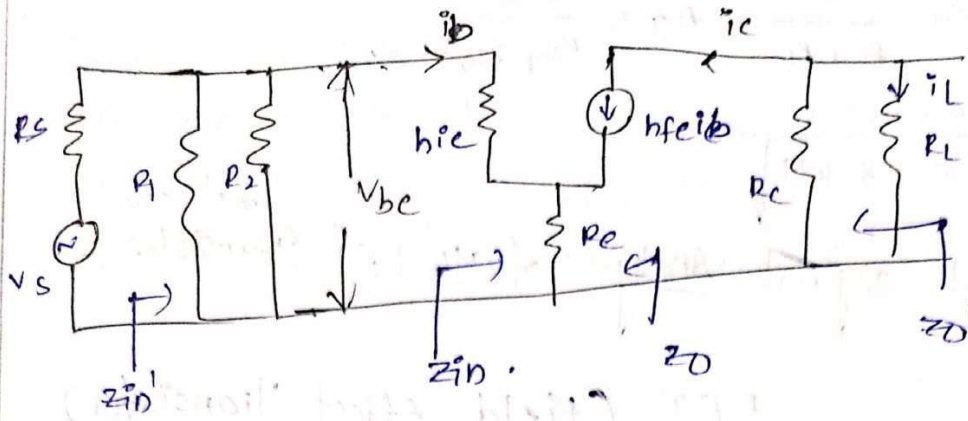

$$\text{Voltage gain } (A_v) = \frac{R_L}{R_e}$$

$$= \frac{545.45}{270}$$

$$A_v = 2.0201$$

$$\text{Overall i/p Impedance } (z_{in}') = R_1 \parallel R_2 \parallel z_{in}$$

$$= 1702.85$$

$$z_{in}' = 1.702 \text{ k}\Omega$$

$$\text{output Impedance } (z_o) = r_c$$

$$\text{overall output Impedance } (z_o') = R_c \parallel z_o$$

$$= \frac{1}{545.45} + \frac{1}{\infty}$$

$$= \left(\frac{1}{545.45} \right)$$

$$(z_o') = 545.45 \Omega$$

$$A_{VS} = A_v \times \frac{z_{in}'}{z_{in}' + R_s}$$

$$= 2.0201 \times \frac{1.702 \times 10^3}{1.702 \times 10^3 + 1 \times 10^3}$$

$$= 1.272$$


$$A_{VS} = 1.272$$

$$A_{IS} = \frac{R_C}{R_C + R_L} \times A_{IX} \times \frac{R_S}{R_S + Z_{in}}$$

$$A_{IS} = 8.411$$

Small signal Analysis of MOSFET (Amplified Transistor)

FET (Field effect Transistor)

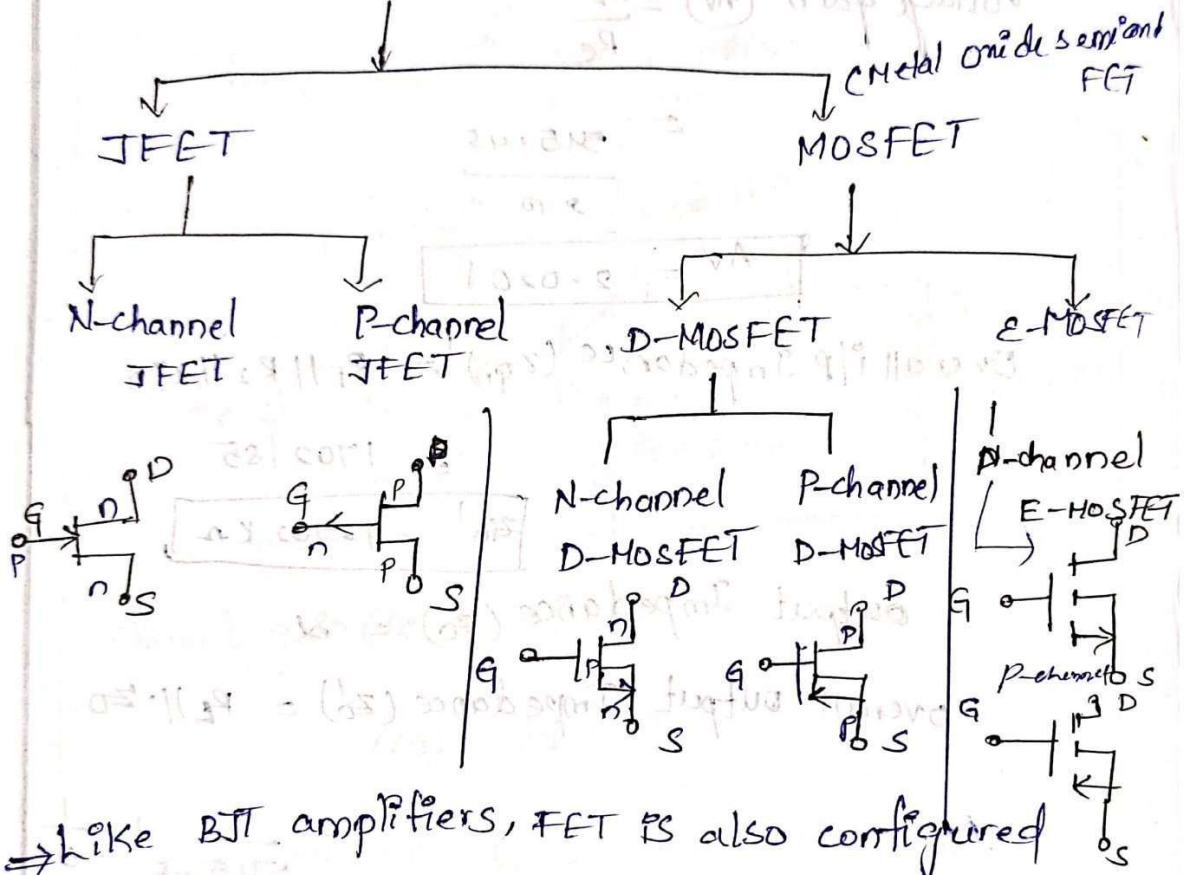

⇒ Like BJT amplifiers, FET is also configured

into three configurations such as 1. common gate, 2. common drain and 3. common source.


⇒ The AC analysis of MOSFET requires the small signal AC model which can be derived from the operation of MOSFET.

1) A major component of the AC model will reflect the AC voltage is applied to the i/p will control the level of output current.

It can be represented as by the voltage source across the inputs and a current source across the output terminals.

2) The current source as its arrow pointing down to establish a 180° phase shift b/w input and output.

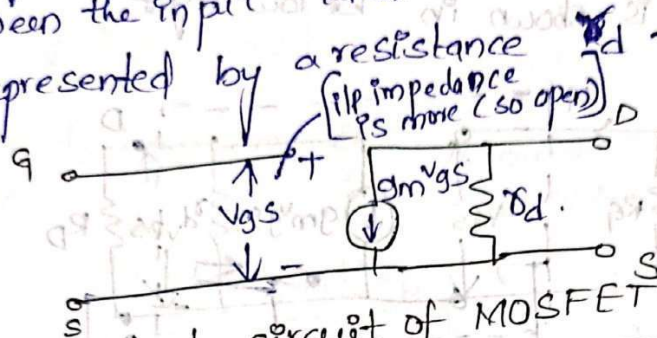3) As we know the input impedance of MOSFET is very high and it can be represented as open ckt between the input terminals, and output impedance is represented by a resistance r_d .



AC equivalent circuit of MOSFET.

where g_m is called **transconductance**.
 \Rightarrow It is the ratio of o/p current to i/p voltage.

$$g_m = \frac{i_d}{v_{gs}}$$

$$g_m = \frac{i_d}{v_{gs}}$$

$\frac{1}{y_{os}} = r_d$
 y_{os} is called output admittance.


$$g_m = g_{m0} \left[1 - \frac{v_{gs}}{V_p} \right]$$

where $g_{m0} = \frac{2 I_{DSS}}{|V_p|}$ (saturation current of drain / pinchoff voltage).


Analysis of Common Source Amplifier:

As we know, in common source, the input voltage is applied b/w gate terminal to source terminal and the output voltage is taken across drain terminal to source terminal.

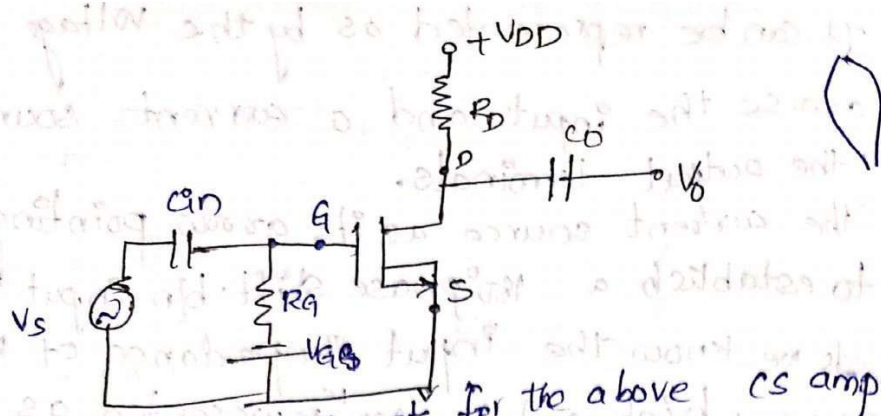\rightarrow The below figure shows CS amplifier with fixed bias.



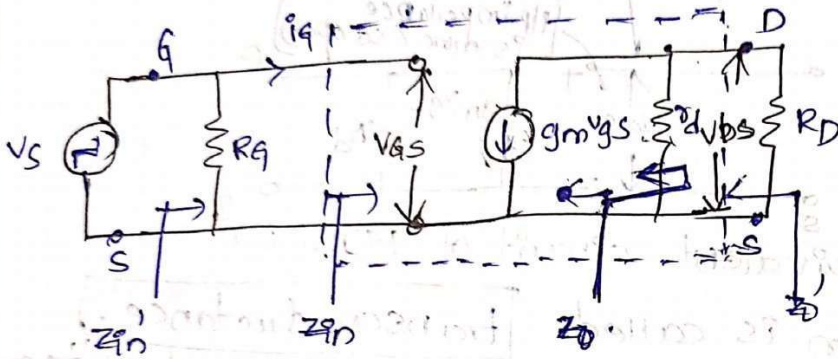The AC equivalent circuit for the above CS amplifier circuit is shown in below fig:



Input Impedance (Z_{in}): In CS amplifier, input voltage is V_{gs} and i/p current is i_g .

$$\therefore Z_{in} = \frac{V_{gs}}{i_g}$$

From input circuit, i/p terminals are open circuited,

i.e., which indicates $i_g = 0$.

$$\therefore Z_{in} = \frac{V_{gs}}{0}$$

$$Z_{in} = \infty$$

overall i/p Impedance: $Z_{in}^{total} = R_g \parallel Z_{in}$

$$= R_g \parallel \infty$$

$$Z_{in} = R_g$$

output impedance (z_0) :- In CS amplifier, output voltage is v_{DS} and o/p current is i_D .

$$\therefore z_0 = \frac{v_{DS}}{i_D} \quad \left| \quad v_{GS} = 0 \right.$$

From o/p circuit :-


$$v_{GS} = 0 \Rightarrow g_m(v_{GS}) = 0$$

$$\therefore z_0 = r_D$$

overall o/p Impedance (z_0') :-

$$z_0' = z_0 \parallel R_D$$

$$z_0' = r_D \parallel R_D$$

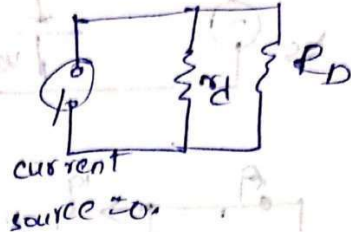

Voltage gain (A_v) :- In CS amplifier, o/p voltage is v_{DS} and i/p voltage is v_{GS} .

$$A_v = \frac{v_{DS}}{v_{GS}}$$

From o/p circuit :-

$$v_{DS} = -g_m v_{GS} (r_D \parallel R_D)$$

$$A_v = \frac{-g_m v_{GS} (r_D \parallel R_D)}{v_{GS}}$$

$$A_v = -g_m (r_D \parallel R_D)$$



The fixed bias configuration of CS amplifier as an operating point defined by $v_{GS0} = -2V$

$I_{DQ} = 5.625 \text{ mA}$, with $I_{DSS} = 10 \text{ mA}$ and $V_{p} = -8V$

The resistor values are $R_g = 1 \text{ M}\Omega$, $R_D = 2 \text{ k}\Omega$. The parameter $V_{GS} = 40 \text{ mS/V}$.

↳ output admittance

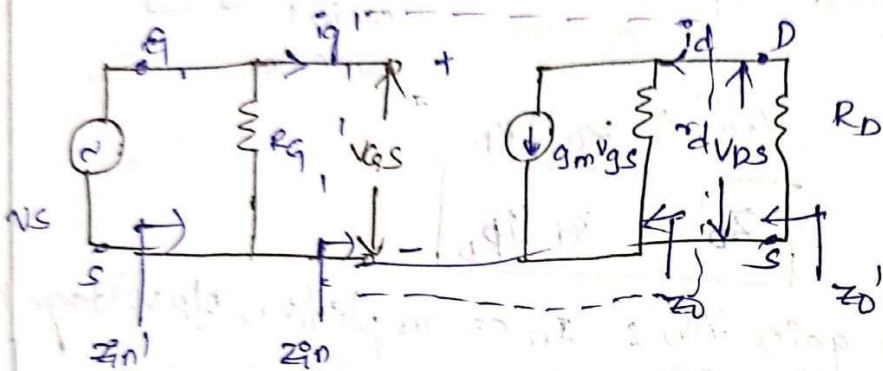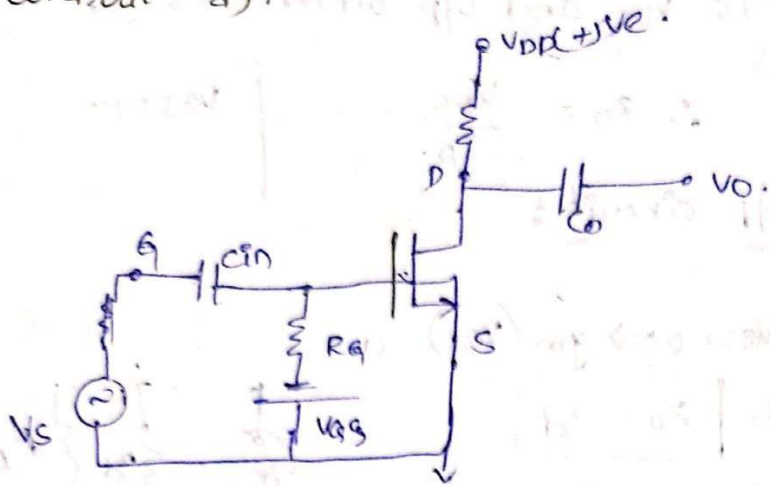Calculate g_m , δ_d , z_{in} , z_{in}' , z_o , z_o' , A_v (with and without δ_d)?



$$\begin{aligned}
 \textcircled{1} \quad I_D &= I_{DSS} \left[1 - \frac{V_{GS}}{V_p} \right]^2 \\
 &= 10 \times 10^{-3} \left[1 - \left(\frac{-2}{-8} \right) \right]^2 \\
 &= 10 \times 10^{-3} \left[1 - \frac{1}{4} \right]^2 \quad \text{no need} \\
 &= 10 \times 10^{-3} \left[\frac{3}{4} \right]^2 \\
 &= 10 \times 10^{-3} \left[\frac{9}{16} \right] = 0.005625
 \end{aligned}$$

$$I_D = 5.625 \mu\text{Amp}$$

$$g_{m0} = \frac{2 I_{DSS}}{|V_p|} = \frac{2 \times 10 \times 10^{-3}}{8} = \boxed{2.5 \text{ mSemen}}$$

$$g_m = g_{m0} \left[1 - \frac{V_{GS}}{V_p} \right] = 2.5 \times 10^{-3} \left[1 - \left(\frac{-2}{-8} \right) \right] = 1.87 \text{ mSemen}$$

$$R_i = \frac{1}{\frac{1}{40k} + \frac{1}{40 \times 10^{-6}}} = \frac{1}{\frac{1}{40k} + 25000} = 25k\Omega$$

$$R_i = 25k\Omega$$

$$z_{in} = \alpha$$

$$z_{in}' = z_{in} \parallel R_g$$

$$= \alpha \parallel R_g$$

$$z_{in}' = 1M\Omega$$

$$z_o = r_d$$

$$z_o' = r_d \parallel R_D$$

$$= 25k\Omega \parallel 2k\Omega$$

$$z_o' = 1.85k\Omega$$

$$A_v (\text{with } r_d) = -g_m (r_d \parallel R_D)$$

$$= -1.87 \times 10^{-3} [25k\Omega \parallel 2k\Omega]$$

$$= -1.87 \times 10^{-3} [1.85 \times 10^3]$$

$$A_v = -3.46$$

$$A_v (\text{without } r_d) = -g_m (R_D)$$


$$= -1.87 \times 10^{-3} [2 \times 10^3]$$

$$A_v (\text{without } r_d) = -3.74$$


Analysis of CD Amplifier (or) Source Follower

→ In CD amplifier, the ^{input} (source) voltage is applied b/w gate and drain terminal and output voltage is taken b/w source and drain terminal.

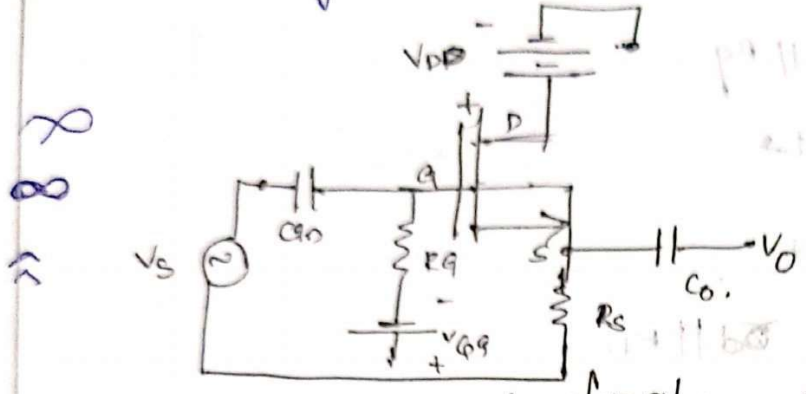
→ The below figure shows the CD amplifier with fixed bias



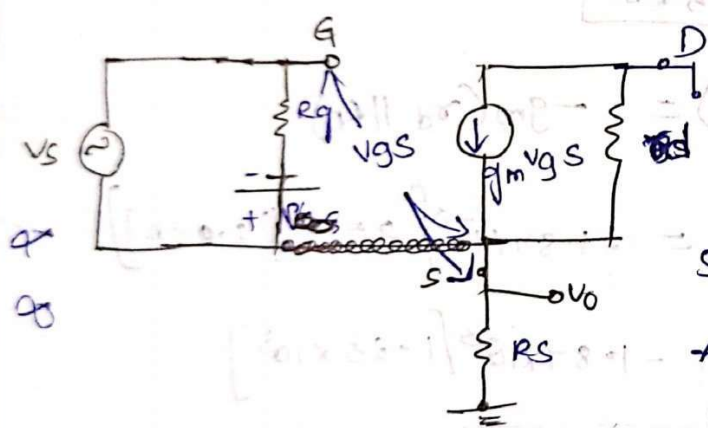AC equivalent circuit for above fig shows below



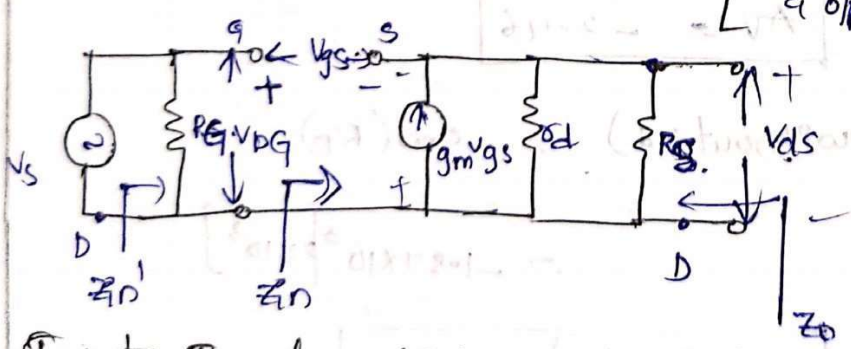→ It is difficult to analyse
 So again equivalent AC circuit.
 AS i/p circuit at left
 & o/p circuit at right



Input Impedance (Zin) =

$$(Z_{in}) = \frac{V_g}{I_g}$$

From equivalent i/p circuit the i/p terminal is open circuit i.e. $I_g = 0$.

$$Z_{in} = \infty$$

Overall input Impedance (Z_{in}') =

$$Z_{in}' = Z_{in} \parallel R_g \Rightarrow \infty \parallel R_g$$

$$Z_{in}' = R_g$$

Output Impedance (Z_o) =

$$Z_o = \frac{V_{DS}}{I_S}$$

$$Z_o = \frac{V_{DS}}{I_S}$$

Voltage gain (with r_d) =

$$A_v = \frac{V_{DS}}{V_{GS}}$$

Apply KCL at Node S

$$g_m V_{GS} + I_S = I_{rd} + I_{RS}$$

$$I_S = I_{rd} + I_{RS} - g_m V_{GS} \text{ (opposite)}$$

$$I_S = \frac{V_{DS}}{r_d} + \frac{V_{DS}}{R_S} - g_m (-V_{DS})$$

$$I_S = V_{DS} \left[\frac{1}{r_d} + \frac{1}{R_S} + g_m \right]$$

$$\therefore Z_o = \frac{V_{DS}}{V_{DS} \left[\frac{1}{r_d} + \frac{1}{R_S} + g_m \right]}$$

$$Z_o = \frac{1}{\frac{1}{r_d} + \frac{1}{R_S} + g_m} \approx r_d \parallel R_S \parallel \frac{1}{g_m}$$



Voltage gain (A_v) = (with r_d) or without

$$A_v = \frac{V_{DS}}{V_{GS}}$$

$$A_v = \frac{V_{DS}}{V_{GS}} = \frac{V_{DS}}{V_{GS}}$$

$$V_{DS} = g_m V_{GS} (r_d \parallel R_S)$$

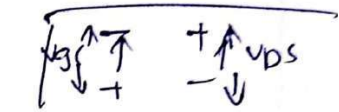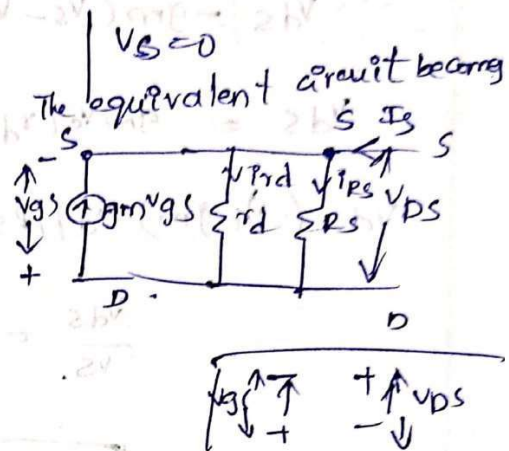
$$V_{DS} = g_m V_{GS} (r_d \parallel R_S)$$



Apply KVL to entire circuit

$$V_s - V_{gs} - V_{ds} = 0$$

$$V_{gs} = V_s - V_{ds}$$

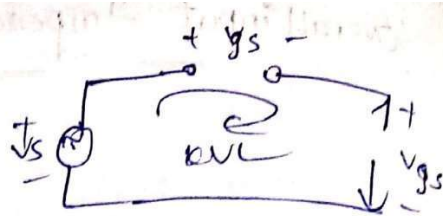

$$V_{ds} = g_m (V_s - V_{ds}) (r_d || R_s)$$

$$V_{ds} = g_m V_s (r_d || R_s) - g_m V_{ds} (r_d || R_s)$$

$$V_{ds} (1 + g_m (r_d || R_s)) = g_m V_s (r_d || R_s)$$

$$\frac{V_{ds}}{V_s} = \frac{g_m (r_d || R_s)}{1 + g_m (r_d || R_s)}$$

$$A_v = \frac{g_m (r_d || R_s)}{1 + g_m (r_d || R_s)}$$


Resistance connected at source r_m

The DC analysis of the source follower [CD amplifier] will result in

$$V_{GSQ} = -2.86V, I_{DQ} = 4.55mA \text{ with } I_{DSS} = 16mA, V_p = -4V \text{ with } R_g = 1M\Omega, R_s = 2.2k\Omega$$

The parameter $Y_{os} = 25 \mu A/V$ (or) 25×10^{-6} seimen. calculate

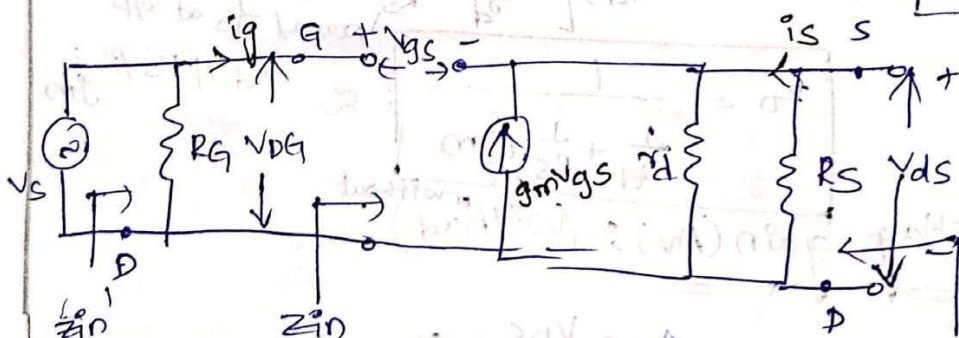$g_m, r_d, Z_{in}, Z_o, A_v$ (with and with r_d)?
 If $g_{m0} = 2mS$ we should take if they not given



$$Z_{in} = \frac{V_{gd}}{i_g}$$

$$Z_{in} = \frac{V_{gd}}{i_g}$$

$$Z_{in} = r_d$$

$$g_{m0} = 2 \frac{I_{DSS}}{|V_p|} = \frac{2 \times 8 \times 10^{-3}}{4} = 8 \text{ mS} \quad \boxed{8 \text{ mS}}$$

$$g_m = g_{m0} \left[1 - \frac{V_{GS}}{V_p} \right] = 8 \times 10^{-3} \left[1 - \frac{2.086}{4} \right] = 8 \times 10^{-3} \left[1 - \frac{2.086}{4} \right]$$

$$= 0.002280$$

$$r_d = \frac{1}{y_{os}} = \frac{1}{25 \times 10^{-6}} = 40 \text{ k}\Omega$$

$$= 2.28 \text{ mS} \quad \boxed{2.28 \text{ mS}}$$

$$z_{in} = R_g = R_g = 1 \text{ M}\Omega$$

$$z_o = \frac{1}{\frac{1}{r_d} + \frac{1}{R_s} + g_m} = \frac{1}{\frac{1}{40 \times 10^3} + \frac{1}{2 \times 10^3} + 2.28 \times 10^{-3}} = 362.378 \Omega$$

$$\boxed{362.378 \Omega}$$

$$A_v = \frac{g_m [r_d \parallel R_s]}{1 + g_m (r_d \parallel R_s)}$$

$$A_v = \frac{2.28 \times 10^{-3} \left[\frac{40 \times 10^3 \times 2 \times 10^3}{40 \times 10^3 + 2 \times 10^3} \right]}{1 + 2.28 \times 10^{-3} \left[\frac{40 \times 10^3 \times 2 \times 10^3}{40 \times 10^3 + 2 \times 10^3} \right]}$$

$$= \frac{2.28 \times 10^{-3} \times 2 \times 10^3}{1 + 2.28 \times 10^{-3} \times 2 \times 10^3} = 0.8262$$

$$\boxed{A_v = 0.8262}$$


$$A_v (\text{without } r_d) = \frac{g_m (R_s)}{1 + g_m (R_s)} = \frac{2.28 \times 10^{-3} \times 2 \times 10^3}{1 + 2.28 \times 10^{-3} \times 2 \times 10^3} = 0.8337$$

$$\boxed{A_v = 0.8337}$$


Analysis of common gate (CG) amplifier:

In CG amplifier, the input voltage is applied b/n source and gate terminal and output voltage is taken across drain and gate terminal.

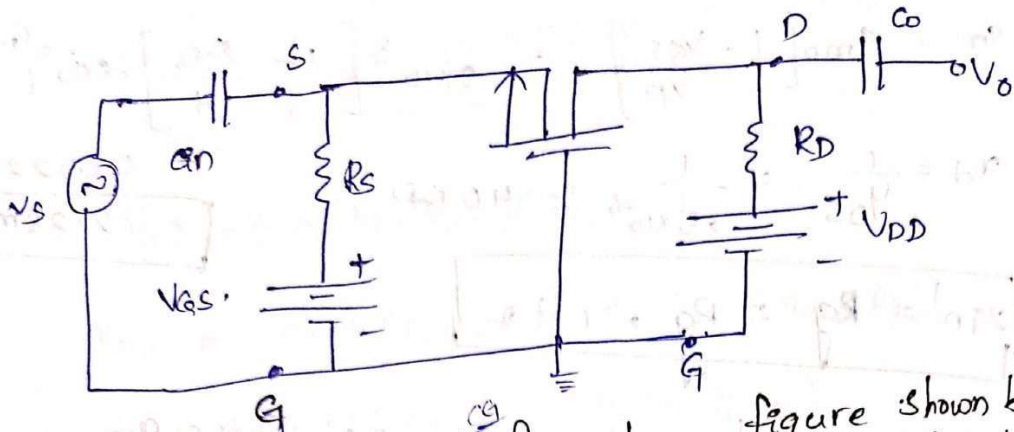The below figure shows the common gate amplifier with fixed bias.



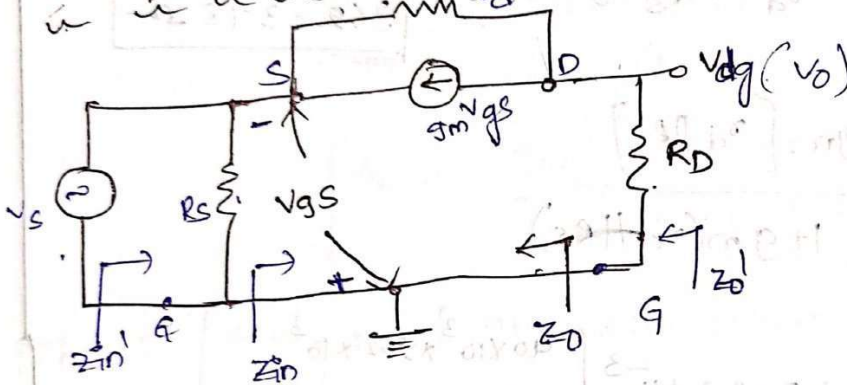AC equivalent circuit for above figure shown below.



Input Impedance (Z_{in}): In CG amplifier, input voltage is v_{gs} and i/p current is I_s . Then

$$Z_{in} = \frac{v_{gs}}{I_s}$$

$$Z_{in} = \frac{v_{gs}}{I_s}$$


Redraw the equivalent circuit as shown in figure to find Input Impedance:

Apply KVL to o/p parameter of networks.

$$v_{gs} - v_{sd} - v_{RD} = 0$$

$$v_{gs} = v_{sd} + v_{RD}$$

$$v_{sd} = v_{gs} - v_{RD}$$

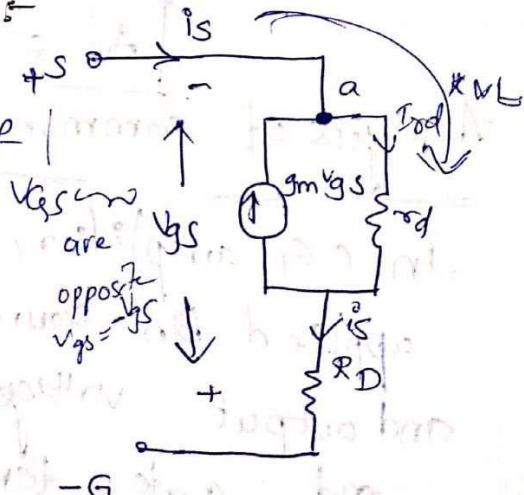

$$I_{DQ} = \frac{V_{GS} - V_{TP}}{R_s} = \frac{V_{GS} - I_{DQ} R_D}{r_d}$$

Apply KCL at node "a".

$$I_{S1} + g_m V_{GS} = I_{DQ}$$

$$I_{S1} = I_{DQ} - g_m V_{GS}$$

$$= \frac{V_{GS} - V_{TP}}{r_d} - g_m (-V_{GS})$$

$$I_{S1} = \frac{V_{GS}}{r_d} - \frac{V_{TP}}{r_d} + g_m (V_{GS})$$

$$I_{S1} = \frac{V_{GS}}{r_d} - \frac{I_{S1} R_D}{r_d} + g_m V_{GS}$$

$$I_{S1} + \frac{I_{S1} R_D}{r_d} = V_{GS} \left[\frac{1}{r_d} + g_m \right]$$

$$I_{S1} \left[1 + \frac{R_D}{r_d} \right] = V_{GS} \left[\frac{1}{r_d} + g_m \right]$$

$$\frac{V_{GS}}{I_{S1}} = \frac{\left[1 + \frac{R_D}{r_d} \right]}{\left(\frac{1}{r_d} + g_m \right)} = \frac{r_d + R_D}{1 + g_m r_d}$$

Overall i/p Impedance = $Z_{in} = \frac{r_d + R_D}{1 + g_m r_d}$

$Z_{in} = Z_{in} \parallel R_{S1}$

output Impedance (Z_o): In CG amplifier,

output voltage is V_{DQ} and o/p current is I_{DQ} .

$$\therefore Z_o = \frac{V_{DQ}}{I_{DQ}}$$

By keeping i/p voltage of V_{GS}

$$V_{GS} = 0$$

(or)

$$V_{GS} = 0$$

with $V_{GS} = 0$ / $V_{GS} = 0$ i/p circuit becomes short

So, R_{S1} becomes short (≈ 0) and when $V_{GS} = 0$

then current source open circuit. Then r_d is connected b/n D and source (ground),

$$Z_D = r_D$$

$$\therefore Z_D' = R_D \parallel Z_D$$

$$Z_D' = R_D \parallel r_D$$

Voltage gain (A_V) =

In CE amplifier, o/p voltage is V_{dg} and i/p voltage is V_{gs} .

$$\therefore A_V = \frac{V_{dg}}{V_{gs}}$$

From equivalent circuit,

$$V_{in} \text{ (or) } V_{gs} = -V_{gs}$$

$$V_{dg} \text{ (or) } V_o = I_D R_D$$

The voltage across r_D (V_{rd}) = $V_o - V_{in}$

$$I_{rd} = \frac{V_o - V_{in}}{r_D}$$

Apply KCL at node B'

[By neglecting (I_{RD})]

$$I_D = g_m V_{gs} + I_{rd}$$




$$I_D = \frac{V_o - V_{in}}{r_D} + g_m V_{gs}$$

$$I_D = \frac{(V_o + V_{gs})}{r_D} + g_m V_{gs}$$

sub I_D in V_o then

$$V_{dg} \text{ (or) } V_o = \left[\frac{V_o + V_{gs}}{r_D} + g_m V_{gs} \right] R_D$$
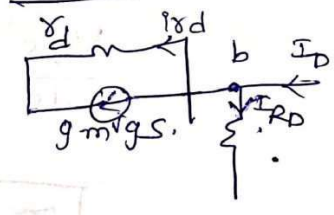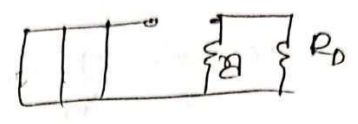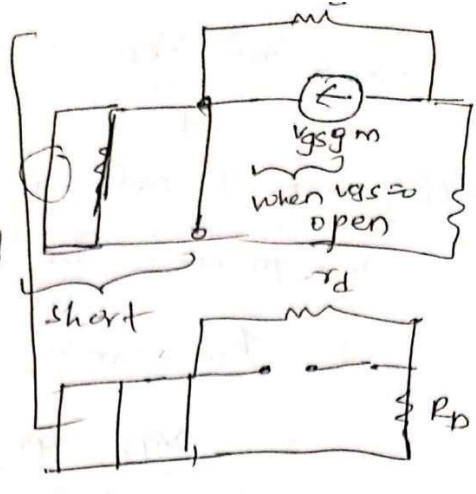
$$V_{dg} = V_o = \frac{R_D (V_o + V_{gs})}{r_D} + g_m V_{gs} R_D$$



$$V_{dg} = V_o \Rightarrow \frac{R_D V_o}{r_d} + \frac{V_{gs} R_D}{r_d} + g_m V_{gs} R_D$$

$$V_{dg} = \frac{R_D V_{dg}}{r_d} = \frac{V_{gs} R_D}{r_d} + g_m V_{gs} R_D$$

$$V_{dg} \left[1 - \frac{R_D}{r_d} \right] = V_{gs} \left[\frac{R_D}{r_d} + g_m R_D \right]$$

$$\frac{V_{dg}}{V_{gs}} = \frac{\left[\frac{R_D}{r_d} + g_m R_D \right]}{\left[1 - \frac{R_D}{r_d} \right]}$$

$$A_v = \frac{R_D + g_m r_d R_D}{r_d - R_D}$$

The DC Analysis of CG amplifier, $V_{gs} = -2.2V$ and $I_{DSS} = 8.03mA$, with $I_{DSS} = 10mA$ and $V_p = -4V$ and $y_{os} = 50\mu A/V$. Calculate g_m , r_d , Z_{in} , Z_{in}' , Z_o , Z_o' , A_v ? with and without (r_d)? $R_S = 1.1k\Omega$, $R_D = 3.6k\Omega$?

$$g_{m0} = \frac{2 |I_{DSS}|}{|V_p|} = \frac{2 |10 \times 10^{-3}|}{4} = 0.0050 = \boxed{5 \text{ mS/cm}}$$

$$g_m = g_{m0} \left[1 - \frac{V_{gs}}{V_p} \right] = 5 \times 10^{-3} \left[1 - \left(\frac{-2.2}{-4} \right) \right] = 0.00225 = \boxed{2.25 \text{ mS/cm}}$$

$$r_d = \frac{1}{y_{os}} = 20000 = \boxed{20k\Omega}$$

$$Z_{in} = \frac{r_d + R_D}{1 + g_m r_d} = \frac{513.0434 \Omega}{1 + 2.25 \text{ mS/cm} \cdot 20k\Omega}$$

$$Z_{in}' = Z_{in} || R_S = \boxed{349.845 \Omega}$$

$$Z_o = r_d = 20k\Omega$$

$$Z_o' = R_D || r_d = 3050.84 = \boxed{3.050k\Omega}$$

$$(A_v \text{ without } R_D) \div \left[\frac{R_D + g_m r_D R_D}{R_D - R_D} \right]$$


$$= \frac{3.6 \times 10^3 + 2.25 \times 10^{-3} \times 3.6 \text{ k}\Omega \times 20 \text{ k}\Omega}{2.25 \times 10^{-3} - 3.6 \text{ k}\Omega}$$

$$A_v = \frac{165.6 \times 10^3}{-3599.77} = -0.046007$$

$$= \boxed{-46}$$

$$(A_v \text{ without } R_D) \div \left[\frac{R_D + g_m R_D}{1 - R_D} \right]$$

$$A_v = -1.00225$$

verified


9/1/22

UNIT - II

Differential and Multistage Amplifiers

Q. Multistage Amplifier: Amplification is carried out at more than one stage is called multistage amplifier.

(or)
Transistor circuit have two (or) more than two transistors called multistage amplifier.

Q. Why Multistage Amplifier:
Imp The o/p of a single stage amplifier is usually insufficient to drive an as a output devices.

→ The gain of a single stage amplifier is insufficient for particular purposes, then additional amplification over two (or) more stages is required.

→ To achieve this, the o/p of each amplifier stage is coupled to the next stage.

→ The resulting system is called as multistage amplifier.

Q. Transistor circuit containing more than one stage of amplifier is known as "multistage amplifier".

Purpose of coupling device:
→ The purpose of coupling device is to transfer the ac signal from one stage to next stage and it isolate the DC conditions from one stage to next stage.

→ In multistage amplifier, a no. of single stage amplifiers are connected in Cascade arrangement.

→ (ie) The o/p of one stage is connected as an input for the next stage with suitable coupling device,

called as passive elements [L, R, C, Transformer]


Q. Need for Cascading / Multistaging:

→ Many times, the primary requirements of the

of the amplifier cannot be achieved with single stage amplifier then go for cascading in the following cases:-

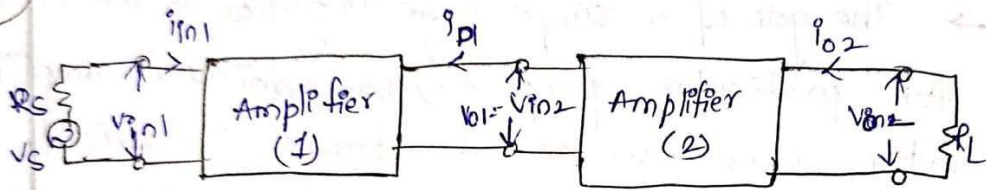- 1) When the amplification of single stage is not sufficient.
- 2) When the input and o/p impedances are of not correct magnitude.
- 3) When the voltage gain of single stage amplifier

can vary (unstable) \rightarrow (instability).
 Consider a Multistage amplifier shown in fig:-



In the above figure, $V_{in1} = V_s$ input of 1st stage.

V_{o1} is o/p of stage-1; V_{o2} is o/p of stage-2.

V_{in2} is i/p of stage 2

\rightarrow We know that voltage gain (A_v) is the ratio of o/p voltage to i/p voltage.

$$A_v = \frac{V_{o2}}{V_s} = \frac{V_o}{V_{in}}$$

For above circuit $A_v = \frac{V_{o2}}{V_{in1}}$

$$A_v = \frac{V_{o2}}{V_{in2}} \times \frac{V_{in2}}{V_{in1}}$$

$$\Rightarrow A_v = \frac{V_{o2}}{V_{in2}} \times \frac{V_{o1}}{V_{in1}} \quad \left| \because V_{in2} = V_{o1} \right.$$

$$A_v = A_{v2} \times A_{v1}$$

overall voltage gain $A_v = A_{v1} \times A_{v2} \times A_{v3} \times \dots \times A_{vn}$

$\left. \begin{array}{l} A_v \& P_v \text{ asked} \\ \text{for EM SO} \\ \text{write from} \\ \text{Diagram.} \end{array} \right\} \left\{ \begin{array}{l} A_v \& P_v \text{ in} \\ \text{dB} \end{array} \right.$

voltage gain is the product of individual (voltage gains) stages.

Def:

Power gain (P_v) :- It is the ratio of o/p power to i/p power.

$$P_v = \frac{P_o}{P_i} = \frac{V_o I_o}{V_i I_i}$$

$$P_v = P_{v1} \times P_{v2} \times \dots \times P_{vn}$$

The overall power gain is the product of powers of individual stages.

→ The voltage gain in dB can be expressed as.

$$A_v(\text{dB}) = 20 \log(A_v) = 20 \log(A_{v1}) + 20 \log(A_{v2}) + \dots + 20 \log(A_{vn})$$

The overall voltage gain in (dB) for Multistage amplifier's

$$A_v(\text{dB}) = 20 \log(A_{v1}) + 20 \log(A_{v2}) + 20 \log(A_{v3}) + \dots + 20 \log(A_{vn})$$

From above eqn:-

→ The overall gain in (dB) is sum of voltage gains in (dB) of individual stages.

Def

$$P_v(\text{dB}) = 20 \log(P_{v1}) + 20 \log(P_{v2}) + 20 \log(P_{v3}) + \dots + 20 \log(P_{vn})$$

$$P_v(\text{dB}) = 20 \log(P_{v1}) + 20 \log(P_{v2}) + \dots + 20 \log(P_{vn})$$

Classification of Multistage Amplifiers :-

① Based on type of Configurations :-

- a) CE-CE amplifier
 - b) CE-CC amplifier
 - c) CE-CB amplifier
 - d) CC-CC amplifier
- } Cascade amplifier
- } Darlington amplifier


② Based on coupling method :-

- a) RC coupled amplifier.
- b) Transformer coupled amplifier.
- c) Direct coupled amplifier.

Two stage RC coupled amplifier:

This is the most popular type of coupling because it is cheap and provides excellent audio ^{amplification} fidelity over a wide range of frequencies.

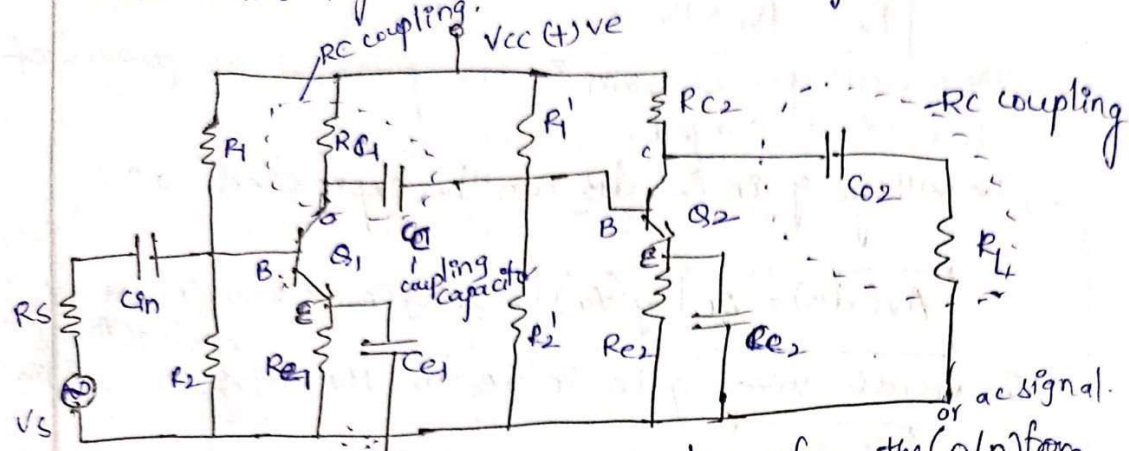- It is usually used for voltage amplification.
- The below figure shows the two stage RC coupled amplifier.



→ Coupling capacitor is used to transfer the (o/p) from one stage to next stage.


→ In above fig, transistor is configured as CE-CE with voltage divider bias. Hence it is also called two stage **CE-CE** cascade amplifier.

→ When an AC i/p signal is applied to the base of the first transistor it appears in the amplified form across its collector resistor (R_{c1}).

→ The amplified signal across (R_{c1}) is given to base of next stage through coupling capacitor (C_c)

→ Then the second stage, thus further amplification of the signal. In this way the cascaded stages amplify the signal and the overall gain is considerably increases.

Frequency Response:

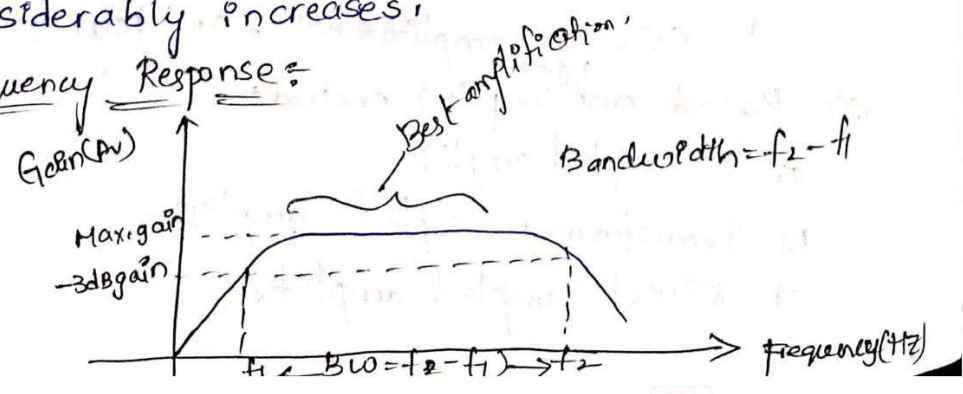

The above fig (Frequency Response) shows the frequency response of a two-stage RC coupled amplifier.

From fig, it is clear that at low frequencies the gain of the amplifier increases and at high frequencies the gain of the amplifier decreases whereas at mid-frequencies gain of the amplifier is constant.

→ From graph, we can say that two-stage RC coupled amplifier provides excellent frequency response over a mid-frequencies.

Frequency Response:

2M Advantages of RC coupled:

→ It has excellent frequency response over audio

frequency Range [20Hz - 20KHz]

→ It has easiest ^{easy to construct} and low cost, since resistors & capacitors are cheap. _{circuit weight less.}

→ The circuit is very compact (less) as the modern resistors and capacitors are small and light weight.

2M Disadvantages:

→ It has low voltage and power gain. (no voltage gain)

→ It has poor impedance matching, due to resistors.

→ This circuit has tendency to become noisy with aging.

2M Applications:

→ Widely used as voltage amplifiers.


→ These are generally used in last stage of amplification.

Drawback (low voltage & power gain) overcome through transformer.

Transformer coupled amplifiers :-

Drawback of RC coupled amplifier [low voltage gain and poor impedance matching] are overcome

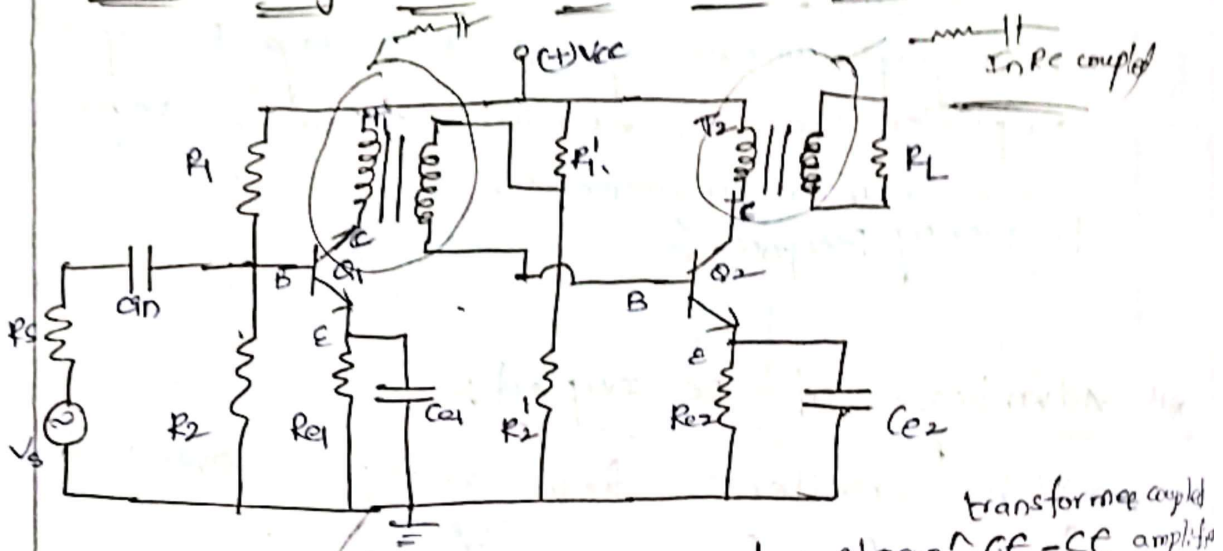with the help of transformer coupled amplifier. The below fig. shows transformer coupled amplifier :-



→ The above figure shows the two stage ^{transformer coupled} CE-CE amplifier

where collector resistor R_c is replaced with primary of the transformer and its secondary is connected to the base of the next (second) stage

Operation :-


When an AC signal is applied to base of the first transistor it appears in amplified form across primary of the coupling transformer.

→ The voltage developed across primary is transferred to the input of the next stage by the transformer secondary.

→ In second stage, it is further amplified and appears across primary of second transformer (T_2) and to the load connected to the secondary.

Frequency Response =

Gain (dB)

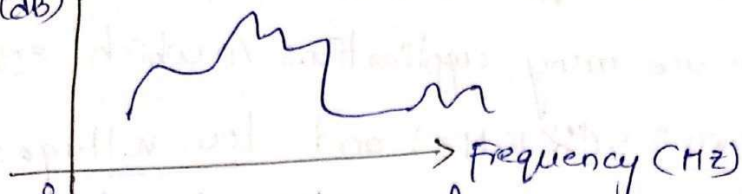

The above fig. shows the frequency response of transformer coupled amplifier.

→ It is clear that, frequency response is poor (i.e.) gain is not constant, gain is constant over only a small range of frequencies.

→ It is due to transformer losses such as leakage inductance and interwinding capacitance.

Advantages = (2M)

1) It provides an excellent impedance matching

due to transformer

2) It provides high voltage and power gains.

3) No signal loss in collector / base resistors.

Disadvantages = (2M)

1) It has poor frequency response.

2) The coupling transformers are bulky and expensive.

3) It ~~has~~ (provides) frequency distortions.

Applications = (2M)

1) Used for impedance matching.


2) Used in Radio & TV receivers, to amplify

RF (Radio Frequency 20kHz - 200kHz) signals

Direct Coupled Amplifiers

There are many applications in which extremely low frequencies ($\sim 10\text{Hz}$) and low voltages (i.e. in order of nano / picovolts) are to be amplified with the help of direct coupled amplifier

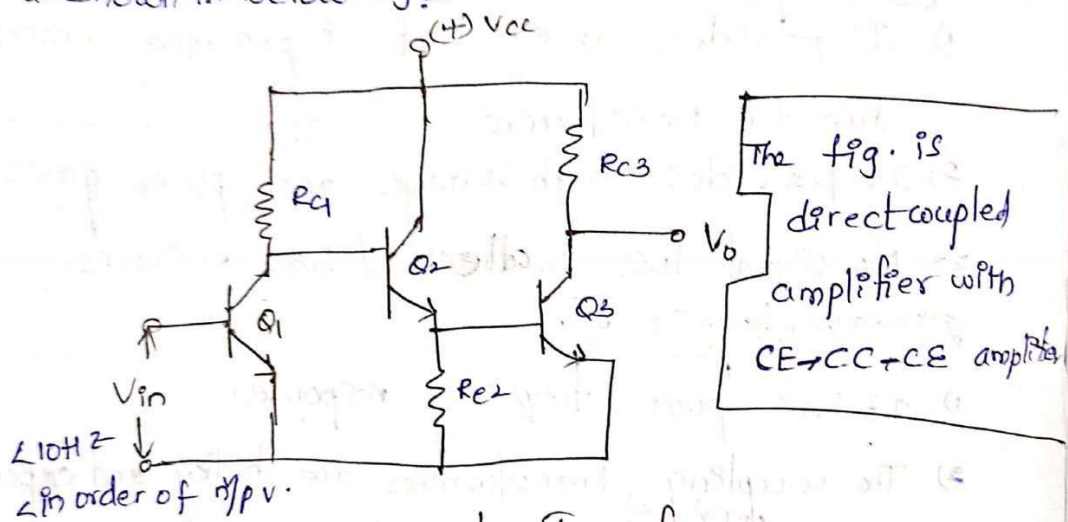→ Ex: The signals such as ECG [Electro cardiography] (or) photoelectric (or) thermoelectric (or) EEG, EMG signals are having small amplitudes and low frequency signals.
→ These can be amplified with direct coupled amplifier as shown in below fig:




operation is similar to Transformer.
Here weak signal is applied to i/p of Q_1 and it is (Frequency Response)

amplified and the o/p voltage is taken across R_{C1} .

→ The o/p voltage at R_{C1} is directly connected to base of Q_2 and it further amplifies and --so on.

→ The o/p voltage at R_{E2} is connected to base of Q_3 and further amplifies then the o/p voltage is taken across R_{C3} .

Frequency Response:

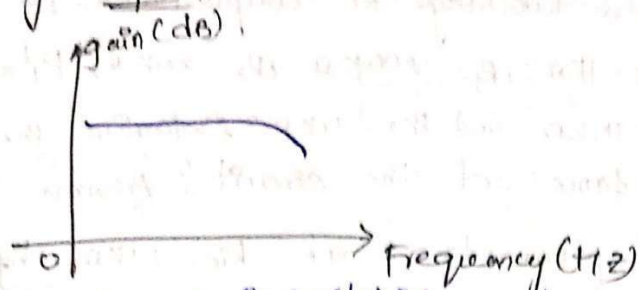

At low frequencies gain in (dB) is constant.

Advantages:

- 1) The circuit arrangement is simple because of minimum resistors.
- 2) The circuit cost is low because of absence of expensive coupling devices.

Disadvantages:

- 1) It cannot be used for amplification of high frequencies.

2) The operating point is shifting from one point to another, due to direct coupling.

Applications:


→ It can be used for low voltages and low frequencies.

→ It is mainly used in initial stages in multistage amplifiers.

Analysis of CE-CE Amplifier:

Note: In analysis of multistage amplifiers, first we should analyse last stage then go for preceding stages, because the o/p impedance of last stage will act as a load resistor for the preceding stage.

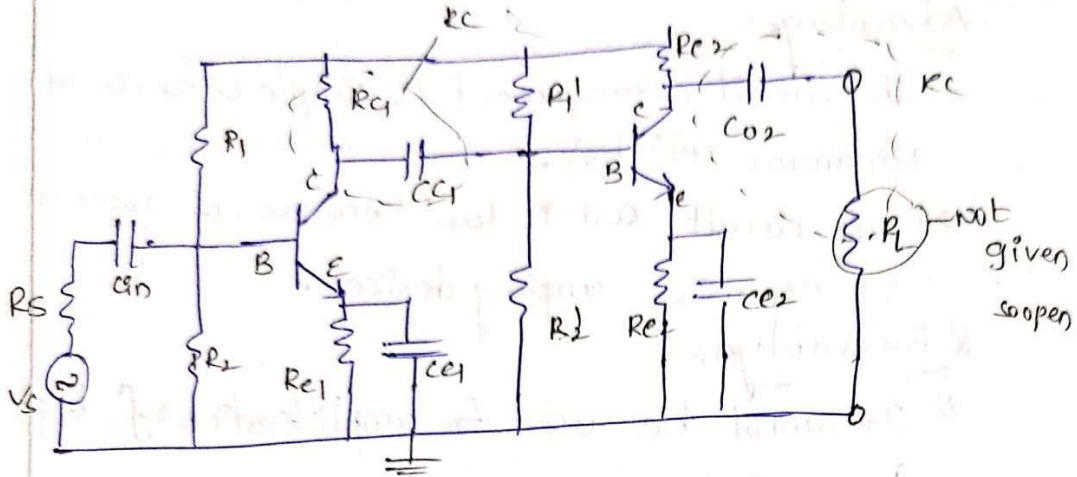Consider a two stage RC coupled CE-CE amplifier with $R_S = 1k\Omega$, $R_1 = 200k\Omega$, $R_2 = 20k\Omega$, $R_1' = 47k\Omega$, $R_2' = 4.7k\Omega$, $R_{C1} = 15k\Omega$ and $R_{C2} = 4k\Omega$. Determine the gain's & impedances of the circuit? Assume the typical values of h-parameters are $h_{ie} = 1.1k\Omega$, $h_{fe} = 50$, $h_{oe} = 2.4 \times 10^{-4}$, $h_{oe} = 25 \mu A/V$?



$$\therefore R_L = R_{C2}$$


$$R_L = 4k\Omega$$

$$h_{oe} R_L = 25 \times 10^{-6} \times 4 \times 10^3$$

$$= 100 \times 10^{-3}$$

$$= 0.1 < 0.1$$

Hence use simplified Model,

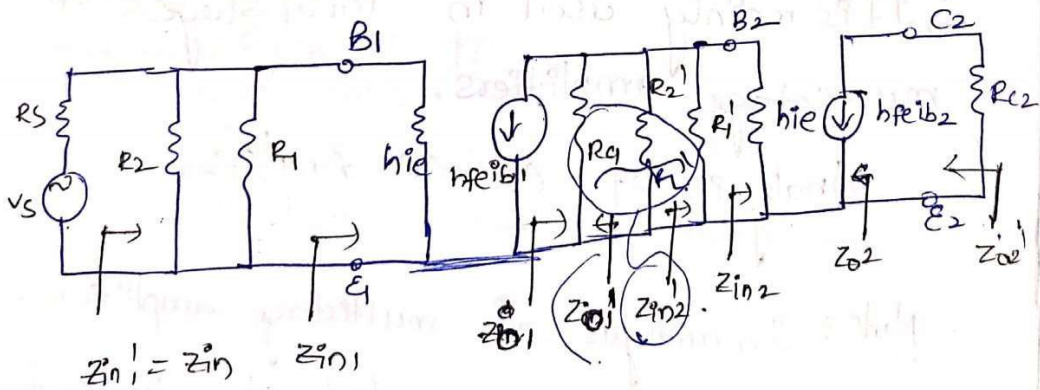

Analysis of stage-2 [CE]

$$A_{i2} = h_{fe} = 50$$

$$Z_{in2} = h_{ie} = 1.1k\Omega$$

$$3) \underline{z_{in2}'} = R_1' \parallel R_2' \parallel z_{in2} = 47k\Omega \parallel 4.7k\Omega \parallel 1.1k\Omega$$

$$= \boxed{874.78 \Omega}$$

$$4) \underline{A_{v2}} = \frac{A_{I2} \times R_L}{z_{in2}} = \frac{50 \times 4k\Omega}{1.1k\Omega} = \boxed{181.81}$$

$$5) \underline{z_{o2}} = \alpha$$

$$6) \underline{z_{o2}'} = z_{o2} \parallel R_{C2} = 4k\Omega \parallel \alpha = \boxed{4k\Omega}$$

Analysis of stage-1 [cc]:

$$\text{Load resistance } R_{L1} = z_{in2}' \parallel R_{C2}$$

$$= 874.78 \parallel 15k\Omega$$

$$\underline{R_{L1}} = \underline{826 \Omega}$$

$$\text{condition is } h_{oe} \times R_{L1} = 826 \times 25 \times 10^{-6}$$

$$= 0.02 < 0.1$$

Hence use simplified Model.

$$A_{I1} = h_{fe} = 50$$

$$z_{in1} = h_{ie} = 1.1k\Omega$$

$$z_{in1}' = R_1 \parallel R_2 \parallel z_{in1} = 200k\Omega \parallel 20k\Omega \parallel 1.1k\Omega$$

$$= 1037 \Omega$$

$$\underline{A_{v1}} = \frac{A_{I1} \times R_{L1}}{z_{in1}} = \frac{50 \times 826}{1.1k\Omega} = \underline{37.54}$$

$$z_{o1} = \alpha$$

$$\underline{z_{o1}'} = R_{L1} \parallel z_{o1} = 826 \parallel \alpha = \underline{826 \Omega}$$

$$A_{vS} = R_S$$

For overall Amplifier:

$$A_I = A_{I1} \times A_{I2} = 50 \times 50 = 2500$$

$$A_v = A_{v1} = 181.81 \times 37.54 = 6825$$

$$z_{in} = z_{in1}' = 1037 \Omega$$

$$z_o = z_{o2}' = 4k\Omega$$

with $R_s \neq \infty$ $A_{vs} = \frac{Z_{in}^1}{Z_{in}^1 + R_s} \times A_v$

Increase if particularly they ask do this

$A_{vs} = \frac{1037}{1037 + 1k\Omega} = 0.509 \times 6825$


$A_{vs} = 3474.48$

with $R_s \neq \infty$ $A_{is} = \frac{R_s}{Z_{in}^1 + R_s} \times A_I$


$A_{is} = \frac{I_L}{I_s} = \frac{I_L}{I_{c2}} \times \frac{I_{c2}}{I_{b2}} \times \frac{I_{c1}}{I_{b1}} \times \frac{I_{b1}}{I_s}$

$A_{is} = 1227.29$

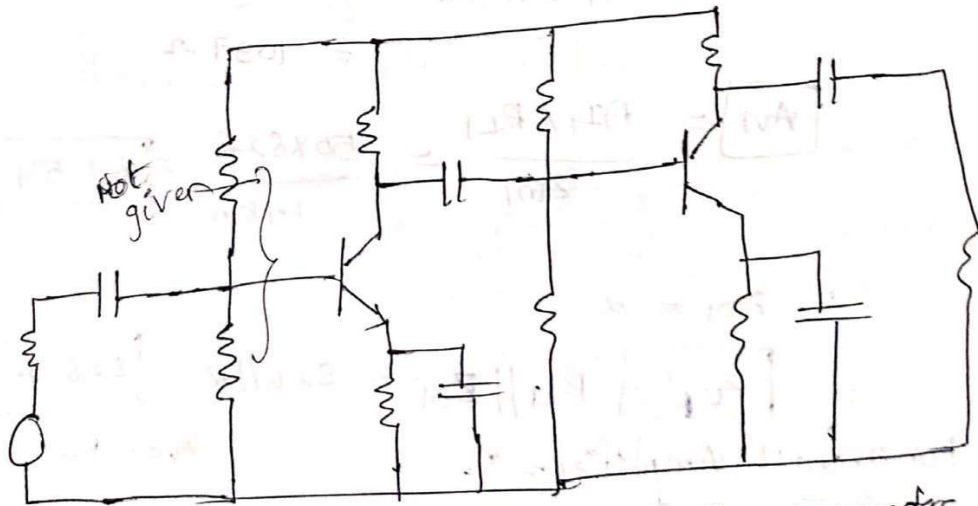Consider a two stage RC coupled CE-CC amplifier with $R_s = 1k\Omega$, $R_{c1} = 10k\Omega$, $R_{e2} = 5k\Omega$. Assume transistor parameters are its typical values. Calculate voltage gain, current gain, Z_{in} and Z_o of the amplifier?



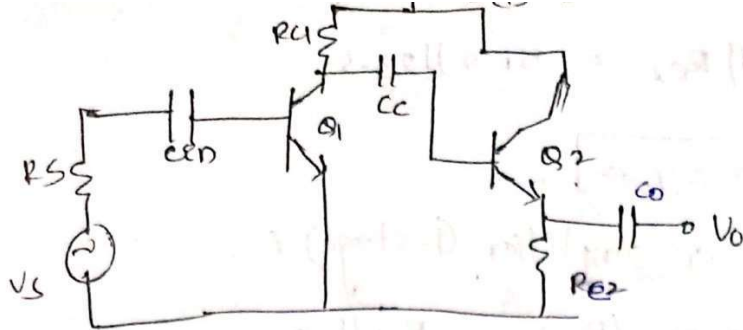This is RC coupled circuit but given parameters are only R resistors.



h-parameters


$$h_{ie} = 1.1 \text{ k}\Omega, \quad h_{fe} = 50, \quad h_{oe} = 2.4 \times 10^{-4} \text{ A/V}, \quad h_{oe} = 25 \times 10^{-6} \text{ A/V}$$

$$h_{ic} = 1.2 \text{ k}\Omega, \quad h_{fc} = -51, \quad h_{oc} = 1, \quad h_{oc} = 25 \times 10^{-6} \text{ A/V}$$

condition is $h_{oe} R_{E2} = 2.5 \times 10^{-6} \times 5 \times 10^3$

$$= 0.125 > 0.1$$

Hence use exact model

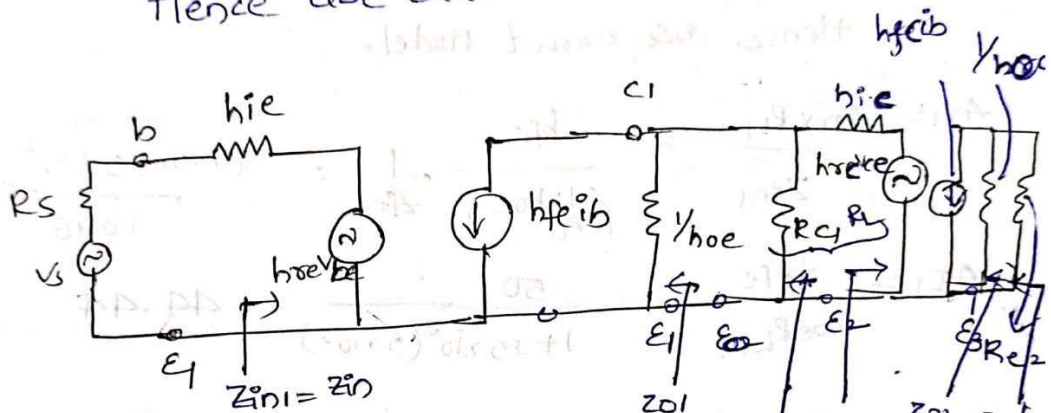

Analysis of CC Amplifier (2-stage) = Z_{o1}

$$A_{I2} = \frac{h_{fc}}{h_{oc} R_{L2} + 1} = \frac{45.33}{1 + 25 \times 10^{-6} \times 5 \times 10^3} = \frac{51}{1 + 0.125} = 45.33$$

$$Z_{in2} = h_{ie} - \frac{h_{fc} h_{re}}{h_{oc} + 1/R_{L2}} \Rightarrow 1.2 \text{ k} - \frac{(51)(1)}{25 \times 10^{-6} + \frac{1}{5 \times 10^3}}$$

$$Z_{in2} = 227.866 \text{ k}\Omega$$

$$A_{V2} = \frac{A_{I2} \times R_{L2}}{Z_{in2}} = \frac{45.33 \times 5 \times 10^3}{227.866 \times 10^3} = 0.994$$

$$Z_{o2} = \frac{h_{ic}}{h_{ic} h_{oc} - h_{fc} h_{oc}} = \frac{1.2 \text{ k}\Omega}{1.2 \times 10^3 \times 25 \times 10^{-6} - (-51)(1)}$$

$$Z_{o2} = 23.515 \Omega$$

$$Z_{o2}' = Z_{o2} \parallel R_{e2} = 5k\Omega \parallel 23.5$$

$$Z_{o2}' = 23.39\Omega$$

Analysis of ce amplifier (1-stage) :-

$$\begin{aligned} \text{load resistance } (R_{L1}) &= R_{c1} \parallel Z_{in2} \\ &= 10k\Omega \parallel 227.88k\Omega \\ &= 9.57k\Omega \end{aligned}$$

$$\begin{aligned} \text{The condition is } h_{oe} R_{L1} &= 9.57k\Omega \times 25 \times 10^{-6} \\ &= 0.237 \approx 0.1 \end{aligned}$$

Hence use exact Model.

$$A_{V1} = \frac{A_{V1} \times R_{L1}}{Z_{in1}} = \frac{-h_{fe}}{\left(\frac{1+h_{oe}}{R_L}\right) Z_{in}} = \frac{44.44 \times 5 \times 10^3}{1046} = 212.42$$

$$A_{V1} = \frac{h_{fe}}{h_{oe} R_{L1} + 1} = \frac{50}{1 + 25 \times 10^{-6} (5 \times 10^3)} = 44.44$$

$$Z_{in1} = \frac{h_{ie} - \frac{h_{fe} h_{re}}{h_{oe} + 1/R_L}}{1} = \frac{1.1k\Omega - \frac{(50 \times 2.4 \times 10^{-4})}{25 \times 10^{-6} + 1/5 \times 10^3}}{1} = 1046\Omega$$

$$Z_{o1} = \frac{h_{ie}}{h_{ie} h_{oe} - h_{fe} h_{re}} = \frac{1.1 \times 10^3}{(1.1) \times 10^{-3} (25 \times 10^{-6}) - 50 \times 2.4 \times 10^{-4}} = 70.967k\Omega$$

$$Z_{o1}' = Z_{o1} \parallel R_{c1} = \frac{70.967 \times 10^3 \times 10 \times 10^3}{70.967 \times 10^3 + 10 \times 10^3} = 8764 = 8.764k\Omega$$

For Overall Amplifier :-

cc-CE Amplifier [Cascode Amplifier]

$$A_V = A_{V1} \times A_{V2} = 2014.46$$

$$A_V = A_{V1} \times A_{V2} = 211.145$$


$$Z_{in} = Z_{in1}' =$$

$$Z_o = Z_{o2}' = 23.39\Omega$$

CE-CB Amplifier [Cascode Amplifier]

The cascode amplifier consists of CE amplifiers in series with CB amplifiers as shown in below fig:

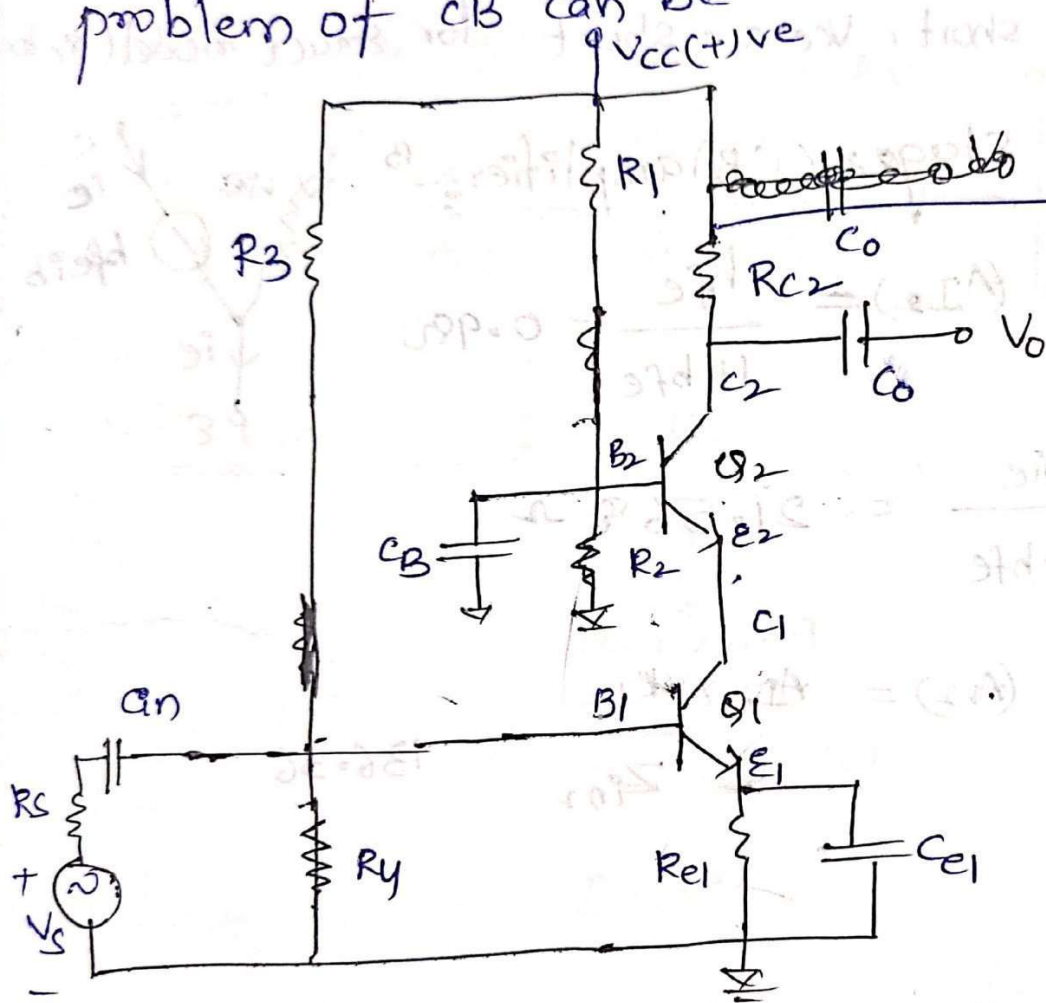→ With this connection the low i/p impedance problem of CB can be eliminated.



R_{C1} is not short because one terminal is not short & only one terminal is short (V_{CC})

CE is in series with CB configuration.


Consider a Cascode (CE-CB) amplifier with circuit parameters $R_s = 1k\Omega$, $R_3 = 200k\Omega$, $R_4 = 20k\Omega$ and $R_L = 3k\Omega$

(or) $R_L = 3k\Omega$ and the transistor parameters for both transistors are $h_{ie} = 1k\Omega$, $h_{fe} = 50$. Calculate i_i , Z_{in} , A_I , A_v and Z_o of the amplifier.

From given data, we can use

Simplified model using as shown in below figure

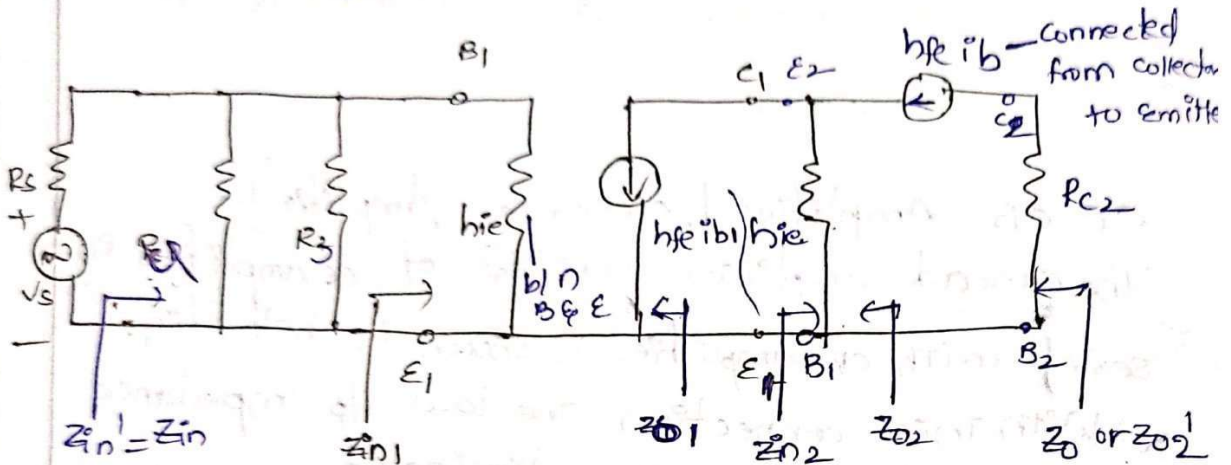
There is no need with R_1, R_2, R_4 because they are ground & R_4 is short due to CE.



capacitors are short, V_{cc} are short for exact model (in before fig)

Analysis of stage 2 (CB) amplifier
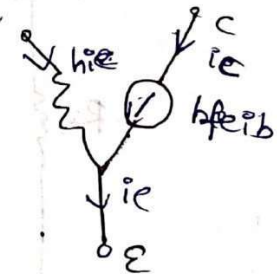
$$\text{Current gain } (A_{I2}) = \frac{h_{fe}}{1+h_{fe}} = 0.980$$



$$Z_{in2} = \frac{h_{ie}}{1+h_{fe}} = 21.568 \Omega$$

$$\text{Voltage gain } (A_{v2}) = A_{I2} \times \frac{R_L}{Z_{in2}} = 136.36$$

$$Z_{o2} = \alpha$$

$$Z_{o2}^{\uparrow} = R_{C2} \parallel Z_{o2} = 3k\Omega \parallel \alpha = 3k\Omega$$

$$Z_o = Z_{o2}^{\uparrow} = 3k\Omega$$

Analysis of CE (1st stage)

$$A_{I1} = h_{fe} = 50$$

$$z_{in} = h_{ie} = 1.1 k\Omega = z_{in1}$$

$$A_v = -h_{fe} \times \frac{R_{L1}}{z_{in1}} = 0.98 \quad (\text{or}) \quad A_{I1} \times \frac{R_{L1}}{z_{in1}} = z_r$$

$$A_{v1} = 0.98 = R_3 || R_4 || z_{in1}'$$

$$z_{o1}' = z_{o1} || R_L \quad z_{in1}' = 200 k\Omega || 10 k\Omega || 1.1 k\Omega$$

$$z_{o1} = 21.56 \Omega \quad = 986.10 \Omega$$

$$z_{o1}' = 21.56 \Omega$$

Overall Amplifier

$$A_I = A_{I1} \times A_{I2} = 50 \times 0.98 = 49$$

$$A_v = A_{v1} \times A_{v2} = 136.36 \times 0.98 = 133.6$$

$$z_{in} = z_{in1}' = 986.10 \Omega$$

$$z_o = z_{o2}' = 3 k\Omega$$

with $R_S = A_{VS} = \frac{z_{in1}' \times A_v}{z_{in1}' + R_S}$

$$A_{VS} = 66.34$$

MOSCASCOPE
C

with $R_S = A_{VS} = \frac{R_S}{z_{in1}' + R_S} \times A_I$

$$= \frac{1 \times 10^3 \times 49}{986.10 + 1 \times 10^3}$$

$$= 24.67$$

0.001354

(cc-cc) [Darlington Amplifier] (cc) Two


Stage Emitter follower :-

We know that out of three configurations (CE, CB, CC) common collector (CC) or emitter follower ~~base~~ circuit has high i/p impedance [i.e. typically (200-500)kΩ]

→ A single stage emitter follower circuit can give input impedance upto (500kΩ). However the i/p impedance by considering biasing resistors R_s considerably decreases, because $Z_{in}' = R_1 || R_2 || Z_{in}$

→ To keep the i/p impedance of the circuit $\ll R_2$ has high, by direct coupling of (cc-cc) amplifier.

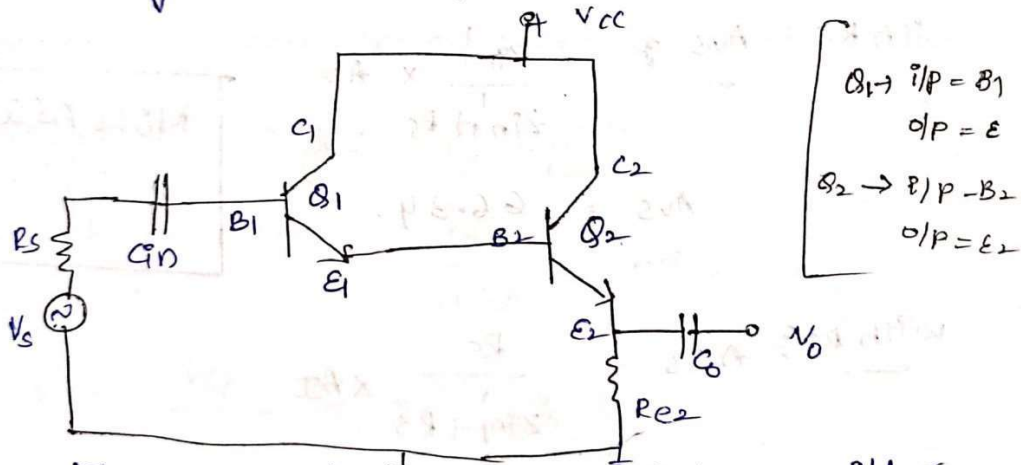
→ The below fig. shows the direct coupling of a two stage cc-cc amplifier.



$Q_1 \rightarrow i/p = B_1$
 $o/p = E$
 $Q_2 \rightarrow i/p = B_2$
 $o/p = E_2$

→ This cascade connection of two emitter followers is also called Darlington amplifier

ⓐM Darlington pair Diagram :-

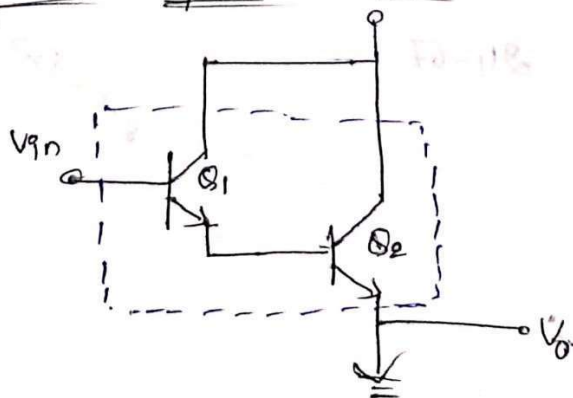

In single stage due to resistors i/p impedance dec. so we use Darlington

Analysis of stage-2 (CC) Amplifier:-

Assume that load resistor (of ^{second} stage-2) ($R_{L2} = R_{e2}$) will satisfy the condition $h_{oe} R_{L2} \approx h_{oe} R_{e2} < 0.1$
Hence use simplified Model.

$$\begin{aligned} A_{V2} &= 1 + h_{fe} \\ Z_{in2} &= h_{ie} + (1 + h_{fe}) R_{e2} \\ A_{V2} &= \frac{A_{V2} R_{L2}}{Z_{in2}} \\ Z_{o2} &= \frac{R_S + h_{ie}}{1 + h_{fe}} \end{aligned}$$

cc in terms of ce
(or) $A_{V2} = 1 - \frac{h_{ie}}{Z_{in2}}$

$$R_S = Z_{in2}$$

Analysis of stage-1 (CC) amplifier:-

The load resistance $R_{L1} = Z_{in2}$ (in range of $100 \text{ k}\Omega$)
Generally Z_{in2} is high, usually it does not meet the requirement ($h_{oe} R_{L1} < 0.1$).

Hence we have to use exact method for analysis of stage-1.

→ In some cases, if we know only ce parameters then cc analysis can be done with following assumption.

$$\begin{aligned} h_{fc} &= -(1 + h_{fe}) & h_{oc} &= h_{oe} \\ h_{ic} &= h_{ie} & h_{rc} &= 1 \end{aligned}$$

$$\begin{aligned} h_{ie} &= 1.1 \text{ k}\Omega & h_{ic} &= 1.2 \text{ k}\Omega \\ h_{fe} &= 50 \\ h_{oe} &= 20 \mu\text{A/V} \\ h_{oc} &= 25 \mu\text{A/V} \\ h_{fc} &= -51 \\ h_{rc} &= 1, h_{oc} = 25 \mu\text{A/V} \end{aligned}$$

From above assumptions;

$$A_{V1} = \frac{-h_{fc}}{1 + h_{oc} R_{L1}} = \frac{+(1 + h_{fe})}{1 + h_{oe} R_{L1}}$$

$$Z_{in1} = \frac{h_{ic} - h_{rc} h_{fc}}{h_{oc} + 1/R_{L1}} = \frac{h_{ie} + (1 + h_{fe})}{h_{oe} + 1/R_{L1}}$$

$$A_{V1} = \frac{h_{fc}}{h_{oc} + 1/R_{L1}} \cdot \frac{1}{Z_{in1}} = \frac{-(1 + h_{fe})}{h_{oe} + 1/R_{L1}} \cdot \frac{1}{Z_{in1}} \quad (\text{or}) \quad \frac{A_{V1} R_{L1}}{Z_{in1}}$$

$$Z_{o1} = \frac{h_{ic}}{h_{rc} h_{oc} - h_{fe} h_{rc}} = \frac{h_{ie}}{h_{ie} h_{oe} + (1 + h_{fe})}$$


Consider Darlington (cc-cc) amplifier with

$$R_S = 3\text{ k}\Omega \text{ \& } R_{E2} = R_L = 3\text{ k}\Omega$$

The typical h-parameters for both transistors


$$h_{ie} = 1.1\text{ k}\Omega; \quad h_{fe} = 50; \quad h_{oe} = 25 \times 10^{-6} \text{ S/V}$$

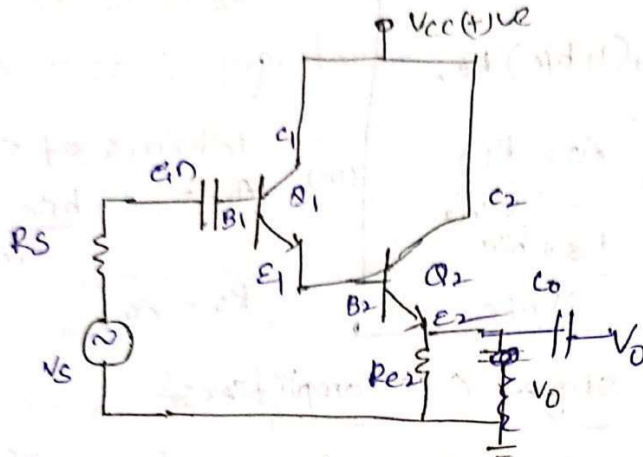calculate A_I , Z_{in} , A_v , Z_o of amplifier.



$$h_{oe} R_L = 25 \times 10^{-6} \times 3 \times 10^3 = 75 \times 10^{-3} = 0.075 \ll 1$$

Hence use simplified Model.

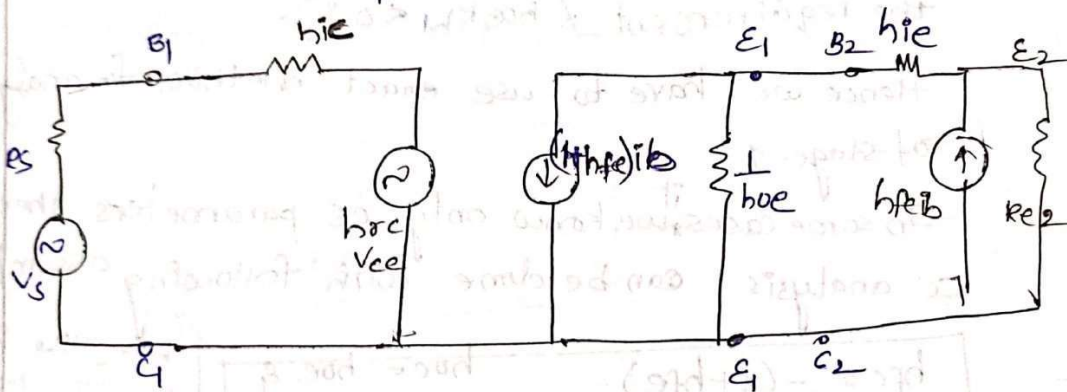

Analysis of stage 2 (cc) amplifier =

$$A_{I2} = 1 + h_{fe} \quad R_L = R_{E2} = 3\text{ k}\Omega$$

$$A_{I2} = 1 + 50 = 51$$

$$Z_{in2} = h_{ie} + (1 + h_{fe}) R_L$$

$$Z_{in2} = 1.1\text{ k}\Omega + (1 + 50) 3 \times 10^3 = 154.1\text{ k}\Omega$$

$$A_{v2} = A_{I2} \times \frac{R_{L2}}{Z_{in2}} = \frac{1 - h_{fe}}{Z_{in2}} = 0.99$$

$$Z_{o2} = \frac{R_s + h_{ie}}{1 + h_{fe}} = \frac{154 \cdot 10^3 + 1 \cdot 10^3}{51} = 3.043 \text{ k}\Omega$$

$$Z_o = Z_{o2}' = Z_{o2} \parallel R_L = 3.043 \times 10^3 \times 3 \text{ k}\Omega = 1.500 \text{ k}\Omega$$

Analysis of stage-1 (CC) Amplifier.

Using Exact Model. $R_{L1} = Z_{in2} = 154 \text{ ohm}$

$$A_{I1} = \frac{+h_{fc} (\otimes)}{(h_{oc} R_L + 1)}$$

using ac parameters

$$= \frac{+(1 + h_{fe})}{1 + h_{oe} R_{L1}}$$

$$= -10.51$$

$$Z_{in} = Z_{in1} = h_{ie} - \frac{h_{re} h_{fc}}{h_{oc} + 1/R_L}$$

$$= h_{ie} + \frac{(1 + h_{fe})}{h_{oe} + 1/R_{L1}}$$

$$= 1.62 \text{ M}\Omega$$

$$A_{V1} = \frac{h_{fc}}{h_{oc} + 1/R_L} \cdot \frac{1}{Z_{in1}}$$

$$= A_{I1} \frac{R_{L1}}{Z_{in1}} = 0.99$$

$$Z_{o1} = \frac{h_{ie}}{h_{ic} h_{oe} - h_{fc} h_{re}}$$

$$= \frac{h_{ie}}{h_{ie} h_{oe} + (1 + h_{fe})}$$

$$Z_{o1} = 21.55 \Omega$$

Overall Amplifier:

$$A_I = A_{I1} \times A_{I2} = 536$$



$$A_V = A_{V1} \times A_{V2} = 0.98$$

$$Z_{in} = Z_{in1} = 1.62 \text{ M}\Omega$$

$$Z_{o2}' = Z_o = 1.5 \text{ k}\Omega$$

Miller's Theorem:

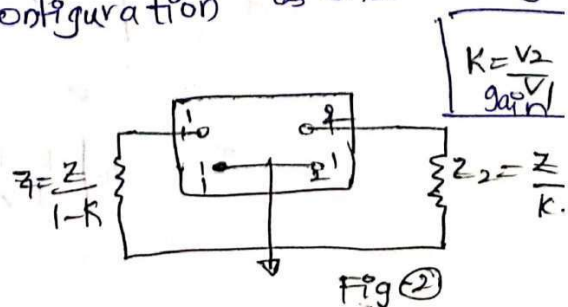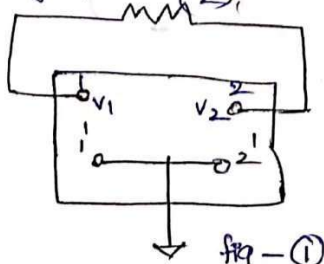In general the miller's theorem is used for converting any circuit having configuration in fig 1; into another configuration as shown in fig 2




Statement: It states that "an impedance z is connected b/w two nodes then it can be replaced by two separate impedances (z_1 & z_2) where z_1 is connected b/w node and ground and z_2 is connected b/w node & ground. and its magnitudes/values depends on i/p & o/p voltages. Ratio and given by $z_1 = \frac{z}{1-k}$ and $z_2 = \frac{z \cdot k}{k-1}$ where $k = \frac{V_o}{V_i}$

proof: From above statement the effect of impedance z on the i/p side is the ratio of i/p voltage to current (i) which flows from i/p to o/p side.

$$z_1 = \frac{V_i}{I}$$
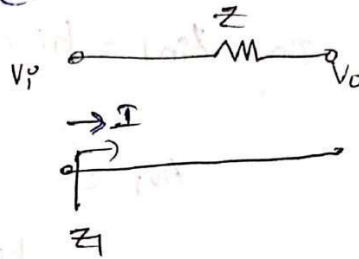
$$\text{where } I = \frac{V_i - V_o}{z}$$



$$I = \frac{V_i \left[1 - \frac{V_o}{V_i} \right]}{z}$$

$$I = \frac{V_i [1 - k]}{z}$$


$$\text{Then } z_1 = \frac{V_i}{\frac{V_i [1 - k]}{z}} = \frac{z}{1 - k}$$

$$\boxed{z_1 = \frac{z}{1 - k}} \text{ where 'k' is gain of amplifier } \left(\frac{V_o}{V_i} \right) \text{ or } \left(\frac{V_o}{V_i} \right)$$

Case ii: From Miller's theorem, the effect of impedance (z) on o/p circuit is the ratio of o/p voltage (V_o) to the current (I) flows from o/p to i/p.

$$z_2 = \frac{V_o}{I}$$
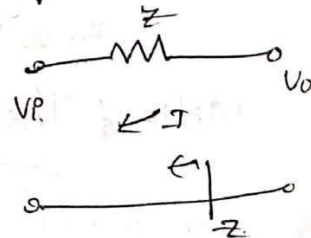
$$\text{where } I = \frac{V_o - V_i}{z}$$




$$I = \frac{V_o \left[1 - \frac{V_i}{V_o} \right]}{z} = \frac{V_o \left[1 - \frac{1}{k} \right]}{z}$$

$$I = \frac{V_o \left[\frac{k-1}{k} \right]}{z}$$


$$Z_2 = \frac{V_o}{V_o \left[\frac{k-1}{k} \right]}$$

$$Z_2 = \left[\frac{k r_e}{k-1} \right]$$

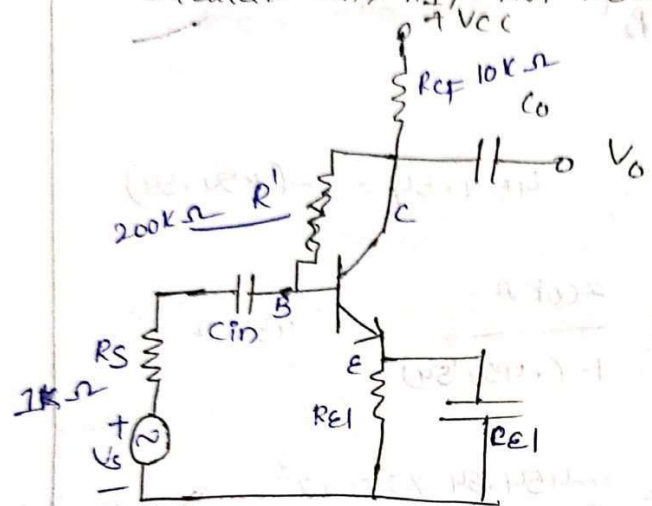
Consider a CE amplifier with collector-to Base biasing with $R_s = 1k\Omega$, $R_c = 10k\Omega$, and $R' = 200k\Omega$. The transistor parameters are $h_{re} = 1.1k\Omega$ & $h_{fe} = 50$. Calculate Z_{in} , A_i , A_v , Z_o , A_{vS} , A_{iS} ?



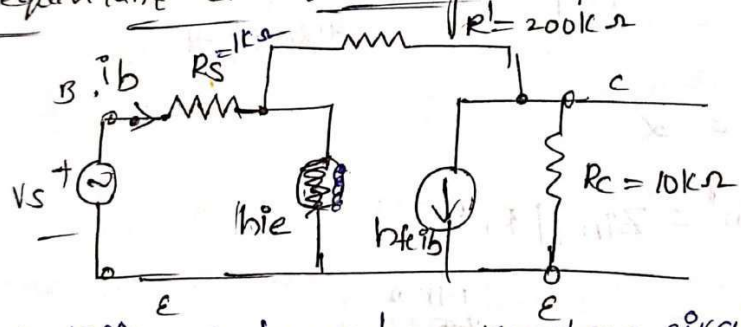The equivalent circuit using simplified model:



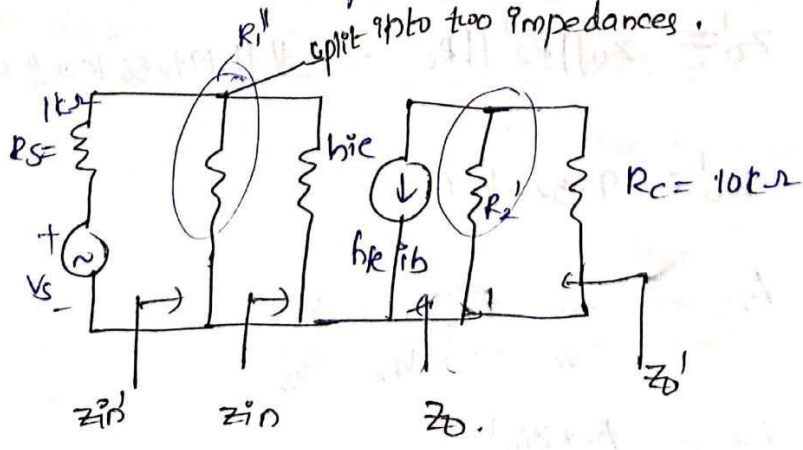It is difficult to analyse the above circuit, so by using millers theorem the above equivalent circuit can be simplified model as shown below:



Input Impedance:

$$R_1' = \frac{R_1}{1-k} ; R_2' = \frac{kR_1}{k-1}$$

$$Z_{in} = h_{ie} = 1.1k\Omega$$

$$k = A_v = \frac{V_o}{V_i} = 200$$

$$A_v = h_{fe} = 200$$

$$Z_o = \alpha$$

$$Z_o' = Z_o \parallel R_c \parallel R_1'$$

$$k = A_v = \frac{A_v R_L}{Z_{in}} = 454.54 = -(454.54)$$

$$R_1' = \frac{R_1}{1-k} = \frac{200k\Omega}{1-(-454.54)} = 439\Omega$$

$$R_2' = \frac{kR_1}{k-1} = \frac{-454.54 \times 200 \times 10^3}{-454.54 - 1} = 199.58k\Omega$$

$$Z_o = \alpha$$

$$Z_{in}' = Z_{in} \parallel R_1'$$

$$= \frac{439 \times 1.1k\Omega}{439 + 1.1k\Omega} = 313.76\Omega$$

$$Z_o' = Z_o \parallel R_2' \parallel R_c = \alpha \parallel 199.58k\Omega \parallel 10k\Omega$$

$$Z_o' = 9.522k\Omega$$


$$A_{VS} = \frac{V_o}{V_s} = \frac{V_{ce}}{V_{be}} \frac{V_{be}}{V_s}$$

$$A_{VS} = \frac{A_v \times Z_{in}'}{Z_{in}' + R_s} = -108.55$$

$$A_{VS} = \frac{I_o}{I_s} = \frac{\beta}{\beta_c} \times \frac{I_c}{I_b} \times \frac{V_{fb}}{I_s} \Rightarrow \frac{-\beta_c'}{\beta_c' + \beta_c} \times \frac{\beta \times R_s}{R_s + Z_{in}}$$

$$= \frac{\beta \times R_s}{R_s + Z_{in}} \rightarrow \text{using this}$$

$$A_{VS} = -36.242$$

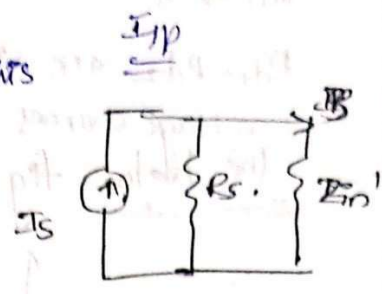

$$A_{VS} = -199.56 \text{ k}\Omega$$

$$\frac{199.56 \text{ k}\Omega + 10 \text{ k}\Omega}{1 \text{ k}\Omega + 313.76 \Omega} \times 50 \times \frac{1 \text{ k}\Omega}{1 \text{ k}\Omega + 313.76 \Omega}$$

Differential Amplifiers :- / pairs

→ This amplifier is most widely used building blocks in analog electronic circuit design.

Ex:- The i/p stage of every OP-amp (operation amplifier) is differential amplifier, and also BJT differential amplifier is the basis of very high speed logic circuit family.

→ This amplifiers are used most widely because of these two reasons


1) The performance of the differential amplifier depends critically on the matching b/n two sides of the circuit.

2) These amplifiers utilise ^{more components} than single ended circuits.

→ Differential Amplifier. ∴ It is defined as its output is the difference b/n the two i/p signals.

$$\text{i.e.) } V_o = V_{in2} - V_{in1} \quad (\text{OR}) \quad V_o = V_{in1} - V_{in2}$$

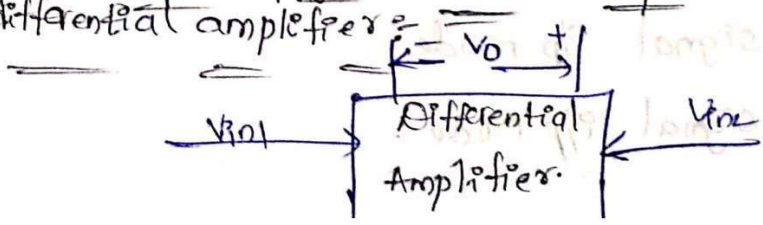The below fig shows the simple block diagram of differential amplifier :-



$$V_o = A_d (V_{in2} - V_{in1}) = A_d V_{id} \text{ where } V_{id} = V_{in2} - V_{in1}$$

Where $A_d \rightarrow$ differential gain


MOS Differential Amplifier

Q_1, Q_2 are two mosfets (1)

R_{D1}, R_{D2} are resistors (2), current source (1)

2 voltage sources for biasing.

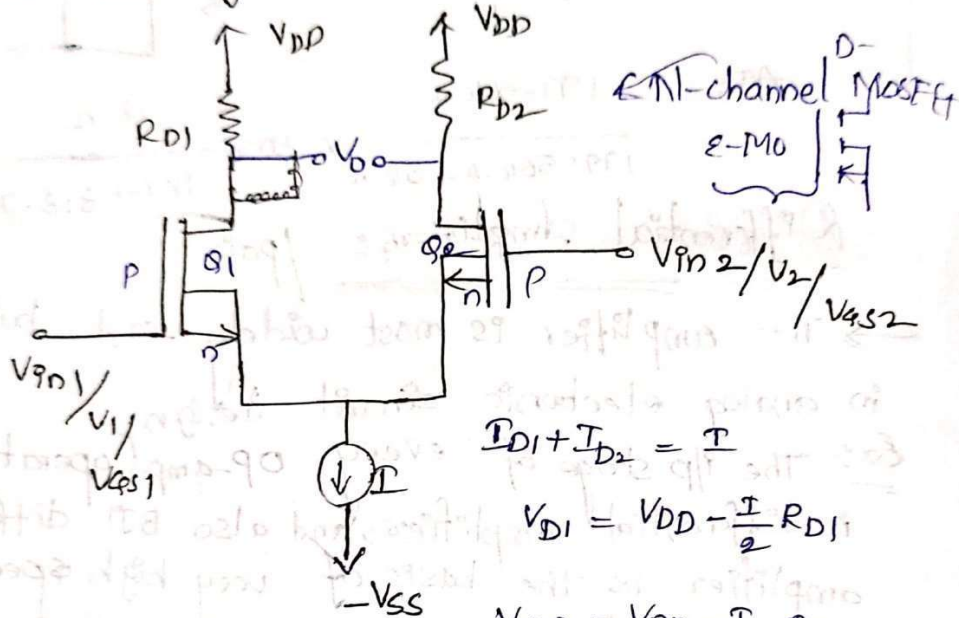The below fig shows the MOSFET differential amplifier



$$I_{D1} + I_{D2} = I$$

$$V_{D1} = V_{DD} - \frac{I}{2} R_{D1}$$

$$V_{D2} = V_{DD} - \frac{I}{2} R_{D2}$$

$$V_o = V_{D2} - V_{D1} \text{ or } V_{D1} - V_{D2} \text{ (or) } V_{GS1} - V_{GS2}$$

The above circuit work as an differential amplifier with the following conditions are satisfied.

\rightarrow Both transistors (Q_1 & Q_2) are identical [Both-n or Both-p]
ratio of Q_1 transistor.

$$\rightarrow I_{D1} + I_{D2} = I$$

$$V_{D1} = V_{DD} - \frac{I}{2} R_{D1} \text{ \& } V_{D2} = V_{DD} - \frac{I}{2} R_{D2}$$

$$V_o = V_{D2} - V_{D1} \text{ (or) } V_{D1} - V_{D2} \text{ (or) } V_{GS1} - V_{GS2}$$


$$V_{GD} = V_{GS1} - V_{GS2} \text{ (or) } V_1 - V_2, \text{ or } (V_2 - V_1) \text{ (or) } V_{GS2} - V_{GS1}$$

Differential amplifier operates on 4 modes :-

- ① Common P/p mode
- ② differential i/p Mode
- ③ Large signal P/p mode
- ④ Small signal P/p Mode.

Differential Amplifier as a Common mode is applied b/w two i/p signals = CM Mode.

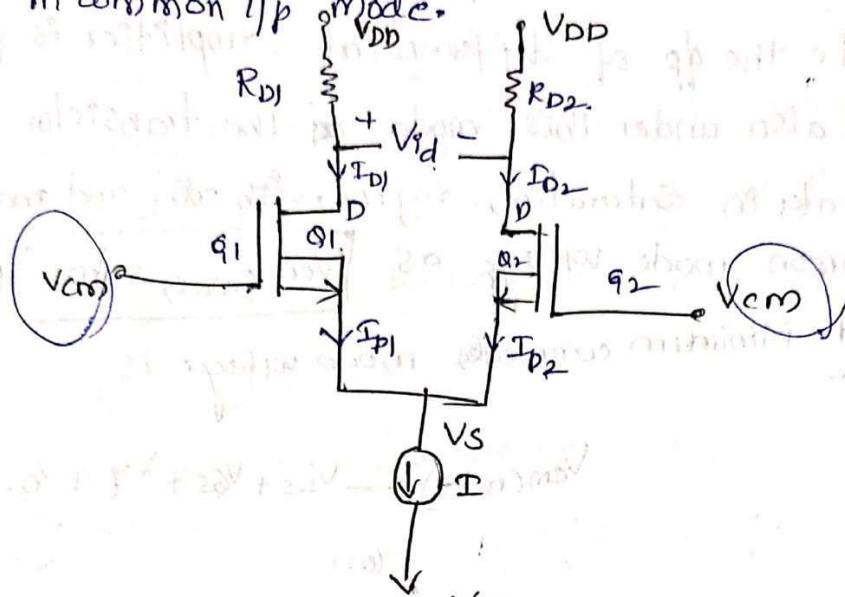If same voltage (V_{in1} & V_{in2}) applied at Q_1 & Q_2 transistors then the differential amplifier operates in common i/p mode.



From above circuit, if same i/p voltage is applied to Q_1 & Q_2 then both transistors will turn on and they operate in saturation region.

such that $I_{D1} = I_{D2} = \frac{I}{2} \Rightarrow \boxed{I_{D1} + I_{D2} = I}$.

→ We know that drain current of a MOSFET is

$$I_D = \frac{k_n'}{2} \left[\frac{W}{L} \right] (V_{GS} - V_t)^2$$

width
length of oxide layer.
gm

$$V_{GS} = V_{OV}$$

For Q_1 & Q_2

$$I_{D1} = \frac{I}{2} = \frac{k_n'}{2} \left(\frac{W}{L} \right) (V_{OV})^2$$

where V_{OV} - Over drive voltage.

$$(V_{OV})^2 = \frac{\frac{I}{2}}{\left(\frac{k_n' W}{L} \right)} \Rightarrow V_{OV} = \sqrt{\frac{\frac{I}{2}}{k_n' (W/L)}}$$

From drain side:

$$V_{D1} = V_{DD} - \frac{I}{2} R_{D1}$$

$$V_{D2} = V_{DD} - \frac{I}{2} R_{D2}$$

From common mode i/p signal:

$$V_{D1} = V_{D2}$$

$\Rightarrow V_D = 0$ voltage

Thus the difference b/w two drains must be zero (ideal)
 \Rightarrow Under this mode of operation called as common mode the op of differential amplifier is zero.

and also under this mode of the transistors operates in saturation region, with min and maximum common mode voltage as $V_{cm(max)} = V_D + V_{T}$

and Minimum common mode voltage is

$$V_{cm(min)} = -V_{SS} + V_{GS} + V_{T} + V_{OV}$$


(or)

$$V_{cm(min)} = -V_{SS} + V_{GS} + V_{GS}$$

voltage across current source.

MOS Differential Amplifier with differential i/p

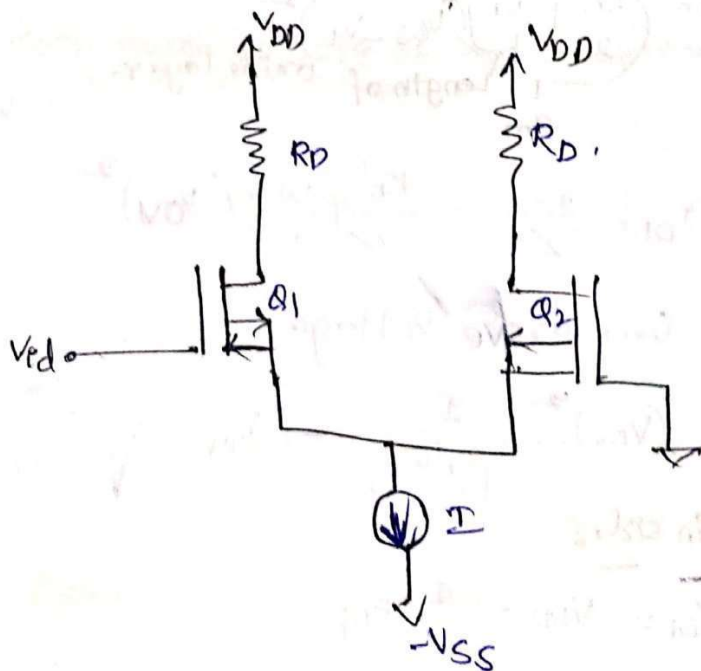\Rightarrow If we apply differential i/p voltage by grounding the gate of Q_2 and apply a i/p signal V_{id} to Q_1



We can see that $V_{ID} = V_{GS1} - V_{GS2}$ (or) $V_{G1} - V_{G2}$

→ If V_{ID} is positive, V_{GS1} will be greater than V_{GS2} and hence I_{D1} will be greater than I_{D2} and $V_{D2} - V_{D1}$ will be (+)ve. Hence Q_1 is ON and Q_2 will OFF.

Similarly,
→ If V_{ID} is negative, V_{GS2} will be greater than V_{GS1} and hence I_{D2} will be greater than I_{D1} . and $V_{D1} - V_{D2}$ will be (-)ve such that Q_2 is ON and Q_1 is OFF

→ The output voltages are given by

$$\begin{aligned} V_{D1} &= V_{DD} - I_{D1} R_D \\ V_{D2} &= V_{DD} - I_{D2} R_D \end{aligned}$$

→ From above equations the o/p voltage does not become zero. ($V_{D2} - V_{D1} \neq 0$ (or) $V_{D1} - V_{D2} \neq 0$)
→ Under this conditions, the current through (Q_1) is

$$I_{D1} = \frac{1}{2} K_n' \left(\frac{W}{L} \right) (V_{GS1} - V_T)^2$$

Hence $I_{D1} = I = \frac{K_n' \left(\frac{W}{L} \right) (V_{GS1} - V_T)^2}{2}$

$$I_{D1} = I = \frac{K_n' \left(\frac{W}{L} \right) (V_{OV})^2}{2}$$

$$I_{D1} = I = \frac{K_n' \left(\frac{W}{L} \right) \left(\sqrt{\frac{I}{K_n' \left(\frac{W}{L} \right)}} \right)^2}{2}$$

$$V_{OV} = \sqrt{\frac{2I}{K_n' \left(\frac{W}{L} \right)}}$$

V_{OV} - keep as it is.

$$V_{OV} = V_{GS1} - V_T$$

$$V_{GS1} = V_T + V_{OV}$$

$$V_{GS1} = V_T + \sqrt{2} V_{OV}$$

$$V_{id(max)} = V_{GS} - V_T$$

$$= \sqrt{2} V_{OV} + V_T - V_T$$

$$V_{id(max)} = \sqrt{2} V_{OV}$$


$$V_{id(min)} = -\sqrt{2} V_{OV}$$

Range of differential i/p voltage is $-\sqrt{2} V_{OV} \leq V_{id} \leq \sqrt{2} V_{OV}$

$$-\sqrt{2} V_{OV} \leq V_{pd} \leq \sqrt{2} V_{OV}$$

For the MOS differential pair (amplifier) with a common mode voltage (V_{cm}) is applied. if $V_{DD} = V_{SS} = 1.5V$; $K_n' (\frac{W}{L}) = 4 \text{ mA/V}^2$; $V_T = 0.5V$
 $I = 0.4 \text{ mA}$, $R_D = 2.5 \text{ k}\Omega$ and assume current source (I) is required minimum voltage of $0.4V$ to operate properly. Find

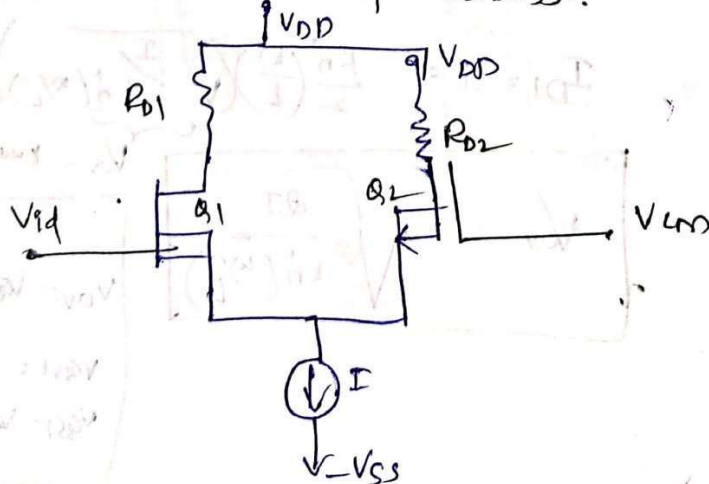- V_{OV}
- V_{GS} for each transistor
- For $V_{cm} = 0$, Find V_S , I_{D1} , I_{D2} , V_{D1} & V_{D2}
- Repeat c) if, $V_{cm} = 1V$
- Repeat c) if, $V_{cm} = -0.5V$
- Find $V_{cm(max)}$ & $V_{cm(min)}$?



$$I_{D1} = I_{D2} = \frac{I}{2}$$

we know that

$$I_{D1} = \frac{k_n'}{2} \left(\frac{W}{L}\right) (V_{GS1} - V_T)^2$$

$$\frac{I}{2} = \frac{k_n'}{2} \left(\frac{W}{L}\right) (V_{OV})^2 \quad \left[\frac{I}{k_n' \left(\frac{W}{L}\right)} \right. \\ \left. \text{(or)} \right]$$

$$0.4 \times 10^{-3} = 4 \times 10^{-3} (V_{OV})^2$$

$$V_{OV} = 0.316V$$

b) V_{GS} for each transistor

$$V_{OV} = V_{GS1} - V_T$$

$$V_{GS} = V_{OV} + V_T$$

$$V_{GS} = 0.316 + 0.5 = 0.816V$$

c) When $V_{cm} = 0$,

$$V_{S1} = V_{DD} - \frac{I_{D1}}{2} (R_D)$$

$$= 1.5 - \frac{0.4 \times 10^{-3}}{2} (2.5 \times 10^3)$$

$$V_{D1} = 1V$$

$$V_{D2} = 1V$$

$$I_{D1} = \frac{I}{2} = 0.4 \text{ mAmp} = 0.2 \text{ mA}$$

$$I_{D2} = \frac{I}{2} = 0.4 \text{ mAmp} = 0.2 \text{ mA}$$

$$V_S = \frac{V_{cm}}{2} - V_{GS}$$

$$V_S = -0.816V$$

$$V_S = -0.816V$$

$$V_{cm} = 1 \text{ then } V_S = V_{cm} - V_{GS}$$

$$V_S = 1 - 0.816 = 0.184 \text{ V}$$

$$V_{cm} = -0.2 \text{ V then}$$

$$V_S = -0.2 - 0.816 = -1.016 \text{ V}$$

$$V_{cm(max)} = V_D + V_t$$

$$= 1 + 0.5 \text{ V}$$

$$V_{cm(max)} = 1.5 \text{ V}$$

$$V_{cm(min)} = -V_{SS} + V_{GS} + V_{GS}$$

$$= -1.5 \text{ V} + 0.4 \text{ V} + 0.816$$

$$V_{cm(min)} = -0.284 \text{ V}$$

For the MOS differential amplifier operated in differential mode, mentioned as above problem.

- calculate a) the value of V_{ID} , that causes Q_1 to conduct the entire current (I) and corresponding values of V_{D1} & V_{D2} ?
- b) Find the value of V_{ID} that causes Q_2 to conduct entire current (I) and corresponding V_{D1} & V_{D2} ?
- c) Find the Range of differential V_{diff} voltage & o/p Voltage?

$$d) V_{ov} = \sqrt{\frac{2I}{k_n'(W/L)}} = \sqrt{\frac{2(60 \mu \text{A}) \times 10^{-3}}{4 \times 10^{-3}}}$$

$$V_{ov} = 0.44 \text{ V}$$

$$V_{ID} = \sqrt{2} V_{ov} = \sqrt{2} \times 0.44 = 0.622$$

$$a) V_{D1} = V_{DD} - I_{D1} R_D$$

$$= 1.5V - 0.4 \times 10^{-3} (2.5 \times 10^3)$$

$$\boxed{V_{D1} = 0.5V}$$

$$V_{D2} = V_{DD} - I_{D2} R_D$$

$$= 1.5V - 0 (2.5 \times 10^{-3})$$

$$\boxed{V_{D2} = 1.5V}$$

Q_2 is off so
 $I_{D2} = 0$

b) For second case: $V_{D1} = -\sqrt{2} V_{OV} = -\sqrt{2} (0.44) = -0.622V$

$$V_{D1} = V_{DD} - I_{D1} R_D$$

$$= 1.5 - 0 (R_D)$$

$$\boxed{V_{D1} = 1.5V}$$

$$V_{D2} = V_{DD} - I_{D2} (R_D)$$

$$= 1.5 - (0.4) \times 10^{-3} (2.5 \times 10^3)$$

$$\boxed{V_{D2} = 0.5V}$$

Q_1 is off and
 Q_2 is on
so $I_{D1} = 0$

c) In 1st case

$$V_{D2} - V_{D1} = 1.5V - 0.5V$$

$$\boxed{V_{D2} - V_{D1} = 1V}$$

In 2nd case


$$V_{D2} - V_{D1} = 0.5V - 1.5V$$

$$= -1V$$

$$\therefore \boxed{V_{od} = -1V \text{ to } +1V} \text{ o/p}$$

$$\boxed{V_{id} = -0.622 \text{ to } +0.622V} \text{ i/p}$$

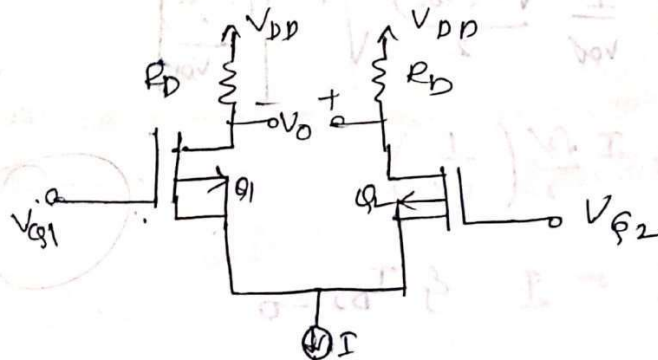MOS Differential Amplifier in Large Signal Mode:



The figure shows the differential amplifier in large signal mode.

Under this conditions current is different (i.e.)

$$I_{D1} = \frac{k_n'}{2} \left(\frac{W}{L}\right) (V_{GS1} - V_T)^2$$

The transistors drive different currents and they are given by I_{D1} & I_{D2} .

$$\sqrt{I_{D1}} = \sqrt{\frac{k_n'}{2} \left(\frac{W}{L}\right) (V_{GS1} - V_T)^2} \rightarrow (1)$$

$$\sqrt{I_{D2}} = \sqrt{\frac{k_n'}{2} \left(\frac{W}{L}\right) (V_{GS2} - V_T)^2} \rightarrow (2)$$

$$\sqrt{I_{D1}} - \sqrt{I_{D2}} = \sqrt{\frac{k_n'}{2} \left(\frac{W}{L}\right) (V_{GS1} - V_{GS2})^2}$$

$$\sqrt{I_{D1}} - \sqrt{I_{D2}} = \sqrt{\frac{k_n'}{2} \left(\frac{W}{L}\right) (V_{id})^2} \rightarrow (3)$$

we know that

$$I_{D1} + I_{D2} = I \rightarrow (4)$$

By solving eqn (3) & (4)

$$I_{D1} = \frac{I}{2} + \left(\frac{I}{V_{OV}}\right) \left(\frac{V_{id}}{2}\right) \sqrt{1 - \left(\frac{V_{id}}{2V_{OV}}\right)^2} \rightarrow (5) > \frac{I}{2}$$

$$I_{D2} = \frac{I}{2} - \left(\frac{I}{V_{OV}}\right) \left(\frac{V_{id}}{2}\right) \sqrt{1 - \left(\frac{V_{id}}{2V_{OV}}\right)^2} \rightarrow (6) < \frac{I}{2}$$

suppose if $V_{id} = \sqrt{2} V_{OV}$

$$I_{D1} = \frac{I}{2} + \frac{I}{V_{OV}} \frac{\sqrt{2}(V_{OV})}{2} \sqrt{1 - \left[\frac{\sqrt{2}V_{OV}}{2}\right]^2} \quad \begin{matrix} 1 - \frac{2}{4} \\ \sqrt{1 - \frac{1}{2}} = \frac{1}{\sqrt{2}} \end{matrix}$$

$$I_{D1} = \frac{I}{2} + I \frac{\sqrt{2}}{2} \left(\frac{1}{\sqrt{2}}\right)$$


$$I_{D1} = 2 \frac{I}{2} = I \quad \& \quad I_{D2} = 0$$

If $V_{pd} = -\sqrt{2}V_{ov}$

$I_{D1} = 0$ & $I_{D2} = I$

The range of differential voltage is
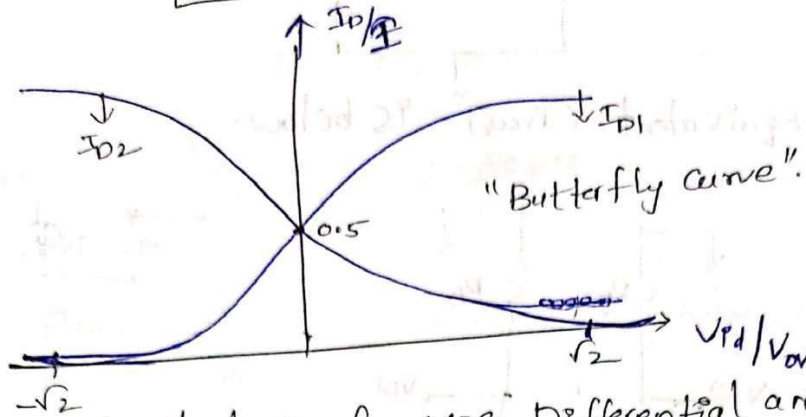
$$-\sqrt{2}V_{ov} \leq V_{pd} \leq \sqrt{2}V_{ov}$$



Small signal analysis of MOS Differential amplifier:


Here we can apply an i/p voltage to the gates of

Q_1 & Q_2 of a magnitude of $V_{cm} \pm \frac{V_{pd}}{2}$ by

considering $V_{G1} = V_{cm} + \frac{V_{pd}}{2}$


$V_{G2} = V_{cm} - \frac{V_{pd}}{2}$

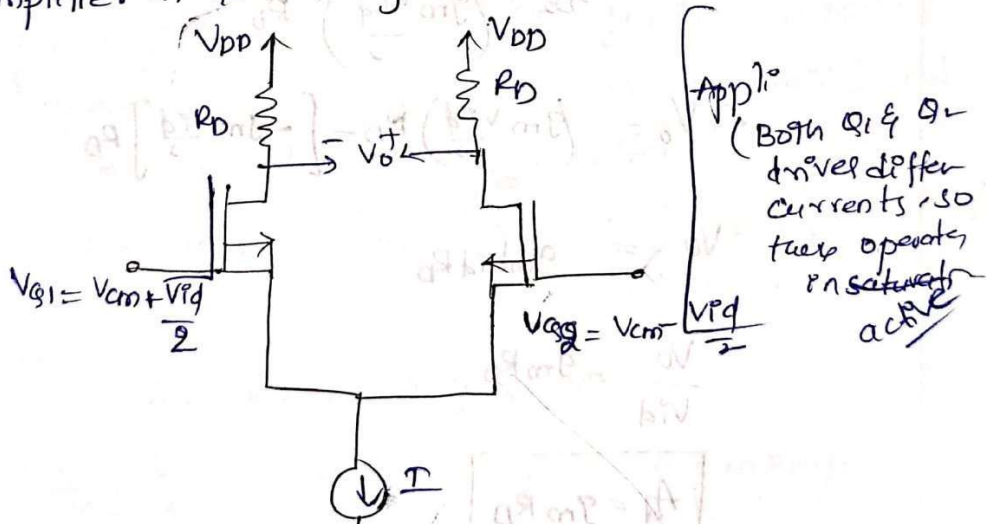The below figure shows the MOS differential amplifier in small signal.




From above circuit, the transistor Q_1 & Q_2 operates in linear (active) region by drawing (drives) an equal currents I_{D1} & I_{D2} .
 → here the MOS transistors operates in active region.

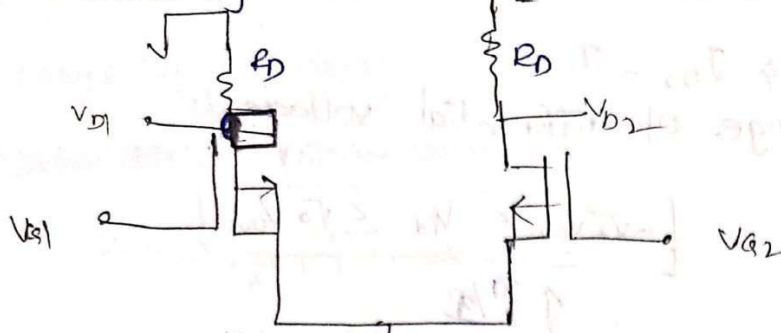The below fig. shows the AC equivalent circuit



Capacitor, current/voltage source are shorted

T-Equivalent Circuit is below.

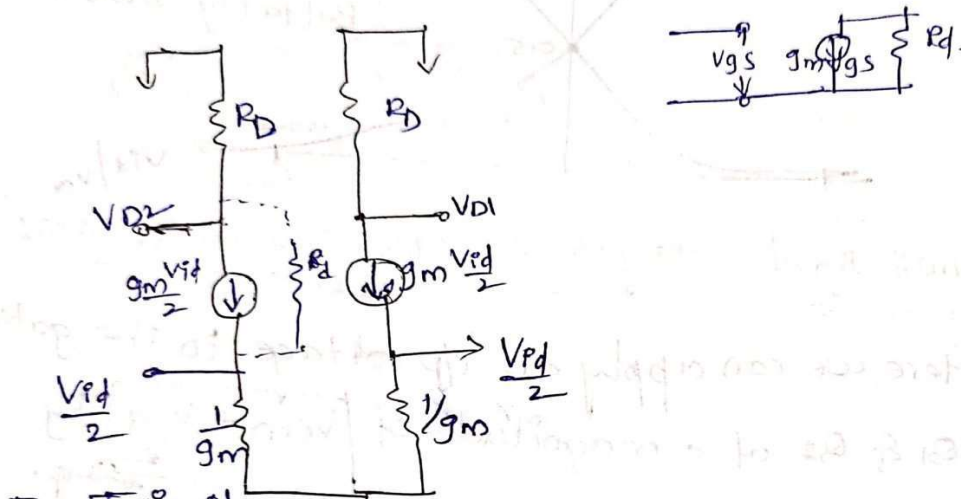

From T-circuit:

The drain voltages are given by

$$V_{D1} = \left(g_m \frac{V_{id}}{2} \right) R_D$$

$$V_{D2} = \left(g_m \frac{V_{id}}{2} \right) R_D$$

$$\therefore V_o = \left(g_m \frac{V_{id}}{2} \right) R_D - \left[-g_m \frac{V_{id}}{2} \right] R_D$$

$$V_o = g_m V_{id} R_D$$

$$\frac{V_o}{V_{id}} = g_m R_D$$

$$A_d = g_m R_D$$

If \$r_d\$ is considered then

$$A_d = g_m (R_D \parallel r_d)$$

Transconductance $g_m = \frac{\partial I}{\partial V_{ov}}$

Consider a MOS differential amplifier is operated at a total current of 0.8 mA using MOSFET with $(\frac{W}{L})$ ratio is 100, $\mu_n C_{ox} = 0.2 \text{ mA/V}^2$, $V_A = 20 \text{ V}$ and $R_D = 5 \text{ k}\Omega$ calculate V_{ov} , g_m , r_d , A_d

$$V_{ov} = \sqrt{\frac{I}{k_n'(\frac{W}{L})}} = 0.2 \text{ V}$$

$$g_m = \frac{\partial I}{\partial V_{ov}} = 0.531 \times 10^{-3} = 0.531 \text{ mA/V}$$

$$r_d = \frac{2V_A}{I} = 50 \text{ k}\Omega$$

$$A_d = g_m(R_D || r_d) = 8 \times 10^{-3} [50 \text{ k}\Omega || 5 \text{ k}\Omega]$$

$$A_d = 36.36$$

A MOS differential amplifier operates in common mode at a biasing current I of 0.4 mA. If $\mu_n C_{ox} = 0.2 \text{ mA/V}^2$ (k_n') find the requirement length of $(\frac{W}{L})$ and resulting g_m if, the MOSFETs are operated at $V_{ov} = 0.2 \text{ V}$, 0.3 V and 0.4 V and also for each value of V_{ov} maximum V_{id} for which the term involves V_{id} is $\left[\frac{V_{id}/2}{V_{ov}}\right]^2$ is limited to 0.1.

Given:

$$V_{ov} = 0.2 \text{ V}, 0.3 \text{ V}, 0.4 \text{ V}$$

$$\therefore \frac{I}{2} = \frac{I}{2} = \frac{0.4 \times 10^{-3} \text{ Amp}}{2} = 0.2 \text{ mA}$$

$$I = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L}\right) (V_{ov})^2$$

$$\frac{W}{L} = \frac{2 \times 0.2 \text{ mA}}{\mu_n C_{ox} (V_{ov})^2} = 50$$

$$g_m = \frac{g_f}{V_{ov}} = \frac{2 \times 0.2 \times 10^{-3}}{0.2} = \boxed{2 \text{ mA/V}}$$

$$\left[\frac{V_{id}}{0.2} \right]^2 = 0.1$$

$$\frac{(V_{id})^2}{(0.2)^2} = 0.1 \times 0.1$$

$$(V_{id})^2 = 0.1 \times 0.16$$

$$V_{id} = \sqrt{0.1 \times 0.16}$$

$$\boxed{V_{id} = 0.126 \text{ V}}$$

when $V_{ov} = 0.3 \text{ V}$

$$I = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right) (V_{ov})^2$$

$$\left(\frac{W}{L} \right) = \frac{0.2 \times 10^{-3} \times 2}{0.2 \times 10^{-3} \times (0.3)^2} = \boxed{22.22 \text{ V/1V}}$$

$$g_m = \frac{g_f}{V_{ov}} = \frac{2 \times 0.2 \times 10^{-3}}{0.3} = \boxed{1.33 \text{ mA/V}}$$

$$\left[\frac{V_{id}}{0.3} \right]^2 = 0.1$$

$$\left(\frac{V_{id}}{0.3} \right)^2 = 0.1$$

$$(V_{id})^2 = 0.1 \times 0.36$$

$$\boxed{V_{id} = \sqrt{0.036} = 0.1897 \text{ V}}$$

when $V_{ov} = 0.4 \text{ V}$

$$\left(\frac{w}{L}\right) = \frac{0.2 \times 10^{-3} \times 2}{0.2 \times 10^{-3} \times (0.4)^2} = \boxed{12.5}$$

$$g_m = \frac{2I}{V_{ov}} = 1 \text{ mA/V}$$

$$\left(\frac{V_{id}}{2}\right)^2 = 0.1$$

$$(V_{id})^2 = 0.1 \times 0.64$$

$$V_{id} = \sqrt{0.1 \times 0.64}$$


$$V_{id} = 0.2529 \text{ V}$$

BJT Differential Amplifier:

⇒ It consists of two BJTs (Q_1 & Q_2) and their emitters are connected to each other.

⇒ It consists of 2 resistors, 2 voltage sources

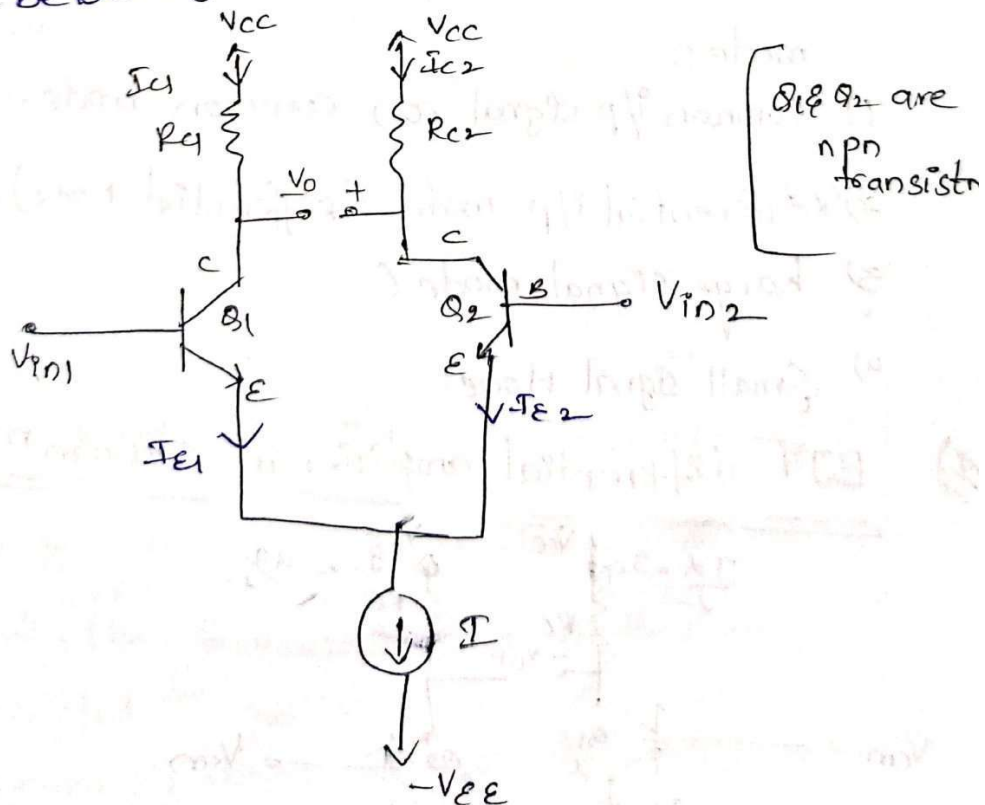⇒ The below fig. shows the BJT differential amplifier



⇒ Under BJT differential amplifier the collector & emitter current are different as a relation of

$$I_C = \alpha I_E$$

where $\alpha < 1$ (eg 0.98)

⇒ If the above circuit work as an differential amplifier it emits the following conditions.

1) Two transistor Q_1 & Q_2 are of same type ($\beta_1 = \beta_2$)

2) Total Current $I = I_{E1} + I_{E2}$

3) $R_{C1} = R_{C2} = R$

4) $V_{C1} = V_{CC} - I_{C1} R_{C1}$

$V_{C2} = V_{CC} - I_{C2} R_{C2}$

5) $V_O = V_{C1} - V_{C2}$ (or) $V_{C2} - V_{C1}$

6) $V_{fd} = V_{B1} - V_{B2}$ (or) $V_{B2} - V_{B1}$

Ideal conditions of E & for MOSFET also notations are di. (like V_{d1} , R_{d1} , I_{d1})

⇒ BJT differential amplifier can operate in 4 diff modes.


1) Common i/p signal (or) common mode.

2) Differential i/p mode. (Differential Mode).

3) Large signal mode

4) Small signal Mode.

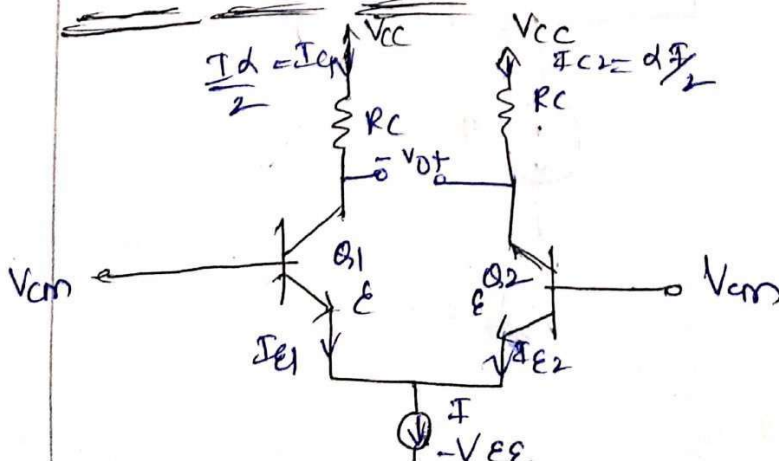1) BJT differential amplifier in common mode:



Here we can apply common i/p signal to both Q_1 & Q_2 transistor, then it is called BJT differential amplifier in common mode.

→ The ~~below~~ ^{above} fig shows the BJT differential amplifier of common mode

→ If same voltage is applied b/n Q_1 & Q_2 both transistors ^{will} drives into saturation (i.e. turn on) so they will draw equal currents.

$$I_{E1} = I_{E2} = \frac{I}{2}$$

$$I_{E1} + I_{E2} = I$$

$$I_{C1} = \frac{\alpha I}{2}$$

$$I_{C2} = \frac{\alpha I}{2}$$

∴ collector voltage same $V_{C1} = V_{C2} = V_{CC} - \left(\frac{\alpha I}{2}\right) R_C$

$$V_{C2} = V_{CC} - \left(\frac{\alpha I}{2}\right) R_C$$

$$o/p \text{ voltage } V_O = V_{C2} - V_{C1}$$

$$= V_{C2} - V_{C1}$$

$$V_O = 0V$$

→ From above eqn, o/p voltage of common mode differential amplifier is zero (V).

Max & min values of common mode voltage is given as

$$V_{cm(max)} = V_C + 0.4V$$


For Si 0.3V for Ge.
voltage across current source

$$V_{cm(min)} = -V_{EE} + V_{CS} + V_{BE}$$

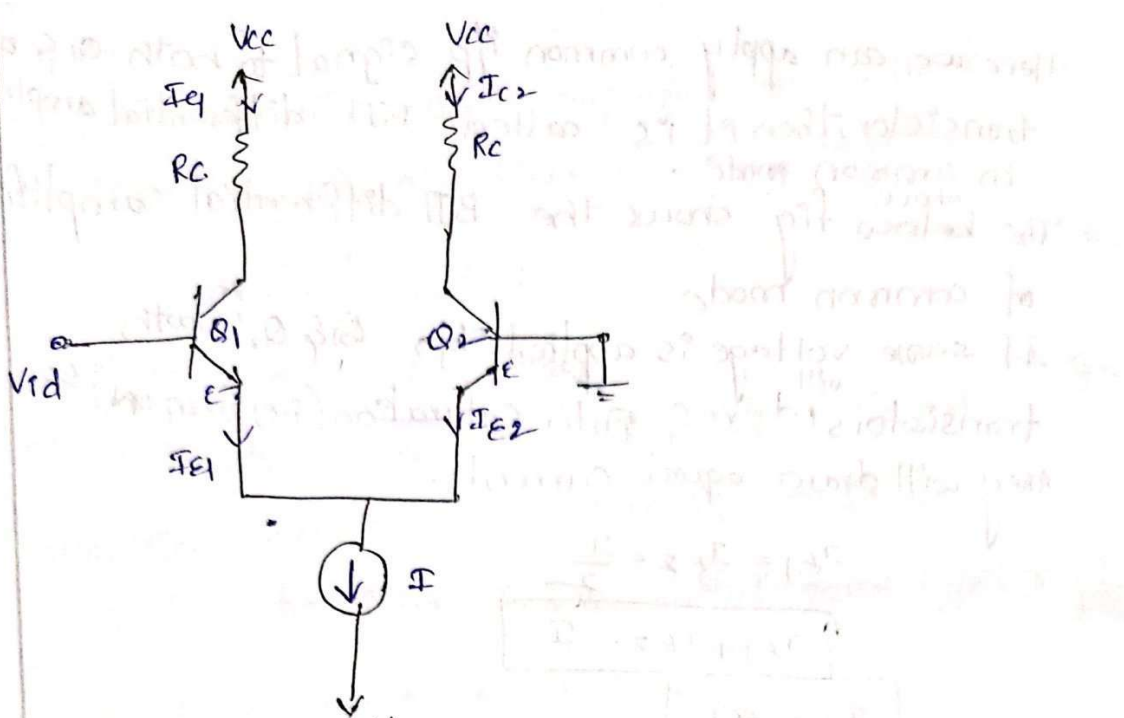2) BJT differential amplifier in differential mode :-

→ ~~if~~ Here we can apply a differential voltage to one of ^{base} the transistors and another base will be connected to ground.

→ The below fig. shows the BJT differential amplifier in differential mode.



Under this mode if V_{id} is (+)ve if $V_{B1} > V_{B2}$

then $V_{C1} > V_{C2}$

$$\therefore I_{C1} > I_{C2}$$

Hence Q_1 ON & Q_2 OFF [$I_{C1} = I$ & $I_{C2} = 0$]

$$\therefore V_{C1} = V_{CC} - \alpha I R_C \quad ; \quad V_{C2} = V_{CC} - 0$$

$$V_0 = V_{C1} - V_{C2} = V_{CC} - [V_{CC} - \alpha I R_C]$$

$$\boxed{V_0 = \alpha I R_C}$$

If $V_{B1} < V_{B2}$ (ie V_{id} is (-)ve) then

$$V_{C1} < V_{C2} \quad (<)$$

$$I_{C1} < I_{C2} \quad (<)$$

Hence Q_1 is OFF & Q_2 is ON. [$I_{C1} = 0$, $I_{C2} = I$]

$$V_{C1} = V_{CC} - 0$$

$$V_{C2} = V_{CC} - \alpha I R_C$$


$$\therefore \boxed{V_0 = -\alpha I R_C}$$

BJT differential Amplifier in large signal Modes

- We can apply different i/p voltages to bases of Q_1 and Q_2 transistors then it is called large signal mode
- here both transistors are in saturation, but they do not share equal currents. such that there is a change in current of ΔI .

$$I_{E1} = \frac{I}{2} + \Delta I$$

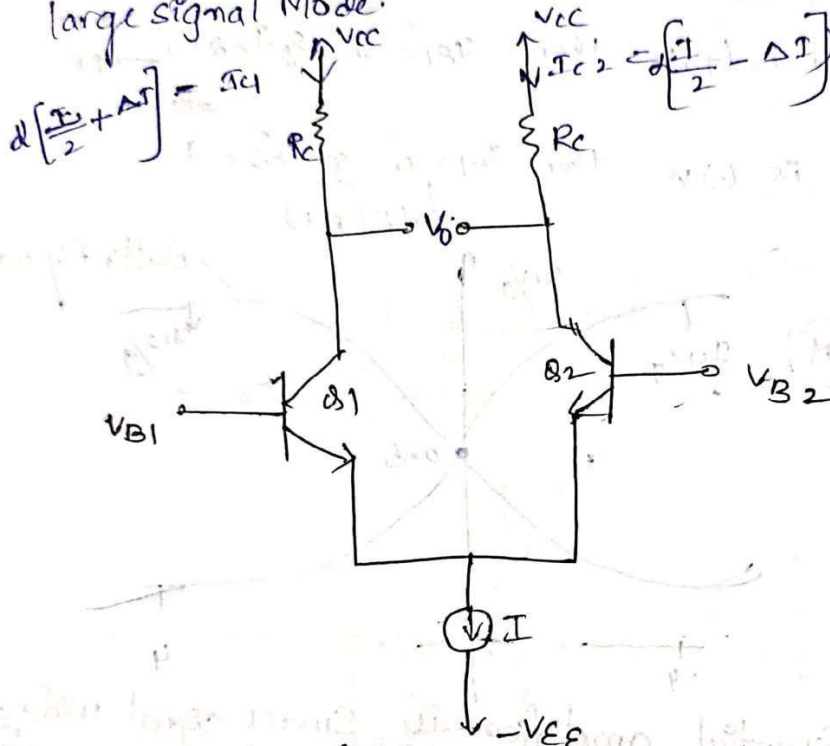The below figure shows the BJT diff. amplifier in large signal Mode.



Assumption
 $V_{B1} > V_{B2}$
 So
 $I_{E1} > I_{E2}$
 $I_{E1} = \frac{I}{2} + \Delta I$
 here transistor operates in non-linear region

The collector (o/p) voltages are given by

$$V_{O1} = V_{CC} - \left[\frac{I}{2} + \Delta I \right] R_C$$

$$V_{O2} = V_{CC} - \left[\frac{I}{2} - \Delta I \right] R_C$$

We know, when transistor operates in non-linear region

then the collector current $I_C = I_S e^{V_{BE}/V_T}$

$$I_{E1} = \frac{I_S}{\alpha} e^{V_{BE1}/V_T} \rightarrow (1)$$

$$I_{E2} = \frac{I_S}{\alpha} e^{V_{BE2}/V_T} \rightarrow (2)$$

$$\left. \begin{aligned} I_C &= \alpha I_E \\ I_E &= I_C / \alpha \end{aligned} \right\}$$

$$\frac{I_{E1}}{I_{E2}} = \frac{I_S}{2} \frac{[V_{BE1} - V_{BE2}]}{V_T} \rightarrow (3)$$

$$I_{E1} + I_{E2} = I \rightarrow (4)$$

By solving (3) & (4)

$$I_{E1} = \frac{I}{1 + e^{-V_{id}/V_T}} \rightarrow (5)$$


V_{id} is (+)ve
 $I_{E1} = 0$
 $I_{E2} = +I$

$$I_{E2} = \frac{I}{1 + e^{V_{id}/V_T}} \rightarrow (6) \quad [V_{id} = V_{BE1} - V_{BE2}]$$

From (5) & (6)

If V_{id} is (+)ve then $I_{E1} = I$ & $I_{E2} = 0$ - cutoff

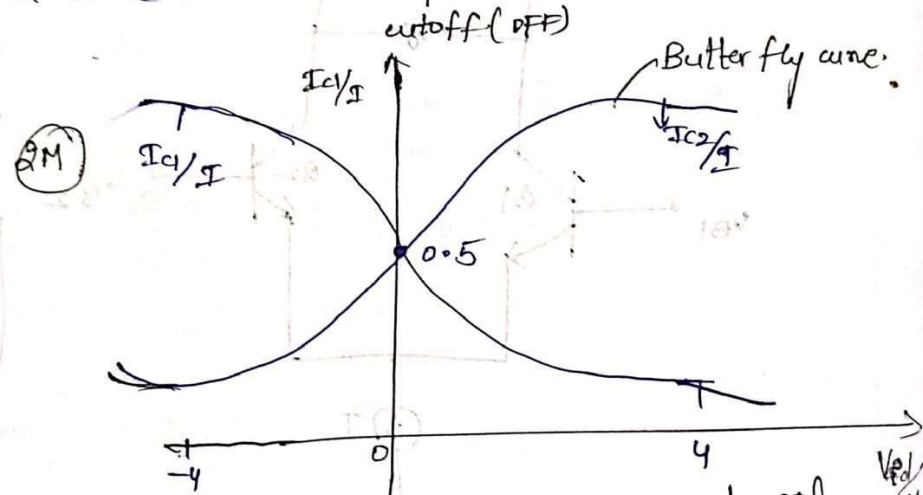If V_{id} is (-)ve then $I_{E1} = 0$ & $I_{E2} = I$ - cutoff




BJT differential amplifier in small signal mode (Analysis)

Here we can apply input voltages for Q_1 & Q_2 is

$$V_{B1} \& V_{B2} = V_{cm} \pm \frac{V_{id}}{2}$$

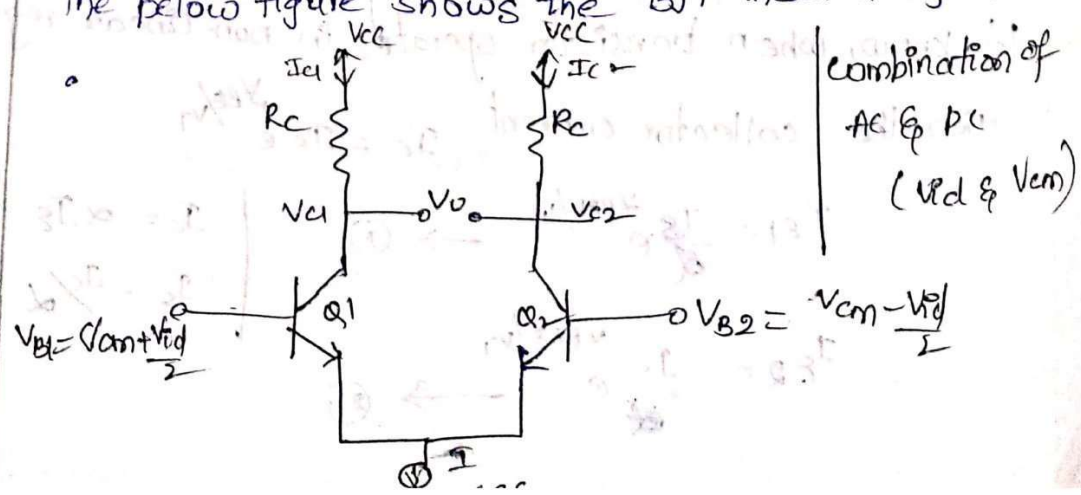The below figure shows the BJT in small signal mode



Here collector currents are given by


$$I_{C1} = I_{C2} = \frac{\alpha V_{id} R_c}{2r_e}$$

The collector voltages are given by

$$V_{C2} = V_{C1} = \frac{\alpha V_{id} R_c}{2r_e}$$


$$V_{C1} = -\frac{\alpha V_{id} R_c}{2r_e}$$

AC equivalent circuit is shown below:

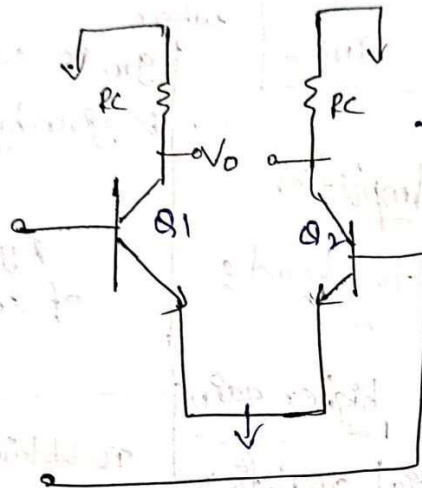

In AC circuit, all ~~capacitors~~ current sources are short

Here h_{ie} is replaced with r_e .

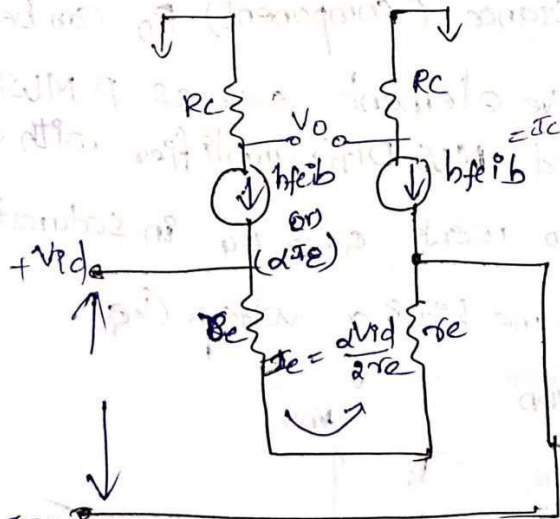

Equivalent T-Model (r-model).

collector equations output voltage is given by

$$V_O = V_{C2} - V_{C1}$$

$$V_O = \frac{\alpha V_{id} R_c}{2r_e} + \frac{\alpha V_{id} R_c}{2r_e}$$

$$V_O = \frac{2\alpha V_{id} R_c}{2r_e}$$

$$\frac{V_o}{V_{id}} = \frac{\alpha R_c}{r_e}$$

$$A_d = \frac{\alpha R_c}{r_e}$$

$$A_d = \frac{\alpha R_c}{r_e + R_E}$$
 if an

external resistor R_E at emitters of Q_1 & Q_2 than differential gain is

$$A_d = \frac{\alpha R_c}{r_e + R_E}$$

We can also express A_d in terms of transconductance

(g_m) as

$$A_d = g_m R_c$$

where

g_m is called transconductance

$$\text{is given by } \frac{\alpha}{r_e} = g_m$$

Dynamic resistance of emitter diode $\frac{dI}{dV}$
 $\rightarrow 26\text{mV}$
 at room temp

MOS Differential Amplifier


with Active load =

→ In order to obtain higher gains of MOS Differential amplifier

to obtain high gains we use this.


the passive resistance (component) R_D can be replaced with an active element such as P-MOSFET then it is called MOS Diff. amplifier with active load.

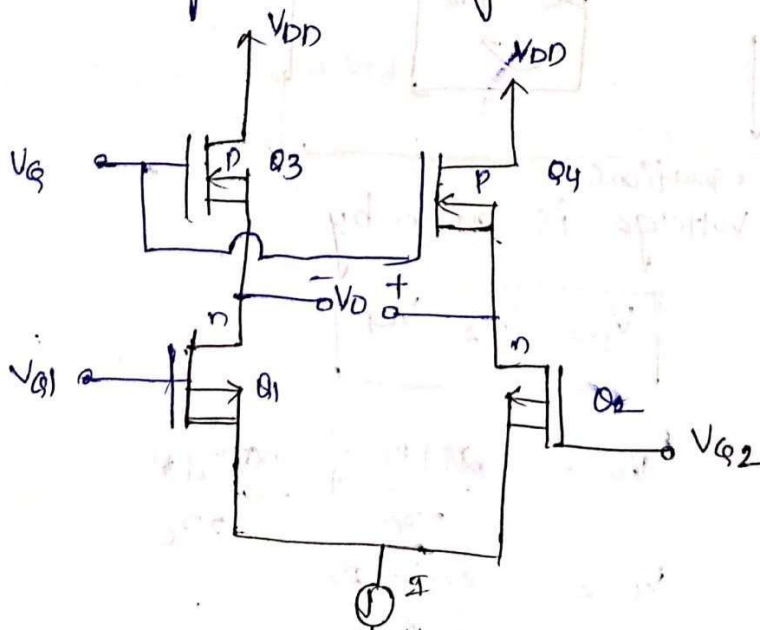→ Here in order to work Q_3 & Q_4 in saturation, we can apply some biasing voltage (V_{G1}).



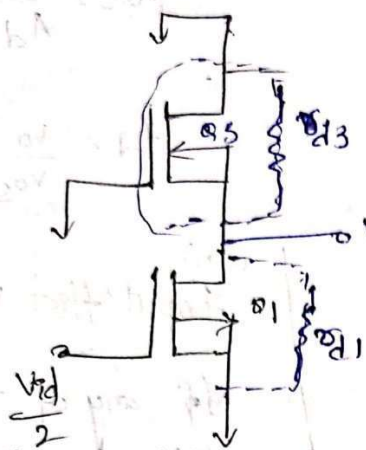ii) The charge constrain.

Now we can analyse the above circuit using small signal half circuit method instead of analyzing full differential amplifier.



$$V_{od} = g_m V_{id} (R_D || r_{d1})$$

$$\frac{V_{od}}{V_{id}} = \frac{g_m}{2} [R_D || r_{d3}]$$

$$A_v = \frac{g_m}{2} [R_D || r_{d1}]$$

with $R_D = r_{d1} = r_{d3}$ then


$$A_v = \frac{g_m}{2} \left[\frac{r_d}{2} \right] = \frac{g_m r_d}{4}$$

⇒ Nonideal characteristics of MOS-Differential Amplifier.


⇒ We studied MOS differential amplifier if same voltage is applied to the inputs then output becomes zero, under ideal conditions, such as:

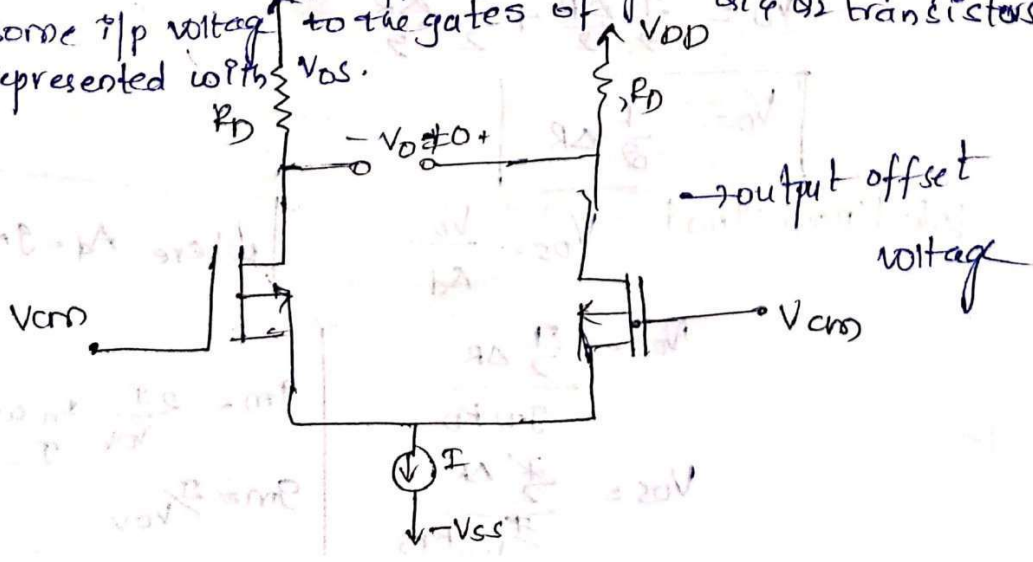- (i) If both resistances (R_{D1}, r_{d1}) are same.
- (ii) Both transistors have same $(\frac{W}{L})$ ratio.
- (iii) Both transistor have same threshold voltage (V_T)
- (iv) Suppose if any one of the above conditions are not satisfied then output ^{will not} becomes zero, which is

known as: o/p offset voltage.
 ⇒ To make the o/p offset voltage as zero by applying some i/p voltage to the gates of Q_1 & Q_2 transistors represented with V_{os} .



Input offset voltage (2M)

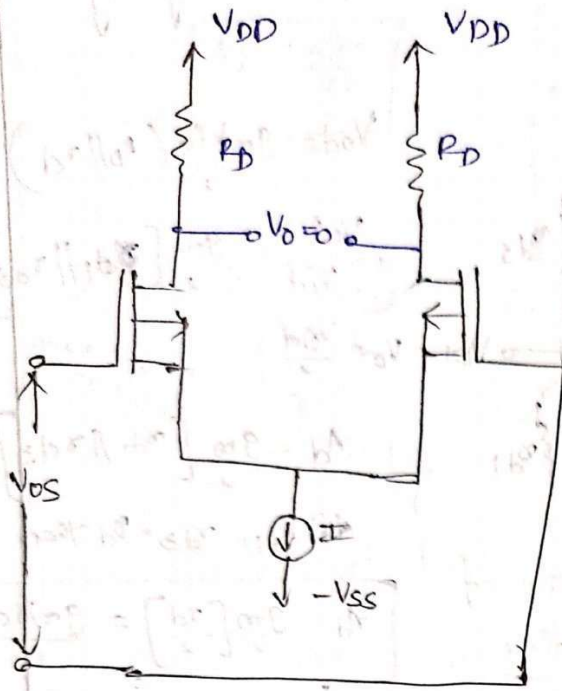

$$V_{OS} = \frac{V_O}{A_d}$$

$$A_d = \frac{V_O}{V_{OS}} \text{ or } \frac{V_O}{V_{IS}}$$

(RM) Input offset voltage

If any of the ideal conditions are not satisfied then V_O voltage becomes zero which is known as i/p offset voltage.

Case (i) 1st Non-ideal Conditions:

Drain resistances are not equal, there is a change in drain resistance.

$$R_{D1} = R_D + \frac{\Delta R}{2}; R_{D2} = R_D - \frac{\Delta R}{2}$$

$$V_{D1} = V_{DD} - \frac{I}{2} \left(R_D + \frac{\Delta R}{2} \right)$$

$$V_{D2} = V_{DD} - \frac{I}{2} \left(R_D - \frac{\Delta R}{2} \right)$$

$$\therefore V_{O1} = V_{D2} - V_{D1} \Rightarrow V_{DD} - \frac{I}{2} R_D + \frac{I}{2} \frac{\Delta R}{2} - \left[V_{DD} - \frac{I}{2} R_D - \frac{I}{2} \frac{\Delta R}{2} \right]$$

$$V_O = \frac{I}{2} \frac{\Delta R}{2} + \frac{I}{2} \frac{\Delta R}{2}$$

$$V_O = \frac{I}{2} \Delta R$$

We know that $V_{OS} = \frac{V_O}{A_d}$

$$V_{OS} = \frac{\frac{I}{2} \Delta R}{g_m R_D}$$

$$V_{OS} = \frac{\frac{I}{2} \Delta R}{\frac{I}{2} V_{OV} R_D}$$

where $A_d = g_m R_D$

$$g_m = \frac{2I}{V_{OV}} \text{ in common mode}$$

$$g_m = \frac{I}{V_{OV}}$$

$$V_{os} = \frac{V_{ov}}{2} \times \frac{\Delta R}{R_D}$$

Case ii: 2nd Non-ideal conditions:

Both transistors ($\frac{W}{L}$) ratios are not same.

$$\left(\frac{W}{L}\right)_1 = \left(\frac{W}{L}\right) + \frac{1}{2} \Delta\left(\frac{W}{L}\right)$$

$$\left(\frac{W}{L}\right)_2 = \left(\frac{W}{L}\right) - \frac{1}{2} \Delta\left(\frac{W}{L}\right)$$

So, as the ($\frac{W}{L}$) changes so drain current changes.

$$I_{D1} = \frac{I}{2} \left[\frac{1 + \Delta\left(\frac{W}{L}\right)}{2\left(\frac{W}{L}\right)} \right] = \frac{I}{2} \left[1 + \frac{\Delta\left(\frac{W}{L}\right)}{2\left(\frac{W}{L}\right)} \right]$$

$$I_{D2} = \frac{I}{2} \left[1 - \frac{\Delta\left(\frac{W}{L}\right)}{2\left(\frac{W}{L}\right)} \right]$$

Change in current is given by:

$$I_D = I_{D2} - I_{D1}$$

$$I_D = \frac{I}{2} \left[\frac{\Delta\left(\frac{W}{L}\right)}{2\left(\frac{W}{L}\right)} - \left(1 - \frac{\Delta\left(\frac{W}{L}\right)}{2\left(\frac{W}{L}\right)} \right) \right]$$

$$I_D = \frac{I}{2} \left[\frac{(-)\Delta\left(\frac{W}{L}\right)}{\left(\frac{W}{L}\right)} \right] \quad \left[\begin{array}{l} (+) (+) (+) \\ (-) (-) (-) \\ \text{convention} \end{array} \right]$$

$$V_{os} = \frac{V_o}{A_V}$$

$$V_{os} = \frac{V_o}{g_m R_D} = I$$

$$V_{os} = \frac{I}{g_m} = \frac{I}{2} \left[\frac{\Delta\left(\frac{W}{L}\right)}{\left(\frac{W}{L}\right)} \right]$$

$$V_{os} = \frac{V_{ov}}{2} \left[\frac{\Delta\left(\frac{W}{L}\right)}{\left(\frac{W}{L}\right)} \right]$$

Case iii: rd Non-ideal conditions :-

→ Both transistors threshold voltages are not same

$$[i.e] V_{t1} \neq V_{t2}$$

$$V_{t1} = V_t + \frac{\Delta V_t}{2}$$

$$V_{t2} = V_t - \frac{\Delta V_t}{2}$$

Due to these changes, drain currents will differ by

$$I_{D1} = \frac{k_{n1}}{2} \left(\frac{W}{L} \right) \left(V_{GS} - \left(V_t + \frac{\Delta V_t}{2} \right) \right)^2$$

$$I_{D2} = \frac{k_{n2}}{2} \left(\frac{W}{L} \right) \left(V_{GS} - \left(V_t - \frac{\Delta V_t}{2} \right) \right)^2$$

The above eqns can be simplified using Taylor's series

$$I_{D1} = \frac{I}{2} \left(1 - \frac{\Delta V_t}{V_{GS} - V_t} \right)$$

$$I_{D2} = \frac{I}{2} \left(1 + \frac{\Delta V_t}{V_{GS} - V_t} \right)$$

Change in current $\Delta I = I_{D2} - I_{D1}$

$$\Delta I = \frac{I}{2} \left(1 + \frac{\Delta V_t}{V_{GS} - V_t} \right) - \frac{I}{2} \left(1 - \frac{\Delta V_t}{V_{GS} - V_t} \right)$$

$$\Delta I = I \frac{\Delta V_t}{V_{GS} - V_t} = \frac{I \Delta V_t}{V_{OV}}$$

Input offset voltage (V_{OS}) = $\frac{I}{g_m}$ (or) $\frac{\Delta I}{g_m}$

$$V_{OS} = \frac{I}{I/V_{OV}} \Rightarrow V_{OS} = \frac{I \Delta V_t / V_{OV}}{I/V_{OV}} = \Delta V_t$$

$$\boxed{V_{OS} = \Delta V_t}$$


suppose if the above 3 conditions will occur at a time then expression for Input offset Voltage

$$V_{OS} = \sqrt{\left(\frac{V_{OV}}{2} * \frac{\Delta R}{R_D}\right)^2 + \left(\frac{V_{OV}}{2} * \frac{\Delta V_T}{V_T}\right)^2 + (\Delta V_T)^2}$$

Non-Ideal characteristics of BJT

Differential Amplifier :-

Input offset voltage :-

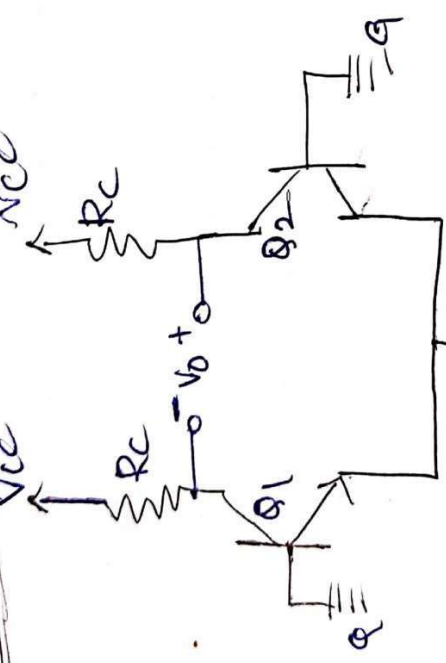

$$R_{C1} = R_C + \frac{R_C}{2}; R_{C2} = R_C - \frac{R_C}{2}$$


By adding all conditions and square because effective at a time

$$V_{OS} = V_T \left(\frac{\Delta R_C}{R_C}\right)$$

$$V_{OS} = V_T \left(\frac{\Delta I_S}{I_S}\right)$$

$$\frac{d}{dR_C} = V_T$$

$$dC = \frac{V_T}{I}$$

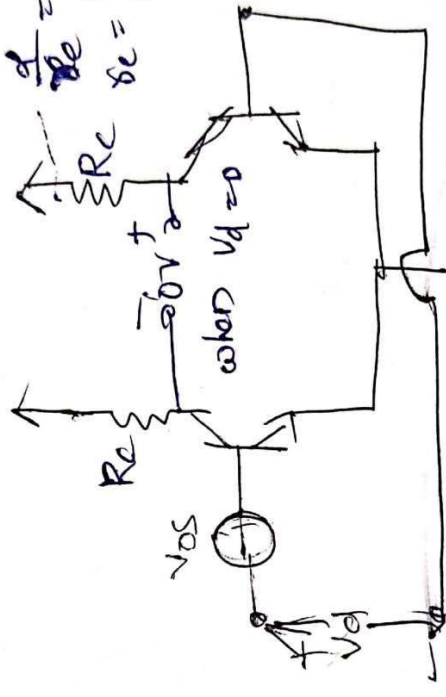

Input bias currents can be mismatched.

Common Mode Rejection Ratio (CMRR) :-

$$CMRR = \frac{A_d}{A_{cm}}$$

CMRR refers how much the common mode i/p signal can be rejected by the differential amplifier and it can also tell the how the differential amplifier respond to differential input and completely rejects the common mode signal.

⇒ Based on this, CMRR is defined as it is the ratio of differential gain to common mode gain of differential amplifier (i.e. $CMRR = \frac{A_d}{A_{cm}}$)

$CMRR = \frac{A_d}{A_{cm}}$ in general, for a differential amplifier, common mode i/p signal is zero. So

$$\therefore CMRR = \frac{A_d}{0}$$


only theoretically possible

$$CMRR = \infty$$


Differential amplifier has i.e. high CMRR ratio

Most cases: In general the CMRR can be derived

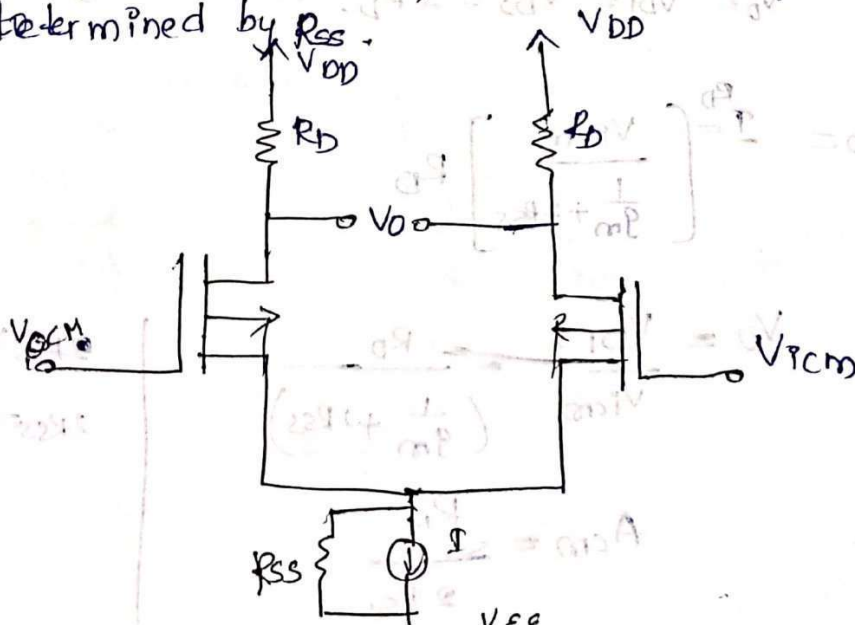
by considering the diff. amplifier in common mode. with an incremental change in (V_{cm}) by considering (a resistor in parallel to) current source (I) in parallel determined by $R_{SS} \cdot \frac{V_{DD}}{V_{SS}}$



AC equivalent circuit is shown below

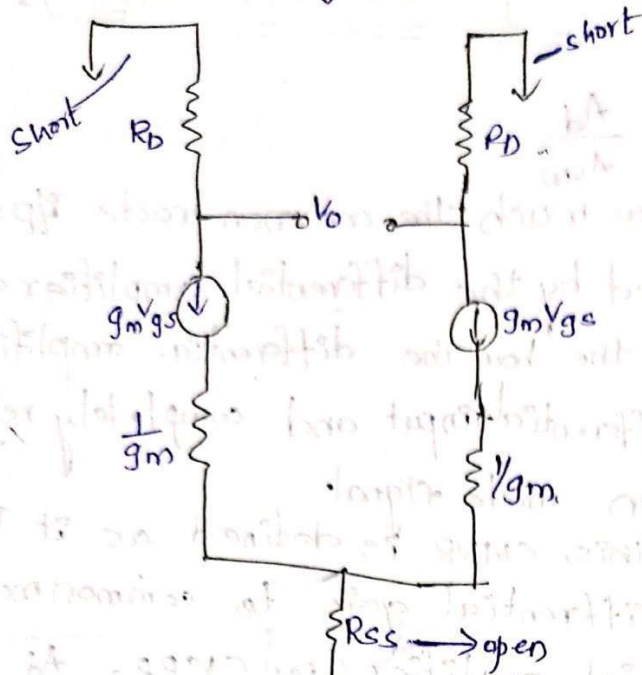

Half circuit

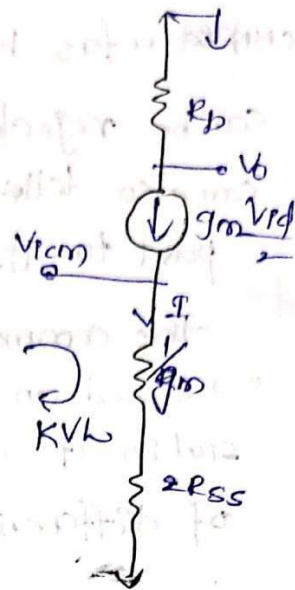

From AC equivalent circuit

By apply KVL to i/p loop.

$$V_{icm} - \frac{I}{g_m} - 2IR_{SS} = 0$$

$$V_{icm} - I/g_m - 2IR_{SS} = 0$$

$$V_{icm} = I \left[\frac{1}{g_m} + 2R_{SS} \right]$$

$$I = \frac{V_{icm}}{\left[\frac{1}{g_m} + 2R_{SS} \right]}$$

$V_o = V_{D1} = V_{D2} = IR_D$. (No mismatch)

$$V_o = \frac{R_D}{\left[\frac{1}{g_m} + 2R_{SS} \right]} V_{icm}$$

$$V_o = \frac{V_{D1}}{V_{icm}} \cdot \frac{R_D}{\left(\frac{1}{g_m} + 2R_{SS} \right)}$$

$$A_{cm} = \frac{R_D}{2R_{SS}}$$

$$2R_{SS} \gg \frac{1}{g_m}$$

$$2R_{SS} = \frac{1}{g_m} + 2R_{SS}$$

∴ Then $CMRR = \frac{A_d}{A_{cm}} = \frac{g_m R_D}{\frac{R_D}{2R_{SS}}}$

$$CMRR = 2g_m R_{SS} \quad \text{Imp}$$

If there is a mismatch in R_D , then

$$R_D = \Delta R_D$$

$$A_{CMRR} = \frac{\Delta R_D}{2R_{SS}}$$

∴ $CMRR = \frac{A_d}{A_{cm}}$

$$CMRR = \frac{g_m R_D}{\frac{\Delta R_D}{2R_{SS}}}$$

$$CMRR = \frac{2g_m R_{SS}}{\frac{\Delta R_D}{R_D}}$$

suppose if there is a mismatch in g_m


$$CMRR = \frac{2g_m R_{SS}}{\left(\frac{\Delta g_m}{g_m}\right)}$$

g_m is very high


$$CMRR \text{ in dB} = 20 \log \left[\frac{A_d}{A_{cm}} \right]$$

$$CMRR \text{ in dB} = 20 \log (CMRR)$$


CMRR for BJT

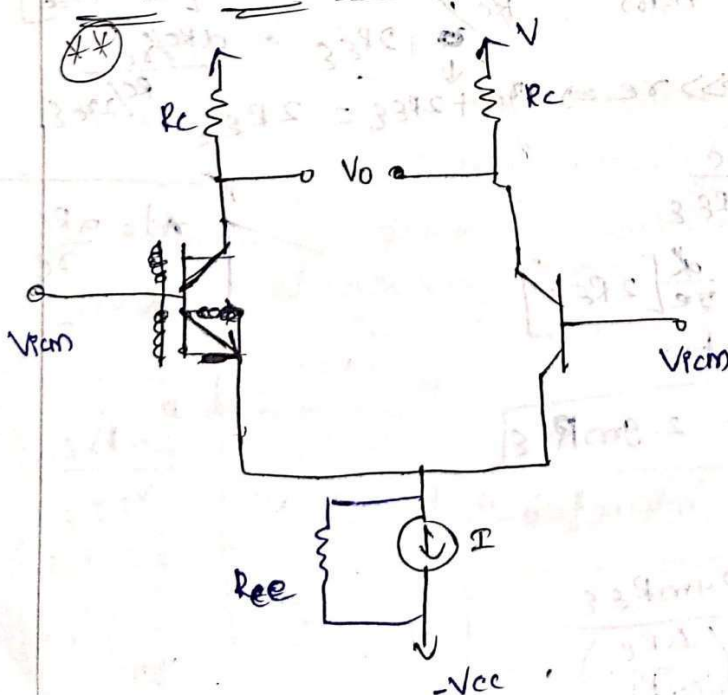

AC circuit

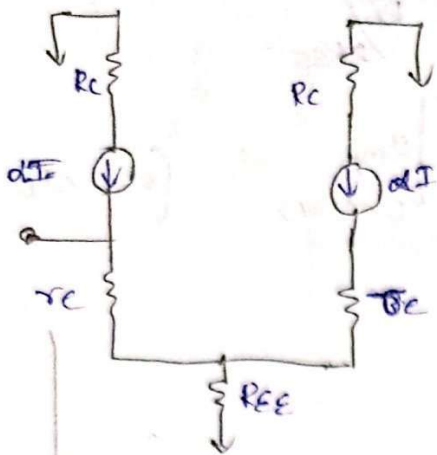

Half-circuit

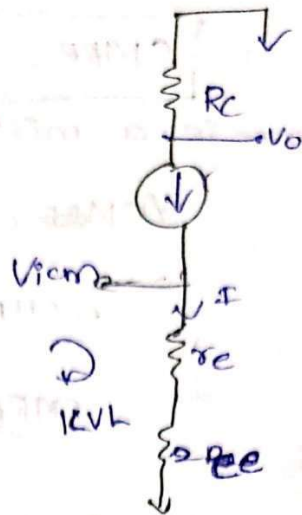

Apply KVL to input loop:

$$V_{icm} = I [r_e + 2R_{EE}]$$

$$I = \frac{V_{icm}}{r_e + 2R_{EE}}$$

$$V_o = V_{c1} = V_{c2} = \alpha R_c I$$

$$V_o = \left(\frac{V_{icm}}{r_e + 2R_{EE}} \right) R_c \Rightarrow \frac{V_o}{V_{icm}} = \left[\frac{R_c}{r_e + 2R_{EE}} \right]$$

$$A_{cm} = \frac{R_c}{r_e + 2R_{EE}} \quad \text{if } 2R_{EE} \gg r_e \Rightarrow 2R_{EE}$$

$$\therefore CMRR = \frac{A_d}{A_{cm}} = \frac{\alpha R_c / r_e}{R_c / (r_e + 2R_{EE})} = \alpha \left[\frac{r_e + 2R_{EE}}{r_e} \right]$$

if $2R_{EE} \gg r_e \Rightarrow r_e + 2R_{EE} = 2R_{EE}$

$$A_{cm} = \frac{R_c}{2R_{EE}}$$

$$\therefore CMRR = \frac{\alpha}{r_e} [2R_{EE}]$$

we know that

$$CMRR = 2 g_m R_{EE}$$

if there is a mismatch in R_c ,

$$CMRR = \frac{2 g_m R_{EE}}{\left(\frac{\Delta R_c}{R_c} \right)}$$

$$CMRR_{dB} = 20 \log \left(\frac{2 g_m R_{EE}}{\left(\frac{\Delta R_c}{R_c} \right)} \right)$$

$$A_d = \frac{\alpha R_c}{r_e}$$

$$r_e = \frac{V_T}{I_E}$$

$$\frac{2 \alpha R_{EE}}{V_T / I_E}$$

$$\frac{2 I_C R_{EE}}{V_T}$$

$$\frac{2 g_m R_{EE}}{g_m}$$

$$\frac{2 g_m R_{EE}}{g_m}$$



Effect of Cascading on Gain and Bandwidth of Multistage amplifiers

1) Effect of cascading on gain

→ We know that, in Multistage amplifiers, the overall gain is equal to the product of individual voltage gains. i.e. $A_v = A_{v1} \times A_{v2} \times \dots \times A_{vn}$.

→ We know that $A_v = (A_m)^n$ in mid frequencies.

→ If 'n' no. of identical stages are cascaded then overall gain follows $A_{mv} = (A_m)^n$ at mid frequencies.

(2) At low frequencies, the gain of the amplifier for a single stage is

$$A_L = \frac{A_m}{\sqrt{1 + \left(\frac{f}{f_L}\right)^2}}$$

in low freq
 $f_L = \frac{1}{RC}$
Av depends on low pass circuit


For 'n' identical stages $(A_v) = (A_m)^n$

(3) At high frequencies, the gain of the amplifier for single stage is

$$A_H = \frac{A_m}{\sqrt{1 + \left(\frac{f}{f_H}\right)^2}}$$

$f_H = \frac{1}{2\pi RC}$
Gain depends on high pass circuit
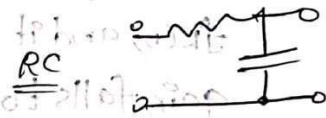
$$A_H = \frac{(A_m)^n}{\left[1 + \left(\frac{f}{f_H}\right)^2\right]^{n/2}}$$



1) A multistage amplifier with four identical stages each of which has a lower cutoff frequency of

$f_L = 20\text{Hz}$ and upper cutoff frequency of $f_H = 20\text{kHz}$

Calculate the gain of the Multistage amplifier at mid frequency, 7.5Hz and 200kHz ? Assume mid band gain (A_m) of each stage is 10?

$f_L = 20\text{Hz}; f_H = 20\text{kHz}; A_m = 10; n = 4$
At mid frequencies
 $= A_{mv} = (10)^4$

$A_{mv} = 10000$
At $f = 7.5\text{Hz}$ (low frequency)

$$\therefore A_L = \frac{A_m}{\sqrt{1 + \left(\frac{f}{f_L}\right)^2}} = \frac{10}{\sqrt{1 + \left(\frac{20}{7.5}\right)^2}} = 1.232 \times 10^4 = 12320$$

$A_H = 200 \text{ kHz}$ (\rightarrow upper cutoff so use at high frequency)

$$A_H = \frac{(A_m)^n}{\left[1 + \left(\frac{f}{f_H}\right)^2\right]^{n/2}}$$

$$A_H = \frac{(10)^4}{\left[1 + \left(\frac{200 \text{ kHz}}{20 \text{ kHz}}\right)^2\right]^{4/2}}$$

$$A_H = 0.98$$

Effect of cascading on bandwidth:

Bandwidth is the difference between upper cutoff frequency and lower cutoff frequency $(\text{BW} = f_H - f_L)$.
 \Rightarrow In multistage amplifiers, due to cascading, the frequency response and bandwidth of the amplifier get affected and the bandwidth of cascaded amplifier is always less than that of a single stage amplifier.

For cascaded amplifiers: Lower 3dB frequency = cascaded

The lower 3dB frequency of 'n' identical stages is $f_L(n)$ and it is the frequency at which the overall gain falls to $\left(\frac{1}{\sqrt{2}}\right)$ times of its mid band gain ($\text{max } A_V$)

$$\Rightarrow \text{we know that } A_{HL} = \frac{(A_m)^n}{\left[1 + \left(\frac{f}{f_L(n)}\right)^2\right]^{n/2}} = \frac{(A_m)^n}{\sqrt{2}}$$

$$A_L \Rightarrow \frac{1}{\left[1 + \left(\frac{f}{f_L(n)}\right)^2\right]^{n/2}} = \frac{1}{\sqrt{2}}$$

$$\left[1 + \left(\frac{f}{f_L(n)}\right)^2\right]^{n/2} = \sqrt{2}$$

Squaring on both sides.

$$2 = \left[1 + \left(\frac{f}{f_L(n)}\right)^2\right]^n$$

$$2^{1/n} = 1 + \left(\frac{f}{f_L(n)}\right)^2$$

$$2^{1/n} - 1 = \left(\frac{f}{f_L(n)}\right)^2$$

Taking square root on both sides.

$$\sqrt{(2^{1/n} - 1)} = \frac{f_L}{f_L(n)}$$

$$f_L(n) = \frac{f_L}{(2^{1/n} - 1)^{1/2}}$$

Similarly: we know that $A_{H1} = \frac{(A_m)^n}{\left[1 + \left(\frac{f}{f_H}\right)^2\right]^{n/2}}$
 upper cutoff frequency $f_H(n)$ is the at which the gain of the amplifier decreases to $(\frac{1}{\sqrt{2}})$ times of its mid band frequency.

$$A_H \Rightarrow \frac{(A_m)^n}{\left[1 + \left(\frac{f_H(n)}{f_H}\right)^2\right]^{n/2}} = \frac{(A_m)^n}{\sqrt{2}}$$

$$\left[1 + \left(\frac{f_H(n)}{f_H}\right)^2\right]^{n/2} = \sqrt{2}$$

$$\left(\frac{f_H(n)}{f_H}\right)^2 = \sqrt{2}^{2/n} - 1$$

$$\sqrt{2} = \left[1 + \left(\frac{f_H(n)}{f_H}\right)^2\right]^{n/2}$$


$$2^{1/n} = 1 + \left(\frac{f_H(n)}{f_H}\right)^2$$

$$2^{1/n} - 1 = \left(\frac{f_H(n)}{f_H}\right)^2$$

$$f_H(n) = f_H \sqrt{2^{1/n} - 1}$$

Upper cutoff frequency for n identical stages

From above eqns

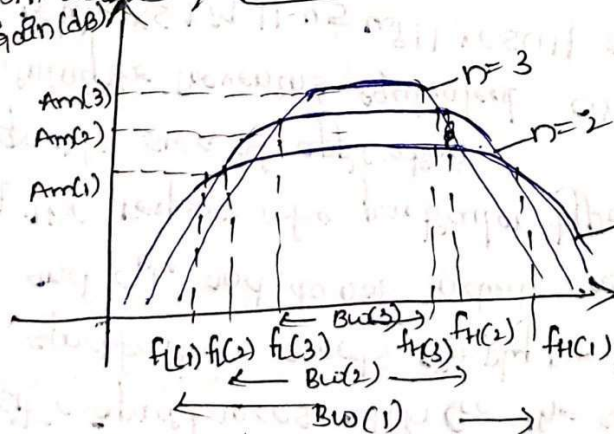


TO overcome drawback (Feedback Amplifier)

As identical stages increases, Bandwidth decreases so, it is not good for amplifier (BW should be high for good amplifier)

Frequency Response of BJT & MOSFET Amplifier

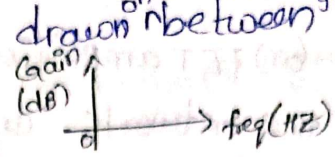
Frequency Response: It is the graph drawn on ^{semi logarithmic} between ^{graph} frequency (vs) gain of the amplifier.



Frequency range: low Hz to MHz.

→ It is a non-linear graph.

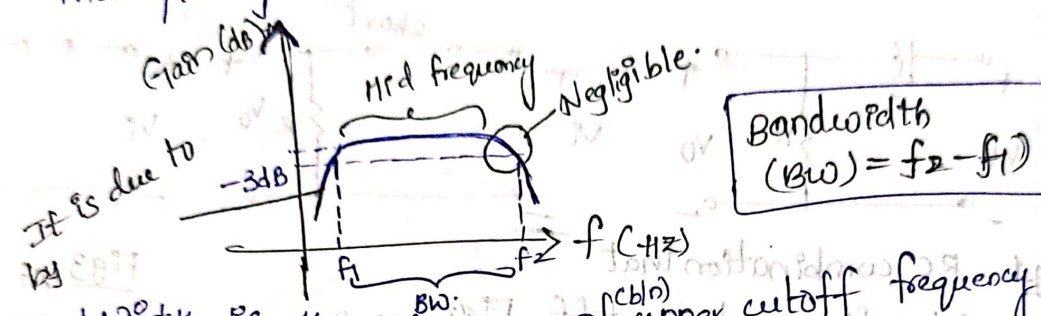→ On x-axis, frequencies are considered as a multiple of decade.



Band Width is the difference of upper cutoff frequency and lower cutoff frequency.

Why -3dB we considered?

The decreased gain is negligible, so at that curve we considered (-3dB).

⊛ Lower cutoff Frequency: The gain of the amplifier increases. At low frequency, gain is fall off because coupling and bypass capacitor.

→ The frequency at which the gain drops by 3dB below its mid band frequency is called lower cutoff frequency (f_L)

Upper cutoff frequency:

→ At higher frequencies, the gain of the amplifier falls because ^{of internal} junction capacitances of the ^{BJT} transistor (or) MOSFET's.

→ The frequency at which the gain drops by 3dB ^{above} its midband frequency.

Low Frequency Analysis of BJT and MOSFET:

→ In the low frequency region of the single-stage BJT or FET amplifier, it is the RC combinations formed by the network capacitors C_c , C_e and C_m and the network resistive parameters that determine the cutoff frequency.

→ Fig-1 can be established for each capacitive element and the frequency at which the output voltage drops to 0.707 of its maximum value determined.

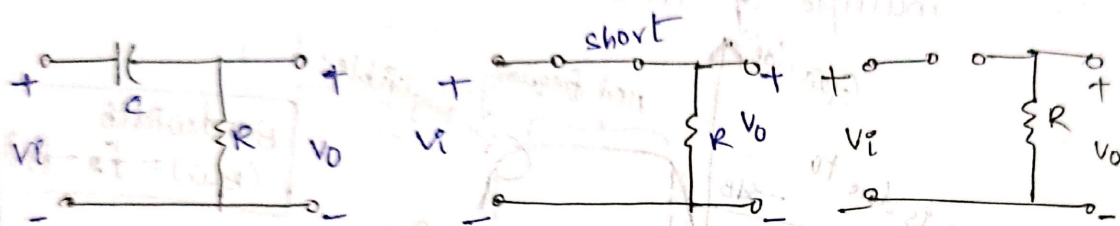


Fig 1: RC combination that will define a low cutoff frequency.

Fig 2: At high frequency

Fig 3: At low frequency

→ Once the cutoff frequencies due to each capacitor are determined, they can be compared to establish which will determine the low-cut-off frequency for the system.

→ Our analysis, therefore, will begin with the series R-c combination of fig. 1 and the development of a procedure that will result in a plot of the frequency response with a minimum of time and effort.

→ At high frequencies, $X_c = \frac{1}{\omega C} = 0$


and short-circuit equivalent can be substituted for the capacitor as shown in fig. 2. The result is that $V_o = V_i$ at high frequencies

→ At $f = 0 \text{ Hz}$, $X_c = \frac{1}{2\pi f C} = \frac{1}{2\pi(0)} = \infty$

and the open circuit approximation can be applied shown in Fig. 3 with the result that $V_o = 0V$ (when $R = \infty$)

$$A_v = \frac{V_o}{V_i}$$

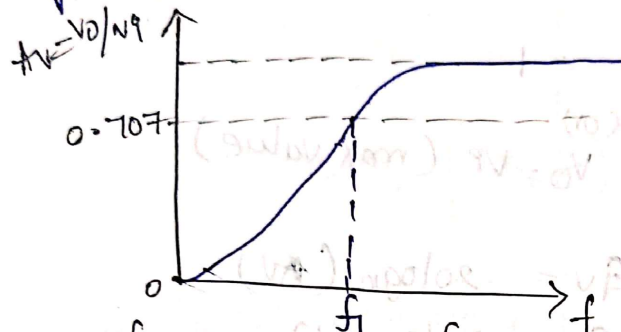
As the frequency increases, the capacitive reactance decreases and more of the input voltage appears across the output terminals. (so short)



low frequency response for RC circuit

The op and i/p voltages are related by the voltage-divider rule

$$V_o = \frac{R V_i}{R + X_c}$$

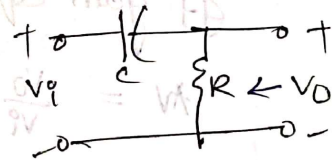

Magnitude of V_o

$$V_o = \frac{R V_i}{\sqrt{R^2 + X_c^2}}$$

when $X_c = R$,

$$V_o = \frac{R V_i}{\sqrt{R^2 + R^2}} = \frac{R V_i}{\sqrt{2} R} = \frac{V_i}{\sqrt{2}}$$

$$|A_v| = \frac{V_o}{V_i} = \frac{\frac{V_i}{\sqrt{2}}}{V_i} = \frac{1}{\sqrt{2}}$$

$$|A_v| = \frac{1}{\sqrt{2}}$$

At the frequency of which $X_c = R$, the o/p will be 70.7% (0.707) (3dB) of the i/p of network.

The frequency at which this occurs is as

$$X_c = \frac{1}{2\pi f_c} = R$$

$$f_c = \frac{1}{2\pi RC}$$

In terms of logs,

$$G_v = 20 \log_{10} A_v = 20 \log_{10} \frac{1}{\sqrt{2}}$$

$$\boxed{G_v = -3 \text{ dB}}$$

When

$$A_v = \frac{V_o}{V_i} = 1$$

(or)
 $V_o = V_p$ (max value)

$$G_v = 20 \log_{10} (A_v)$$

$$G_v = 20 \log_{10} (1) \Rightarrow$$

$$\boxed{G_v = 0 \text{ dB}}$$

If gain equation is written as

$$A_v = \frac{V_o}{V_i} = \frac{R}{R - jX_c}$$

$$A_v = \frac{1}{1 - j(X_c/R)}$$

$$= \frac{1}{1 - j(1/\omega CR)}$$

$$= \frac{1}{1 - j(1/2\pi fCR)}$$

$$f_c = 1/2\pi RC$$

$$A_v = \frac{1}{1 - j(f_c/f)}$$

Magnitude and phase form

$$A_v = \frac{V_o}{V_i} = \frac{1}{\underbrace{\sqrt{1 + (f_c/f)^2}}_{\text{Mag of } A_v}}$$

$$\tan^{-1}(f_c/f)$$

↓ phase angle by which V_o leads V_i

The magnitude when $f = f_1$

$$|A_v| = \frac{1}{\sqrt{1+1}} = \frac{1}{\sqrt{2}} = 0.707 \Rightarrow -3\text{dB}$$

In log form, the gain in dB is

$$A_v(\text{dB}) = 20 \log_{10} \frac{1}{\sqrt{1+(f/f_1)^2}} = 20 \log_{10} \left[\sqrt{1+(f/f_1)^2} \right]^{-1}$$

$$= -20 \log_{10} \left[1 + \left(\frac{f}{f_1} \right)^2 \right]^{1/2}$$

$$= -\frac{1}{2} (20) \log_{10} \left[1 + \left(\frac{f}{f_1} \right)^2 \right]$$

$$= -10 \log_{10} \left[1 + \left(\frac{f}{f_1} \right)^2 \right]$$

$$A_v(\text{dB}) = -10 \log_{10} \left[\left(\frac{f}{f_1} \right)^2 \right] \quad f \ll f_1 \text{ (or } (f/f_1)^2 \gg 1)$$

$$\text{XXX} \quad A_v(\text{dB}) = -20 \log_{10} \left(\frac{f}{f_1} \right) \quad (f \ll f_1)$$


At $f = f_1$; $A_v(\text{dB}) = -20 \log_{10}(1) = 0\text{dB}$.

At $f = \frac{1}{2} f_1$; $A_v(\text{dB}) = -6\text{dB}$

At $f = \frac{1}{4} f_1$; $\frac{f_1}{f} = 4$; $-20 \log 4 = -12\text{dB}$.

At $f = \frac{1}{10} f_1$; $\frac{f_1}{f} = 10$ and $A_v(\text{dB}) = -20 \log_{10}(10)$


$= -20\text{dB}$.

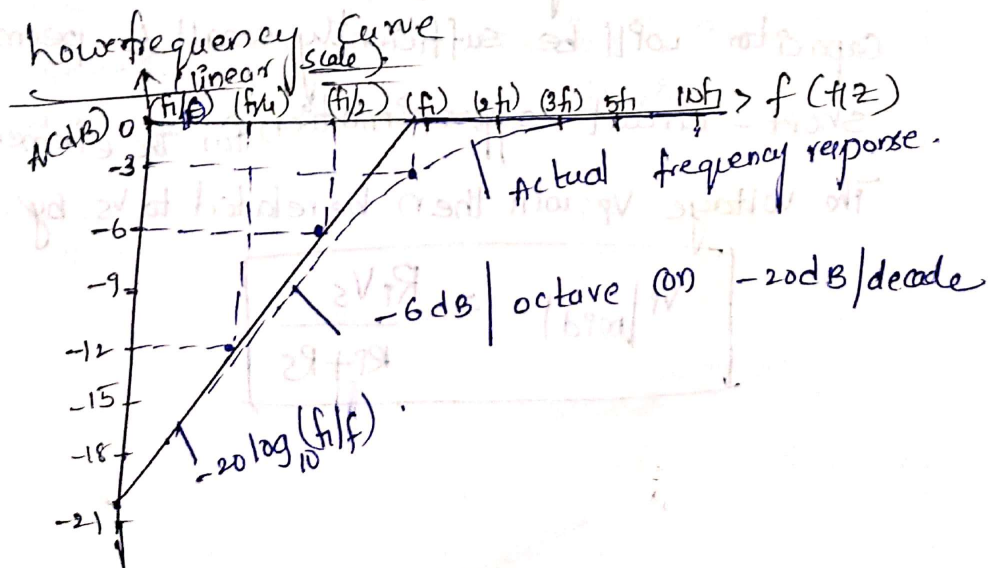

Low Frequency Analysis of BJT


The analysis of low frequency response of BJT amplifier will employ the loaded voltage divider BJT bias configuration, but results can be applied to any BJT configuration.

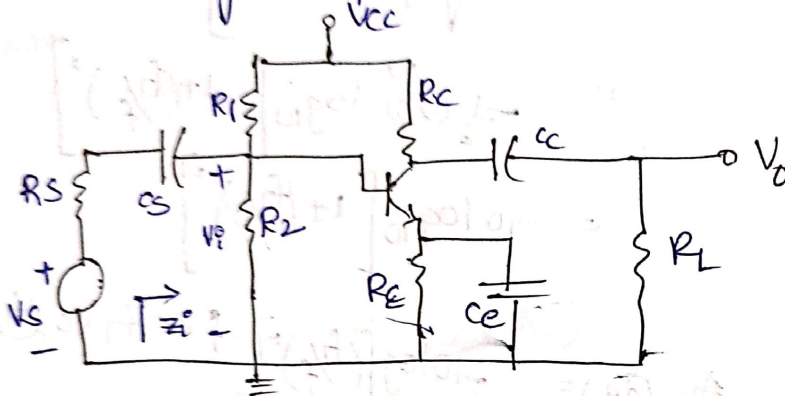→ The capacitors C_s , C_c and C_e will determine the low-frequency response.



C_s : C_s is normally connected b/w the applied source and the active device, the general form of configuration is established as shown in fig. The total resistance ($R_s + R_i$) and the cutoff frequency as established.
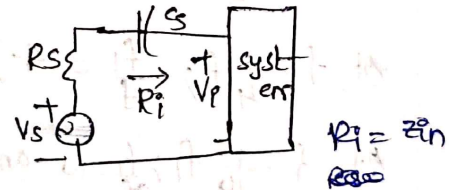
$$f_{LS} = \frac{1}{2\pi(R_s + R_i)C_s}$$



→ At mid (or) high frequencies, the reactance of the capacitor will be sufficiently small to permit a short-circuit approximation for the element.

The voltage V_p will then be related to V_s by


$$V_p |_{\text{mid}} = \frac{R_i V_s}{R_i + R_s}$$

At f_{hs} , the voltage V_i will be 70-71% of the value determined by above $V_i(\text{mid})$ equation, assuming that C_s is the only capacitive element controlling the low-frequency response.

For the network of fig1, when we analyze the effects of C_s we must make the assumption that C_e and C_c are performing their designed function or the analysis becomes too unwieldy, that is, the magnitude of the reactances of C_e and C_c permits employing a short circuit equivalent in comparison to the magnitude of the other series impedances. Using the hypothesis, the ac equivalent network for the input section of fig1 will appear as shown in below fig:-

$$R_i = R_1 || R_2 || \beta r_e$$

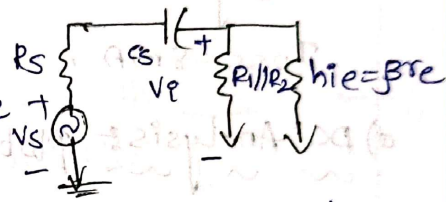→ The voltage (V_i) applied to the input of the active device




can be calculated using the voltage divider rule

$$V_i = \frac{R_i V_s}{R_s + R_i - jX_{C_s}}$$

→ C_s Since the coupling capacitor is normally connected b/w the o/p of the active device and the applied load, the R-C combination that determines the low cutoff frequency due to C_s appears in below Fig.

Total series resistance is now $R_o + R_L$ and the cutoff frequency due to C_s is determined by
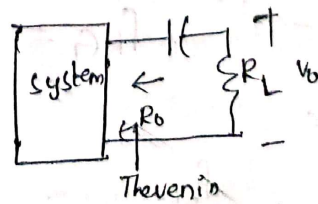
$$f_{hc} = \frac{1}{2\pi (R_o + R_L) C_s}$$




Determine the effect of lower cutoff frequency.

C6 For the source capacitor C_s , the resistance level of importance is defined by R_{eq} below. The cutoff frequency will be defined by

$$f_{hs} = \frac{1}{2\pi R_{eq} C_s}$$

The resulting value of R_{eq} is

$$R_{eq} = \frac{R_s}{1 + R_s(1 + g_m r_d) / (r_d + R_D || R_L)} \quad \left| \begin{array}{l} r_d \approx \alpha \Omega \text{ becomes} \\ R_{eq} = R_s || \frac{1}{g_m} \end{array} \right.$$

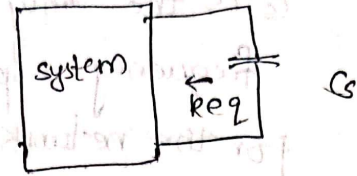

P Determine the lower cutoff frequency for the network of fig 11-3a using the following parameters?

$C_g = 0.01 \mu F$, $C_c = 0.5 \mu F$ $C_s = 2 \mu F$ $R_s = 1 k\Omega$
 $R_{sig} = 10 k\Omega$, $R_g = 1 M\Omega$ $R_D = 4.7 k\Omega$ $V_{DD} = 20V$
 $I_{DSS} = 8 mA$, $V_p = -4V$ $r_d = \alpha \Omega$ $R_L = 2.2 k\Omega$

a) DC Analysis: plotting the transfer curve of

$I_D = I_{DSS} \left[1 - \frac{V_{GS}}{V_p} \right]^2$ and superimposing the curve defined by $V_{GS} = -I_D R_s$ will result in an intersection at $V_{GS0} = -2V$ & $I_{D0} = 2mA$.

$$g_{m0} = \frac{2I_{DSS}}{|V_p|} = \frac{2(8 \times 10^{-3})A}{4V} = 4mS$$

$$g_m = g_{m0} \left[1 - \frac{V_{GS0}}{V_p} \right] = 4mS \left[1 - \left(\frac{-2V}{-4V} \right) \right] = 2mS$$

Cg

$$f_{hg} = \frac{1}{2\pi (10k\Omega + 1M\Omega) (0.01\mu F)} \approx 15.8 Hz$$

Cc

$$f_{hc} = \frac{1}{2\pi (4.7k\Omega + 2.2k\Omega) (0.5\mu F)} \approx 46.13 Hz$$

$$C_{S \approx} Req = R_s \parallel \frac{1}{g_m} = 1k\Omega \parallel \frac{1}{2mS} = 11k\Omega \parallel 0.5k\Omega$$

$$Req = 333.33\Omega$$

$$f_{hs} = \frac{1}{2\pi (333.33)(2\mu F)} = 238.73117$$

Since, f_{hs} is the largest of the three cutoff frequencies, it defines the low cutoff frequency for the network.

(b) The midband gain of the system is determined by

$$A_v(\text{mid}) = \frac{V_o}{V_i} = -g_m(R_D \parallel R_L)$$

$$= -2mS(4.7k\Omega \parallel 2.2k\Omega)$$

$$A_v(\text{mid}) = -3$$

Internal capacitive effects and the high-frequency Model of the MOSFET and the BJT:

→ While coupling and bypass capacitors cause the gain of transistor amplifiers to fall at the low frequency end, the gain falloff at high frequency is caused by the capacitive effects internal to the transistors.

→ In this section we shall briefly consider these effects and, more importantly, show how the device small-signal model can be augmented to take these effects into account.

MOSFET: From physical operation of the MOSFET, we know that the device has internal capacitances

→ We used one of these, gate-to-channel capacitance, in our derivation of the MOSFET $i-v$ characteristics.

We did, however, implicitly assume that the steady-state charges on these capacitances are acquired instantaneously.

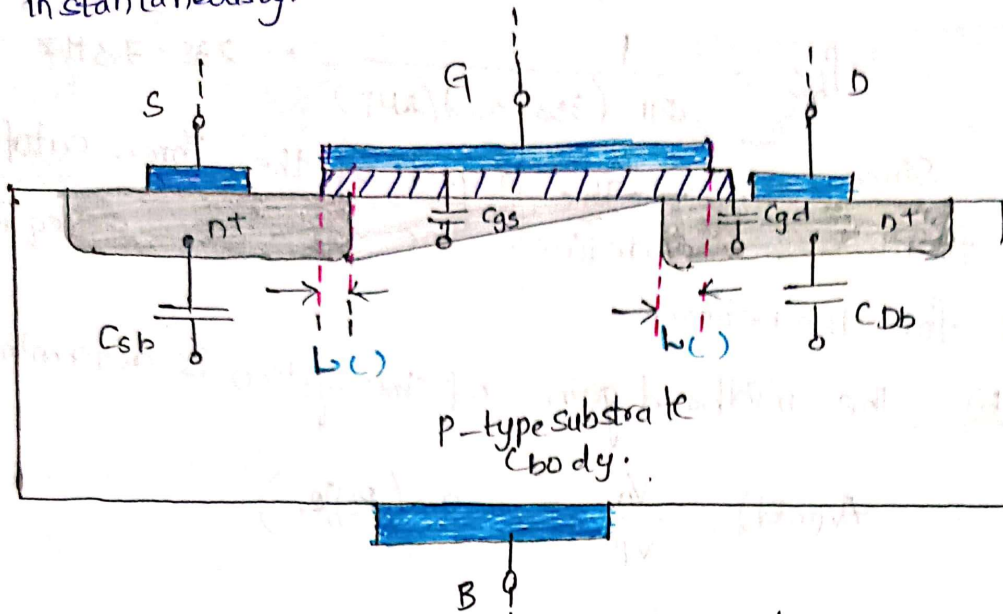


Fig: A cross section of the n-channel MOSFET operating in the saturation region. The four internal capacitances - C_{gs} , C_{gd} , C_{sb} , C_{db} are indicated.

Note: The bias voltage are not shown. Also not shown that to keep the diagram simple, is the depletion region.

→ Fig: shows the cross section of an n-channel MOSFET operating in the saturation region, as signified by the tapered n-channel that is pinched off at the drain end.

→ There are four internal capacitances:

1) Two of these C_{gs} and C_{gd} , result from the gate-capacitance effect.

2) The other, C_{sb} , C_{db} are the depletion capacitances of the pn junctions formed by the source region and the substrate, and the drain region and the

Low frequency Response of MOSFET (or) CS Amplifier.

→ The analysis of the MOSFET amplifier in the low-

substrate respectively.

→ The gate-capacitive effect means that, the polysilicon gate forms a parallel-plate capacitor with the channel region, with the oxide layer serving as the capacitor dielectric.

→ The gate (or) oxide capacitance per unit gate area is denoted C_{ox} .

→ When the channel is tapered and pinched off the gate capacitance is given by $\frac{2}{3} W L C_{ox}$.

→ In addition to this capacitance there are two other small capacitances resulting from the overlap of the gate with the source region (or source diffusion) and the drain region (or drain diffusion).

→ Each of these overlaps has a length l_{ov} and thus the resulting overlap capacitances C_{ov} are given by

$$C_{ov} = W l_{ov} C_{ox}$$

Typically $l_{ov} = 0.05$ to $0.1 W$.

→ We can express the gate-source capacitance

$$C_{gs} \text{ as } \boxed{C_{gs} = \frac{2}{3} W L C_{ox} + C_{ov}}$$

→ For the gate-to-drain capacitance, we note that the channel pinch-off at the drain end causes C_{gd} to consist entirely on the overlap component C_{ov} . $\boxed{C_{gd} = C_{ov}}$

→ The depletion layer capacitances of the two reverse-biased pn junctions formed b/w each of the source and the drain diffusions and the p-type substrate (body) can be determined and the source-body capacitance, (C_{sb})

$$C_{sb} = \frac{C_{sb0}}{\sqrt{1 + \frac{V_{SB}}{V_0}}}$$

C_{sb0} = value of C_{sb} at zero body-source bias.

V_{SB} = Magnitude of Reverse-bias Voltage.

V_0 = Junction built-in voltage (0.6V to 0.8V)

Similarly, for the drain diffusion, we have the drain-body capacitance

$$C_{db} = \frac{C_{db0}}{\sqrt{1 + \frac{V_{DB}}{V_0}}}$$

C_{db0} = capacitance value at zero reverse-bias voltage

V_{DB} = Magnitude of the reverse bias voltage.

Note: we have assumed that for both junctions,

the grading coefficient $m = \frac{1}{2}$

P: For an n-channel MOSFET with $t_{ox} = 10\text{nm}$, $h = 1\mu\text{m}$

$W = 10\mu\text{m}$, $h_{ov} = 0.05\mu\text{m}$, $C_{sb0} = C_{db0} = 10\text{fF}$, $V_0 = 0.6\text{V}$

$V_{SB} = 1\text{V}$, and $V_{DS} = 2\text{V}$, calculate the following capacitances when the transistor is operating in saturation: C_{ox} , C_{ov} , C_{gs} , C_{gd} , C_{sb} and C_{db} ?

Given: $C_{ox} = \frac{\epsilon_{ox}}{t_{ox}}$
 ϵ_{ox} is permittivity of the silicon dioxide.

$$\epsilon_{ox} = 3.9\epsilon_0 = 3.9 \times 8.854 \times 10^{-12} = 3.45 \times 10^{-11} \text{ F/m}$$

$$C_{ox} = \epsilon_{ox} / t_{ox} = \frac{3.45 \times 10^{-11} \text{ F/m}}{10 \text{ nm}} = 3.45 \text{ fF}/\mu\text{m}^2$$


$$C_{ov} = W_{ov} C_{ox} = 10 \mu\text{m} \times 1.0 \mu\text{m} \times 3.45 \text{ fF}/\mu\text{m}^2$$

$$C_{ov} =$$

$$C_{gs} = \frac{2}{3} W L C_{ox} + C_{ov}$$


High-Frequency MOSFET Model

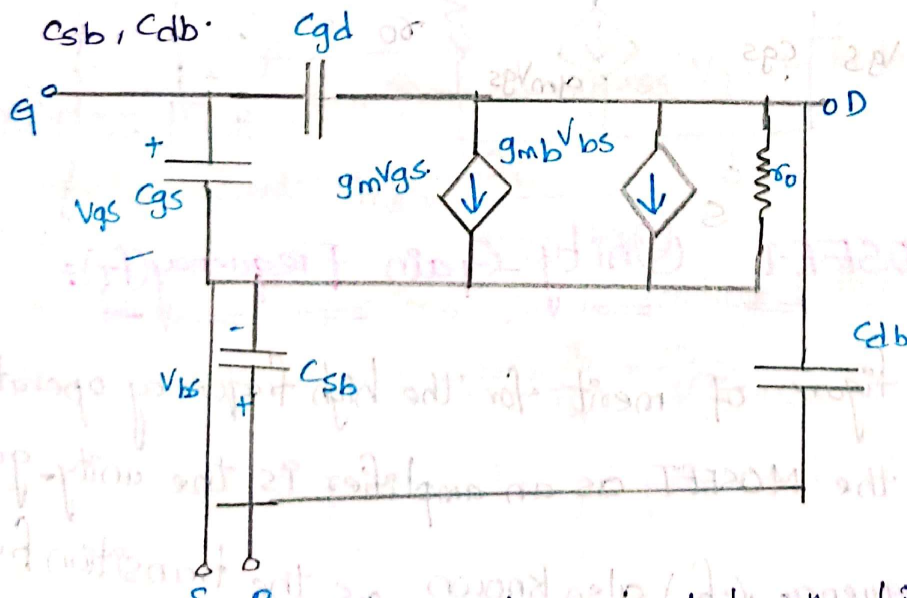* The below figure shows the small-signal model of the MOSFET, including the four capacitances C_{gs} , C_{gd} , C_{sb} , C_{db} .




→ This model can be used to predict the high-frequency response of MOSFET amplifiers. It is, however, quite complex for manual analysis, and its use is limited to computer simulation using SPICE.

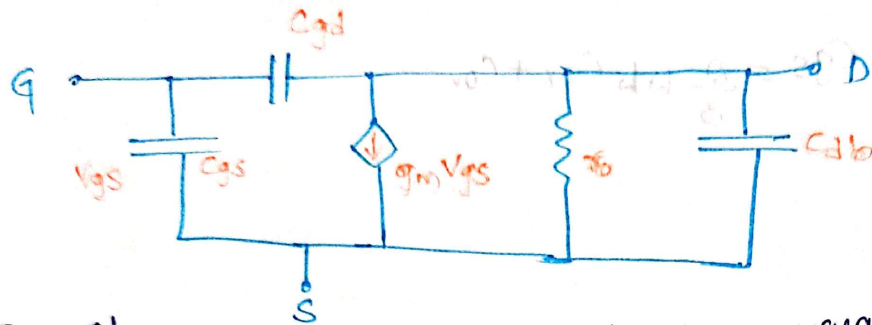⇒ Fortunately, when the source is connected to the body, the model simplifies considerably, as shown in below fig. In this model, C_{gd} , although small, plays a significant role in determining the high-frequency response of amplifiers and thus must be kept in model.



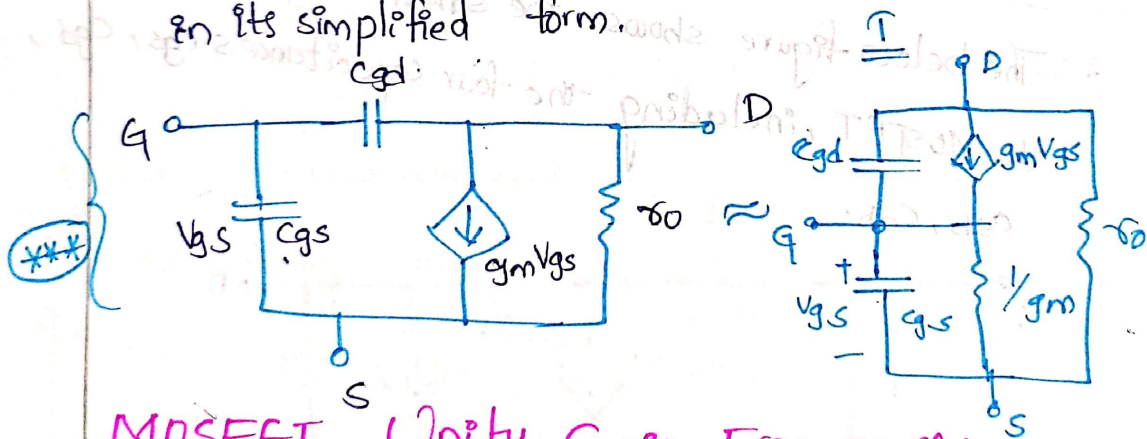⇒ Capacitance C_{db} , on the other hand, can usually be neglected, resulting in significant simplification of manual analysis. The resulting circuit is shown in below fig. Finally, we show in fig. the high-frequency (τ) model in its simplified form.




MOSFET Unity Gain Frequency (f_T):

⇒ A figure of merit for the high frequency operation of the MOSFET as an amplifier is the unity-gain frequency, (f_T) also known as the transition frequency, which gives rise to the subscript (τ).

⇒ It is defined as the frequency at which the short-circuit current gain of the common-source configuration becomes unity.

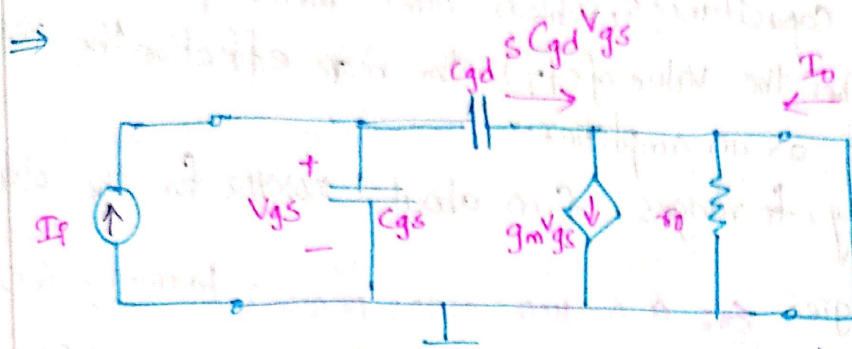⇒ The below figure shows the MOSFET hybrid π model with the source as the common terminal b/n the i/p and o/p ports.



⇒ To determine the short-circuit current gain, the i/p is i_i with a current-source signal I_i and the o/p terminals are short-circuited. It can be seen that the current in the short circuit is given by

$$I_o = g_m V_{gs} - s C_{gd} V_{gs}$$

⇒ Recalling that C_{gd} is small, at the frequencies of interest we can neglect the second term in this equation.

$$I_o = g_m V_{gs}$$

⇒ From above figure, we can express V_{gs} in terms of

$$\text{the i/p current } V_{gs} = \frac{I_i}{s(C_{gs} + C_{gd})}$$

⇒ The above two equations can be combined to obtain the short-circuit current gain $\frac{I_o}{I_i} = \frac{g_m}{s(C_{gs} + C_{gd})}$.


⇒ For physical frequencies $s = j\omega$, it can be seen that the magnitude of the current gain

$$\left| \frac{I_o}{I_i} \right| = \frac{g_m}{\omega(C_{gs} + C_{gd})}$$

⇒ It becomes unity at the frequency $\omega_T = g_m / (C_{gs} + C_{gd})$

∴ Unity-gain frequency (f_T) = $\omega_T / 2\pi$ Hz
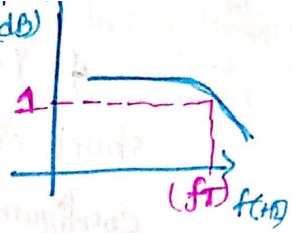
$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$



⇒ f_T is proportional to g_m , which determines the mid band gain, and inversely proportional to the MOSFET internal capacitances, which limit the amplifier bandwidth, the higher the value of (f_T), the more effective the MOSFET becomes as an amplifier.

⇒ Typically, f_T ranges from about 100 MHz for the older technologies (e.g. 5- μm CMOS process) to many GHz for newer high-speed technologies (e.g. a 0.13- μm CMOS process).

High Frequency Model of BJT:

⇒ At low frequencies, we analyse the transistor using h-parameters, But for high frequencies the h-parameters model is not suitable for the following reasons:-

- 1) ⇒ Values of h-parameters are not constant at high frequencies.
- 2) h-parameter model is simple, and inaccurate because it neglects the early effect.

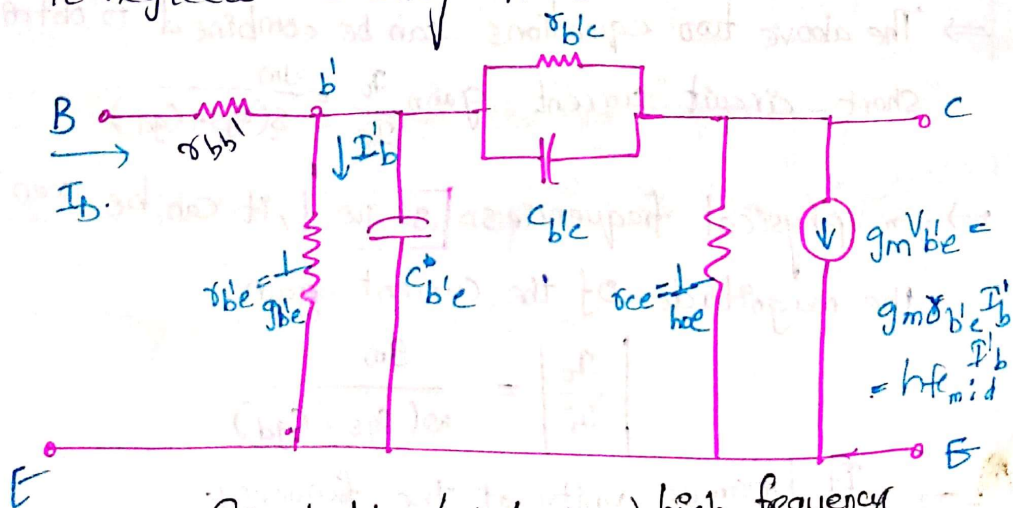


Fig. 2 Giacoletto (hybrid- π) high frequency transistor small-signal ac equivalent circuit

⇒ In above reasons hybrid- π model is used for the analysis of the reasonable compromise b/w accuracy and simplicity to do high frequency analysis of the transistor.

⇒ Analysis of circuits using this model are not too difficult and gives result which are in excellent at all frequencies for which the transistor gives reasonable amplification.

⇒ The below fig. shows the hybrid π model for a transistor in CE configuration. It is also called "Glaucotto model".

1) C_{be} = The capacitive effect of normally forward biased base-emitter junction of the transistor represented by C_{be} (or) C_e in the hybrid- π model. It is due to the diffusion capacitance of forward bias emitter diode. Its typical value is 100PF.

2) C_{bc} = The capacitive effect of normally reverse biased base collector junction of the transistor is represented by C_{bc} (or) C_c in the hybrid- π model. It is due to the transition capacitance of reverse bias collector diode. Its typical value is 3PF.

3) r_{be} = The resistive effect of normally forward biased base emitter junction of the transistor is represented by r_{be} in the hybrid- π model. This resistance is the portion of the base emitter which may be thought of as being "in series" with the collector junction. Its typical value is 1K Ω .

$r_{b'c}$:- The resistive effect of normally reverse biased base collector junction of the transistor is represented by $r_{b'c}$ in the hybrid- π model. This resistance is due to the early effect which is the varying voltage across the collector to emitter junction results in base width modulation. A change in ^{the effective} base width causes the emitter current to change. This feedback effect b/w output and input is taken by connecting $r_{b'c}$. Its typical value is $4M\Omega$.

$r_{bb'}$:- The resistance effect of bulk resistance b/w the external node 'B' and internal base node 'b'. This resistance is called base spreading resistance. Its typical value is 100Ω .

r_{ce} :- The resistance effect of o/p terminals is represented by r_{ce} in hybrid- π model. It is also due to the early effect. Its typical value is $80k\Omega$.

$g_m V_{be}$:- Due to small changes in voltage V_{be} across the emitter junction, there is excess minority carrier concentration injected into the base which is proportional to the V_{be} . Therefore resulting small signal current is proportional to V_{be} . This effect accounts for the current generator $g_m V_{be}$, where g_m is called transconductance. Its typical value is $50mS$.


Determination of hybrid- π parameters:

→ Let us consider, for a given collector current the conductances and resistances of the hybrid- π parameters can be calculated from the low frequency h-parameter values in the CE configuration.

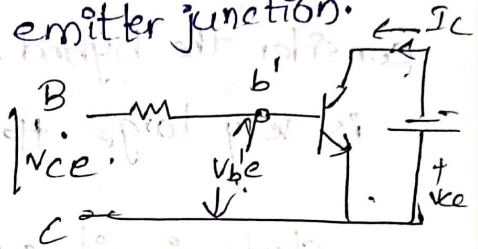1) Transistor transconductance (g_m) :- Let us consider, a n-p-n transistor in the CE configuration with V_{CC} bias in the collector circuit.

→ Transconductance is the ratio of the change in the voltage ($V_{b'e}$) across the emitter junction.

$$g_m = \frac{\Delta I_C}{\Delta V_{b'e}}$$



We know that $I_C = \alpha I_E$

$$g_m = \frac{\Delta \alpha I_E}{\Delta V_{b'e}}$$

$$g_m = \alpha \frac{\Delta I_E}{\Delta V_{b'e}}$$

From fig: $V_{b'e} \approx V_e$

$$= \alpha \frac{\Delta I_E}{\Delta V_e}$$

$$g_m = \frac{\alpha}{r_e}$$

$$\frac{1}{r} = I \quad r = \frac{V}{I}$$

$$\frac{1}{r} = \frac{I}{V}$$

→ The emitter diode is forward biased diode and its dynamic resistance is given as $r_e = \frac{V_T}{I_E}$


$$g_m = \alpha \frac{I_E}{V_T} = \frac{I_C}{V_T}$$

At room temp;

$$g_m = \frac{I_C}{26 \text{ mV}}$$

Input Conductance ($g_{b'e}$) :- From figures of hybrid- π model

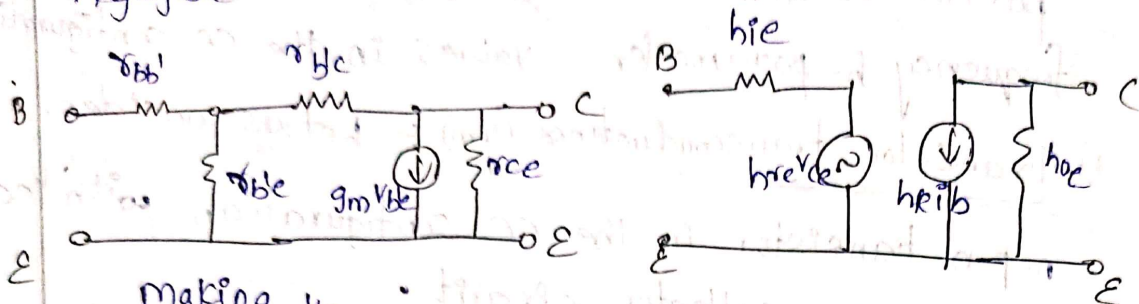At and the h-parameters model for CE configuration at low frequency. At low frequency all capacitors are negligible.



Making $v_{c'e} \Rightarrow$

$$\Rightarrow h_{f'e} = \frac{I_c}{I_b} \quad \left[I_c = h_{f'e} I_b + h_{o'e} V_{c'e} \right]$$

Consider the hybrid- π model for CE configuration, $r_{b'e}$

is very large. Hence I_b flows in $r_{b'e}$, then $V_{b'e} = I_b r_{b'e}$

short circuit current gain is given by

$$I_c = g_m V_{b'e} = g_m I_b r_{b'e}$$

$$\frac{I_c}{I_b} = g_m r_{b'e}$$

$$\Rightarrow r_{b'e} = \frac{h_{f'e}}{g_m} \quad \text{and} \quad g_{b'e} = \frac{g_m}{h_{f'e}} \quad \left[\because g_{b'e} = \frac{1}{r_{b'e}} \right]$$

Feedback Conductance $g_{b'c}$:- From h-parameter model,

for CE configuration with i/p open circuit

$$I_b = 0, V_i = h_{r'e} V_{c'e} \Rightarrow h_{r'e} = \frac{V_{b'e}}{V_{c'e}}$$

For hybrid- π model for CE configuration with i/p open circuit, $I_b = 0$

$$h_{r'e} = \frac{V_{b'e}}{V_{c'e}} = \frac{I_b r_{b'e}}{I_b (r_{b'e} + r_{b'c})}$$

$$h_{re} = \frac{r_{b'e}}{r_{b'e} + r_{b'c}}$$

$$r_{b'e} = h_{re} r_{b'c} + h_{re} r_{b'e}$$

$$(1 - h_{re}) r_{b'e} = h_{re} r_{b'c}$$

$$r_{b'c} = \frac{(1 - h_{re}) r_{b'e}}{h_{re}}$$

$$r_{b'c} = \frac{r_{b'e}}{h_{re}}$$

$$(1 - h_{re} \ll 1)$$

then

$$g_{b'c} = \frac{h_{re}}{r_{b'e}} = h_{re} \cdot g_{b'e}$$

$$\therefore r_{b'c} = \frac{1}{g_{b'c}}$$

Base Spreading Resistance ($r_{bb'}$) - The input resistance with output shorted ($V_{ce} = 0$) is h_{ie} with hybrid- π model, input resistance with output shorted, is $r_{bb'} + r_{b'e}$

$$\therefore h_{ie} = r_{bb'} + r_{b'e}$$

$$r_{bb'} = h_{ie} - r_{b'e}$$

$$r_{bb'} = h_{ie} - \frac{h_{fe}}{g_m}$$

Output Conductance (g_{ce}) - Using h-parameters the output conductance is given as $h_{oe} = \frac{I_c}{V_{ce}}$

consider hybrid- π model for CE configuration,

$$I_c = \frac{V_{ce}}{r_{ce}} + g_m V_{b'e} + \frac{V_{ce}}{r_{b'e} + r_{b'c}}$$

$$\therefore I_c = \frac{V_{ce}}{r_{ce}} + g_m \left[\frac{V_{ce} \cdot r_{b'e}}{r_{b'c} + r_{b'e}} \right] + \frac{V_{ce}}{r_{b'e} + r_{b'c}} \quad \left. \begin{array}{l} V_{b'e} = \frac{V_{ce} \cdot r_{b'e}}{r_{b'e} + r_{b'c}} \end{array} \right\}$$

$$\frac{I_c}{V_{ce}} = \frac{1}{r_{ce}} + \frac{g_m r_{b'e}}{r_{b'c} + r_{b'e}} + \frac{1}{r_{b'e} + r_{b'c}} \quad \left\{ \begin{array}{l} r_{b'e} = \frac{h_{fe}}{g_m} \\ h_{fe} = g_m r_{b'e} \end{array} \right.$$

$$\frac{I_c}{V_{ce}} = \frac{1}{r_{ce}} + \frac{h_{fe}}{r_{b'c} + r_{b'e}} + \frac{1}{r_{b'e} + r_{b'c}}$$

$$\frac{I_c}{V_{ce}} = \frac{1}{r_{ce}} + \frac{(1+h_{fe})}{r_{b'c} + r_{b'e}}$$

$\underbrace{\hspace{10em}}_{hoe}$

$$hoe = \frac{1}{r_{ce}} + \frac{(1+h_{fe})}{r_{b'c} + r_{b'e}}$$

$$\frac{1}{r_{ce}} = hoe - \left[\frac{1+h_{fe}}{r_{b'c} + r_{b'e}} \right]$$

$$\left(r_{b'c} \gg r_{b'e} \right)$$

$$\frac{1}{r_{ce}} = hoe - \left[\frac{1+h_{fe}}{r_{b'c}} \right]$$

$$\frac{1}{r_{ce}} = hoe - (1+h_{fe})g_{b'c}$$

$$\frac{1}{r_{ce}} = hoe - h_{fe}g_{b'c}$$

$$\left(h_{fe} \gg 1 \right)$$

$$\boxed{g_{ce} = hoe - h_{fe}g_{b'c}}$$

Summary: The relationship b/w low frequency h-parameters and high frequency hybrid- π parameters are

1) $g_m = \frac{I_c}{V_T}$

2) $r_{b'e} = \frac{h_{fe}}{g_m}$ & $g_{b'e} = \frac{g_m}{h_{fe}}$

3) $r_{b'c} = \frac{r_{b'e}}{h_{re}}$ & $g_{b'c} = \frac{h_{re}}{r_{b'e}} = h_{re}g_{b'e}$

4) $r_{bb'} = h_{ie} - r_{b'e} = h_{ie} - \frac{h_{fe}}{g_m}$

5) $\frac{1}{r_{ce}} = g_{ce} = hoe - h_{fe}g_{b'c}$

CE Short Circuit Current gain

Consider a single stage CE transistor amplifier with load resistor (R_L) as shown in figure.


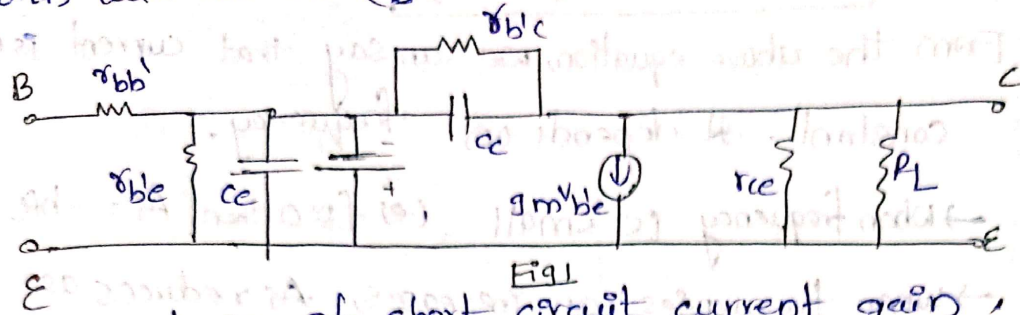


Fig 1

For the analysis of short circuit current gain, assume $R_L = 0$ with $R_L = \infty$, the o/p short circuited r_{cc} becomes zero, v_{be} , C_c and C_e appears in parallel.

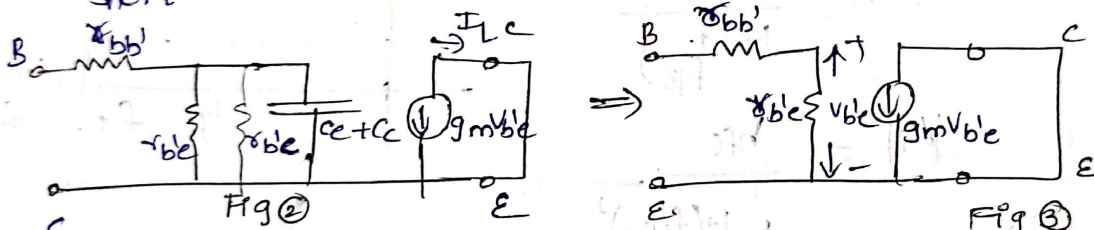→ As $r_{b'e} \gg r_{b'e}$, $v_{b'e}$ is neglected. With these approximation we get simplified hybrid- π model for short circuit CE transistor as shown in fig.



parallel combination of $r_{b'e}$ and $C_e + C_c$ is

$$Z = \frac{r_{b'e} \times \frac{1}{j\omega(C_e + C_c)}}{r_{b'e} + \frac{1}{j\omega(C_e + C_c)}} = \frac{r_{b'e}}{1 + j\omega r_{b'e}(C_e + C_c)}$$

From fig 3;

$$\text{We can write, } V_{b'e} = I_b Z \Rightarrow Z = \frac{V_{b'e}}{I_b}$$

The short circuit current gain is given by

$$A_I = \frac{I_c}{I_b} = \frac{-g_m V_{b'e}}{I_b}$$

$$= -g_m(Z)$$

$$= -g_m \left[\frac{r_{b'e}}{1 + j\omega(r_{b'e}(C_e + C_c))} \right]$$

We know that $h_{fe} = g_m \beta h'_e$

$$A_i = \frac{-h_{fe}}{1 + j\omega \beta h'_e (C_e + C_c)}$$

From the above equation, we can say that current is not constant. It depends on frequency.

→ When frequency is small (i.e) $f \ll 0$ then $A_i = -h_{fe}$

→ When frequencies are increases, A_i reduces as shown in fig.


In above (A) equation, let us substitute.

$$f_\beta = \frac{1}{2\pi \beta h'_e (C_e + C_c)}$$

then

$$A_i = \frac{-h_{fe}}{1 + j \frac{f}{f_\beta}}$$

$$|A_i| = \frac{h_{fe}}{\sqrt{1 + (f/f_\beta)^2}}$$

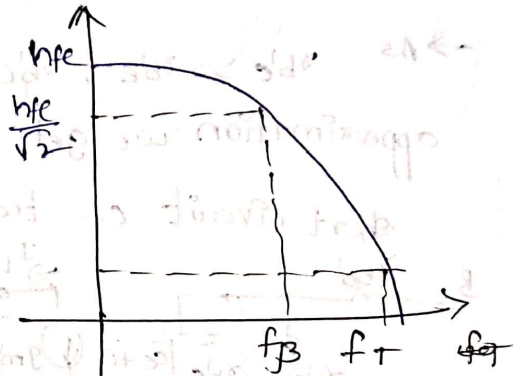

At $f = f_\beta$

$$|A_i| = \frac{h_{fe}}{\sqrt{2}}$$

Gain Bandwidth product :- It is the frequency at which the short circuit (CE) current gain becomes unity.

At $f = f_T$ and $A_i = 1$ then eqn $A_i = \frac{h_{fe}}{\sqrt{1 + (f/f_\beta)^2}}$

$$1 = \frac{h_{fe}}{\sqrt{1 + (f_T/f_\beta)^2}}$$

The ratio f_T/f_β is very large [$f_T/f_\beta = f_T/f_\beta$]

$$1 = \frac{h_{fe}}{f_T/f_\beta}$$

$$1 = \frac{h_{fe} \cdot f_\beta}{f_T}$$

$$f_T = h_{fe} f_\beta$$

$$f_T = h_{fe} \left[\frac{g_{b'e}}{2\pi (C_e + C_c)} \right]$$

$$= \frac{h_{fe} g_m}{h_{fe} 2\pi (C_e + C_c)}$$

$$= \frac{g_m}{2\pi (C_e + C_c)}$$

$$\left. \begin{array}{l} g_{b'e} = g_m \\ h_{fe} \end{array} \right\}$$

$$f_T = \frac{g_m}{2\pi (C_e + C_c)}$$

Since $C_e \gg C_c$ then

$$f_T = \frac{g_m}{2\pi C_e}$$

$$\Rightarrow \boxed{C_e = \frac{g_m}{2\pi f_T}}$$

similarly,

$$\boxed{C_c = \frac{g_m}{2\pi f_T}}$$

P At $I_c = 1\text{mA}$, and $V_{ce} = 10\text{V}$, a certain transistor data shows $C_c = C_{b'c} = 3\text{pF}$, $h_{fe} = 200$, $\omega_T = 500\text{Mrad/sec}$. Calculate g_m , $r_{b'e}$, $C_e = C_{b'e}$ and ω_β ?

$$1) \quad g_m = \frac{I_c}{V_T} = \frac{1\text{mA}}{26\text{mV}} = 38.46\text{mA/V}$$

2)

$$r_{b'e} = \frac{h_{fe}}{g_m} = \frac{200}{38.46\text{mA/V}} = 5.2\text{k}\Omega$$

$$3) \quad f_T = \frac{g_m}{2\pi (C_e + C_c)} \Rightarrow (C_e + C_c) = \frac{g_m}{2\pi f_T} = \frac{g_m}{\omega_T}$$

$$C_e + C_c = 76.92\text{pF}$$

$$\therefore \omega_T = \frac{g_m}{C_e + C_c}$$

$$C_e + C_c = 76.92\text{pF}$$

$$C_e = 76.92\text{pF} - 3\text{pF}$$

$$C_e = 73.92\text{pF}$$

$$4) f_T = h_{fe} f_{\beta}$$

$$\omega_T = h_{fe} \omega_{\beta}$$

$$\omega_T = h_{fe} \omega_{\beta}$$

$$\omega_{\beta} = \frac{\omega_T}{h_{fe}} = \frac{500 \mu \text{ rad/sec}}{200} = 2.5 \mu \text{ rad/sec.}$$

2) Short circuit CE current gain of transistor is 25 at a frequency of 2 MHz. If $f_{\beta} = 200 \text{ kHz}$. Calculate f_T , h_{fe} and A_i at frequency of 10 MHz and 100 MHz.

$$1) f_T = A_i \times f = 25 \times 2 \times 10^6 = 50 \text{ MHz}$$

$$2) h_{fe} = \frac{f_T}{f_{\beta}} = \frac{50 \text{ MHz}}{200 \text{ kHz}} = 250$$

3) We know that $A_i = \frac{h_{fe}}{\sqrt{1 + (f/f_{\beta})^2}}$

$$\text{at } f = 10 \text{ MHz, } A_i = \frac{250}{\sqrt{1 + (10 \text{ MHz}/200 \text{ kHz})^2}}$$

$$A_i = \frac{250}{\sqrt{1 + 2500}} = \frac{250}{\sqrt{2501}}$$

$$A_i = 4.999 \approx 5$$

$$\text{at } f = 100 \text{ MHz, } A_i = \frac{250}{\sqrt{1 + (100 \text{ MHz}/200 \text{ kHz})^2}}$$

$$= \frac{250}{\sqrt{1 + 250000}}$$

$$= \frac{250}{\sqrt{250001}}$$

$$= 0.4999$$

$$\hat{A}_i \approx 0.5$$

High Frequency Response - BJT Amplifiers

⇒ At the high frequency end, there are two factors that will define the -3dB point; the network capacitance (parasitic & introduced) and the frequency dependence of $h_{fe}()$.

⇒ In the high-frequency region, the RC network of concern has the configuration appearing in fig 11.42. At increasing frequencies, the reactance (X_c) will decrease in magnitude, resulting in a shorting effect across the o/p and a decrease in gain.

⇒ The deviation leading to the corner frequency for this RC configuration follows along similar lines to that encountered for the low-frequency region. The most significant difference is in the general form of A_v , as belows-

$$A_v = \frac{1}{1 + j(f/f_2)}$$

where $f_2 = 1/2\pi RC$

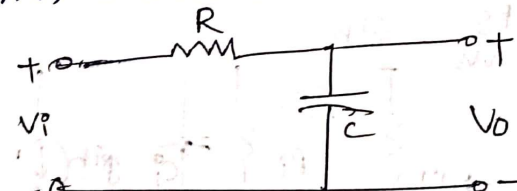


Fig 11.42: R-C combination that will define a high cutoff frequency.


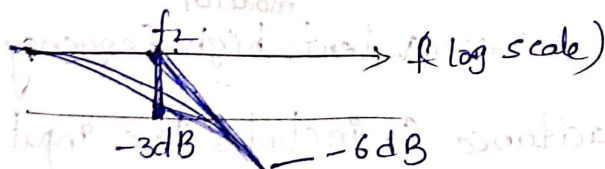


Fig 11.43: Asymptotic plot as (11:43).

⇒ In fig 11:44, the various parasitic capacitances (C_{be} , C_{bc} , C_{ce}) of the transistor have been included and the wiring capacitances (C_{wi} , C_{wo}) introduced during construction.

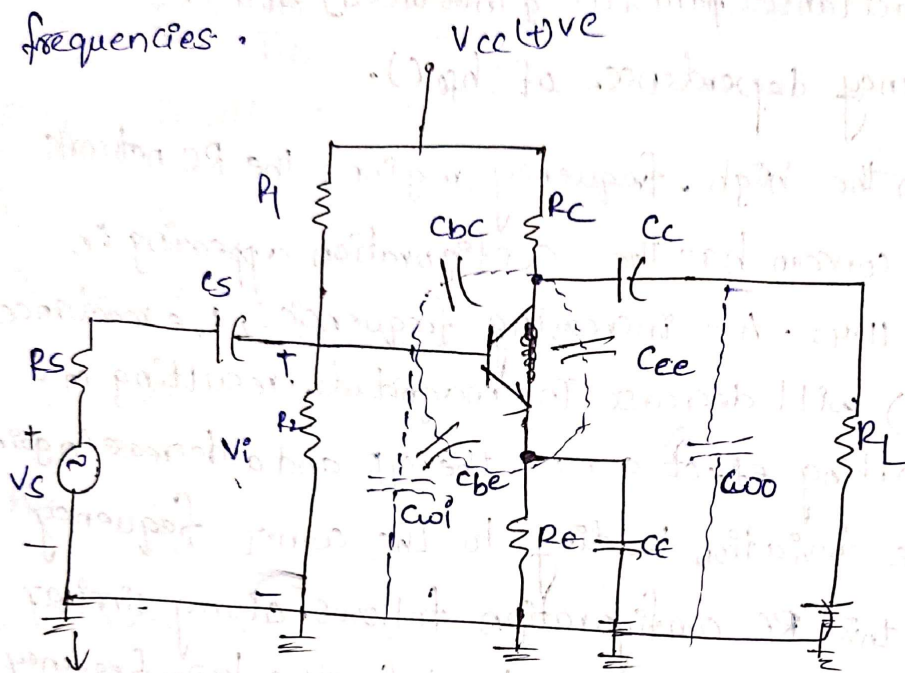→ The high frequency equivalent model for the network of Fig. 11.44 appears in (Fig. 11.45). Note the absence of the capacitors (C_{s1} , C_{c1} , C_e), which are all assumed to be in the short-circuit state at these frequencies.



$C_i = C_{w0} + C_{be} + C_{M1}$; $C_o = C_{w0} + C_{ce} + C_{M2}$
Fig 11.44 Capacitors that affect the high-frequency response

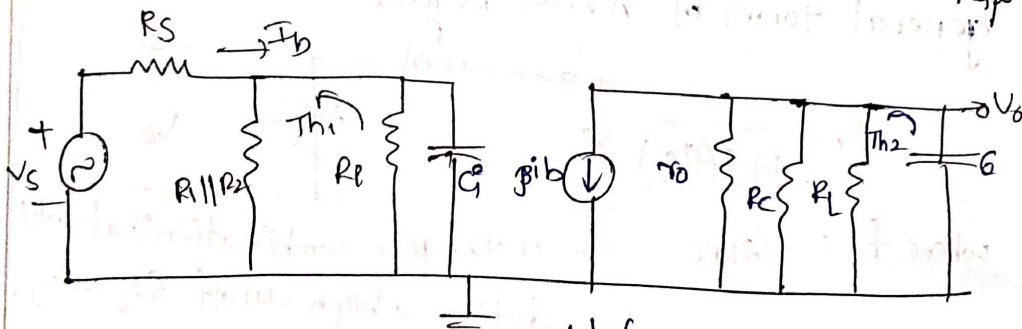



Fig 11.45 model of AC equivalent high-frequency response

→ The capacitance C_i includes the input wiring capacitance C_{w0} , the transition capacitance C_{be} , and Miller capacitance C_{M1} . The capacitance C_o includes the o/p wiring capacitance, C_{w0} , the parasitic capacitance C_{ce} and the o/p Miller capacitance C_{M2} .

⇒ In general, the capacitance C_{be} is the largest of the parasitic capacitances, with C_{ce} the smallest. In fact, most specification sheets simply provide the levels of C_{be} and C_{bc} and do not include C_{ce} unless it will affect the response of a particular type of transistor in a specific area of application.

→ Determining the Thevenin's equivalent circuit for the i/p and o/p networks Fig 11.45 will result in the configurations of Fig 11.46.

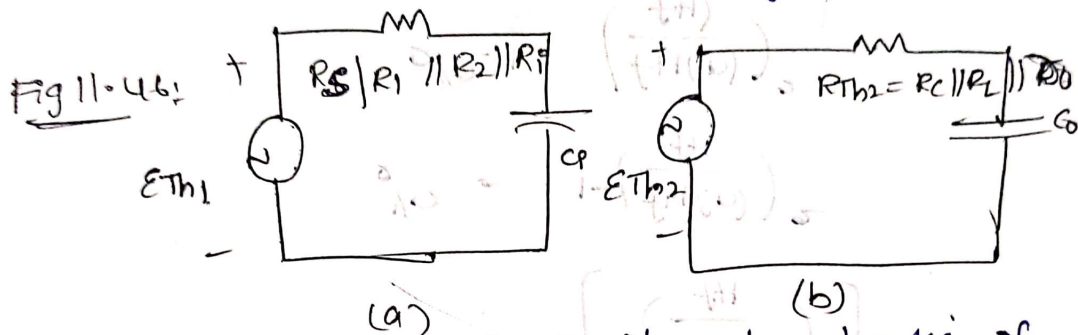→ For the i/p network, the 3-dB frequency is defined by



Thevenin circuits for the i/p & o/p networks of the network in Fig 11.45.

$$f_{HI} = \frac{1}{2\pi R_{Th1} C_i}$$

$$R_{Th1} = R_S \parallel R_1 \parallel R_2 \parallel R_i$$

$$C_i = C_{wi} + C_{be} + C_{MP} = C_{wi} + C_{be} + (1 - A_v) C_{bc}$$


For o/p Network:

$$f_{HO} = \frac{1}{2\pi R_{Th2} C_o}$$

Verified

$$R_{Th2} = R_c \parallel R_L \parallel R_o$$

$$C_o = C_{wo} + C_{ce} + C_{Mo}$$

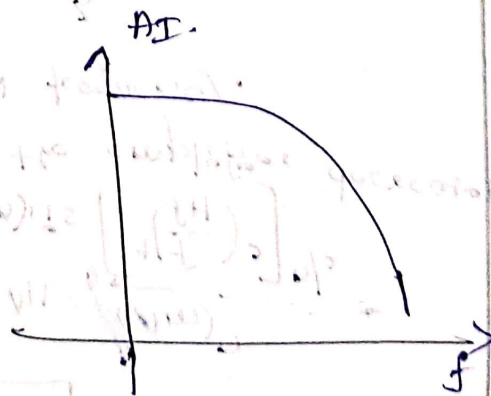

A. FEEDBACK AMPLIFIERS

⇒ We know that input impedance, current gain, voltage gain, Output impedance and bandwidth are some of the important characteristics of an amplifier.

⇒ These characteristics are not constant for an amplifier.

Drawback of single stage amplifier: ⇒ As these characteristics are not constant we can observe in single stage amplifiers, gains are not sufficient and there is a mismatch in Z_{in} and Z_o .

⇒ These drawbacks of single stage amplifier is overcome in multistage amplifiers.


Drawback of Multi stage amplifier: ⇒ In multistage amplifiers, the gain increases but at the same time, the circuit provides instability (& Bandwidth is decrease) to overcome above problem we go for feedback amplifiers.

⇒ Feedback plays an important role in almost all electronic circuits

⇒ It is used to improve the performance and to make it more ideal.

Feedback means, process of combining a fraction of output back to the input.

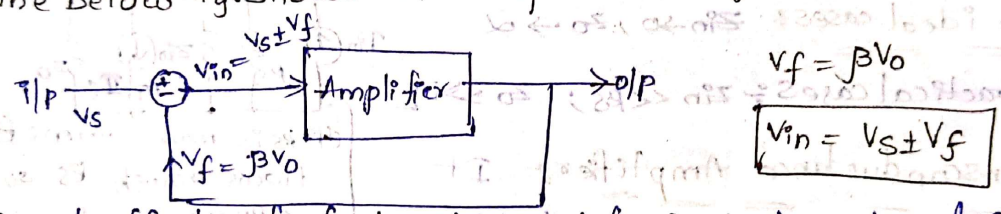2 types ⇒ The below fig. shows the simple block diagram of feedback amplifier



① If, net effect of feedback (amplifier) signal is to reduce the magnitude of input signal, then it is called (-ve or) inverse (or) Degenerative feedback. i.e. $V_{in} = V_s - V_f$ (or) $I_{in} = I_s - I_f$

② If, net effect of feedback signal is to increase the magnitude of input signal then it is called (+ve or) Direct (or) Regenerative feedback. i.e. $V_{in} = V_s + V_f$ (or) $I_{in} = I_s + I_f$

⇒ Negative feedback reduces the gain of the amplifier, but it has the following advantages:-

- 1) stabilisation of gain
- 2) Reduction in distortion
- 3) Reduction in Noise
- 4) change in i/p & o/p impedances.
- 5) Increases the bandwidth (Range of Uniform amplification).

⇒ Positive feedback increases the gain of the amplifier, but it has following disadvantages:

- 1) It provides instability.
- 2) It increases the Noise

Due to this disadvantages positive feedback is not used in amplifier but it is used in oscillator circuit to produce oscillations.

Classification of Amplifiers:

Before proceeding with the concept of feedback it is necessary to understand the classification of amplifiers based on the magnitude of the input and output impedances of an amplifier relative to the source and load resistor (R_L)

Based on this, amplifiers are classified into four types.

- 1) Voltage Amplifier
- 2) Current Amplifier
- 3) Transconductance amplifier
- 4) Transresistance amplifier

Voltage Amplifier: It produces output voltage \propto (proportional) to input voltage


$$V_o \propto V_{in} \Rightarrow V_o = A_v V_{in}$$

here for ideal case:

$$A_v = \frac{V_o}{V_{in}}$$

For practical, $Z_{in} \gg R_s$; $Z_o \ll R_L$

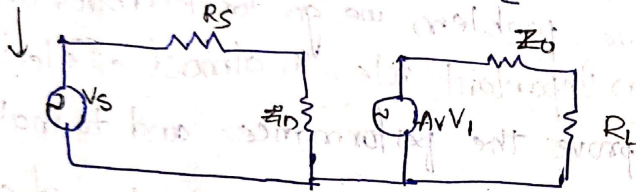If Z_o is high it will drop at R_L if Z_{in} is small it will drop at R_s (source)




Current Amplifier: It produces output current proportional to input current i.e., $I_o \propto I_{in} \Rightarrow I_o = A_i I_{in}$

$$A_i = \frac{I_o}{I_{in}}$$

For ideal cases: $Z_{in} \rightarrow 0$, $Z_o \rightarrow \infty$

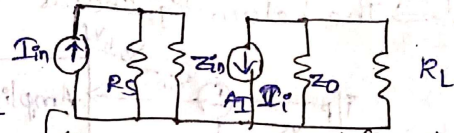practical cases: $Z_{in} \ll R_s$; $Z_o \gg R_L$




If R_s is more current flows through R_s so Z_{in} is $<$ to allow current to input voltage.

Transconductance Amplifier: It produces output current I_o proportional to input voltage.

$$I_o \propto V_{in} \Rightarrow I_o = G_m V_{in} \Rightarrow G_m = \frac{I_o}{V_i}$$

For ideal cases: $Z_{in} = Z_o \rightarrow \infty$

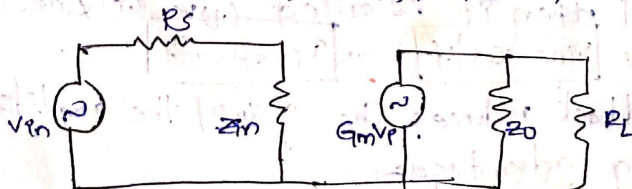
For practical cases: $Z_{in} \gg R_s$; $Z_o \gg R_L$




Transresistance amplifier: It produces output voltage V_o proportional to input current $I_o \propto I_{in} \Rightarrow V_o = R_m I_i \Rightarrow R_m = \frac{V_o}{I_i}$

For ideal cases: $Z_{in} \rightarrow 0$, $Z_o \rightarrow \infty$

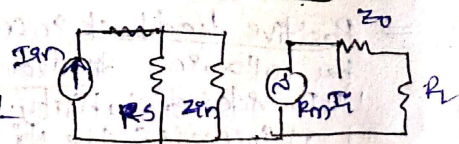practical cases: $Z_{in} \ll R_s$; $Z_o \ll R_L$



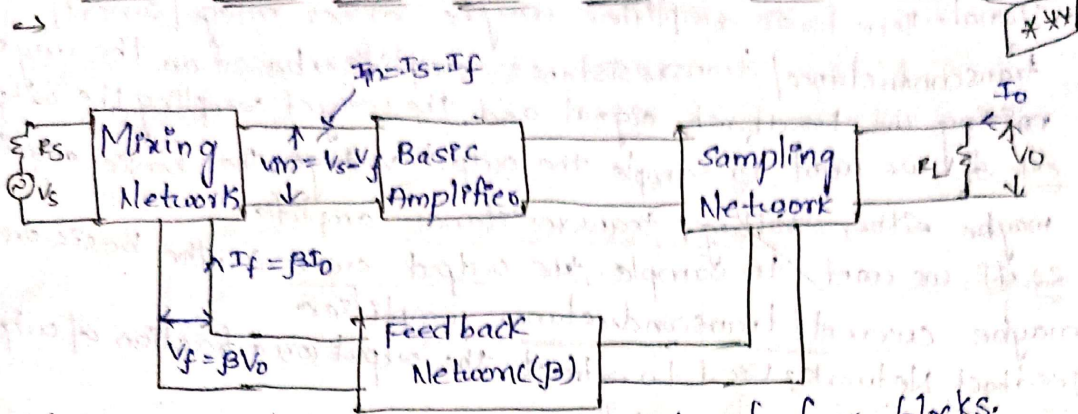BLOCK DIAGRAM OF NEGATIVE FEEDBACK AMPLIFIER



⇒ +ve FEEDBACK AMPLIFIER consists of four blocks.

Mixing Network: The purpose is to combine the feedback signal with the input signal.

⇒ Generally there are two ways of mixing the signal. They are:

- 1) Series Mixing
- 2) Shunt Mixing.

⇒ If the feedback signal is connected in series with V_s then it is called series mixing.

⇒ If the feedback signal is connected in shunt/parallel with V_s then it is called shunt mixing.

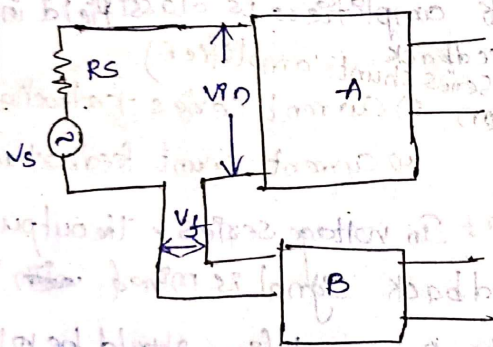


Fig: Series Mixing.

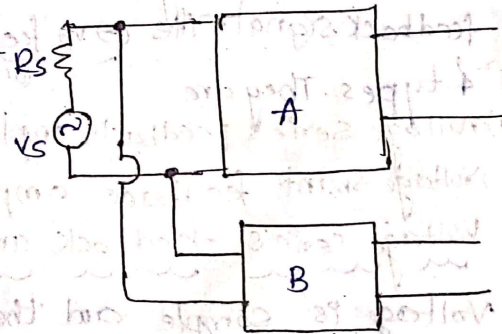



Fig: shunt Mixing.

Sampling Network: It is used to the way of sampling the output signal from the amplifiers.


⇒ Generally amplifier output is voltage (or) current.

⇒ If we want sample voltage the feedback network is connected in shunt/parallel with R_L (output), then it is called voltage sampler.

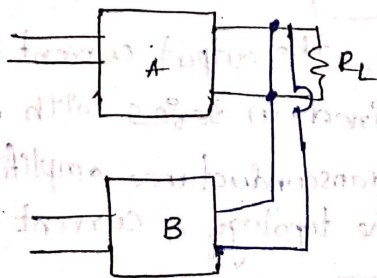⇒ If we want to sample output current the feedback network is connected in series with R_L (output), then it is called Current sampler.



Voltage Sampling.

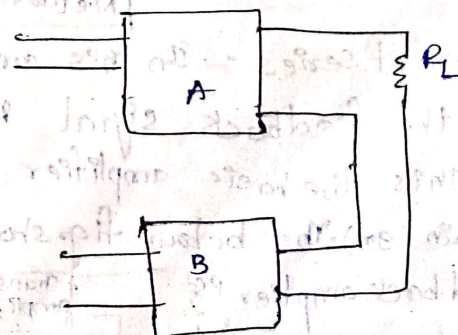

Current Sampling.

Basic Amplifiers - It is used to amplify (strengthen) the weak

signals. Here basic amplifier may be either voltage / current / transconductance / transresistance amplifier, based on the way of mixing the feedback signal and the way of sampling the output.

ex: If we want to sample the output voltage, then basic amplifier may be either voltage / transresistance amplifier

ex: If we want to sample the output current, the basic amplifier may be current / transconductance amplifier

Feedback Network - Used to extract the output (or a fraction of output) signal from basic amplifier.

Generally, it is a passive two port network, which consists of resistors, capacitors and inductors. (-)ve feedback, resistors whereas capacitors & inductors are used in (+)ve feedback, and it provides a reduced portion of output voltage and it can be represented as

$$X_f = \beta X_o$$

feedback $\rightarrow \beta$: Feedback Ratio


Classification of feedback Amplifiers - feedback factor: $(0-1) \times \beta$

Based on the way of sampling the output and mixing the feedback signal. The (-)ve feedback amplifiers is classified into 4 types. They are


- 1) voltage series feedback amplifier (Series shunt amplifier)
- 2) voltage shunt feedback amplifier (Shunt shunt amplifier)
- 3) current series feedback amplifier (Series series amplifier)
- 4) current shunt feedback amplifier (Shunt series amplifier)

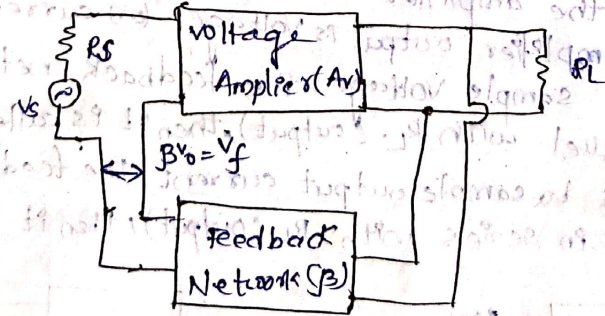1) Voltage series feedback amplifier - In voltage series, the output voltage is sampled and the feedback signal is mixed with in series with input. In this the basic amplifier should be voltage amplifier.


The below fig shows the Topology of voltage-series feedback amplifier



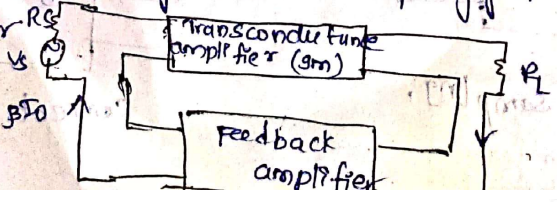
2) Current series - In this amplifier, the output current is sampled and the feedback signal is mixed in series with input. In this the basic amplifier is transconductance amplifier with gain (g_m). The below fig shows the topology of current series feedback amplifier



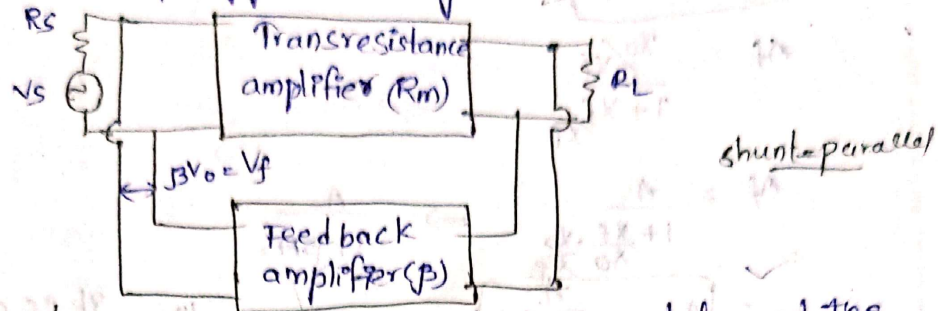3) Voltage shunt :- here output voltage is sampled and the feedback signal is mixed in shunt with input. In this the basic amplifier is an transresistance amplifier. The below fig. shows the topology of voltage shunt feedback amplifier.



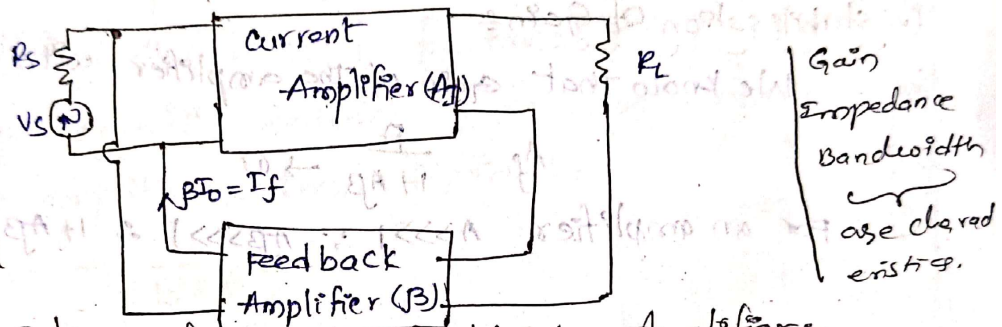4) Current shunt :- here output current is sampled, and the feedback signal is mixed in shunt with i/p. In this basic amplifier is current amplifier (Ai). The below fig. shows the topology of the current shunt feedback amplifier.



Ideal (or) General

Characteristics of Negative feedback Amplifiers:-

- 1) It reduces the gain (transfer gain) of the amplifier.
- 2) It provides stabilisation of gain.
- 3) It reduces the Noise and distortion in amplifier.
- 4) It increases the bandwidth of an amplifier.
- 5) It changes the magnitudes of i/p & o/p impedances.

Effect of (-)ve feedback on amplifier characteristics:-

1) Transfer gain :- Consider a simple block diagram of (-)ve feedback amplifier.

X_s → source voltage (or) current

X_i → Input voltage (or) current

X_o is o/p voltage (or) current

X_f is feedback voltage (or) current


∴ From this we can define

The gain without feedback is $A = \frac{X_o}{X_i}$

Gain with feedback is $A_f = \frac{X_o}{X_s}$

feedback factor (or) Ratio, $\beta = \frac{X_f}{X_o}$

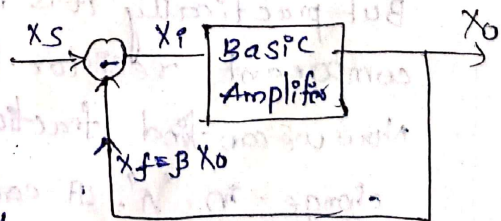Due to (-)ve feedback, the magnitude of i/p signal decreases.



Series -
Impedance
Shunt -
Parallel
-o/p Imp
decrea

From $A_f = \frac{X_o}{X_i}$

$$A_f = \frac{X_o}{X_i + X_f}$$

Divide numerator (or) denominator with (X_i)

$$A_f = \frac{X_o/X_i}{1 + X_f/X_i}$$

$$A_f = \frac{A}{1 + \frac{X_f \cdot X_o}{X_o \cdot X_i} \cdot \frac{1}{A}} \Rightarrow \frac{A}{1 + \beta A}$$

For voltage gain
 $X \rightarrow V$
For current gain
 $X \rightarrow I$

$$\therefore A_f = \frac{A}{1 + \beta A}$$

From this equation it is clear that the gain of the amplifier with feedback reduces by a factor of $(1 + \beta A)$ times of gain of the amplifier (A) without feedback.

(2) Stabilisation of Gain:

We know that gain of the amplifier with feedback is

$$A_f = \frac{A}{1 + \beta A} \rightarrow (1)$$

For an amplifier, $A \gg 1$; $\beta A \gg 1$ $\therefore 1 + \beta A \approx \beta A$

$$A_f = \frac{A}{1 + \beta A}$$

$$A_f = \frac{A}{\beta A}$$

$$A_f = \frac{1}{\beta}$$

From this eqn (2) it is clear that (A_f) depends only on feedback factor (β)

Suppose if we use feedback networks with resistive element as constant then gain should ^{remains} be constant. Then A_f is also constant. But practically it is not possible because the feedback component resistor is variable (varies) due to some reasons. Now we can find fractional change in (A_f) with fractional change in "A". It can be obtained by differentiating eqn (1) w.r.t "A".

$$\frac{dA_f}{dA} = \frac{(1 + \beta A)^{-1} \cdot -A(\beta)}{(1 + \beta A)^2}$$

$$\frac{dA_f}{dA} = \frac{-1}{(1 + \beta A)^2} \rightarrow (3)$$

$$dA_f = \frac{-dA}{(1 + \beta A)^2} \quad (3)$$

Divide eqn (5) by (4)

$$\frac{dA_f}{A_f} = \frac{dA}{(1+A\beta)^2}$$

$$\frac{dA_f}{A_f} = \frac{dA}{(1+A\beta)^2} \times \frac{(1+A\beta)}{A}$$

$$\frac{dA_f}{A_f} = \frac{dA}{A} \times \frac{1}{(1+A\beta)}$$

$$\frac{dA_f/A_f}{dA/A} = \frac{1}{1+A\beta}$$

$$S = \frac{1}{1+A\beta}$$

Ratio (S) is called sensitivity.
Sensitivity is the ratio of fractional change in gain of the amplifier with feedback to fractional change in gain of the amplifier without feedback.

Here $\frac{1}{1+A\beta} \ll 1$

Hence; $\frac{dA_f}{A_f} \ll \frac{dA}{A}$

Reciprocal of sensitivity is called desensitivity.

$$D = 1 + A\beta$$

1) Calculate the gain of (-ve) feedback amplifier with an internal gain of 200 and feedback factor of $\frac{1}{20}$ (β)?

Given: $A = 200$

$$\beta = \frac{1}{20}$$

$$A_f = \frac{A}{1+A\beta}$$

$$A_f = 18.1818$$

2) Overall gain of Multistage amplifier is 100 when a (-ve) feedback is applied gain reduces to 10. Find the fraction of output (i.e.) feedback to the I/P?

Given: $A = 100$

$$A_f = 10$$

$$A_f = \frac{A}{1+A\beta}$$

$$1 + A\beta = \frac{A}{A_f} \Rightarrow \beta = \left(\frac{A}{A_f} - 1 \right) = 0.09$$

3) In a negative feedback amplifier $A=100$; $\beta=0.04$ and

$V_s = 50\text{mV}$. Find

(a) Gain with feedback (b) output voltage (c) feedback voltage

Given: $A=100$; $\beta=0.04$; $V_s=50\text{mV}$

$$(a) A_f = \frac{A}{1+A\beta} = \frac{100}{1+100 \times 0.04} = \boxed{20}$$

(b) output voltage $= A$

$$A_f = \frac{V_o}{V_s}$$

$$V_s \times A_f = V_o$$

$$\boxed{V_o = 1\text{V}}$$

(c) feedback voltage $V_f = \beta V_o$

$$\boxed{V_f = 0.04\text{ Volts}}$$

A negative feedback of $\beta=0.002$ is applied to an amplifier with a gain of 1000 (A). Calculate the % change in overall gain of the feedback amplifier if the gain of the amplifier is subjected to a gain reduction of 15%?

$$A_f = \frac{A}{1+A\beta} ; \frac{dA}{A} = 15\%$$

$$\boxed{\frac{dA_f}{A_f} = \frac{dA}{A} \left[\frac{1}{1+A\beta} \right]}$$

use this formula also. $0.15 \left[\frac{1}{1+1000 \times 0.002} \right]$

$$A_f = \frac{A}{1+A\beta} = \frac{1000}{1+1000 \times 0.002} = 333.33 \quad \frac{dA_f}{A_f} = 0.05 \times 100 = 5\%$$

change of 15% means $A' = (1-0.15) \times 1000 = 850$

$$\text{Then } A_f' = A' \left[\frac{1}{1+A'\beta} \right]$$

$$A_f' = \frac{A'}{1+A'\beta} = 314.8$$

$$\therefore \text{percentage change in gain is } \frac{A_f - A_f'}{A_f} \times 100$$

$$= \frac{333.33 - 314.8}{333.33} \times 100$$

$$\boxed{\% \Delta A_f = 5.559}$$

An amplifier gain changes by $\pm 10\%$. using (+)ve feedback the amplifier is to be modified to give a gain of 100 with $\pm 0.1\%$ variation. Find the required open loop gain of the amplifier and the amount of (-)ve feedback.

closed loop gain A_f

$$A_f = 100$$

$$\frac{dA_f}{A_f} = \pm 10\% = 0.1 \quad \therefore \frac{dA}{A} = \pm 0.1\%$$

$$\frac{dA_f}{A_f} = \pm 0.1\% = 0.001$$

$$\frac{dA_f}{A_f} = \frac{dA}{A} \left[\frac{1}{1+A\beta} \right]$$

$$\frac{1}{1+A\beta} = \frac{dA_f/A_f}{dA/A}$$

$$1+A\beta = \frac{dA/A}{dA_f/A_f} \Rightarrow A\beta = \left[\frac{dA/A}{dA_f/A_f} - 1 \right] \Rightarrow A\beta = \left[\frac{0.1}{0.001} - 1 \right]$$

$$A_f = \frac{A}{1+A\beta}$$

$$1+A\beta = 1+99 = 100$$

$$A_f = \frac{A}{100}$$

$$A = 100 \times 100$$

$$A = 10,000$$

$$1+A\beta = 100$$

$$A\beta = 99$$

$$\beta = \frac{99}{10,000}$$

$$\Rightarrow \beta = 0.0099$$

3) Reduction in Noise (& distortion):

Distortion: Let an amplifier 'A' produces distortion 'D' without

feedback. Suppose (+)ve feedback is applied the gain reduces to

A_f and the distortion becomes D_f .

\Rightarrow Now the fraction of output distortion feedback to input is βD_f .

\Rightarrow After amplification the distorted output is $A\beta D_f$

\therefore Net distortion = original distortion - Distorted output

$$D_f = D - A\beta D_f$$

$$D_f + A\beta D_f = D$$

$$D_f (1+A\beta) = D$$

$$D_f = \frac{D}{1+A\beta}$$

From above eqn, the distortion with feedback reduces by a factor $(1+A\beta)$ of distortion without feedback.

Reduction in Noise:

Let an amplifier produces a noise (N) without feedback.
 → Suppose \ominus ve feedback is applied the gain reduces to A_f and the noise in the output becomes N_f .
 → Now fraction of output noise feedback to i/p is βN_f .
 → After amplification, the noise output is $A_f \beta N_f$.
 Net noise = original noise - Noise output

$$N_f = N - A_f \beta N_f$$

$$(A_f \beta + 1) N_f = N$$

$$N_f = \frac{N}{1 + A_f \beta}$$

From this N_f equation, the noise with feedback reduces by a factor $(1 + A_f \beta)$ times noise without feedback.

An amplifier as an i/p of 10mV and a gain of 200 without feedback. The distortion produced at o/p of an amplifier is 10%. It is desired to reduce distortion to 1% by using negative feedback. Calculate gain, i/p voltage, o/p voltage with feedback?

$$V_s = V_{in} = 10mV$$

$$A = 200$$

$$D_f = 10\% = 0.1$$

$$D = 1\% = 0.01$$

$$D_f = \frac{D}{1 + A_f \beta}$$

$$1 + A_f \beta = \frac{D}{D_f}$$

$$A_f \beta = \frac{D}{D_f} - 1 \Rightarrow \beta = \left(\frac{0.01}{0.1} - 1 \right) = \frac{0.01}{200} = 0.00005$$

$$A_f = \frac{A}{1 + A_f \beta}$$

$$A_f = \frac{200}{1 + 200(0.00005)} = 20$$

$$A = \frac{V_o}{V_{in}} \Rightarrow V_o = A V_{in} \Rightarrow 200 \times 10 \times 10^{-3} = 2V$$

$$A_f = \frac{V_o}{V_s} \Rightarrow V_s = \frac{V_o}{A_f} = \frac{2V}{20} = 0.1V$$

Increase in bandwidth:

We know that $A_f = \frac{A}{1 + A_f \beta}$

By using above eqn, $A_{fmid} = \frac{A_{mid}}{1 + A_{mid} \beta}$

The gain at low frequency $A_{f \text{ low}} = \frac{A_{\text{mid}}}{1 + A_{\text{mid}}\beta}$

The gain at high frequency $A_{f \text{ high}} = \frac{A_{\text{mid}}}{1 + A_{\text{mid}}\beta}$
 Now we can analyse the effect of negative feedback on lower & upper cutoff frequencies of an amplifier.

① Lower cut-off frequency (Lower 3dB frequency) :-

We know that relation b/w gain at low and gain at mid

$$A_{\text{low}} = \frac{A_{\text{mid}}}{1 - j\left(\frac{f_L}{f}\right)}$$

substitute the A_{low} in $A_{f \text{ low}}$

$$A_{f \text{ low}} = \frac{\frac{A_{\text{mid}}}{1 - j\left(\frac{f_L}{f}\right)}}{1 + \frac{A_{\text{mid}}}{1 - j\left(\frac{f_L}{f}\right)}\beta} = \frac{A_{\text{mid}}}{1 + \frac{A_{\text{mid}}\beta}{1 - j\left(\frac{f_L}{f}\right)}}$$

$$A_{f \text{ low}} = \frac{-A_{\text{mid}}}{\left[1 - j\left(\frac{f_L}{f}\right)\right] + A_{\text{mid}}\beta}$$

$$A_{f \text{ low}} = \frac{A_{\text{mid}}}{\left(1 + \frac{A_{\text{mid}}\beta}{1 - j\left(\frac{f_L}{f}\right)}\right)}$$

$$\div (1 + A_{\text{mid}}\beta)$$

$$\frac{A_{\text{mid}}}{1 + A_{\text{mid}}\beta}$$

$$1 - j\left[\frac{f_L}{f(1 + A_{\text{mid}}\beta)}\right]$$

$$= \frac{A_{f \text{ mid}}}{1 - j\left[\frac{f_L}{f(1 + A_{\text{mid}}\beta)}\right]}$$

$$1 - j\left[\frac{f_L}{f(1 + A_{\text{mid}}\beta)}\right]$$

$$\left[\therefore f_{L_f} = \frac{f_L}{1 + A_{\text{mid}}\beta} \right]$$

$$A_{f \text{ low}} = \frac{A_{f \text{ mid}}}{1 - j\left[\frac{f_{L_f}}{f}\right]}$$

Upper Cutoff frequency :-

We know that the relation b/w gain at mid frequency to gain at high frequency is given by

$$A_{\text{high}} = \frac{A_{\text{mid}}}{1 - j\left[\frac{f_H}{f}\right]}$$

Sub value of A_{high} in $A_{f \text{ high}}$.

$$A_{fhigh} = \frac{A_{mid}}{1 - j(f/f_H)} \cdot \frac{1}{1 + \frac{A_{mid}}{1 + j(f/f_H)} \beta}$$

$$A_{fhigh} = \frac{A_{mid}}{1 + A_{mid}\beta \cdot j(f/f_H)}$$

Q. Do both numerator & denominator with $1 + A_{mid}\beta$

$$A_{fhigh} = \frac{A_{mid}}{1 + A_{mid}\beta} \cdot \frac{1}{1 - j(f/f_H)} \cdot \frac{1 + A_{mid}\beta}{1 - j \left[\frac{f}{f_H (1 + A_{mid}\beta)} \right]}$$

$$A_{fhigh} = \frac{A_{mid}}{1 - j \left(\frac{f}{f_{HF}} \right)}$$


∴ called upper cutoff frequency with feedback.

∴ Bandwidth of the feedback amplifier is

$$(B.W)_f = f_{HF} - f_{LF} = f_H (1 + A_{mid}\beta) - f_L$$

From above eqn it is clear that the bandwidth of the amplifier with feedback is always greater than the bandwidth of amplifier without feedback because upper cutoff frequency is multiplied by a factor of $(1 + A_{mid}\beta)$. And the lower cutoff frequency is decreases as it is divided by $(1 + A_{mid}\beta)$ - so overall difference increases.

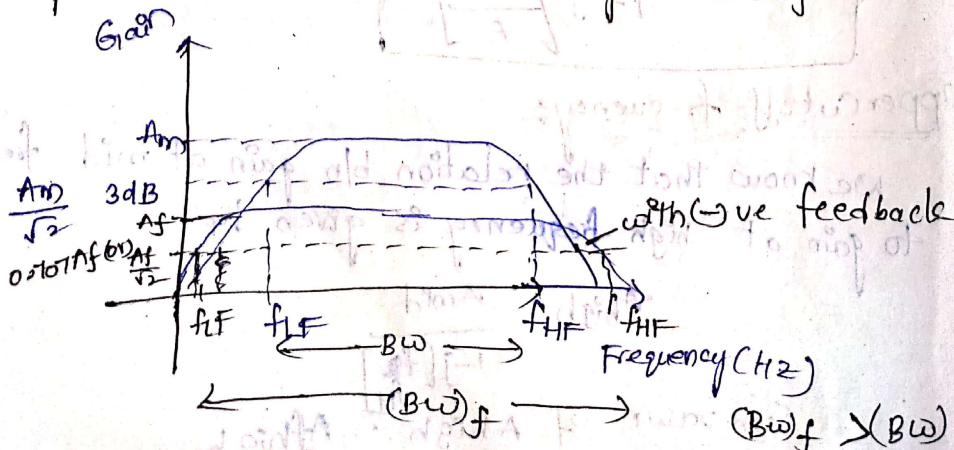The below figure shows the frequency response of the amplifier without feedback, by indicating bandwidths



An Amplifier has a mid frequency gain of 800, Its upper & lower cutoff frequencies are 16kHz & 40Hz respectively. Determine b.w of an amplifier. (Bandwidth) what will be the bandwidth after 2% of the signal is given as (-)ve feedback?

$$M_{id} = 800 \text{ Hz} = A_{mid}$$

$$\beta = 2\%$$

$$f_{H\beta} = 16 \text{ kHz}; \quad f_{L\beta} = 40 \text{ Hz}$$

$$\beta = 0.02$$

$$\text{Band width} = f_H - f_L$$

$$= 16 \text{ kHz} - 40 \text{ Hz}$$

$$\boxed{\text{B.W}} = 15.960 \text{ kHz}$$

$$(\text{B.W})_f = f_H (1 + A_{mid} \beta) - \frac{f_L}{1 + A_{mid} \beta}$$

$$= 16 \text{ kHz} (1 + 800(0.02)) - \frac{40}{1 + (800)(0.02)}$$

$$\boxed{(\text{B.W})_f = 271.997 \text{ kHz}}$$

(5) Change in i/p & o/p impedances:

We know that from topologies of (+)ve feedback amplifier there is a change in i/p & o/p impedances due to the series & parallel connection of feedback network to the basic amplifier at i/p & o/p sides.


Ex: In series mixing the feedback network is connected in series to i/p side of basic amplifier. So Z_{in} increases.

whereas in shunt mixing the feedback is connected in parallel to basic amplifier so Z_{in} decreases.

Ex: For voltage sampling, the feedback network is connected in parallel to o/p of amplifier. So Z_o decreases, whereas in

shunt current sampling, the feedback network is connected in series with o/p side of an amplifier, so Z_o increases.

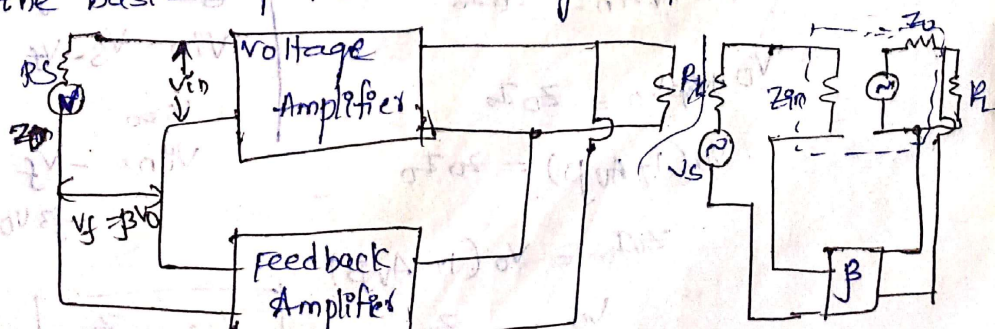(Voltage Series feedback Amplifier) Consider topology of voltage series feedback amplifier, we know that in voltage series, the basic amplifier is voltage amplifier.



Input Impedance :-

$$Z_{in} = \frac{V_{in}}{I_{in}}$$

without feedback

$$Z_{if} = \frac{V_s}{I_{in}}$$

with feedback

Impedance at an input
Pic 1, 17, 18
Z_{in}

From fig;

$$V_{in} = V_s - V_f$$

$$V_s = V_{in} + V_f$$

$$V_s = V_{in} + \beta A V_{in}$$

$$\begin{cases} V_f = \beta V_o \\ V_o = A V_{in} \end{cases}$$

$$V_s = (1 + \beta A) V_{in}$$

$$V_s = (1 + A\beta) V_{in}$$

divide the above eqn with I_{in} on both sides.

$$\frac{V_s}{I_{in}} = \frac{(1 + A\beta) V_{in}}{I_{in}}$$

$$Z_{if} = \frac{(1 + A\beta) V_{in}}{I_{in}}$$

$$\frac{V_{in}}{I_{in}} = Z_{in}$$

$$Z_{if} = Z_{in} (1 + A\beta)$$

Impedance increases by a factor of $(1 + A\beta)$ of Z_{in} .

Output Impedance :-


$$Z_{of} = \frac{V_o}{I_o}$$

$$Z_o = \frac{V_o}{I_o}$$

Let Z_o, Z_{of} are the o/p impedances of with & without feedback.

In order to measure o/p impedance, short circuit the source voltage ($V_s = 0$) and $R_L \rightarrow \infty$ and connect a voltmeter.

Apply KVL to o/p loop. :-

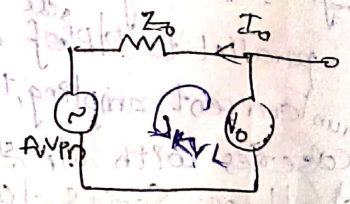

$$V_o = Z_o I_o - A V_{in} \Rightarrow$$

$$V_o = Z_o I_o + A V_{in}$$

$$V_o - A V_{in} = Z_o I_o$$

$$V_o + \beta V_o = Z_o I_o$$

$$V_o (1 + \beta A) = Z_o I_o$$

$$Z_o I_o = V_o (1 + \beta A)$$

$$\frac{V_o}{I_o} = \frac{Z_o}{1 + \beta A} \Rightarrow$$


$$Z_{of} = \frac{Z_o}{1 + \beta A}$$

$$\begin{cases} V_s = V_{in} - V_f \\ V_{in} = V_s - V_f \\ V_s = 0 \\ V_{in} = -V_f \\ = -\beta V_o \end{cases}$$

The o/p impedance (Z_{of}), decreases by a factor of $1 + A_{v\beta}$ times of Z_o without feedback.
 in voltage sampling.

Current Series feedback Amplifiers (Series Series Amplifiers)

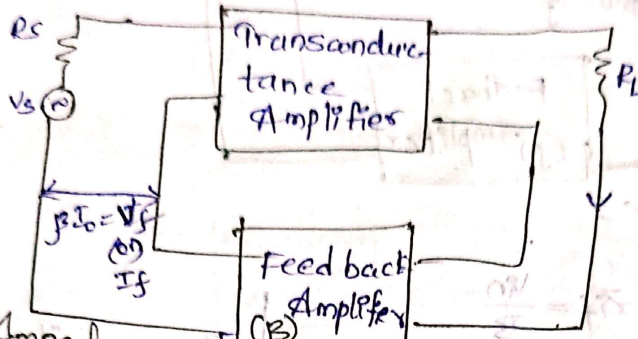⇒ Consider the topology of current series feedback amplifiers.



I_f & V_f are in series

Input Impedance (Z_{in}): Let $Z_{in} = \frac{V_{in}}{I_{in}}$; $Z_{if} = \frac{V_s}{I_{in}}$

From topology, $V_{in} = V_s - V_f$

$$V_s = V_{in} + V_f = V_{in} + G_m \beta V_{in}$$

Divide with I_{in}

$$\frac{V_s}{I_{in}} = \frac{V_{in}}{I_{in}} (1 + G_m \beta)$$

$$Z_{if} = Z_{in} [1 + G_m \beta]$$

Output Impedance (Z_o): Let Z_o & Z_{of} are the o/p impedances without & with feedback.

$$Z_o = \frac{V_o}{I_o}; Z_{of} = \frac{V_o}{I_o}$$

⇒ To measure o/p impedance; $V_s = 0$; $R_L \rightarrow \infty$

By using KCL

$$I_o = G_m V_{in} + \frac{V_o}{Z_o}$$

$$\frac{V_o}{Z_o} = I_o - G_m V_{in}$$

with $V_s = 0$; $V_{in} = -V_f$


$$V_{in} = -\beta I_o$$

$$V_{in} = V_f = \beta I_o \quad \text{--- (1)}$$

$$\frac{V_o}{Z_o} = I_o - G_m (-\beta I_o)$$


$$\frac{V_o}{Z_o} = I_o [1 + G_m \beta]$$
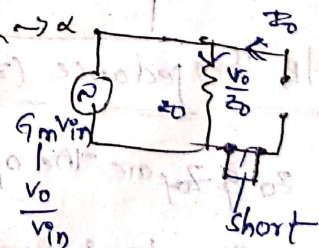
$$\frac{V_o}{I_o} = Z_o [1 + G_m \beta] \Rightarrow Z_{of} = Z_o [1 + G_m \beta]$$



Voltage shunt (shunt shunt amplifier) Amplifier:

(+M) Imp

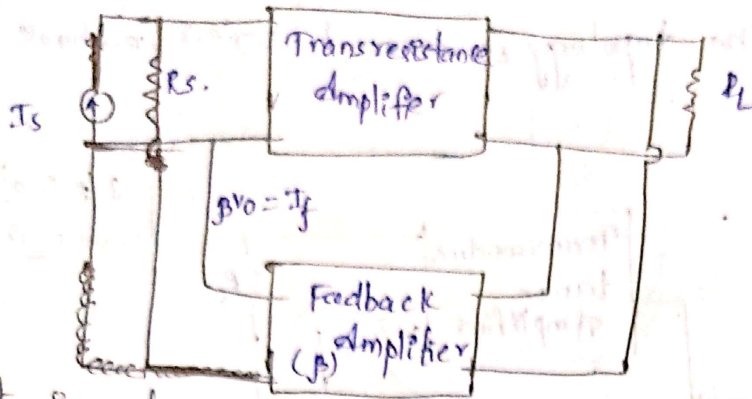

Input impedance:

$$z_{in} = \frac{V_{in}}{I_{in}} ; z_{if} = \frac{V_{in}}{I_s}$$

From topology;

$$I_s = I_{in} + I_f$$

$$I_f = \beta V_o ; V_o = R_m I_{in}$$

$$I_s = I_{in} + \beta V_o$$

$$I_s = I_{in} + \beta (R_m I_{in})$$

$$I_s = I_{in} (1 + \beta R_m)$$

$$\therefore z_{if} = \frac{V_{in}}{I_{in} (1 + \beta R_m)} = \left\{ \frac{V_{in}}{I_{in}} \right\} \left[\frac{1}{1 + \beta R_m} \right]$$

$$z_{if} = \frac{z_{in}}{1 + \beta R_m}$$

o/p Impedance (z_o):

z_o & z_{of} are the o/p impedances

without and with feedback


In order to measure $V_s \rightarrow$ (short) and $R_L \rightarrow \infty$

\therefore By applying KVL

$$V_o - z_o I_o - R_m I_{in} = 0$$

$$V_o = z_o I_o + R_m I_{in}$$

$$z_o I_o = V_o - R_m I_{in}$$

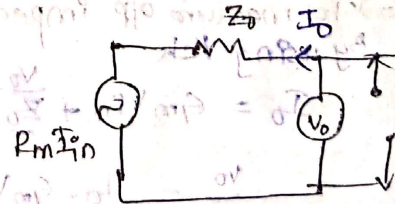

If $I_s \rightarrow$ open.

with $V_s \rightarrow$
 $I_{in} = -I_f$

$$z_{oT_0} = V_0 - R_m[-I_f]$$


$$z_{oT_0} = V_0 + R_m[\beta V_0]$$

$$z_{oT_0} = V_0 [1 + \beta R_m]$$

$$\frac{z_o}{(1 + \beta R_m)} = \frac{V_0}{I_0}$$

$$z_{of} = \frac{z_o}{1 + \beta R_m}$$

Current shunt (series shunt Amplifier)

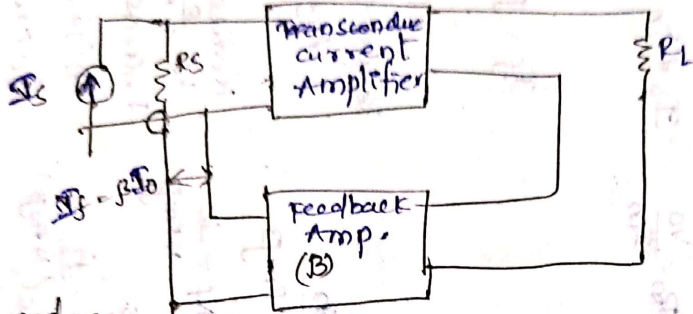

$$I_o = A I_{in}$$

I/p impedances:

$$z_{if} = \frac{V_{in}}{I_s}$$

from topology:

$$I_f = \beta I_o$$

$$I_o = A I_{in}$$

$$\therefore I_s = I_{in} + \beta I_o A I_{in}$$

$$I_s = I_{in} + \beta (A I_{in})$$

$$I_s = I_{in} (1 + \beta A)$$

$$\therefore z_{if} = \frac{V_{in}}{I_{in} (1 + \beta A)}$$

$$z_{if} = \frac{z_{in}}{(1 + \beta A)}$$

o/p Impedance (z_o): $z_{of} = \frac{V_0}{I_0}$


In order to calculate, z_{of} , (o/p impedance)

$$R_L \rightarrow \infty, V_s \rightarrow 0$$

Apply KVL

$$I_0 = \frac{V_0}{z_o} + A I_{in}$$

$$I_0 - A I_{in} = \frac{V_0}{z_o}$$

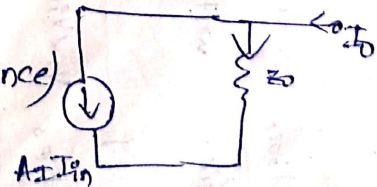

with $V_s = 0, I_s = 0$

$$I_{if} = I_f$$

SUMMARY OF (+)VE FEEDBACK AMPLIFIER.

$$I_o [1 + \beta A_I] = \frac{V_o}{Z_o} \rightarrow \frac{V_o}{I_o} = Z_o (1 + \beta A_I)$$

$$Z_{of} = Z_o [1 + \beta A_I]$$

Type of feedback characteristic	Voltage series	Current series	Voltage shunt	Current shunt
1) Basic Amplifier	voltage amplifier	Transconductance amplifier	Transresistance amplifier	Current Amplifier
2) o/p and gain of Basic amplifier	$V_o \times V_{in} \Rightarrow A_v = \frac{V_o}{V_{in}}$	$I_o \times V_{in} \Rightarrow G_m = \frac{I_o}{V_{in}}$	$V_o \times I_{in} \Rightarrow R_o = \frac{V_o}{I_{in}}$	$I_o \times I_{in} \Rightarrow A_i = \frac{I_o}{I_{in}}$
3) Feedback signal	$V_f = \beta V_o$	$I_f = \beta I_o$	$V_f = \beta V_o$	$I_f = \beta I_o$
4) Gain with feedback	Reduces $A_{vf} = \frac{A_v}{1 + \beta A_v}$	Reduces $G_{mf} = \frac{G_m}{1 + \beta G_m}$	Reduces $R_{of} = \frac{R_o}{1 + \beta R_o}$	Reduces $A_{if} = \frac{A_i}{1 + \beta A_i}$
5) Distortion & Noise	Reduces $DF = \frac{D}{1 + \beta A_v}$	Reduces $DF = \frac{D}{1 + \beta G_m}$	Reduces $DF = \frac{D}{1 + \beta R_o}$	Reduces $DF = \frac{D}{1 + \beta A_i}$
6) Bandwidth	Increases $f_H(1 + \beta A_v) - f_L$	Increases $f_H(1 + \beta G_m) - f_L$	Increases $f_H(1 + \beta R_o) - f_L$	Increases $f_H(1 + \beta A_i) - f_L$
7) I/P Impedance	Increases $R_{in} (1 + \beta A_v)$	Increases $R_{in} (1 + \beta G_m)$	decreases $R_{in} (1 + \beta R_o)$	decreases $R_{in} (1 + \beta A_i)$
8) o/p Impedance	decreases	decreases	decreases	Increases

Methodology of Feedback Amplifiers analysis:

step

1 -> From given circuit, identify the feedback also.

2 -> To find the type of feedback, for this we know the type of sampling & type of mixing.

3 -> To find the ^{type of} sampling,

a) If you short the o/p terminal ($V_o = 0$)

then it is called voltage sampling

b) If you open the o/p terminal ($I_o = 0$)


then it is called current sampling.

4 -> To find the type of mixing:

a) If the feedback signal is subtracted from externally applied signal as a voltage then it is called series mixing

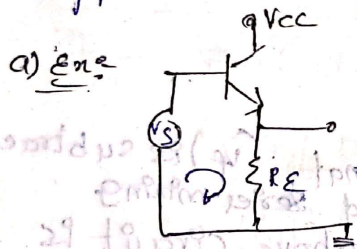b) If the feedback signal is subtracted from externally applied signal as a current then it is called shunt mixing


find sampling
If Resistor which is common in both i/p & o/p eqn is feedback resistor of "



$$V_o = I_e R_e \rightarrow (1)$$

$$V_s - V_{be} - I_e R_e = 0$$

$$V_{be} = V_s - I_e R_e$$

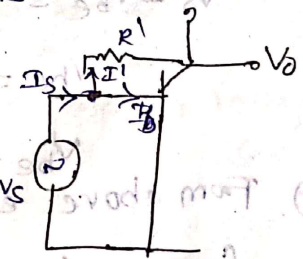

$$I_s = I_b + I_e$$

From step 5 & 1 we can identify type of feedback.

$V_{be} = V_s - V_f$ feedback from V_s (voltage source) so it is voltage

Subtracted from current so it is shunt mixing

6) For the analysis, we have to find (the effect of) feedback also on i/p & o/p circuit.


a) For i/p circuit voltage sampling make ($V_o = 0$) by shorting the o/p.

b) For current sampling, make ($I_o = 0$) by opening the o/p circuit.

b) To find the o/p circuit, for series mixing make ($I_{in} = 0$)

by opening the i/p. For shunt mixing make ($V_{in} = 0$) by shorting the i/p.

For a) For series mixing

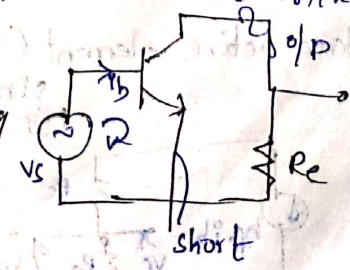


Find the value of open loop gain (A) and feedback factor (β).

⇒ From A & β find A_f, Z_i, Z_o.

EM Voltage Series feedback amplifier (Series-shunt Amplifier)

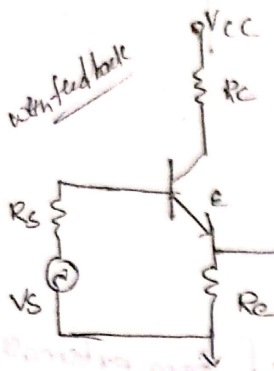⇒ The practical example of this amplifier is emitter follower.



→ In this figure, R_E resistor is feedback resistor, it is common to both i/p & o/p ends.

(V_O = I_ER_E & V_{be} = V_S - I_ER_E)

→ In the above circuit, short the o/p terminal the feedback signal becomes zero.

Fig 1

⇒ Hence it is called voltage sampling.

From i/p circuit Apply KVL


V_S - V_{be} - I_ER_E = 0

V_{be} = V_S - I_ER_E

V_{be} = V_S - V_f

→ From above eqn the feedback signal (V_f) is subtracted from V_S (voltage source), so the above circuit is an example of voltage series feedback amplifier.

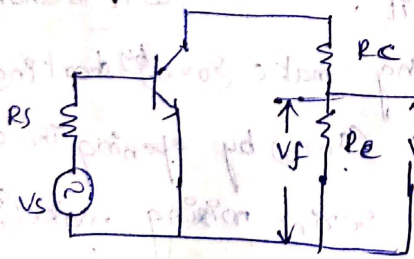⇒ For finding the amplifier without feedback for voltage sampling make (V_O = 0).




for series mixing,

o/p i/p then R_E is connected to o/p side as shown in

Fig 2

Equivalent circuit (Replace active element (transistor) with its

simplified-h parameter model)

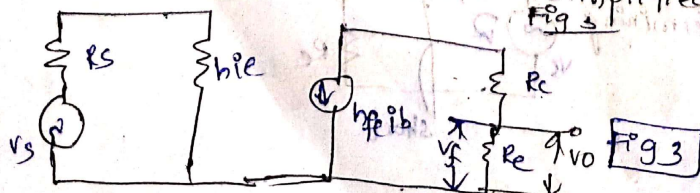

$$\Rightarrow \text{From figs; } V_f = V_o \quad (\text{ie}) \quad \beta = \frac{V_f}{V_o} = \frac{V_f}{V_f} = 1$$

$$\text{Voltage gain } (A_v) = \frac{V_o}{V_{in}}$$

$$A_v = \frac{V_o}{V_{in}} = \frac{h_{fe} i_b R_e}{(R_s + h_{ie}) i_b}$$

$$A_v = \frac{h_{fe} R_e}{(R_s + h_{ie})}$$

$$D = (1 + A_v) \beta$$

$$D = 1 + \left(\frac{h_{fe} R_e}{R_s + h_{ie}} \right) (\beta) = 1$$

$$D = \frac{R_s + h_{ie} + h_{fe} R_e}{R_s + h_{ie}}$$

$$A_{vf} = \frac{A_v}{1 + A_v \beta} = \frac{A_v}{D} = \frac{h_{fe} R_e / (R_s + h_{ie})}{\frac{R_s + h_{ie} + h_{fe} R_e}{R_s + h_{ie}}} = \frac{h_{fe} R_e}{R_s + h_{ie} + h_{fe} R_e}$$

$$Z_{in} = R_s + h_{ie}$$

$$Z_{if} = Z_{in} (1 + A_v \beta)$$

$$= Z_{in} [D]$$

$$= Z_{in} \left[\frac{R_s + h_{ie} + h_{fe} R_e}{R_s + h_{ie}} \right]$$

$$= (R_s + h_{ie}) \left[\frac{R_s + h_{ie} + h_{fe} R_e}{R_s + h_{ie}} \right]$$

$$Z_{if} = R_s + h_{ie} + h_{fe} R_e$$

$$\text{O/p Impedance } (Z_o) = \alpha$$

$$Z_{of} = Z_o \left[\frac{1}{1 + A_v \beta} \right]$$

$$Z_{of} = \frac{\alpha}{R_e} \left[\frac{1}{1 + A_v \beta} \right]$$

$$Z_{of} = \text{Undetermined } (\infty)$$

To determine (Z_{of}) , make $R_e \rightarrow \alpha$

$$Z_{of} = \frac{\alpha}{R_e} \left[\frac{(R_s + h_{ie})}{R_s + h_{ie} + h_{fe} R_e} \right] + \frac{R_e}{R_e}$$

Z_{if} increases in voltage series

$$Z_{of} = R_e \left[R_s + h_{ie} \right]$$

$$R_e \rightarrow \infty \quad \frac{R_e \left[h_{ie} + \frac{R_s + h_{ie}}{h_{fe}} \right]}{h_{fe}}$$

$$Z_{of} \Big|_{R_e \rightarrow \infty} = \frac{R_s + h_{ie}}{h_{fe}}$$

$$Z_{of}' = R_m (Z_{of})$$

$$R_e \rightarrow \infty$$

to remove indeterminacy
we applied limit to R_e

The voltage series feedback of transistor amplifier as the following data of circuit is $R_s = 1k\Omega$, $R_c = 4.7k\Omega$, $R_e = 100\Omega$. Calculate
 (a) β b) A_v c) R_i d) R_{if} e) R_o , R_{of} ? assume the transistor parameters are $h_{ie} = 1.1k\Omega$, $h_{fe} = 50$?

1) $\beta = \frac{V_f}{V_o} = \frac{V_f}{V_f} = 1$

2) $A_v = \frac{h_{fe} R_e}{R_s + h_{ie}} = \frac{50(100)}{1k\Omega + 1.1k\Omega} = 2.38$

3) $D = \frac{R_s + h_{ie}}{1 + A_v \beta} = \frac{1k\Omega + 1.1k\Omega}{3.38} = 0.704$

$$D = \frac{R_s + h_{ie} + h_{fe} R_e}{R_s + h_{ie}} = \frac{1k\Omega + 1.1k\Omega + 50(100)}{1k\Omega + 1.1k\Omega} = 3.3809$$

$D = 3.3809$

4) $R_i = Z_{in} = R_s + h_{ie}$

$$= 1k\Omega + 1.1k\Omega$$

$$= 2.1k\Omega$$

5) $Z_f = R_{if} = R_s + h_{ie} + h_{fe} R_e$


$$= 1k\Omega + 1.1k\Omega + 50(100)$$

$$= 7.1k\Omega$$

6) $Z_o = R_o = \infty$


$Z_{of} = \frac{R_{of}}{R_e \rightarrow \infty} \quad \left| \quad R_{of} = R_i (1 + A_v \beta) \right.$

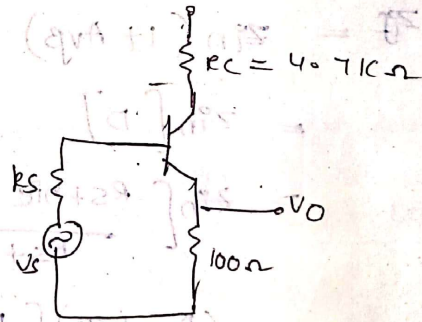$R_{of} = \frac{1k\Omega + 1.1k\Omega}{50} = 42\Omega$



Current Series feedback amplifier (series-series feedback)

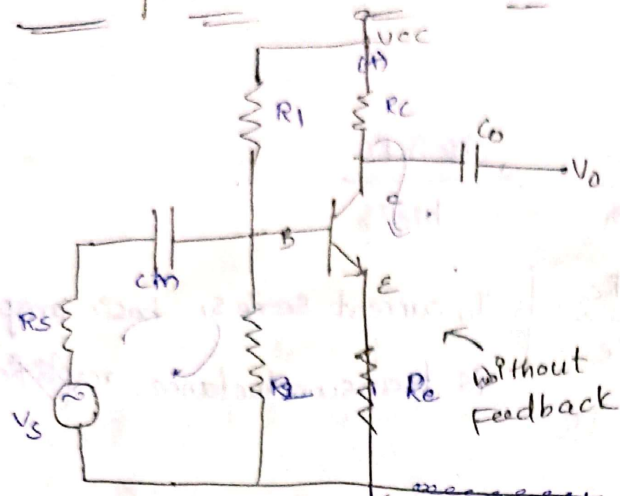The practical circuit (example) of series-series is an common emitter amplifier with ^{out}unbypassed capacitor. (or) CE amplifier with R_E Resistor as shown in Fig 1:



to identify feedback resistor
 o/p KVL
 $V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$
 $V_{CE} = V_{CC} - I_C R_C - I_E R_E$
 i/p KVL
 $V_S - I_S R_S - R_{th} i_b - V_{BE} - I_E R_E = 0$

⇒ In the above circuit R_E resistor acts as feedback resistor. As we can short the o/p terminal then the voltage across the R_E does not become zero. Hence it is not voltage sampling. Hence suppose if we can open o/p terminal $I_C = 0$, then $I_E R_E = 0$. The feedback signal becomes zero. Hence it is current sampling.

From o/p circuit Apply KVL

$$V_{CC} (\text{or } V_S) - I_C R_C - V_{CE} - I_E R_E = 0$$

$$V_{CE} = V_{CC} - I_C R_C - I_E R_E$$



From i/p circuit

$$V_S - I_S R_S - R_{th} i_b - V_{BE} - I_E R_E = 0$$

$$V_{BE} = V_S - I_S R_S - R_{th} i_b - I_E R_E$$

From above eqns, the feedback signal is subtracted from externally applied signal as a voltage. Hence it is series mixing so from above circuit, the type of feedback is current series feedback amplifier.

with feedback

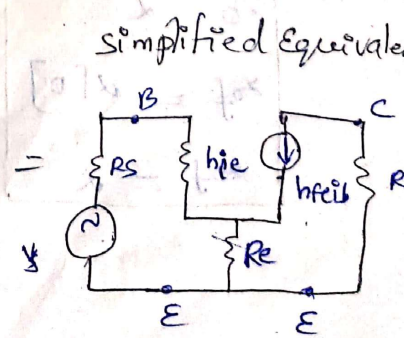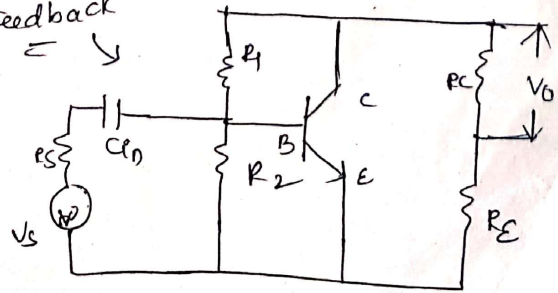

$$\beta = \frac{V_f}{V_b} \quad \text{where } V_f = I_e R_e$$

$$V_b = I_c R_c$$

$$\beta = \frac{I_e R_e}{I_c R_c} \quad \left| I_e \approx I_c \right|$$

$$\boxed{\beta = \frac{R_e}{R_c}}$$

$$A_v \text{ (voltage gain)} = \frac{V_o}{V_i} = \frac{h_f e R_c}{h_i e R_b}$$

$$\boxed{A_v = \frac{h_f e R_c}{h_i e}}$$

In current series, basic amplifier is transconductance amplifier.

$$G_m = \frac{I_o}{V_{in}}$$

$$\boxed{G_m = \frac{h_f e R_c}{h_i e R_b} = \frac{h_f e}{h_i e}}$$

Range of mamp/v

$$D = 1 + G_m \beta$$

$$D = 1 + \left(\frac{h_f e}{h_i e} \right) \beta$$

$$\boxed{D = 1 + \left(\frac{h_f e}{h_i e} \right) \left(\frac{R_e}{R_c} \right)}$$

$$A_{v f} = \frac{G_m}{D}$$

$$A_{v f} = \frac{A_v}{D} = \frac{h_f e R_c}{h_i e} \cdot \frac{1}{1 + \frac{h_f e R_e}{h_i e R_c}} = \frac{h_f e R_c (h_i e R_c)}{h_i e (h_i e R_c + h_f e R_e)}$$

$$\boxed{Z_{in} = h_i e}$$

$$Z_{i f} = Z_{in} (1 + G_m \beta)$$

$$h_i e (R_1 \parallel R_2) \quad \left(\text{if } R_1 \& R_2 \text{ consider} \right)$$

$$\boxed{Z_{i f} = Z_{in} (D)}$$

$$\boxed{\begin{aligned} Z_o &= \alpha \\ Z_{o f} &= \alpha [D] \\ Z_{o f} &= \alpha \end{aligned}}$$

① In current series feedback the following parameters $R_c = 20k\Omega$

$R_e = 28k\Omega$, $R_1 = 1k\Omega$, $R_2 = 100\Omega$, $h_{ie} = 2k\Omega$ & $h_{fe} = 80$. Calculate

B) A_f , A_{vf} , and R_{if}
loop gain (G_m)

$$\beta = \frac{R_e}{R_c} = \frac{100}{1k\Omega} = 0.1$$

$$A = G_m = \frac{h_{fe}}{h_{ie}} = \frac{80}{2k\Omega} = 0.04$$

$$A_f = A_{vf} = \frac{G_m}{D}; \quad D = \frac{0.04}{1.004} = \boxed{0.0398}$$

$$A_f = A_{vf} = G_{mf} = 0.0398$$

$$Z_{of} = R_{if} = Z_{in} [1 + G_m \beta]$$

$$Z_{if} = R_{if} = 2k\Omega [1 + 0.04(0.1)] = \boxed{2.008k\Omega}$$

$$R_{if} = Z_{in} = h_{ie} = 2k\Omega$$

② The current series feedback type of a transistor amplifier as the following data of circuit $R_c = 1k\Omega$,

$R_e = 100\Omega$, $R_1 = 30\Omega$; $R_2 = 20\Omega$; $h_{ie} = 1k\Omega$, $h_{fe} = 100$. Find

A_v , R_i , R_{if} , A_{vf} , loop gain in dB?

$$\beta = \frac{R_e}{R_c} = \frac{100}{1k\Omega} = \frac{100}{1000k} = \frac{1}{10} = 0.1$$

$$A_v = \frac{h_{fe} R_c}{h_{ie}} = \frac{100(1k\Omega)}{1k\Omega} = 100$$

$$R_i = Z_{in} = h_{ie} = h_{ie} [R_1 \parallel R_2] = 1k\Omega \left[\frac{30 \times 20}{50} \right]$$

$$R_i = \underline{12k\Omega}$$

$$R_{if} = Z_{in}(D) = Z_{in}(1 + G_m \beta) = 12k\Omega \left(1 + \left(\frac{h_{fe}}{h_{ie}} \right) (0.1) \right)$$

$$R_{if} = \underline{12.12k\Omega}$$


$$A_{vf} = G_{mf} = \frac{G_m}{D} = \frac{h_{fe}(R_c)}{h_{ie}} = \frac{100(1k\Omega)}{1k\Omega} = 99.009$$

$$\text{loop gain 'n (dB)} = A = \frac{h_{fe}}{h_{ie}} = 0.1$$

$$(dB) = -20 = (-20 \log(A))$$

Voltage shunt Feedback Amplifier:- The example of voltage shunt feedback amplifier is common emitter amplifier with collector to base bias.

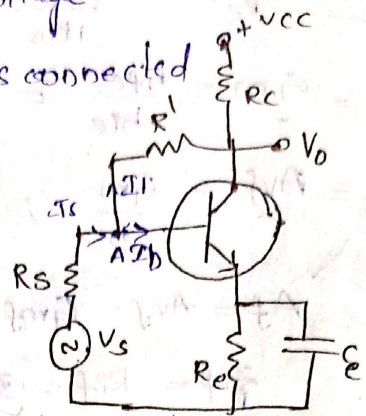The below fig. shows the example of voltage shunt feedback amplifier. In the above circuit, the resistor R' is connected b/w collector to base. As we know in common emitter, base is i/p & collector is o/p. so R' acts as feedback resistor.




In the above circuit, if we short the o/p terminal, then voltage across R' becomes zero. Hence it is called voltage sampling.

→ By applying KCL to i/p loop, At Node 'A', $I_s = I_1 + I_b$
 $\therefore I_b = I_s - I_1$
 $I_b = I_s - I'$



$$I_b = I_s - I'$$

In the above eqn. feedback signal is subtracted from externally applied signal as a current. Hence it is called shunt mixing. In the above circuit, the type of feedback is voltage shunt.

Fig. 2 shows the amplifier without feedback :-

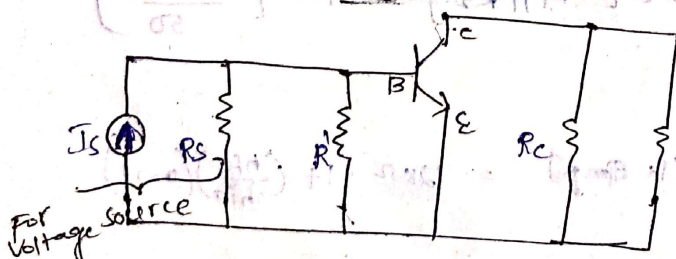

Equivalent Circuit :-

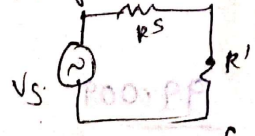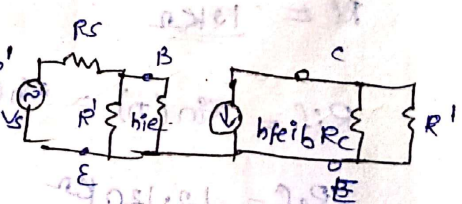

From fig 1, $I_f = \frac{V_{in} - V_o}{R'} \quad | \quad V_{in} \ll V_o \quad (V_{in} - V_o = -V_o)$

Feedback factor (β) = $I_f = -V_o / R'$


$$\frac{I_f}{V_o} = -1/R'$$

$$\beta = -1/R'$$

Voltage shunt Feedback Amplifiers: The example of voltage shunt feedback amplifier or amplifier with collector to Base Bias.

The below fig. shows the example of voltage shunt feedback amplifier. In the above circuit, the resistor R' is connected in collector to base.

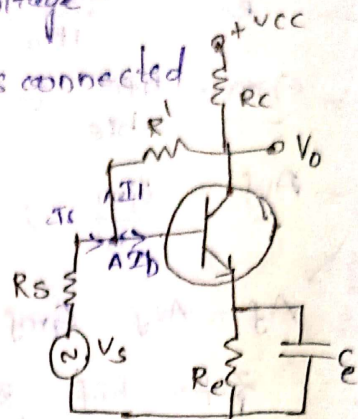As we know in common emitter, base is i/p & collector is o/p. so R' acts as feedback resistor.



In the above circuit, if we short the o/p terminal, then voltage across R' becomes zero. Hence it is called voltage sampling.

→ By applying KCL to i/p loop, At Node 'A', $I_s = I_1 + I_b$


$$\therefore I_1 = I_s - I_b$$

$$I_b = I_s - I_1$$


$$I_b = I_s - I_f$$

In the above eqn. feedback signal is subtracted from externally applied signal as a current. Hence it is called shunt mixing. In the above circuit, the type of feedback is voltage shunt.

Fig. 2 shows the amplifier without feedback:

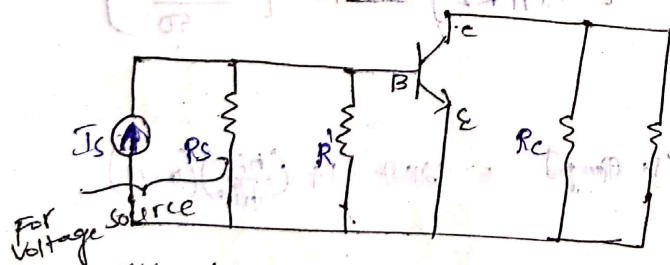

Equivalent Circuit:

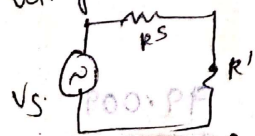

For voltage source I_s and R_s in series. $I_f = \frac{V_{in} - V_o}{R'} \quad | \quad V_{in} \ll V_o \quad (V_{in} - V_o = -V_o)$

Feedback factor $(\beta) = I_f = -V_o / R'$

$$\frac{I_f}{V_o} = -1/R'$$

$$\beta = -1/R'$$

open loop gain $R_m = -\frac{V_o}{I_b}$

$$R_{m0} = h_{fe} R_c \parallel R'$$

$$R_{m0} = -h_{fe} (R_c \parallel R')$$

$$R_m = h_{fe} (R_c \parallel R')$$

$$D = 1 + R_m \beta$$

$$= 1 + \frac{h_{fe} (R_c \parallel R')}{R_i}$$

$$D = 1 + \frac{h_{fe} (R_c \parallel R')}{R_i}$$

$$R_{mf} = \frac{R_m}{D}$$

$$Z_{in} = h_{ie} \parallel R'$$

$$Z_{in}' = Z_{in} / D$$

$$Z_o = \alpha$$

$$Z_o' = \alpha \parallel R_c \parallel R'$$

$$Z_o' = R_c \parallel R'$$

$$Z_{of}' = \frac{Z_o'}{D}$$

Problems:

In voltage shunt feedback amplifier, the parameters are $R_S = 600 \Omega$, $R_B = 40 k\Omega$, $R_L = 2 k\Omega$, $h_{ie} = 5 k\Omega$, $h_{fe} = 80$

calculate A_{vf} , R_{if} , R_{of} ?

$$\beta = -\frac{1}{R_i} = -\frac{1}{40 k\Omega} = -0.000025 = -25 \times 10^{-6}$$

$$A_v = \frac{V_o}{V_{in}} = \frac{-h_{fe} i_b (R_c \parallel R')}{h_{ie} i_b}$$

$$A_v = \frac{-h_{fe} (R_c \parallel R')}{h_{ie}} = -30.476$$

$$R_m = h_{fe} (R_c \parallel R') = 80 (2 k\Omega \parallel 40 k\Omega) = 152.38 k\Omega$$

$$D = (1 + R_m \beta) = 1 + (152.38 k\Omega (-25 \times 10^{-6})) = 4.08$$

$$A_{vf} = \frac{A_v}{D} = \frac{-30.476}{4.08095} = -7.47$$

$$Z_{inf} = (5 k\Omega \parallel 40 k\Omega) = 4.444 k\Omega$$

$$R_{if} = Z_{inf} = \frac{Z_{in}}{D} = \frac{4.444 k\Omega}{4.08095} = 1.09 k\Omega$$

$$R_{of} = Z_o = \alpha$$



$$(Z_o') R_{of} = Z_o \parallel R_c \parallel R'$$

$$(Z_{of}') R_{of} = \frac{Z_o'}{D} = R_c \parallel R' = \frac{1.904 k\Omega}{4.08095}$$

For the transistor feedback amplifier shown in fig. $h_{fe} = 100$
 $h_{ie} = 1k\Omega$, $h_{oe} = h_{oe} = 0$, Determine A_v , R_{if} , R_{of} ?

$$\beta = \frac{-1}{R_1} = \frac{-1}{100k\Omega} = \frac{-1}{100 \times 10^3} = 0.00001 = -10 \times 10^{-6}$$

By assuming $R_e = 0$ (voltage shunt)

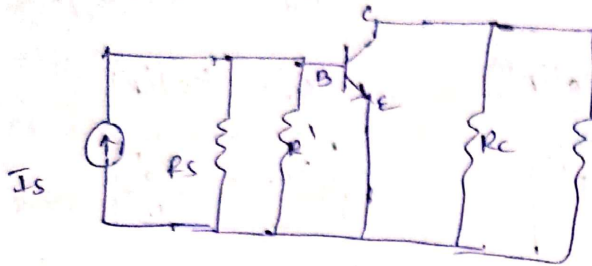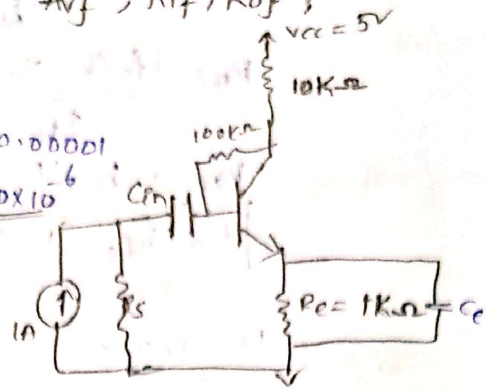

$$A_v = \frac{V_o}{V_{in}} = \frac{-h_{fe} i_b (R_c \parallel R_L)}{h_{ie} i_b} = \frac{-100 (10k\Omega \parallel 100k\Omega)}{1k\Omega}$$

$$A_v = -909.090$$

$$R_m = -h_{fe} (R_c \parallel R_L) = -100 (10k\Omega \parallel 100k\Omega) = 909.090 k\Omega$$

$$D = (1 + R_m \beta) = (1 + R_m \beta) = 1 + (909.090k)(-10 \times 10^{-6}) = 10.090$$

$$A_{vf} = \frac{A_v}{D} = \frac{-909.090}{10.090} = 90.098$$


$$R_{if} = Z_{in} = h_{ie} \parallel R_1 = 909.099 \Omega \quad Z_{of} = R_{if} = \frac{Z_{in}}{D} = 98.1267$$

$$R_o = Z_o = \infty$$

$$R_{of} = Z_o' = R_c \parallel R_L = 10k\Omega \parallel 100k\Omega = 9.090 k\Omega$$

$$R_{of}' = Z_{of}' = \frac{Z_o'}{D} = 900.98$$

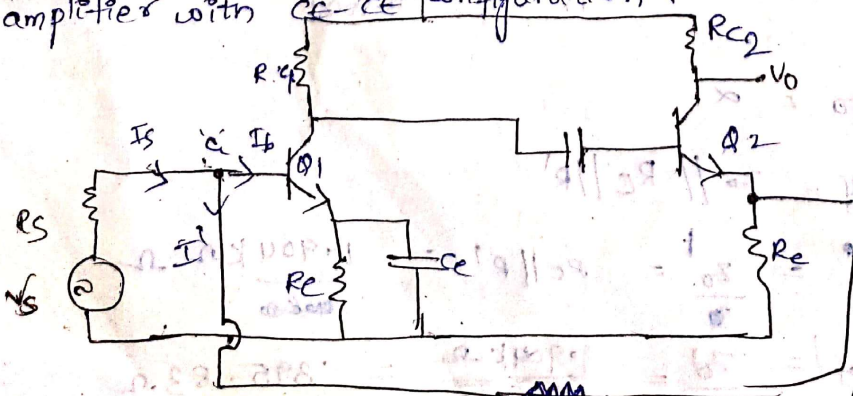current shunt feedback amplifier with $cc-cc$ configuration



if o/p + & feed
 back res - voltage
 & feed res
 are at different
 point then it

In the above circuit, the feedback resistor (R') is connected emitter of Q_2 to base of Q_1 - hence it acts as a feedback resistor.

\Rightarrow As we can short the o/p terminal the feedback signal does not become zero. At the same time, if we open o/p terminal the feedback signal becomes zero. Hence it is current sampling.

From i/p circuit by applying KCL at Node 'A'

$$I_s = I_b + I'$$

$$I_b = I_s - I'$$

$$I_b = I_s - I_f$$



feedback signal is subtracted from externally applied signal as current.

hence it is shunt mixing.

\therefore The type of feedback for above circuit is current shunt feedback.

circuit without feedback

Equivalent Circuit

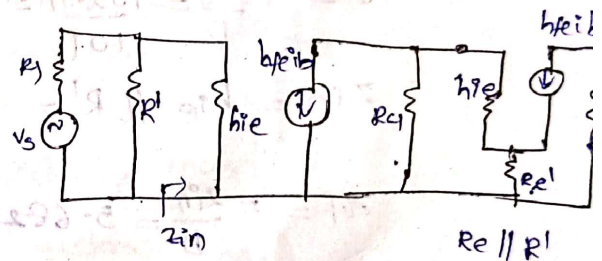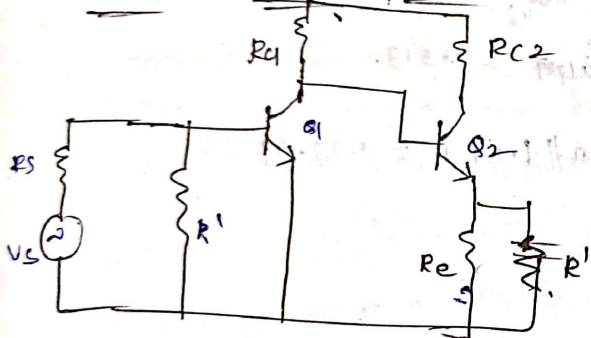

$$\beta = \frac{R_e}{R_e + R'}$$

$$A_I = A_{I1} \times A_{I2}$$

$$A_{I1} = h_{fe} \times h_{fe}$$

$$A_{I2} = (h_{fe})^2$$

$$D = 1 + A_I \beta$$

$$D = 1 + (h_{fe})^2 \left(\frac{R_e}{R_e + R'} \right)$$

$$A_{If} = \frac{A_I}{D} = \frac{(h_{fe})^2}{1 + (h_{fe})^2 \left(\frac{R_e}{R_e + R'} \right)}$$

voltage gain (A_v) = $A_{v1} \times A_{v2}$

$$A_v = \frac{h_{fe} R_{c1}}{h_{ie}} \times \frac{h_{fe} R_{c2}}{h_{ie}} \quad \left\{ \begin{array}{l} \text{For} \\ \text{CE amp} \end{array} \right.$$

$$A_v = \left(\frac{h_{fe}}{h_{ie}} \right)^2 \left[R_{c1} \times R_{c2} \right] \frac{h_{fe}}{h_{ie}} = \frac{h_{fe} R_{c1}}{h_{ie}} \times \frac{h_{fe} R_{c2}}{h_{ie} + (1 + h_{fe}) R_e}$$

$$A_{vf} = \frac{A_v}{D} = \frac{A_v}{D}$$

$$R_o = Z_o = \alpha$$

$$R_{if} = Z_{in} = h_{ie} \parallel R' \quad R_{of} = R_o = Z_o = \alpha \parallel R_{c2} = R_{c2}$$

$$R_{if} = Z_{if} = \frac{Z_{in}}{D}$$

$$Z_{of}' = R_{of}' = Z_o' \times D$$

For circuit shown in Fig. 1 as the following parameters $R_s = 1.2 k\Omega$

$R_{C1} = 3 k\Omega$, $R_{C2} = 500 \Omega$, $R_E = 50 \Omega$, $R' = 1.2 k\Omega$ / The transistors are identical with $h_{fe} = 50$, $h_{ie} = 1.1 k\Omega$, $h_{re} = h_{oe} = 0$. Determine

β , A_I , D , A_{I_f} , A_v , A_{v_f} , Z_{in} , Z_{if} , Z_o , Z_{of} .

$$\beta = \frac{R_E}{R_E + R'} = \frac{50}{50 + 1.2 k\Omega} = 0.04$$

$$A_I = A_{I1} \times A_{I2} = h_{fe} h_{fe} = 2500$$

$$D = 1 + A_I(\beta) = 101$$

$$A_{I_f} = \frac{A_I}{D} = \frac{2500}{101} = 24.7524$$

$$A_v = A_{v1} \times A_{v2}$$

$$= \frac{h_{fe} R_{C1}}{h_{ie}} \times \frac{h_{fe} R_{C2}}{h_{ie} + (1+h_{fe})R'_E} = \frac{50 \times 3000}{1100} \times \frac{50 \times 500}{1100 + 51 \times 50} = 933.997$$

$$R'_E = R_E \parallel R'$$

$$A_{v_f} = \frac{A_v}{D} = \frac{933.99}{101} = 9.2474 = 9.513$$

$$Z_{in} = h_{ie} \parallel R' = 1.1 k\Omega \parallel 1.2 k\Omega = 573.91 \Omega$$

$$Z_{if} = \frac{Z_{in}}{D} = \frac{573.91}{101} = 5.682 \Omega$$

$$R_{of} = Z_o = \frac{Z_o}{D} = \frac{500 \Omega}{101} = 4.95 \Omega$$

$$Z_o' = R_{of}' = Z_o'(D) = 500(101) = 50.5 k\Omega$$

2M We have an amplifier of 60 dB gain. It has an o/p impedance of $10 k\Omega$. It is required to modify its o/p impedance is 500Ω by applying \pm ve feedback. Calculate the values of feedback factor (β) also find the % change in overall gain for a 10% change in gain of the amplifier.

$$A_v = 20 \log(A_v) \text{ dB}$$

$$Z_o = 10 k\Omega$$

$$60 = 20 \log(A_v)$$

$$Z_{of} = 500$$

$$\log(A_v) = 3$$

$$Z_{of} = \frac{Z_o}{1 + A_v \beta}$$

$$A_v = 10^3 \text{ (Inverse log)}$$

$$1 + A_v \beta = \frac{Z_o}{Z_{of}}$$

$$A_v = 1000$$

$$\beta = \frac{Z_o}{Z_{of}} - 1 = 0.019$$

$$\frac{dA_f}{A_f} = \frac{dA}{A} \times \frac{1}{1+A\beta}$$


$$\frac{dA}{A} = 10\% = 0.1$$

$$\frac{dA_f}{A_f} = 0.1 \times \frac{1}{1+1000 \times 0.019}$$

$$\therefore \frac{dA_f}{A_f} = 0.005 \times 100 = 0.5\%$$

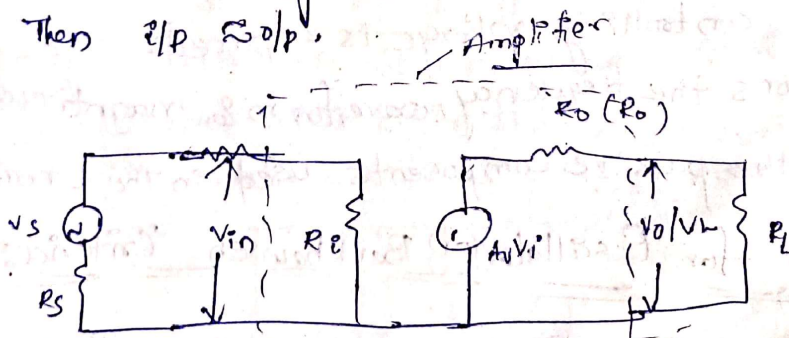- Q.1) What is regenerative (or) degenerative feedback amplification?
- 2) What is sensitivity of amplifier?
- 3) What is the effect of (-ve) feedback on bandwidth?
- 4) Draw the block diagram of feedback amplifier.
- 5) What type of feedback used in emitter follower (CC) amplifier?
- 6) When will (-ve) feedback amplifier circuit be unstable?
- 7) Why current shunt feedback is not used in practical circuit?
- 8) Distortion in an amplifier is found to be 3% when feedback ratio of (-ve) feedback amplifier is 0.04. When feedback is removed the distortion becomes 15%. Find the open & closed loop gains of the amplifier?

For any amplifier, its i/p resistance must be very high in comparison with R_s (source resistance) and o/p resistance must be very less in comparison with R_L (load resistance). Then i/p \approx o/p.



BJT & FET are a switching nature. BJT has switching time is high (less delay). FET switching time is less than BJT.

$$V_o = A_v V_i \left[\frac{R_L}{R_L + R_o} \right]$$

When $R_o \ll R_L$ then

$$V_o \approx A_v V_i$$

i/p \approx o/p

\Rightarrow o/p \approx source

$$V_i = V_s \left(\frac{R_i}{R_i + R_s} \right) \quad R_i \ll R_s$$

$$V_i = V_s \left(\frac{R_i}{R_s} \right) \quad \text{or } R_i \gg R_s$$


$$V_i \approx V_s$$

i/p = source

16/8/22

UNIT-5 (POWER AMPLIFIERS)

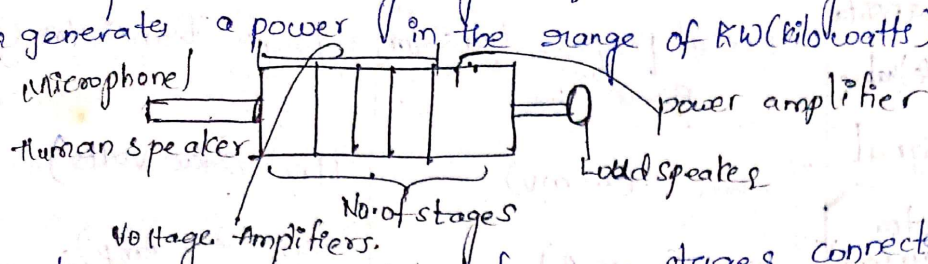Consider a public addressing system / amplified system as shown in fig. which generates a power in the range of kW (kilowatts).



⇒ The above system consists of many stages connected in cascade. Basically it is a multistage amplifier.

→ The i/p & intermediate stages are small signal amplifiers.

i.e. they provide sufficient voltage gain called as voltage amplifier. ⇒ But the last stage (power amplifier) gives up to the loud speaker like a load, hence it must be capable of handling large voltages (or) currents called as large signal amplifier.

⇒ The main aim is to develop sufficient power. Hence voltage gain is not important in the last stage, such a stage which develops sufficient power to the loud speaker to handle large signals is called power amplifier.

⇒ It is defined as the amplifier which raises the power levels of the signal i.e. both voltage as well as current levels of the signal.

⇒ It is also defined as a device / circuit which converts DC power to AC power, and whose action is controlled by i/p signal.

⇒ The transistor suitable for power amplifier is power transistor as it differs from conventional transistors in the following aspects:

- ① The area of collector region of power transistor is large.
- ② The emitter & base regions are heavily doped.
- ③ These are large in size and low β (h_{fe}) value (i.e. $\beta < 100$).

Application: ④ The power amplifiers find applications in public addressing systems, Radio receivers, Tape players (Tape recorder), CRO

etc.

Comparison of voltage amplifier & power amplifier

Characteristics	VA	PA
Basic function	To provide high voltages to load hence voltage gain is important.	To provide high power to the load, hence high voltages & currents are important.

characteristics

- 2) Analysis
- 3) Type of transistor & its β (h_{fe}) values
- 4) Input signal
- 5) o/p (collector current)
- 6) o/p power
- 7) load Resistance
- 8) o/p Impedance
- 9) Type of coupling
- 10) Type of configuration of Transistor

- 1) h-parameter model is used
- 2) General purpose transistor $\beta > 100$ (or) h_{fe}
- 1) low (few mv)
- 2) low (few mA)
- 3) low (few mwatts)
- 4) high (Range of $k\Omega$)
- 5) High (Range of $< 10k\Omega$)
- 6) RC coupling
- 1) CE configuration


- 1) load-line Analysis
- 2) Power transistor ($\beta < 85$) h_{fe}
- 1) High (few volts)
- 2) High (few Amp)
- 3) high (few watts)
- 4) low (in the range of ohms)
- 5) Low ($< 100\Omega$)
- 6) Transformer / Inductive coupling
- 1) CE configuration (Emitter follower)

Classification of Power Amplifiers (Large signal Amplifier)


On the basis of Mode of Operation (i.e) portion of the i/p signal during which collector current flows.

- 1) class-A
- 2) class-B
- 3) class-C
- 4) class AB power amplifier

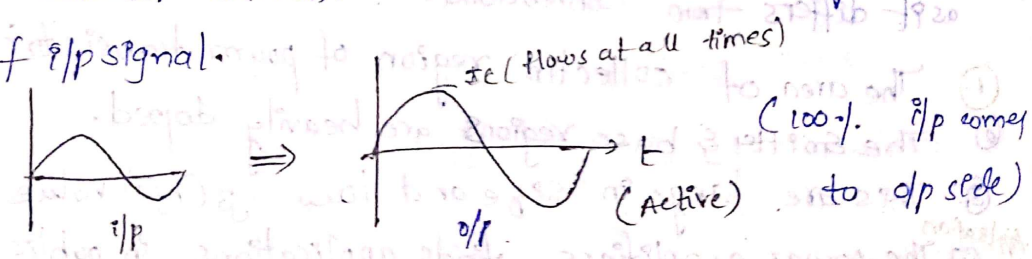
1) When collector current flow at all times during the full cycle of i/p signal.



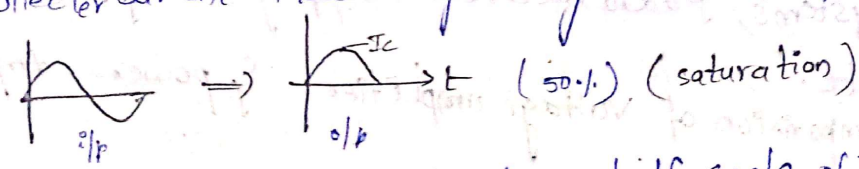
2) class-B: collector current flows only during either +ve / -ve half cycle.



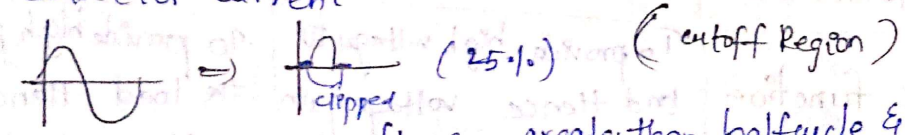3) class-C: collector current flows less than half cycle of the i/p signal.



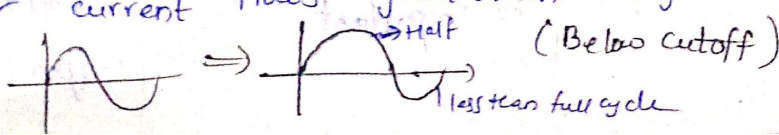4) class AB: collector current flows greater than half cycle & less than full cycle.



Class A Power Amplifiers

⇒ It is the one in which the o/p current flows during the entire cycle of the i/p signal.

⇒ The power amplifier is said to be class A if Q-point (operating or) Quiescent & i/p signal are selected in such a way that the transistor operates only over the linear (Active Region) of its load line.



⇒ For this the Q-point should be selected at middle of the load line.

⇒ For all values of i/p signal, the transistor remains in active region and never enters into saturation or) cutoff region.

⇒ When an AC i/p signal is applied the collector voltage varies sinusoidally. Hence collector current also varies sinusoidally for 360°

(Full cycle) of the i/p signal.

Fig shows the current & voltage wave forms of class A Amplifier with the help of load line & o/p characteristics.

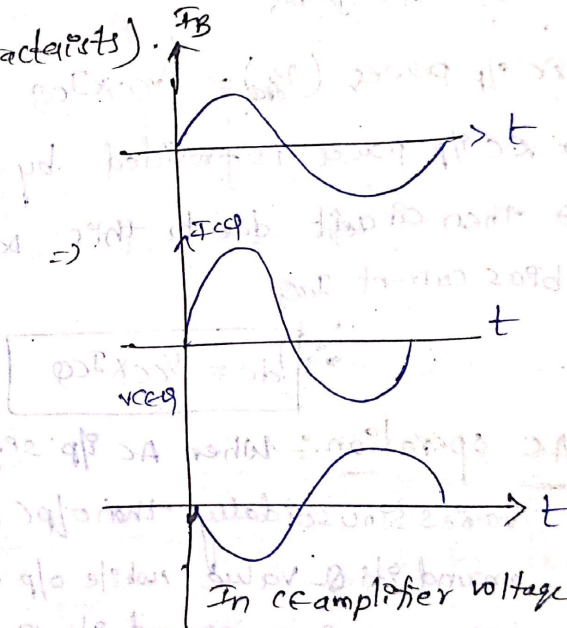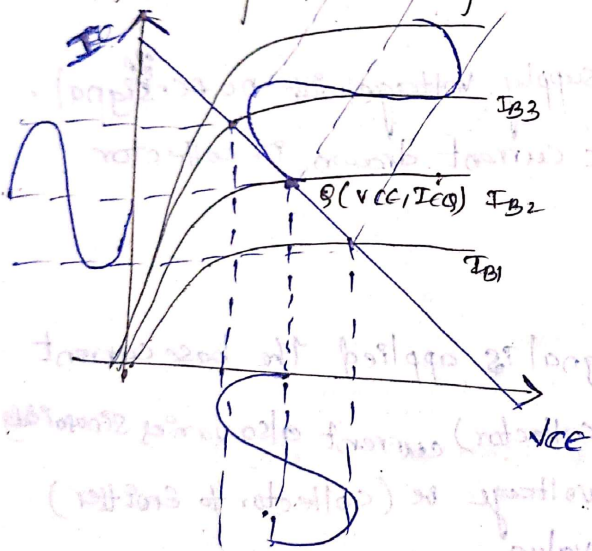

In CE amplifier voltage & current are out of phase. so (-ve to +ve)


Class A = series feed / Direct coupled.
Two types.

The below fig shows series feed class A power Amplifier

→ The circuit is also called direct coupled class A amplifier because o/p is directly connected to

Q (collector) resistance.

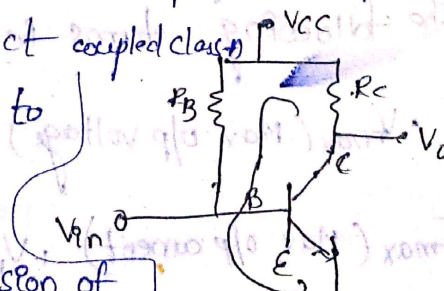→ The difference b/n small signal version of this circuit is i/p signals handled by this circuit is large. (order of volts) This circuit handles large voltages.



⇒ Similarly transistor used is power transistor.

⇒ Here value of R_B is selected in such a way that Q-point lies

centre of the DC load line.

DC operation:

→ We will study the operation of the circuit in absence of i/p AC signal. i.e. by considering supply voltage (V_{CC}).

→ We can evaluate, I_{BQ} , I_{CQ} , V_{CEQ}

→ By apply KVL to i/p loop: → By apply KVL to o/p loop.

$$V_{CC} - I_B R_B - V_{BE} = 0.$$

$$I_{BQ} = \frac{V_{CC} - V_{BE}}{R_B}$$

when $I_{CQ} = \beta I_{BQ}$

$$DC \text{ o/p power } (P_{DC}) = V_{CC} \times I_{CQ}$$

→ DC o/p power is provided by supply voltage with no AC signal.

→ Then circuit due to this DC current drawn is collector bias current I_{CQ}

$$P_{DC} = V_{CC} \times I_{CQ}$$

AC operation: When AC i/p signal is applied the base current varies sinusoidally then o/p (collector) current also varies sinusoidally around its Q-value while o/p voltage v_c (collector to emitter) voltage varies around its Q-value.

→ The varying o/p voltage & o/p current also vary sinusoidally.

→ For alternating o/p voltage & o/p current we can express the following terms be V_{min} , (minimum o/p voltage)

1. V_{max} (Max o/p voltage)

2. I_{min} (minimum o/p current)

I_{max} (Max o/p current) 1. V_{pp} = peak to peak o/p voltage / i/p voltage

I_{pp} - peak to peak o/p current 1. V_m = average o/p voltage

I_m - Average o/p current V_{rms} (RMS value)

I_{rms} = RMS value of o/p current.

Based on that notations,

$$V_{pp} = V_{max} - V_{min}$$

$$I_{pp} = I_{max} - I_{min}$$

$$V_m = \frac{V_{pp}}{2} = \frac{V_{max} - V_{min}}{2}$$

$$I_m = \frac{I_{pp}}{2} = \frac{I_{max} - I_{min}}{2}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$V_{rms} = \frac{V_m}{\sqrt{2}}$$

$$I_{rms} = \frac{I_m}{\sqrt{2}}$$

AC power o/p (P_{ac}) is the $P_{ac} = V_{rms} I_{rms}$

$$P_{ac} = \frac{V_m}{\sqrt{2}} \frac{I_m}{\sqrt{2}}$$

$$= \frac{V_m I_m}{2}$$

$$P_{ac} = \frac{(V_{max} - V_{min})(I_{max} - I_{min})}{2}$$

Efficiency (η) = $\frac{P_{ac}}{P_{dc}}$, It is the amount of AC power delivered (or) transferred to the load from DC source. It is the ratio of AC power o/p to DC power i/p.

$$\eta = \frac{P_{ac}}{P_{dc}}$$

$$\% \eta = \frac{P_{ac}}{P_{dc}} \times 100$$


$$\% \eta = \frac{(V_{max} - V_{min})(I_{max} - I_{min})}{2 \times V_{CC} \times I_{CQ}} \times 100 \quad \text{For class A}$$

It is also called as conversion factor ($\% \eta$).

Maximum Efficiency = we can assume Q point is middle of the load line as shown in fig.

$$V_{max} = V_{CC}, V_{min} = 0$$

$$I_{max} = 2I_{CQ}; I_{min} = 0$$

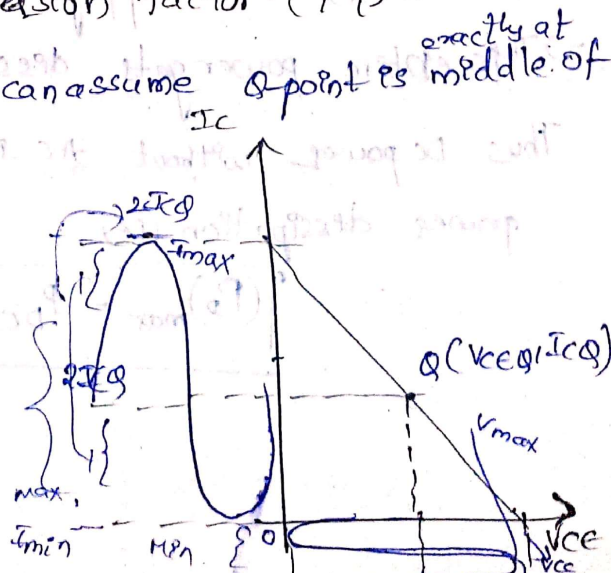

$$\text{Then, \% } \eta_{\max} = \frac{(V_{CC} - 0)(2I_{CQ} - 0)}{8 \times V_{CC} I_{CQ}} \times 100$$

$$= \frac{2 V_{CC} I_{CQ}}{8 V_{CC} I_{CQ}} \times 100$$

$$= \frac{1}{4} \times 100$$

$$\boxed{\% \eta_{\max} = 25\%}$$

Difference b/w ac power o/p to DC power i/p is called power dissipation.

→ For class A power Amplifier, efficiency is very low, i.e. 25%. Remaining 75% of efficiency is wasted within the circuit.

Power dissipation (P_D): The amount of power that must be dissipated by the transistor is the difference b/w DC power i/p and AC power delivered to the load.

$$\boxed{P_D = P_{DC} - P_{AC}}$$

→ The maximum power dissipation occurs when there is zero (AC) i/p signal.

→ When AC i/p signal is zero, the AC o/p power is also zero.

But the transistor operates at Q-point by drawing DC power i/p (P_{DC} i/p) from supply voltage.

→ This entire power gets dissipated in the form of heat.

Thus DC power without AC i/p signal is the maximum power dissipation (i.e.)

$$\boxed{(P_D)_{\max} = P_{DC} = V_{CC} I_{CQ} \text{ (from Q-point)}}$$

Advantages of class A (Direct coupled) :-

- circuit is simple to design & implement.
- load is directly connected to collector, this makes the circuit cheaper. (less cost)
- less no. of components are required.


Disadvantages :- efficiency is very poor (i.e. 25%).

- power dissipation is more (i.e. 75%).
- o/p impedance is high. Hence circuit cannot be used for loud speakers such as low impedance circuits.

Transformer Coupled class A power amplifier (It has impedance matching property)

The fig shows, the load resistor (R_L) is connected to secondary of the transformer and its primary is connected to collector circuit. Hence it is called

Transformer coupled Amplifier.

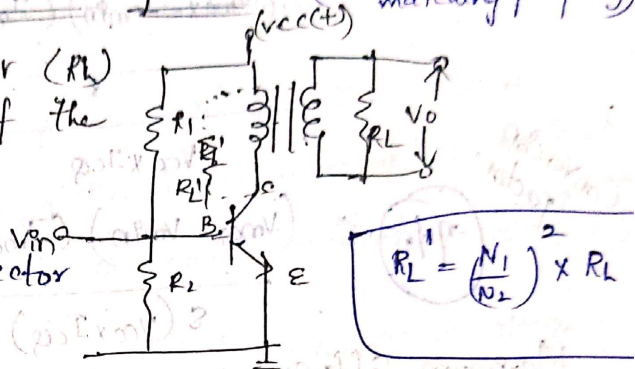

$$R_L' = \left(\frac{N_1}{N_2}\right)^2 \times R_L$$

Transformer coupled Amplifier.

- Due to impedance matching property of the transformer the load resistor (R_L) will appear as a reflective resistance at the primary winding, which is connected to collector circuit and it is given by

$$R_L' = \left(\frac{N_1}{N_2}\right)^2 \times R_L$$

n_1 - No. of turns on primary.

n_2 - No. of turns on secondary.

DC operation :- For this operation, we assume that no AC i/p signal. But we can operate the transistor with supply voltage or DC voltage.

Under this condition it is assumed that winding resistance of the transformer is zero. Hence for DC, resistance is zero.

Apply KVL to o/p

$$V_{CC} - V_{CE} = 0$$

$$V_{CEQ} = V_{CC}$$

$$I_{BQ} = \frac{V_{CC} - 0}{R_B}$$

where $R_B = R_1 // R_2$

$$I_{CQ} = \beta I_{BQ}$$

$$DC \text{ power } P_{DC} = V_{CC} \times I_{CQ}$$

AC operation: AC operation of transformer coupled is same as that of Direct coupled.

} content copy from AC in Direct coupled upto all formulas

$$i.e. P_{AC} = \frac{(V_{max} - V_{min})(I_{max} - I_{min})}{8}$$

$$\text{Hence, } \eta = \frac{P_{AC}}{P_{DC}} \times 100$$

$$= \frac{(V_{max} - V_{min})(I_{max} - I_{min})}{V_{CC} \times I_{CQ}} \times 100$$

Conversion Factor

$$\eta = \frac{(V_{max} - V_{min})(I_{max} - I_{min})}{8(V_{CC} \times I_{CQ})} \times 100$$

Maximum Efficiency:

$$V_{max} = 2V_{CC}$$

$$V_{min} = 0$$

$$I_{max} = 2I_{CQ}$$

$$I_{min} = 0$$

$$\eta_{max} = \frac{(2V_{CC} - 0)(2I_{CQ})}{8(V_{CC} \times I_{CQ})} \times 100$$

$$= \frac{1}{2} \times 100$$


$$\boxed{\eta_{max} = 50\%}$$

Power dissipation: $P_D = P_{DC} - P_{AC}$

$$(P_D)_{max} = P_{DC}$$

$$(P_D)_{max} = V_{CC} I_{CQ}$$

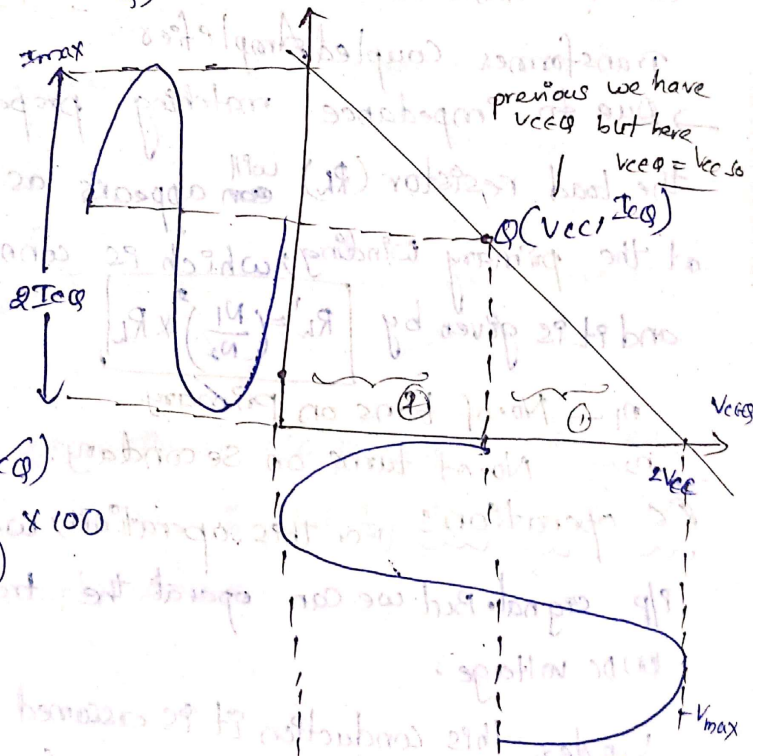for DC (Max power dissipation occurs at i/p ac = 0 only)



2V_{CC} because previous we have only V_{CEQ} only but here V_{CEQ} = V_{CEQ}

Advantages \Rightarrow Efficiency is improved from 25% to 50%

\rightarrow Power dissipation also reduces from 75% to 50% compared to Direct coupled.

\rightarrow Impedance matching is provided.

Disadvantages \Rightarrow Due to transformer, circuit becomes bulky, heavier and costly.

\rightarrow circuit is complex to design.

\rightarrow Frequency response is poor due to transformer.
List the differences b/n Direct coupled & Transformer coupled class-A power Amplifier? (Imp)

class B power Amplifier \Rightarrow The power amplifier is said to be class-B, if the Q-point & i/p signal are selected such that o/p signal is obtained only for ^{one} half cycle (either +ve / -ve) for a full cycle i/p.



\rightarrow For this operation, Q-point is shifted on X-axis i.e. voltage axis. The transistor is biased to cutoff region.


\rightarrow Due to the selection of Q-point on X-axis the transistor remains in active region only for +ve half cycle of the i/p. Hence this half cycle is reproduced at the o/p. (fig 1).

\rightarrow But in a -ve half cycle, transistor enters into cutoff region and no signal is produced at o/p.

\rightarrow The collector current flows only 180° (i.e. half cycle) of the i/p signal.

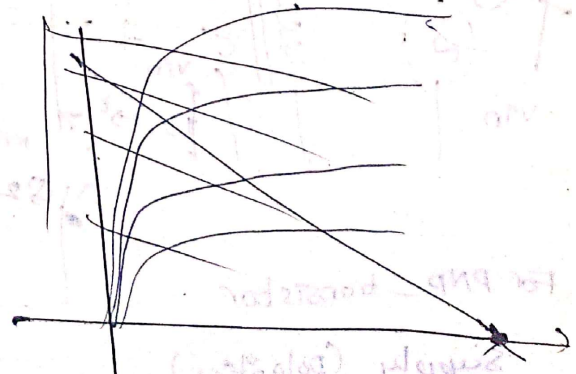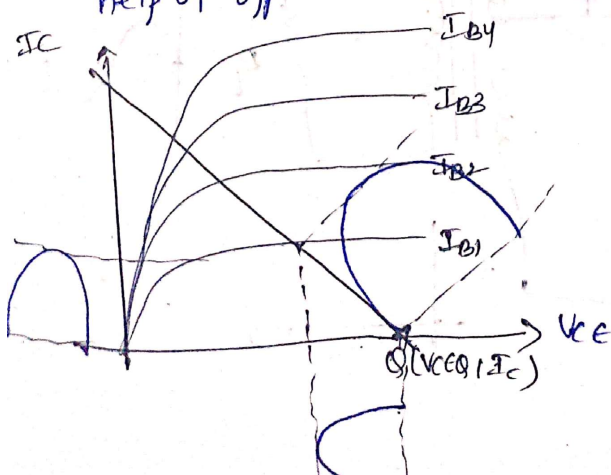\rightarrow The waveforms of I_B , I_{CQ} , V_{CE} are shown in fig. with the help of o/p characteristics with load line.



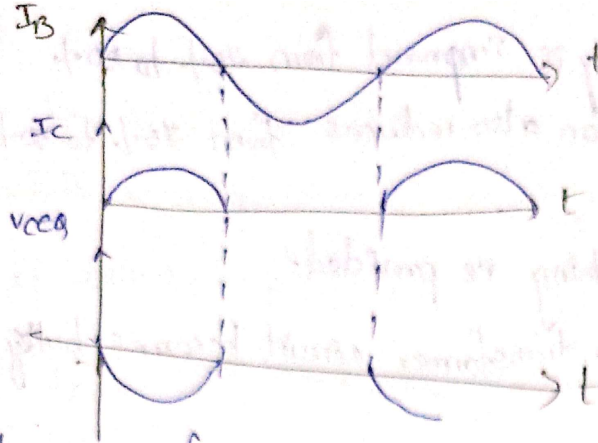

From above wave-forms, for class-B operation the Q-point is selected on y-axis itself due to this I_C (collector current) flows only for half cycle for a given full cycle i/p.

→ Due to this the o/p signal is distorted. To get full cycle o/p across the load a pair of transistors are used in class-B operation.

→ The two transistors conduct in alternate half cycles of i/p and get a full cycle o/p across the load.

→ Depending upon type of transistors whether NPN (or) PNP.

class-B power amplifiers are of two types


1) Push Pull class-B power amplifier (Both transistors are same type)

2) I_C (either NPN (or) PNP).

3) Complementary symmetry class-B: when one transistor is NPN and another transistor is PNP.

Pushpull class-B power amplifiers: It requires two

transformers.

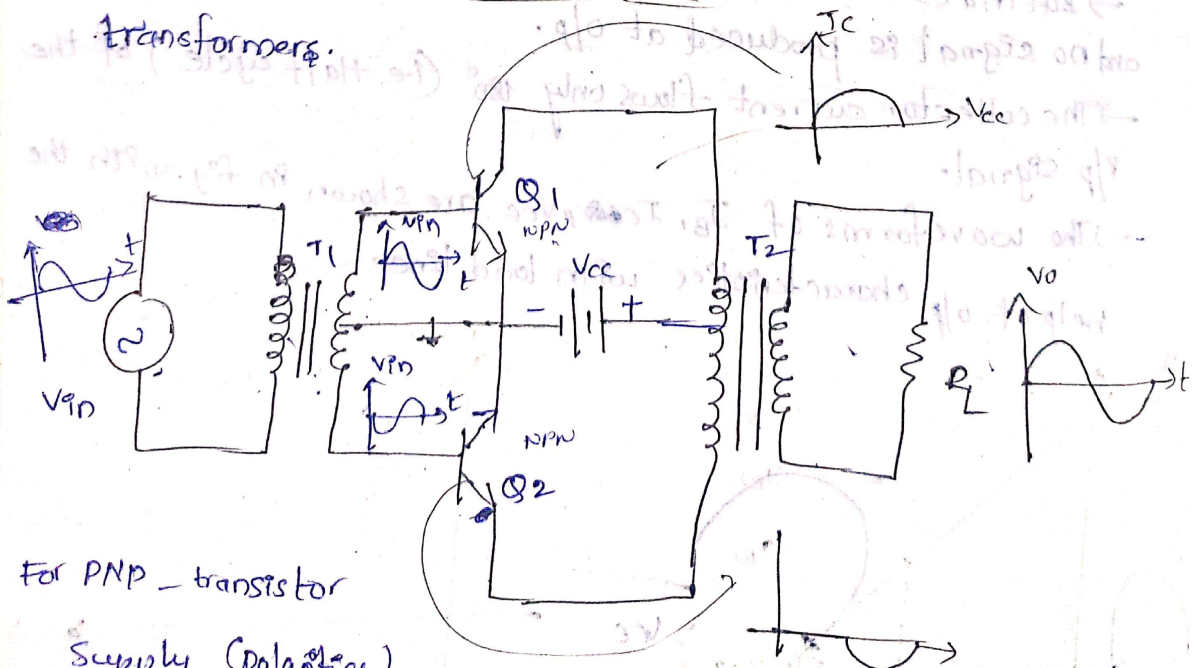

For PNP - transistor

Supply (polarities)

changes $Q_1(+ -)$

The above fig. requires two transformers.

- 1) Input transformer (Driver transformer) and the other to connect to load
- 2) Output transformer the input signal is applied to the primary of driver transformer and the load resistor (R_L) is connected to secondary of output transformer.

→ Both the transformers are of centre tapped transformers.

→ It uses two transistors (Q_1 & Q_2) of same type called NPN


→ Suppose the circuit uses PNP type then the supply voltage must be $(-V_{CC})$ (i.e. $+V_{CC}$).

→ Here both transistors are configured in CE configuration.

→ In a centre tapped for (+ve) cycle of i/p, the Q_1 (ON) transistor conducts while Q_2 transistor is in cutoff (open) and during (-ve) half cycle the Q_1 transistor (OFF) cutoff and Q_2 transistor is active (ON)

→ so o/p voltage across load is a full cycle of o/p for a full cycle of i/p.

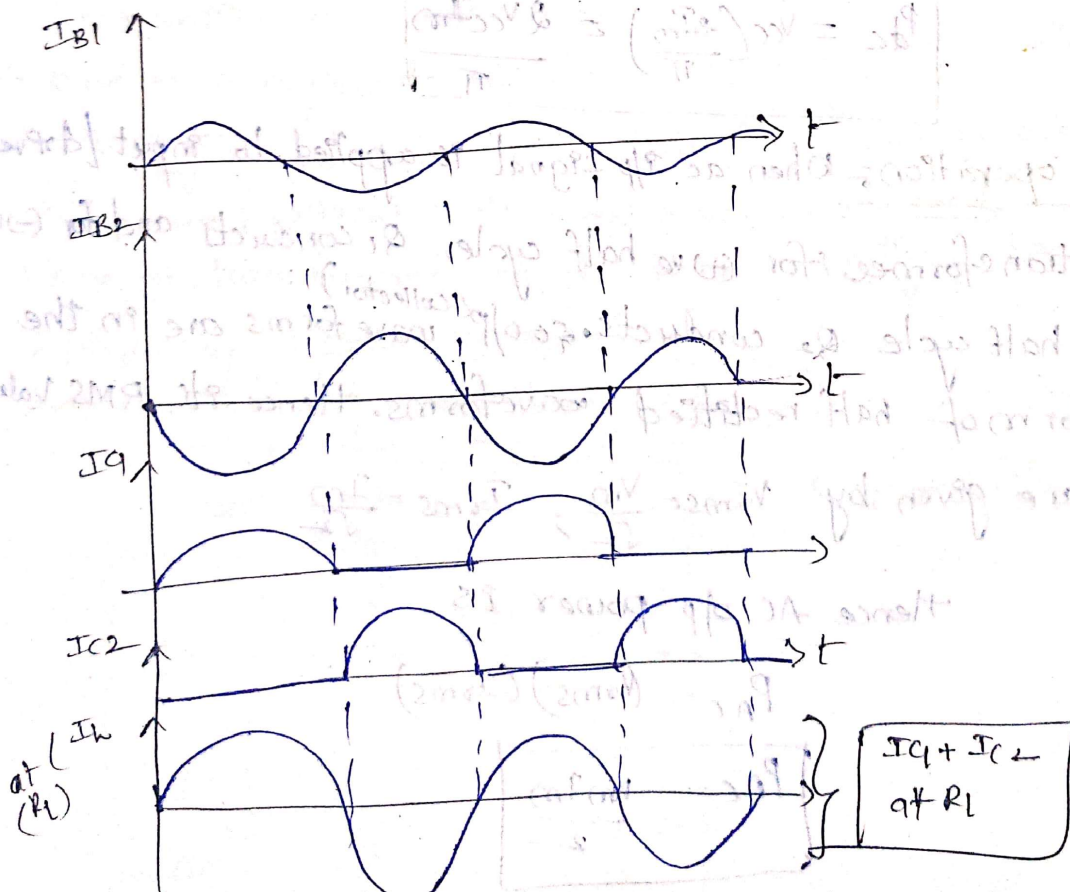The below fig. shows the waveforms of currents.



DC operation: DC biasing point (Q-point) is adjusted

on to the X-axis such that $V_{CEQ} = V_{CC}$ & $I_{CQ} = 0$.

Hence Q-point is $Q(V_{CC}, 0) = Q(V_{CE}, 0)$. There is no d.c.

base bias voltage. [\because as $I_E = 0 \Rightarrow I_B = 0$].

DC input power:

Each transistor o/p is in the form of half-wave rectified wave form. Hence if I_m is the peak value of the output current of each transistor. Then average d.c. value

is $I_{DC} = \frac{I_m}{\pi}$ due to half-wave rectified o/p.

→ For full cycle of o/p, $I_{DC} = \frac{I_m}{\pi}$ for half and $I_{DC} = \frac{I_m}{\pi}$ for next half (-)ve cycle.

$$\therefore I_{DC} = \frac{I_m}{\pi} + \frac{I_m}{\pi}$$

$$I_{DC} = \frac{2I_m}{\pi}$$

$$P_{DC} = V_{CC} \left(\frac{2I_m}{\pi} \right) = \frac{2V_{CC}I_m}{\pi}$$

AC operation: When ac i/p signal is applied to input / driver transformer, for (+)ve half cycle, Q_1 conducts and for (-)ve half cycle Q_2 conducts. So o/p (collector) wave forms are in the form of half-rectified waveforms. Hence its RMS values

are given by $V_{rms} = \frac{V_m}{\sqrt{2}}$; $I_{rms} = \frac{I_m}{\sqrt{2}}$

Hence AC o/p power is

$$P_{AC} = (V_{rms})(I_{rms})$$

$$P_{AC} = \frac{V_m I_m}{2}$$

efficiency $\eta = \frac{P_{ac}}{P_{dc}}$

$\eta \% = \frac{P_{ac}}{P_{dc}} \times 100 = \frac{V_m I_m}{2} \times \frac{\pi}{2 V_{cc} I_{cm}} \times 100$

$\eta \% = \frac{V_m I_m}{2} \times \frac{\pi}{2 V_{cc} I_{cm}} \times 100$

$\eta \% = \frac{\pi}{4} \left(\frac{V_m}{V_{cc}} \right) \times 100$

$\eta \% = \frac{\pi}{4} \left(\frac{V_m}{V_{cc}} \right) \times 100$

Maximum Efficiency:

$\eta \%_{max} = ?$

For maximum efficiency:

$V_m = V_{cc}$ // point is on x-axis

$\therefore \eta \%_{max} = \frac{\pi}{4} \times 100$

$\eta \%_{max} = 78.5\%$

→ Power dissipation is same.

Advantages: Efficiency is improved (higher than class A).

→ when there is no i/p signal power dissipation is zero

(ie transistors are not working).

→ Due to transformers impedance matching is possible.


Disadvantages: Two centre tapped transformers are required

(ie we want alternate cycles (+ve) & (-ve) (ie centre-tapped).

→ Due to transformers circuit becomes costly & heavy.

→ Frequency response is poor.

Complementary Symmetry class-B:

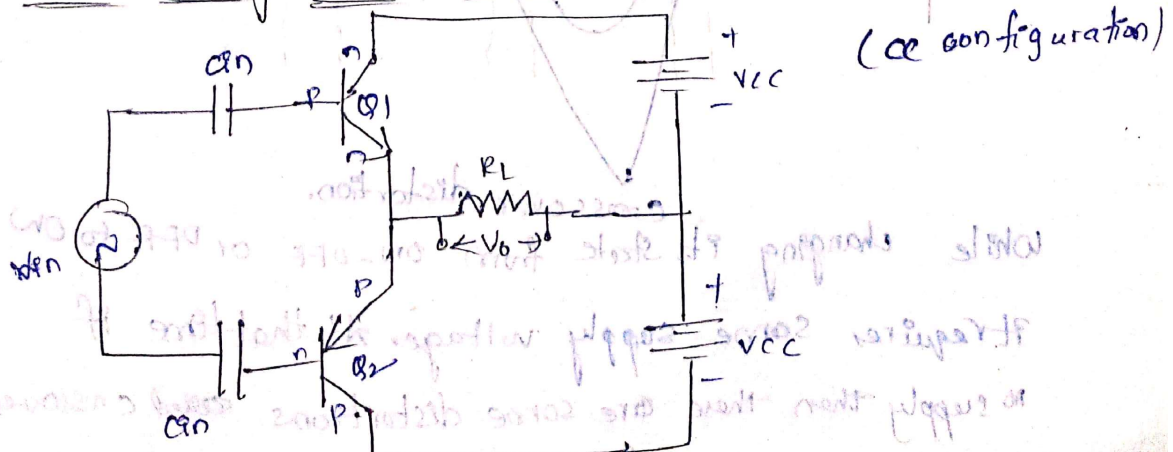

- ⇒ Transformers are removed.
- ⇒ Two supply voltages are required. (+) for NPN, (-) for PNP
- ⇒ The ^{two} transistors are configured in a configuration
- ⇒ The transistors used are NPN & PNP.

operations all are same as pushpull class-B amplifier.

Efficiency also same.
 cc has load of Impedance so we can connect to loud speakers


Advantages:

- As the circuit is transformerless. Hence its weight, size, cost are low.
- Due to common collector, impedance matching is possible
- frequency response improves.

Disadvantages:

- circuit needs two power supplies (1 for NPN & 2nd for PNP)
- output is distorted due to crossover distortion.

Crossover distortion in class B:

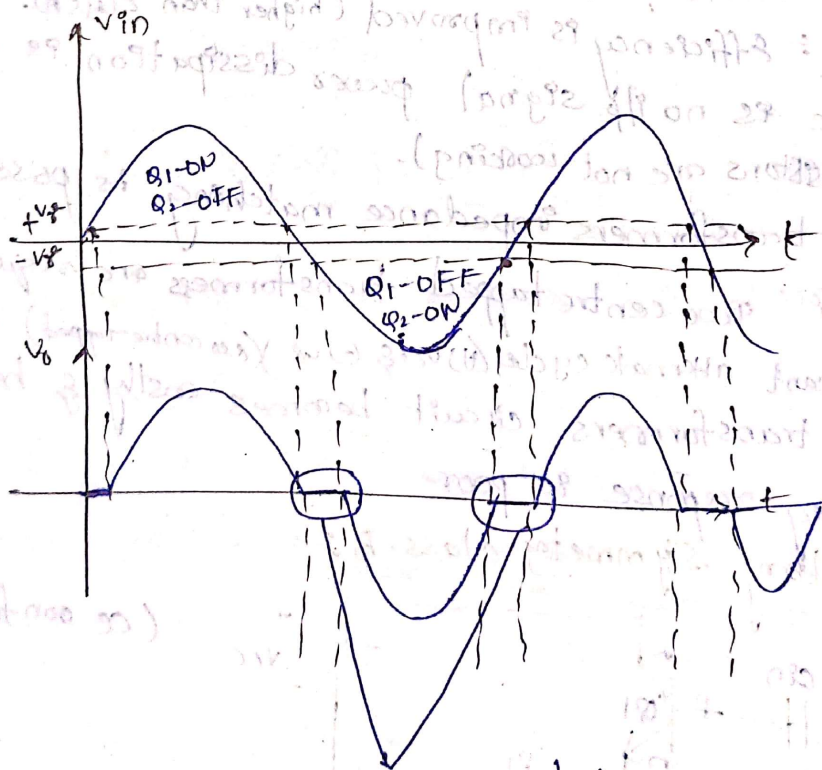

crossover distortion.

while changing its state from on-off or OFF to ON it requires some supply voltage. At that time if no supply then there are some distortions called crossover.

junction must be forward bias. The junction can't be made forward bias till the i/p voltage becomes greater than cut in voltage of the junction for which generally 0.7V for silicon, and 0.3V for Germanium.

Hence as long as the magnitude of the i/p signal, is less than cut in voltage of emitter base junction and greater than cut in voltage, i.e. collector current remains zero and transistor remains in cutoff region. So there is a period / time b/w the crossings of half cycles, for which none of the transistor is in active region & o/p is zero. Such a distorted o/p waveform due to cut in voltage as shown in fig. is called crossover distortion.

→ To eliminate the crossover distortion some modifications are necessary in the basic circuit of class-B which is called class AB power amplifier.

The loudspeaker of 8Ω , is connected to the secondary of o/p transformer of class-A power amplifier. The Q-point collector current is 140mA . The turns ratio of transformer is 3:1. The collector supply voltage is 10V if AC power delivers to the load speak is 0.48watt . Calculate DC power i/p, Efficiency, and power dissipation.

Given $I_{CQ} = 140\text{mA}$

$P_{ac} = 0.48\text{ watt}$

$V_c = 10\text{V}$

$\frac{N_1}{N_2} = 3:1$

$R_L = 8\Omega$

DC i/p power = $V_{CC} \times I_{CQ}$

= $10 \times 140 \times 10^{-3}$

= 1400×10^{-3}

$P(Dc) = 14 \times 10^{-1} = 14\text{ watts}$

$$\eta\% = \frac{\text{AC power o/p}}{\text{DC power i/p}} \times 100$$

$$\boxed{\eta\% = 34.28\%}$$

$$\text{power dissipation} = P_{DC} - P_{AC}$$

$$\boxed{(P_D) = 0.92 \text{ watts}}$$

A class-B push pull amplifier supplies power to a resistive load of 12Ω . The o/p transformer has a turns ratio 3:1 and efficiency of 78.5%. calculate (i) Max o/p power (ii) Max power dissipation in each transistor.

$$N_1 : N_2 = 3:1$$

$$P_{AC} = \frac{V_m I_m}{2} \quad \eta\% = 78.5\%$$

$$P_{AC} = \frac{V_m I_m}{2}$$

$$\text{let us assume } V_m = V_{CC} = 20V, I_m = V_m$$

$$P_{AC} = \frac{V_m^2}{2RL}$$

$$R_L = \left(\frac{N_1}{N_2}\right)^2 \times R_L = 108\Omega$$

$$\text{Max power dissipation } (P_{AC}) = \frac{20^2}{2 \times 108} = 1.85 \text{ watts}$$

We know that

$$P_{DC} = \frac{P_{AC}}{\text{eff}\%} \times 100 \Rightarrow \frac{1.85}{0.785} = 2.356 \text{ watt}$$

$$P_{DC} = 2.356 \text{ watt}$$

$$\therefore \text{Power dissipation} = P_{DC} - P_{AC} = 2.35 - 1.85 = 0.5 \text{ watt}$$

$$\therefore \text{For each transistor} = \frac{P_D}{2} = 0.25 \text{ watts.}$$

class-B pushpull delivers a load of 16Ω , connected to the secondary of ideal transformer ($n_1 = n_2 = 1:1$). Supply voltage is $25V$. If the no. of turns on secondary is 50. Calculate efficiency?

$$R_L = 16\Omega; V_{CC} = 25V; N_2 = 50 = N_1 = 50; R_L' \text{ also } = 16\Omega$$

$$P_{ac} = \frac{V_m I_m}{2}$$

$$P_{dc} = \frac{2V_m^{V_{CC}} (I_m)}{\pi} = 2 \times \frac{25 \times V_{CC}}{\pi R_L}$$

$$P_{dc} = \frac{2 \times 25 \times 25}{\pi \times 16}$$

$$P_{dc} = 24.88 \text{ watts.}$$

$$P_{ac} = \frac{V_m^{V_{CC}} I_m}{2} = \frac{25 \times 25}{2 \times 16} = 19.53 \text{ watts}$$

$$\% \eta = \frac{P_{ac}}{P_{dc}} \times 100 = \frac{19.53}{24.88} \times 100 = \underline{\underline{78.496}}$$

4) A class-B pushpull amplifier supplies power to a load speaker of 10Ω , the o/p transformer turn ratio of $n_1:n_2$ of $4:1$ and efficiency is 95% . Calculate the
 (i) Max power o/p (P_{ac}) (ii) Max power dissipation (P_d)
 (iii) Max Base currents of each transistor.

$$P_{ac} = \frac{V_m I_m}{2}$$

$$\text{Let } V_m = V_{CC} = 20V$$

$$= \frac{(V_m)^2}{2R_L'} = 1.25 \text{ watts.}$$

$$R_L' = \left(\frac{n_1}{n_2}\right)^2 \times R_L = 160\Omega$$

$$P_{dc} = \frac{P_{ac}}{\eta} \times 100 = \frac{1.25}{0.95} = 1.315 \text{ watts}$$

$$P_d = P_{dc} - P_{ac} = 0.065 \text{ watt}$$

$$P_{d/2} = \text{for each transistor} = 0.0325 \text{ watt.}$$

3) For max Base current

$$P_{dc} = \frac{2V_{CC} I_{m0}}{\pi}$$

$$(I_{m0} = I_c)$$

$$I_c = \beta I_B$$

$$I_B = I_c / \beta$$

$$I_{m0} = 0.10322$$


Assume $h_{fe} = 25$

$$I_{B_{max}} = 4.12 \text{ mA}$$


Class-C power amplifier (used in radio frequency amplifiers)


Q-point is selected

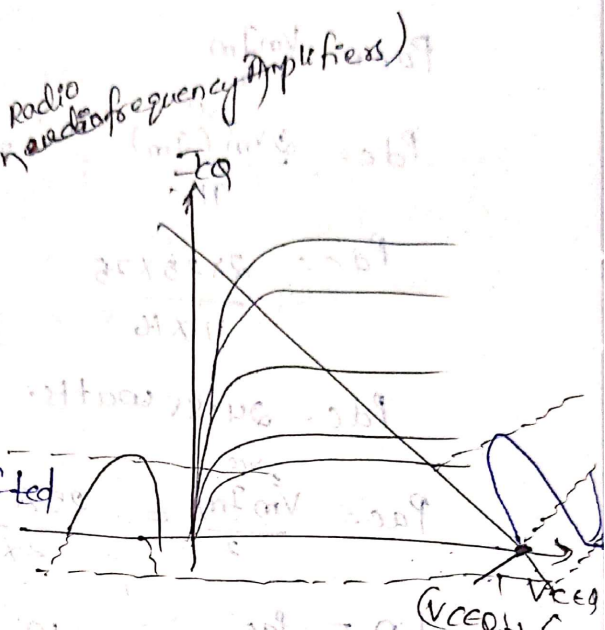For this operation, Q-point is shifted below x-axis (or) voltage axis as shown in figure.



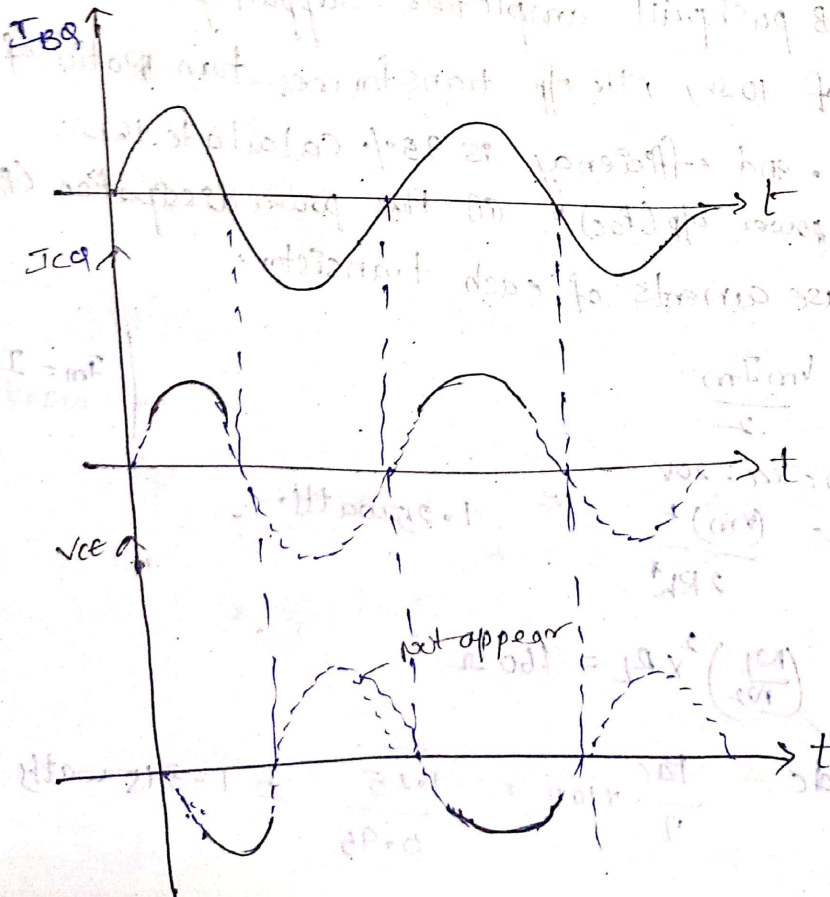The nature of i_B & v_{CE} waveform of class C amplifier



Due to such selection of Q-point transistor remains in active region for less than half cycle. Hence only that much of part is reproduced at the o/p ()

→ for remaining cycle of the i/p transistor remains in cutoff and no signal is reproduced, at the o/p.



→ So collector current flows less than 180° .

→ In class C operation, the transistor is biased behind cutoff region so output is more distorted and it is never used for audio frequency power amplifiers. But it is used in radio frequency power amplifiers because efficiency is much higher and can reach very close to 100%.

Class AB Power Amplifier:

The power amplifier is said to be class AB, if Q-point and the i/p signal are selected such that the o/p signal is obtained for more than 180° but less than 360° for full i/p cycle.

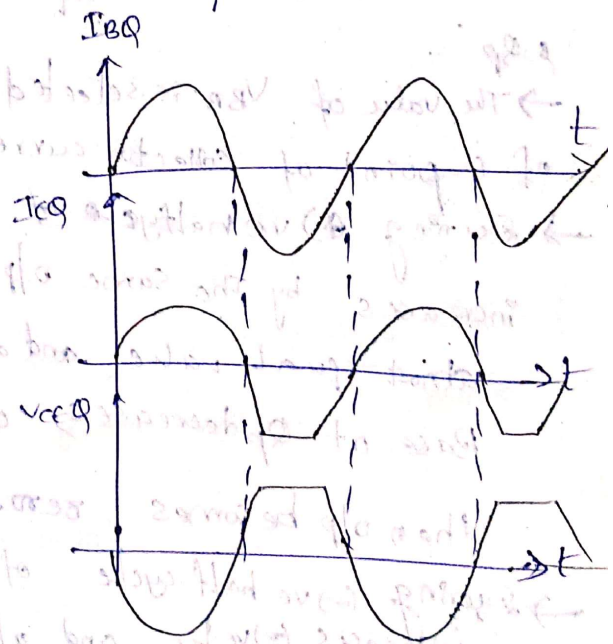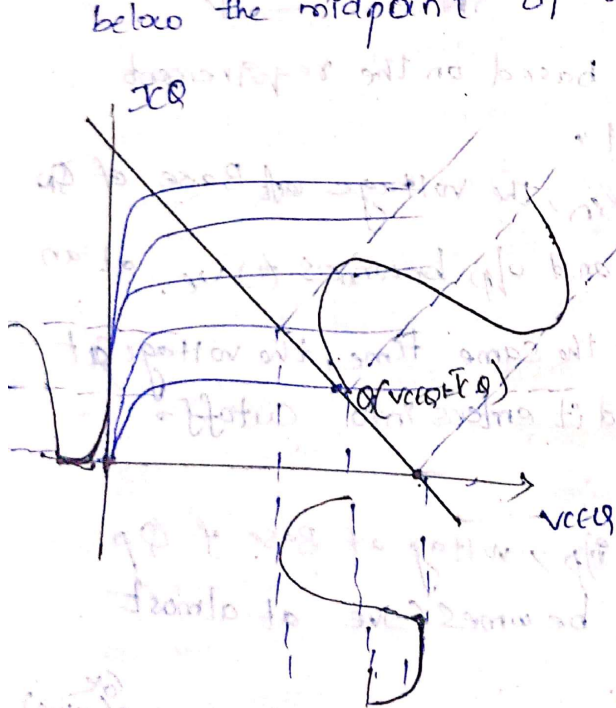→ For this operation, Q-point is selected above x-axis but below the midpoint of load line.



→ In this operation o/p signal is distorted but efficiency is more than class-A and it is important to eliminate crossover distortion of class-B operation (Amplifier)

→ Definition, θ point, efficiency, Distortion, power dissipation, } For differences b/w power Amplifiers

Class AB - power dissipation - Moderate.

Analysis of class AB:


class AB o/p stage:

Crossover distortion can be eliminated by biasing complementary transistors at a small non-zero circuit current.

→ The resultant circuit is the class AB power amplifier.

→ In the circuit, bias voltage (V_{BB}) is applied b/w the bases of Q_N & Q_P .

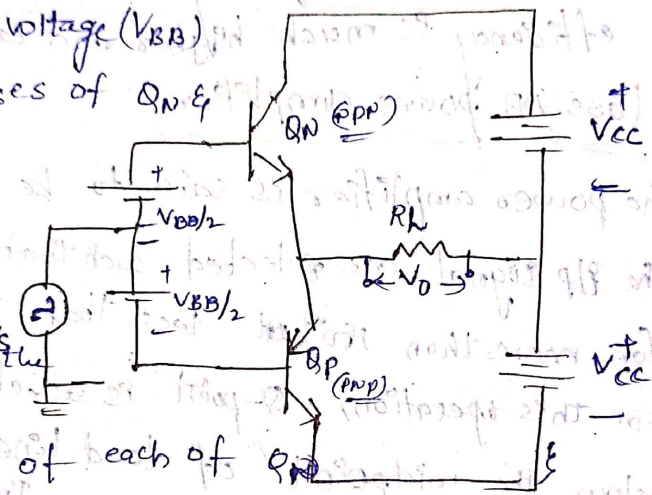→ Suppose for $V_{in} = 0$ and $V_o = 0$ and voltage of V_{BB} appears across the emitter base junctions of each of Q_N & Q_P .



→ The value of V_{BB} is selected based on the requirement of Q-point of collector current.

→ During (+)ve half cycle of V_{in} , the voltage at Base of Q_N increases by the same o/p. and o/p becomes (+)ve, at an almost equal value. and at the same time, the voltage at Base of Q_P decreases, and it enters into cutoff.

then o/p becomes zero.

→ During (-)ve half cycle of i_{ip} , voltage at Base of Q_P increases (-)vely, and o/p becomes (-)ve at almost equal values.

→ At the same time, voltage at Base of Q_N decreases (+)ve then transistor Q_N enters into cutoff. So o/p will current I_c or $V_{CC} = 0$ (o/p voltage)

→ For full cycle of i/p signal, voltage across Load resistor is also full cycle without any distortion.
 Note: ANALYSIS of class AB is same as that of class B Amplifier (DC, AC operation, efficiency)

Advantages
 crossover distortion is eliminated.

→ efficiency is improved.

Disadvantages:

More voltage sources are required. (u)

Various Biasing

Circuits of class AB

① Biasing using diodes:

② Biasing using V_{BE} amplifiers:

→ In fig 1, class AB circuit in which the biasing voltage V_{BE} is generated by passing a constant current source (I_{Bias}) through a pair of diodes D_1 & D_2 .



→ In this circuit it supplies large currents of power, even though biasing diodes are small in size (ie need not be large devices) and quiescent collector current established in Q_N & Q_P will be

$$I_{CQ} = \eta I_{Bias}$$

where $\eta =$ Ratio of emitter junction area of the o/p devices to the junction area of the biasing diodes.
 → Advantage of this arrangement is it can provide thermal stabilisation and it dissipates power under DC ~~power~~ operation also. At the same time

Disadvantage: we can provide constant voltage (ie biasing voltage) in some case it is not sufficient to drive Q_N & Q_P .

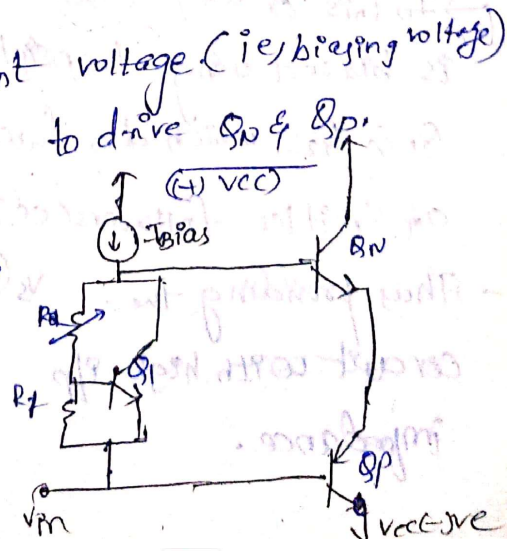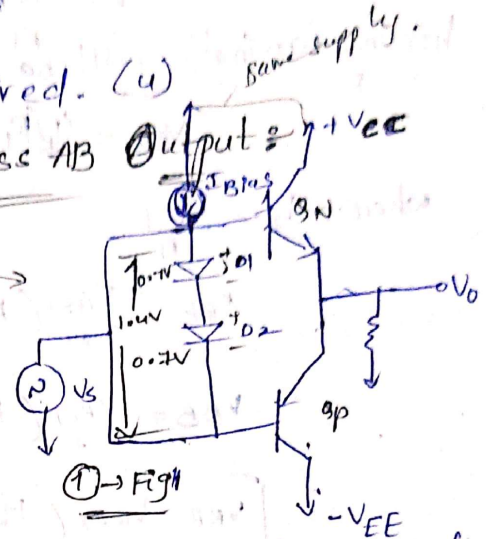③ Biasing using V_{BE} amplifiers:
 The circuit is alternative biasing arrangement that provides with considerable more flexibility.



to change the biasing voltage for Q_n & Q_p transistors. In the basic circuit consists of Transistor Q_1 with R_1 connected b/w base & emitter and R_2 is connected b/w collector & base and resulting two terminals is connected with a constant current source I_{Bias}

→ If we neglect base current of Q_1 then R_1 & R_2 resistors will carry same current is

$I_R = \frac{V_{BE1}}{R_1}$ and the voltage across V_{BB} across biasing terminals will be

$$V_{BB} = I_R(R_1 + R_2)$$

where $I_R = \frac{V_{BE1}}{R_1}$

$$V_{BB} = \frac{V_{BE1}}{R_1} (R_1 + R_2)$$

$$V_{BB} = \frac{V_{BE1}}{\beta} \left(1 + \frac{R_2}{R_1} \right)$$

$$V_{BB} = V_{BE1} \left(1 + \frac{R_2}{R_1} \right)$$

Thus above circuit simply multiplies V_{BE} by a factor $\left(1 + \frac{R_2}{R_1} \right)$ and is known as V_{BE} multiplier. → this multiplication factor depends on the selection of R_1 & R_2 value

Variations on the class AB o/p:

① Use of P/P emitter followers (or) ③


CC provides high P/P impedance.

(or) emitter followers

→ In this circuit class AB o/p stage is biased using transistors Q_1 & Q_2 which also function as emitter followers (CC)

→ Thus providing the circuit with high P/P impedance.

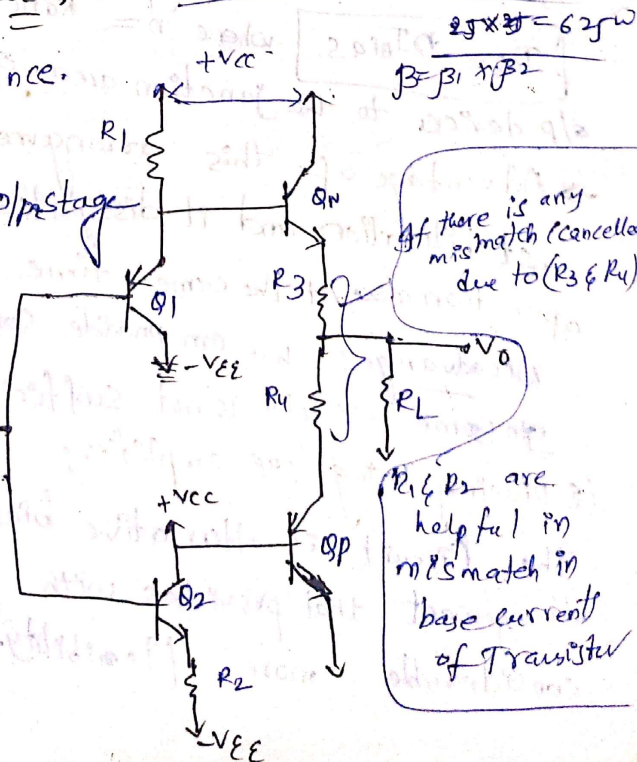Modification of Biasing voltage V_{BE} amplifier.





$\beta = \beta_1 \times \beta_2$

If there is any mismatch (cancel) due to $(R_3 \& R_4)$


R_3 & R_4 are helpful in mismatch in base current of transistor

- Here transistors Q_1 & Q_2 circuit function as unity gain power amplifiers (Buffer amplifiers)
- Since all 4-transistors are usually matched and neglecting the effect of R_3 & R_4 .
- Quiescent currents of Q_n & Q_p are equal to Q_1 & Q_2 .
- The resistors R_1 & R_2 are usually very small and are included, to compensate possible mismatch b/w base currents of transistors.
- Main drawback of this circuit is it requires high quality PNP transistors and it cannot provide high current gains & power gains because of power transistors with low β value.

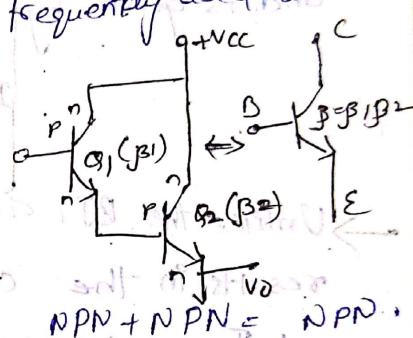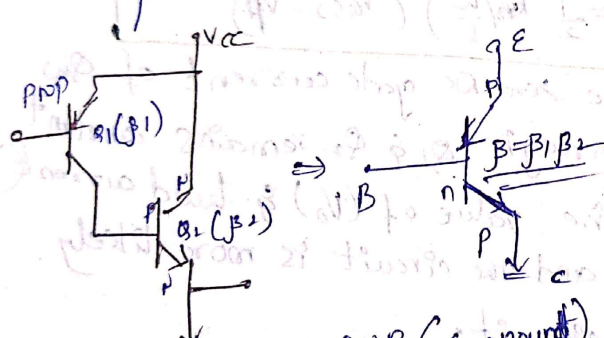② Use of compound devices :- To increase the current gain of the o/p stage transistors and reduce the required base current. Darlington pair is frequently used to replace NPN transistor & a compound pair is frequently used to replace PNP transistor.



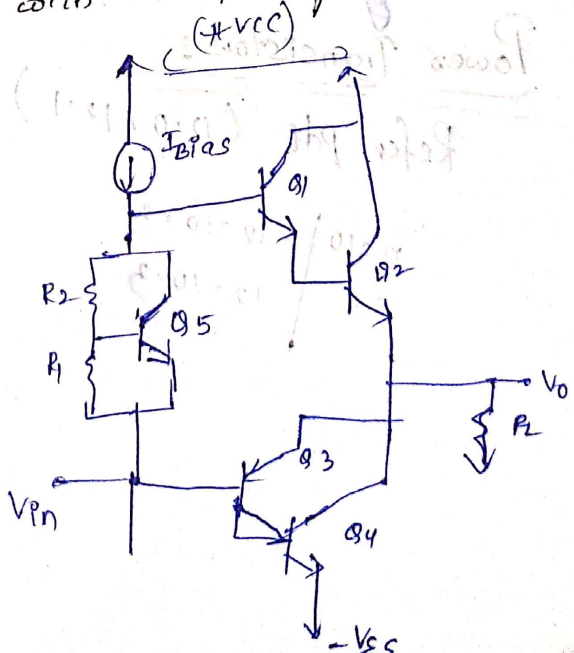
PNP + NPN = PNP (Compound)
 The below fig shows Class AB o/p with use of compound configurations and biased by V_{BE} Multiplier.



CMOS class AB o/p stage:

The circuit shows the classical CMOS class AB o/p stage

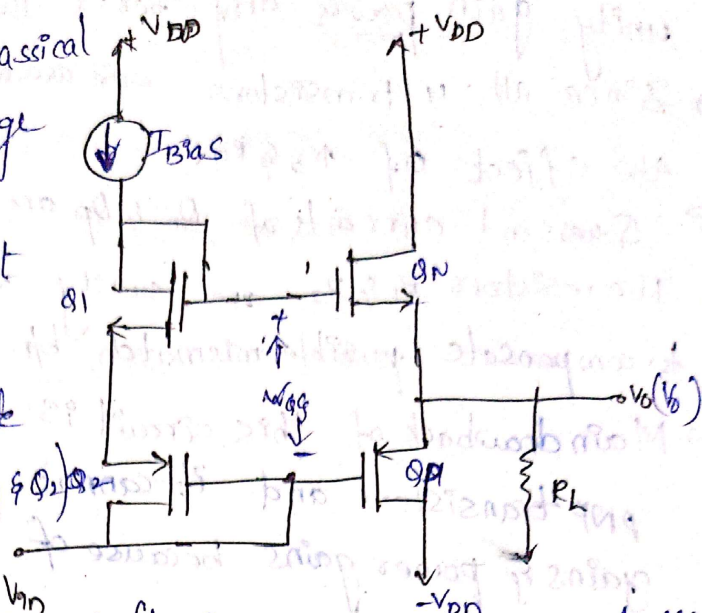→ The circuit is the exact counter part of BJT circuit with the biasing diodes implemented with diode connected transistors Q_1 & Q_2 of same type.



→ The constant current (I_{Bias}) flowing through Q_1 & Q_2 established a DC bias voltage (V_{GS}) b/w gates of Q_N & Q_P . This voltage in turn establish the Quiescent current (I_D) in Q_N & Q_P transistors and is given by

$$I_{D1} = I_{Bias} = \frac{1}{2} k_n' \left(\frac{W}{L}\right) (V_{GS1} - V_{th})^2$$

$$I_{D2} = I_{Bias} = \frac{1}{2} k_p' \left(\frac{W}{L}\right) (V_{GS2} - V_{th})^2$$

→ Unlike the BJT circuit, here zero DC gate current of Q_N results in the current through Q_1 & Q_2 remains constant at I_{Bias} , irrespective of the value of (V_o) & load current (I_L)

→ Thus V_{GS} remains constant and the circuit is more likely ideal as that of BJT circuit.

Power Transistors:

Refer p.d.f (12.0, 12.1)

12.10 → 12.10.2
12.10.3

Refer


6. OSCILLATORS & TUNED AMPLIFIERS

Introduction to oscillators:- The electronic circuit which produces an alternating voltage (or) current is called an oscillator.

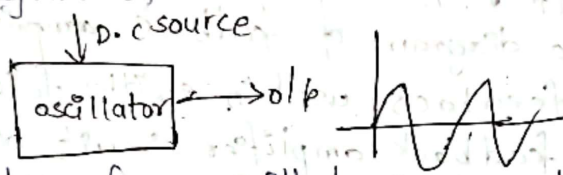(1) Circuit which generates an AC o/p signal without requiring any externally applied i/p signal.

→ It may also be defined as the circuit which converts DC signal to AC signal & is called an oscillator.

→ It is opposite to that of a rectifier. The below fig. shows the block diagram of an oscillator.



→ The function of an oscillator is similar to that of an amplifier. But the basic difference between an amplifier & an oscillator can be stated as follows.

1) The amplifier takes energy from a DC source and converts it into an AC source at signal frequency. In this, the frequency, waveform, and magnitude of the AC signal generated is controlled by the AC signal applied at the i/p.


2) In an oscillator, the frequency, waveform, & magnitude of the AC signal generated is controlled by the circuit itself.

i.e. no external controlling voltage is required.

3) In oscillators, the frequency, waveform, & magnitude are determined by the passive components used in the circuit.

Conditions for Oscillator (or) Barkhausen Criteria

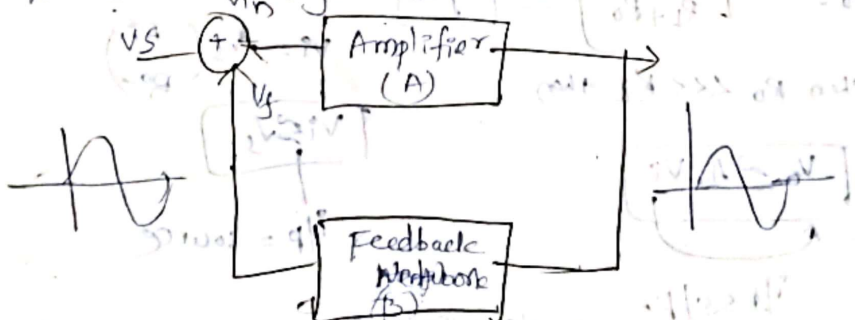1) Consider a non-inverting amplifier with a voltage gain of A , as shown in fig.



2) In this the o/p voltage (V_o) and i/p signal are in phase. Then a part of o/p is feedback to i/p with the help of feedback network then the magnitude of i/p signal increases. Hence it is called positive feedback.


3) From the fig $A = \frac{V_o}{V_{in}}$; $A_f = \frac{V_o}{V_s}$
 Due to +ve feedback $V_{in} = V_s + V_f$ $V_f = \beta V_o$

$V_o = \beta A V_{in}$ $V_s = V_{in} - V_f$
 $V_s = V_{in} - \beta A V_{in}$


$V_s = V_{in}(1 - A\beta)$

$A_f = \frac{V_o}{(1 - A\beta) V_{in}} = \frac{A}{1 - A\beta}$ → gain of amplifier with +ve feedback.

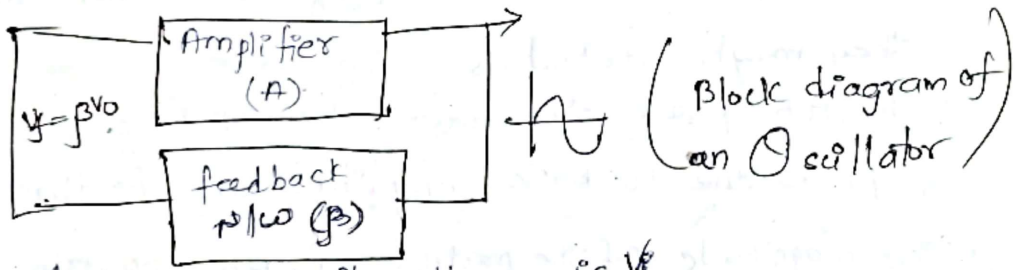Now consider the various values of (β) and corresponding values of A_f for constant amplifier gain A , then at some value of β , then A_f becomes ∞ , This indicates that the circuit can produce o/p without external i/p voltage (ie $V_s = 0$) just by feeding the part of o/p as its own i/p and it is shown in below fig. which is called as a basic block diagram of an oscillator.



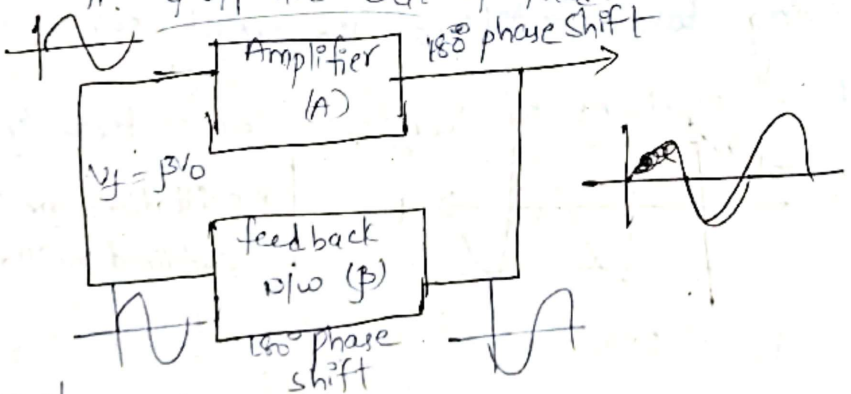$V_i = V_f$ In this circuit i/p voltage is V_f
 From the above circuit if the basic amplifier is ^{inverting} amplifier means i/p & o/p are out of ~~same~~ phase



Then o/p voltage (V_o) = $A V_{in}$

Then the feedback signal $V_f = -\beta V_o$ then $V_f = -\beta A V_{in}$

$V_f = -\beta A V_{in}$

From the above circuit

$$V_f = V_{in}$$

$$V_{in}' = -A\beta V_{in}'$$

$$-A\beta = 1$$

$$A\beta = -1$$

$$\boxed{|A\beta| = 1}$$

's called Magnitude of loop gain.

The above eqn indicates the magnitude of loop gain is equal to 1.

(i.e.) (The product of open loop gain & feedback ratio is equal to 1)

$$\boxed{A\beta = 1}$$

From circuit the phase shift of V_f & V_o are same (i.e.) the

feedback n/w should produce 180° of phase shift in addition to 180° phase shift introduced by inverting amplifiers. It indicates the total phase shift around the loop is 360° , It is called as necessary & sufficient condition.


$A\beta = 1$ is only sufficient condition.

→ The two conditions are required to work circuit as an oscillator are called Barkhausen criteria for oscillations and they may be stated as

1) The total phase shift around the loop is 0° or 360° . This phase shift is due to basic amplifier and feedback network.


→ The magnitude of the product of open loop gain of the amplifiers and feedback n/w (β) is unity (i.e.) $|A\beta| = 1$

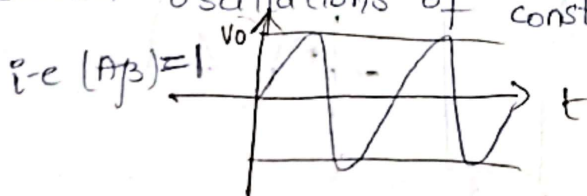By satisfying above conditions the circuit is able to produce sustained oscillations of constant amplitude & frequency




oscillations are called sustained oscillations

→ when the total phase shift around the loop is 360° and $|A\beta| > 1$ then the circuit produces oscillations but the oscillations are exponentially increasing.

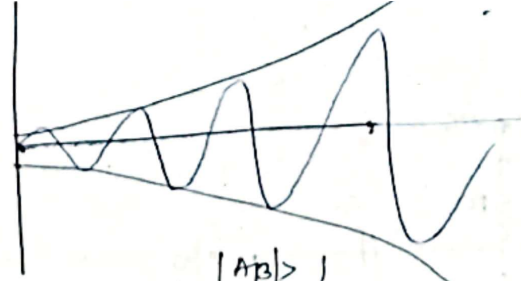

These are called unsustained oscillations

→ when the total phase shift is 360° & $|A\beta| < 1$ then the circuit produces oscillations but they are exponentially decaying.

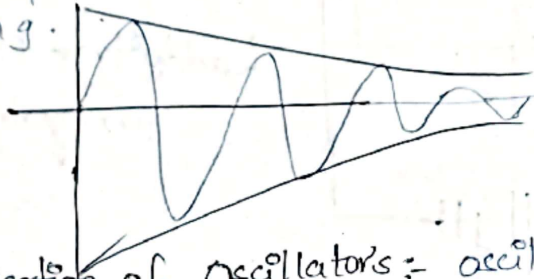

unsustained oscillations.

classification of oscillators :- oscillators are classified based on different parameters.

① Based on o/p signal (waveform) :-

- (a) sinusoidal oscillators
- (b) Non-sinusoidal oscillators. ex (square, triangle, sawtooth)

② Based on feedback network :-

- (i) RC oscillators
 - RC phase shift oscillator
 - Wien bridge oscillators
- (ii) LC oscillators
 - Hartley oscillators
 - Colpitts oscillators
- (iii) crystal oscillators

③ Based on o/p frequency :-

- (i) Audio oscillators (or) low frequency oscillators (20Hz - 20kHz)
- (ii) Radio oscillators (or) high frequency oscillators (20K - 20MHz)
- (iii) Very high frequency oscillators (20M - 200MHz)
- (iv) ultra-high frequency oscillators (200M - 3GHz)
- (v) Microwave frequency oscillators (Above 3GHz)


④ Based on type of feedback :-

- (i) positive feedback oscillators.
- (ii) Non-feedback oscillators ex = Tunnel diode, VJT

(The circuit which operates in \ominus ve resistance region)

① RC phase shift oscillator :-

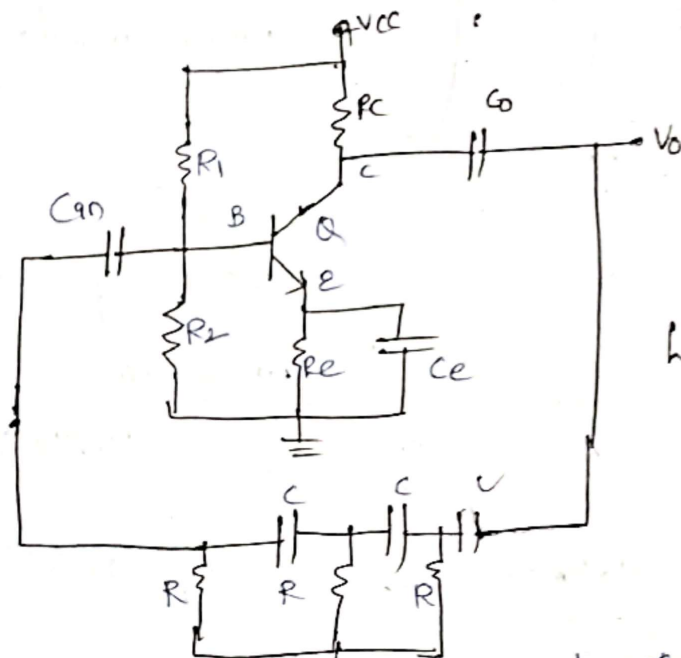It is commonly used sinusoidal low frequency oscillator the below figure shows the circuit diagram of RC phase shift oscillator.



Ladder type RC N/w arrangement

An above circuit uses an npn transistor in common emitter configuration with voltage divider bias of an amplifier and in feedback network consists of 3 identical RC sections connected in ladder fashion.


→ In the above circuit, CE amplifier provides 180° of phase shift and the feedback n/w provides another 180° of phase shift so the total phase shift is 0° or 360° .

In feedback n/w we can choose the suitable values of R & C to get the phase shift as 60°

i.e., $\theta = \tan^{-1} \left[\frac{X_C}{R} \right]$ where X_C is reactance of Capacitor


Expression for frequency of Oscillations: $X_C = \frac{1}{2\pi f C}$, R-resistance

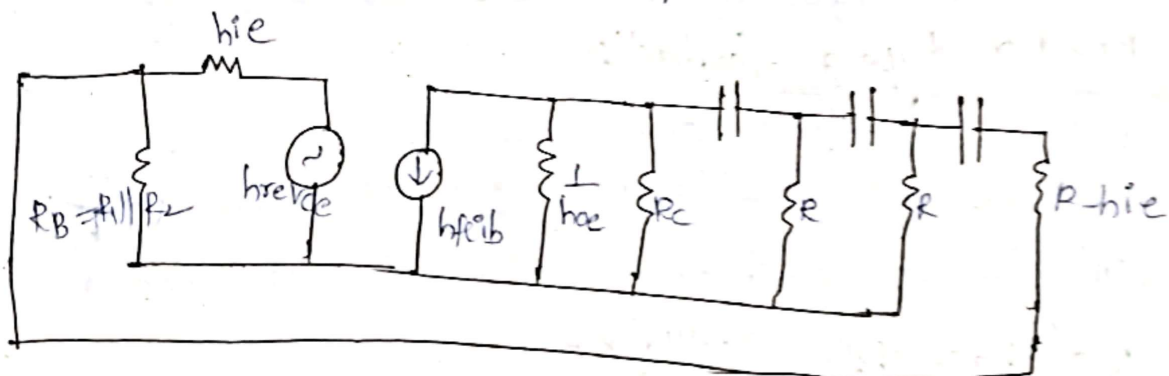The equivalent circuit of RC phase shift oscillator is below.



By making following assumptions we can simplify the above equivalent circuit.

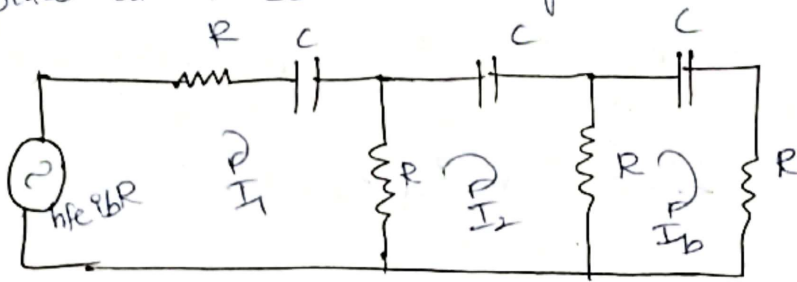Make $R_c = R$, Neglect biasing resistors (R_1, R_2)
 Replace current source with voltage source



By applying KVL to 3 loops we get

loop 1; $\Rightarrow hfeibR + RI_1 + \frac{1}{j\omega C} I_1 + R(I_1 - I_2) = 0.$

$$\left[2R + \frac{1}{j\omega C} \right] I_1 - RI_2 + R hfeib = 0 \rightarrow \textcircled{1}$$

For loop 2: $(I_2 - I_1)R + \frac{1}{j\omega C} I_2 + (I_2 - I_b)R = 0$

$$-RI_1 + \left(2R + \frac{1}{j\omega C} \right) I_2 - RI_b = 0 \rightarrow \textcircled{2}$$

For loop 3:

$$(I_b - I_2)R + \frac{1}{j\omega C} I_b + RI_b = 0$$

$$0I_1 - RI_2 + \left(2R + \frac{1}{j\omega C} \right) I_b = 0 \rightarrow \textcircled{3}$$

From eqn ①, ②, ③ the currents I_1, I_2, I_b are non-vanishing means those does not becomes zero. So the determinants of coefficients of I_1, I_2, I_b must be 0 and

Put $\frac{1}{j\omega C} = -jX_C$

The coefficient matrix is

$$\begin{bmatrix} 2R - jX_C & -R & hfeR \\ -R & 2R - jX_C & -R \\ 0 & -R & 2R - jX_C \end{bmatrix}$$

Then det $\begin{vmatrix} 2R - jX_C & -R & hfeR \\ -R & 2R - jX_C & -R \\ 0 & -R & 2R - jX_C \end{vmatrix} = 0$

$$2R - jX_C \left[(2R - jX_C)^2 - R^2 \right] + R \left[-R(2R - jX_C) - 0 \right] + hfeR \left[R^2 - 0 \right] = 0$$

$$(2R - jX_C)^3 - R^2(2R - jX_C) - R^2(2R - jX_C) + R^3 hfe = 0$$

$$(2R)^3 - 3(2R)^2 jX_c + 3(2R)(jX_c)^2 - (jX_c)^3 - 2R^3 + R^2 jX_c - 2R^3 + R^2 jX_c + R^3 h_{fe} = 0$$

$$\Rightarrow 8R^3 - 12R^2 jX_c + 6R j^2 X_c^2 - j^3 X_c^3 - 4R^3 + 2R^2 jX_c + R^3 h_{fe} = 0$$

$$\Rightarrow 4R^3 - 10R^2 jX_c - 6R X_c^2 + j X_c^3 + h_{fe} R^3 = 0$$

$$4R^3 - 10R^2 jX_c - 6R X_c^2 + j X_c^3 + R^3 h_{fe} = 0$$

$$(4R^3 - 6R X_c^2 + h_{fe} R^3) + j(X_c^3 - 10R^2 X_c) = 0$$

By equating imaginary part to "0".

$$X_c^3 - 10R^2 X_c = 0$$

$$X_c^3 = 10R^2 X_c$$

$$\boxed{X_c^2 = 10R^2}$$

$$X_c = 510R$$

By equating real to zero


$$4R^3 - 6R(10R^2) + h_{fe} R^3 = 0$$

$$4R^3 - 60R^3 + h_{fe} R^3 = 0$$

FET RC phase shift Oscillators = $\frac{1}{2\pi f C}$

$$f = \frac{1}{2\pi R C \sqrt{10}}$$

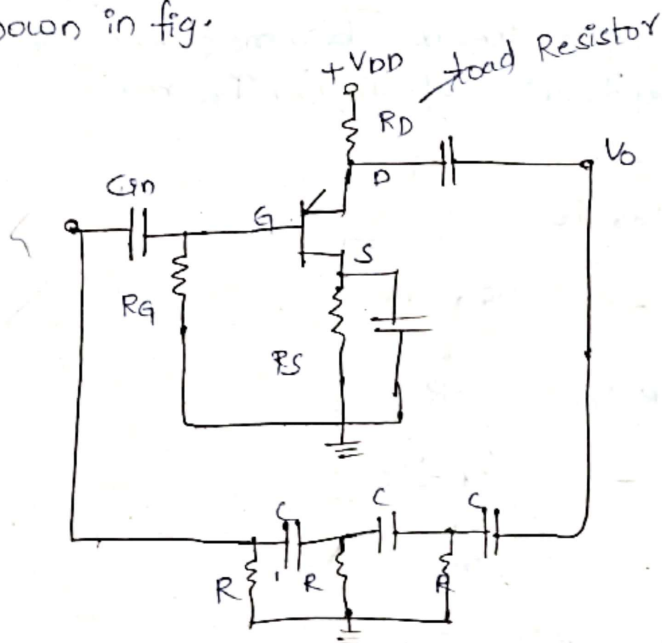The practical circuit of FET RC phase shift oscillator is shown in fig.



In the above circuit for the amplifier stage FET is used in self bias with capacitor bypassed source resistance R_s and the drain resistance (R_D) acts as load resistor. The important parameters of FET are



g_m & R then the gain of the amplifier is given by

$$\boxed{A = g_m R_L}$$

where $R_L = R_D \parallel R_L$

$$R_L = R_D \parallel R_L$$

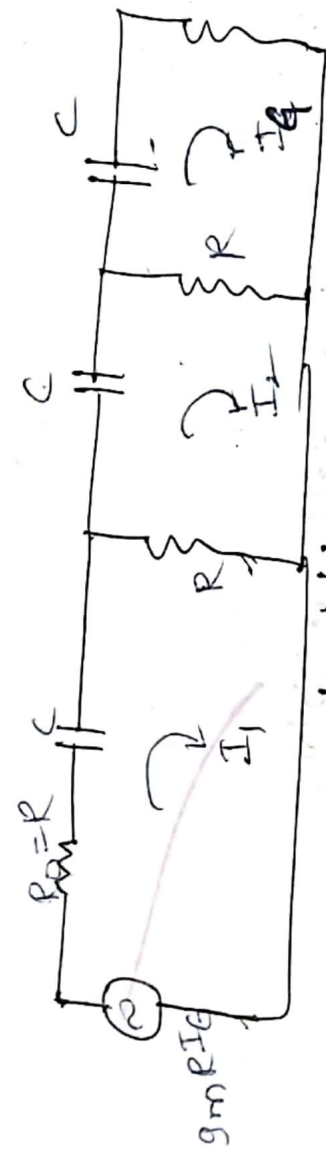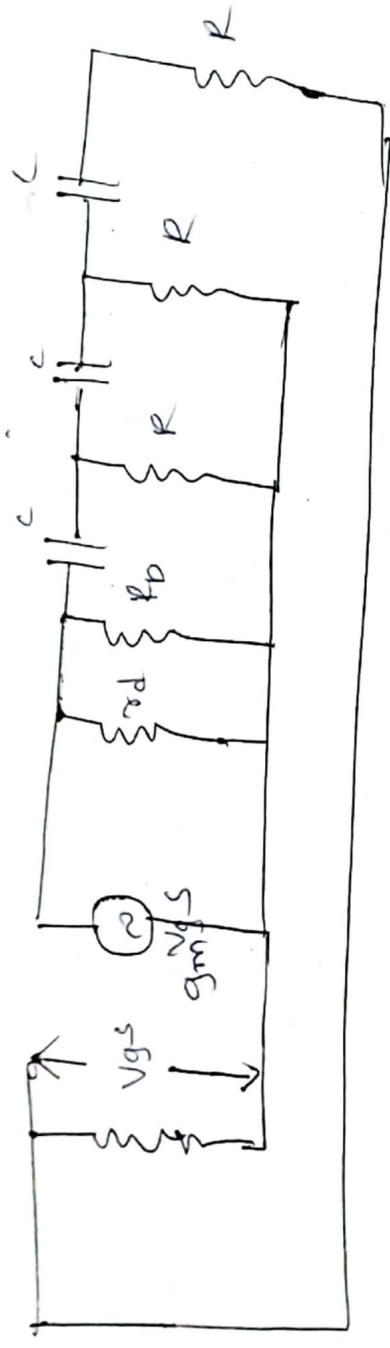For the derivation of frequency response the equivalent circuit



$R_D = R$
 r_d is neglected
 R_{gs} is ∞
 $f = \frac{1}{2\pi\sqrt{6}RC}$
 $|A| \geq 29$

By applying KVL to 3 loops,

loop 1: $g_m I_3 R + R I_1 + j\omega C I_1 + R(I_1 - I_2) = 0$

Advantages of RC phase shift oscillator :-

- 1) The circuit is simple to design.
- 2) It can produce op over audio frequency range.
- 3) It can produce sinusoidal wave form.
- 4) It is a fixed frequency oscillator.

Disadvantages :-

- 1) By changing the values of R & C, the frequency of the oscillator can be changed but the values of R & C of all the sections must be changed simultaneously to satisfy the oscillation conditions.
- 2) But this is practically impossible. Hence the RC phase shift oscillator is considered as a fixed oscillator for all practical cases.

2) The frequency stability is poor due to changes in the values of various components due to effect of temp.
 or Ageing, humidity and so on.

Problem For the RC phase shift oscillator, the feedback n/w uses $R = 6k\Omega$ & $C = 1500pF$. The transistorized amplifier uses as a collector resistance of $18k\Omega$ calculate the frequency of oscillations & minimum value of h_{fe} of transistor?
 We know that in RC phase shift oscillator,

$$f = \frac{1}{2\pi RC\sqrt{6+4K}}$$

Given that

$$R = 6k\Omega, C = 1500pF, R_c = 18k\Omega$$

$$f = \frac{1}{2\pi RC\sqrt{6+4K}}$$

$$K = \frac{R_c}{R} = \frac{18 \times 10^3}{6 \times 10^3} = 3$$

$$f = \frac{1}{2 \times 3.14 \times 6 \times 10^3 \times 1500 \times 10^{-12} \sqrt{6+4(3)}}$$

$$f = 4.17 \text{ KHz}$$

$$h_{fe} = 23 + 4K + \frac{29}{K} = 4(3) + 23 + \frac{29}{3} = 44.66$$

$$h_{fe} \geq 45$$


Wien Bridge Oscillator [Audio frequency].

This is audio frequency oscillator. The advantage of this


is the frequency may be varied in the range of 10Hz to 1MHz. Hence it is a variable frequency oscillator. Generally in an oscillator amplifier stage introduce 180° of phase shift and feedback n/w introduces another 180° of phase shift, to obtain a phase shift of 360° . But in Wien bridge does not produce feedback n/w, i.e. Wien bridge does not produce any phase shift. Because of its series and parallel RC n/w in the bridge circuit.

$$\frac{R_c \sqrt{6+4K}}{R}$$

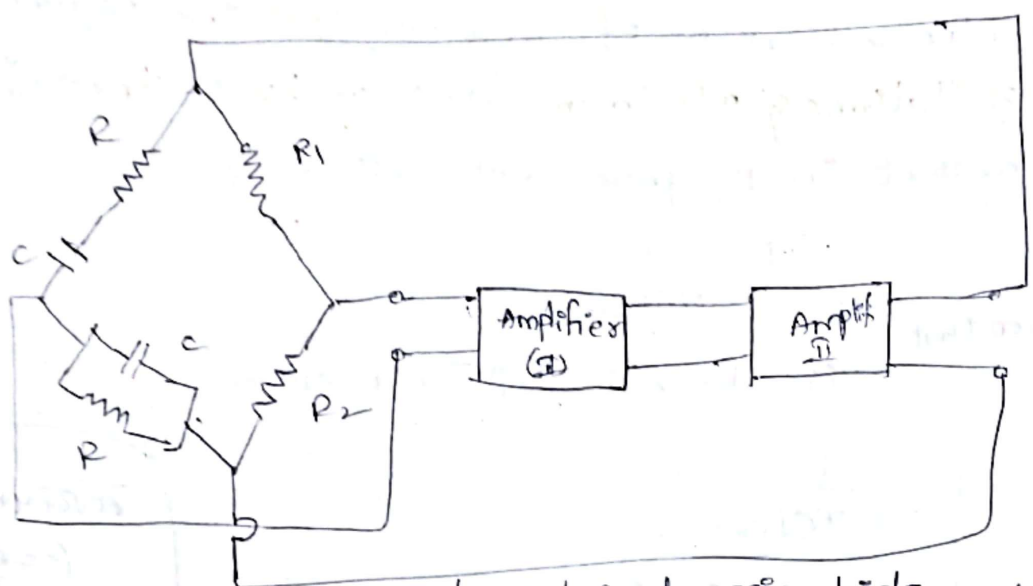Series n/w acts as lead n/w, parallel n/w acts as lag n/w,
 They both get cancelled. In order to produce 0° & 360° phase shift
 we use two stage ce amplifiers.
 The below fig show the block diagram of wein bridge oscillator.



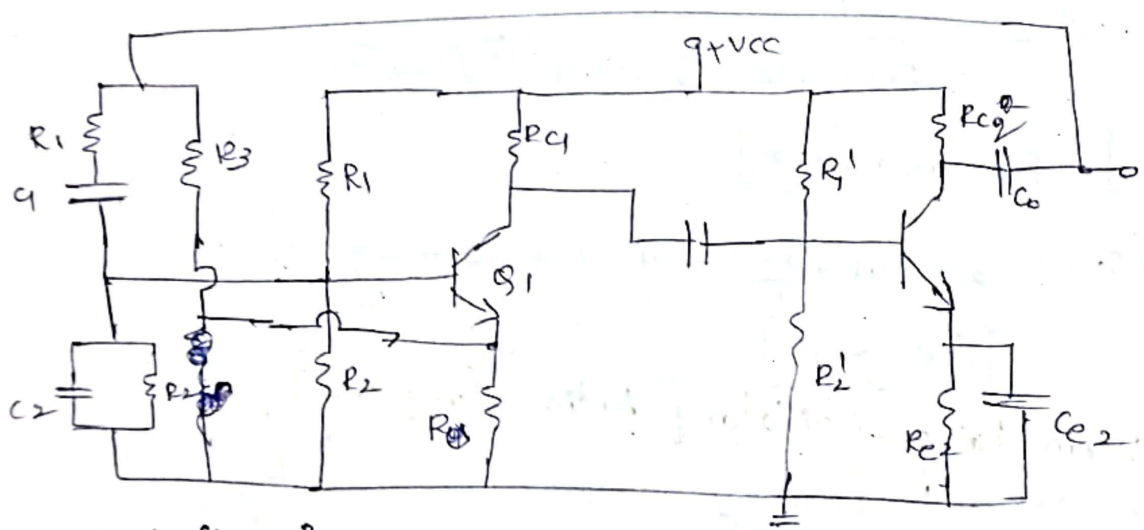The below fig. shows the transistorized wein bridge oscillator.



Continued after $X_C^2 \cong 10R^2$

$$X_C = \sqrt{10} R$$

$$\frac{1}{\omega C} = \sqrt{10} R$$

$$\frac{1}{2\pi f C} = \sqrt{10} R$$

$$f = \frac{1}{2\pi R C \sqrt{10}}$$

If $R_C \neq R_E$, $f = \frac{1}{2\pi R_C \sqrt{6+4K}}$

$$K = \frac{R_C}{R_E}$$

By equating real part = 0

$$4R^3 - 6R^2C^2 + hfcR^3 = 0$$

$$4R^3 - 6R(10R^2) + hfcR^3 = 0$$

$$4 - 60 + hR = 0$$

$hfc = 56$ indicates to get the certain values.

if $R_C = R$,

$$hfc > 4k + 23 + \frac{29}{k} \quad \text{where } k = \frac{R_C}{R}$$


Derivation for frequency of oscillation:

As w.k.t the frequency of oscillations on an oscillator depends on the feedback n/w.

In Wien's bridge oscillator the frequency of oscillation depends

on based on balancing condition of the bridge.

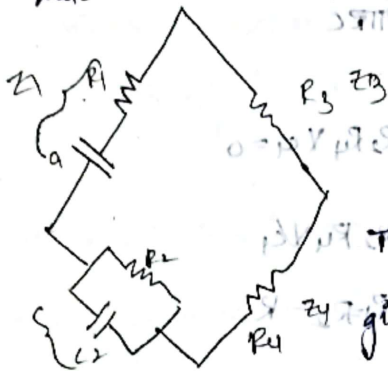If the bridge is balanced means the product of opposite arms impedances are equal or the ratio of adjacent arms are equal.



$$\frac{Z_1}{Z_2} = \frac{Z_3}{Z_4}$$

$$Z_2 Z_3 = Z_1 Z_4$$

The impedance of the bridge are

given $Z_1 = R_1 + j\omega C_1$

Z_2

$$Z_2 = R_2 \parallel j\omega C_2 = \frac{-jR_2 \omega C_2}{R_2 - j\omega C_2}$$

$$Z_2 Z_3 = Z_1 Z_4$$

$$Z_3 = R_3; \quad Z_4 = R_4$$

$$\frac{-jR_2 \omega C_2}{R_2 - j\omega C_2} \times R_3 = (R_1 - j\omega C_1) R_4$$

$$(R_2 - j\omega C_2) - j\omega C_1 R_2 R_3 = (R_1 - j\omega C_1) R_4$$

$$(R_2 - j\omega C_2) R_2 R_3 = (R_1 - j\omega C_1) (R_2 - j\omega C_2) R_4$$

$$-j R_2 \omega C_2 \times R_2 R_3 - j R_3 \omega C_2 = R_1 - j\omega C_1 (R_2 R_4 - j R_4 \omega C_2)$$

$$(-j R_2 \omega C_2 - j R_3 \omega C_2) R_2 R_3 = R_1 R_2 R_4 - j R_2 R_4 \omega C_2 - j \omega C_1 R_2 R_4 + \omega C_1 \omega C_2 R_4$$

$$-jR_2^2 P_3 X_{C2} - jR_3^2 R_2 X_{C2} = R_1 R_2 R_4 - jR_1 R_4 X_{C2} - jX_{C4} R_2 R_4$$

By equating Real part = 0

$$R_1 R_2 R_4 - X_{C4} X_{C2} R_4 = 0$$

$$R_1 R_2 = X_{C4} X_{C2}$$

$$R_1 R_2 = \frac{1}{\omega_1 X_{C4} \omega_2}$$

$$R_1 R_2 C_1 C_2 = \frac{1}{\omega^2}$$

$$\frac{1}{\omega} = \sqrt{R_1 R_2 C_1 C_2}$$

$$\frac{1}{2\pi f} = \sqrt{R_1 R_2 C_1 C_2}$$

$$\frac{1}{f} = 2\pi \sqrt{R_1 R_2 C_1 C_2}$$

$$f = \frac{1}{2\pi \sqrt{R_1 R_2 C_1 C_2}}$$

$$f = \frac{1}{2\pi \sqrt{R^2 C^2}} = \frac{1}{2\pi RC}$$

By making, $\text{Im}g = 0$

$$R_2 R_3 X_{C2} = R_1 R_4 X_{C2} - R_2 R_4 X_{C4} = 0$$

$$X_{C2} (R_2 R_3 + R_1 R_4) = R_2 R_4 X_{C4}$$

$$\text{If } X_{C4} = X_{C2} = X_C \text{ ; } R_1 = R_2 = R$$

$$R(R_3 - R_4) = R R_4$$


$$\frac{R_3}{R_4} = 2$$

The above eqn indicates the condition for sustained oscillations

Here R_3 & R_4 controls the gain of the amplifier which means

$$A = 2 \text{ \& } \beta = \frac{1}{2} \left[\begin{matrix} 1 \\ \beta \end{matrix} \right]$$

FET Wien bridge oscillator

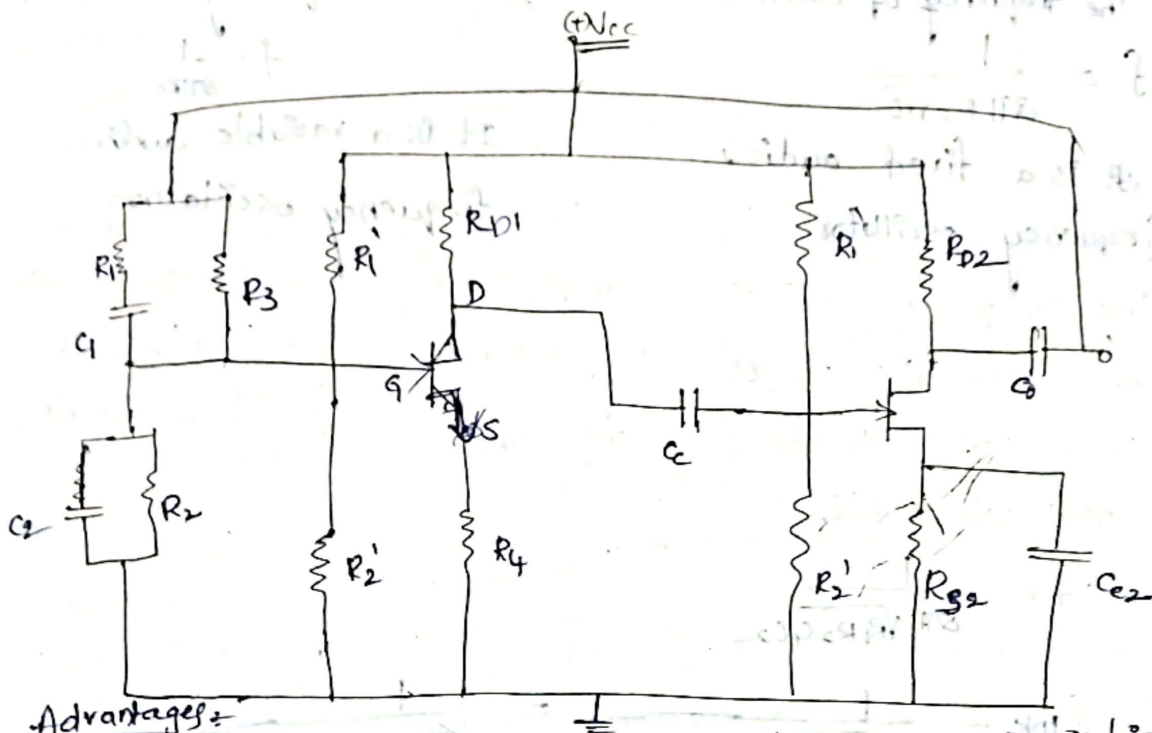

Advantages:

It gives good frequency stability overall gain is high

because of two transistors, 2) overall gain is high because of two transistors, 3) It gives

It gives constant sign wave of a frequency of oscillation can be changed, 4) Frequency of oscillations can be changed

Disadvantage: It requires two transistors and more no. of components circuit becomes complex.

It can't generate radio or high frequency.

Difference b/w RC phase shift & Wien bridge

RC phase shift

1) It consists single stage CE

2) It uses three (3) RC sections arranged in ladder fashion.

3) In this the amplifier produces 180° phase shift

4) In this the feedback n/w produces 180° phase shift

1) It consists (double) two stage RC

2) The feedback n/w consists of bridge circuit with series and parallel RC in two arms and the remaining two arms are resistive.

3) In this the amplifier section produces 360° phase shift

4) The feedback n/w does not produce any shift i.e. 0° .

RC phase shift

5) The frequency of oscillation

$$f = \frac{1}{2\pi RC\sqrt{10}}$$

6) It is a fixed audio frequency oscillator

① The frequency sensitive arms of the Wien bridge oscillator

uses $C_1 = C_2 = 0.001 \mu F$ & $R_1 = 10K \Omega$, R_2 is kept variable. The frequency is to varied from $10KHz$ to $50KHz$. Find min & max value of R_2 ?

$$f = \frac{1}{2\pi \sqrt{R_1 R_2} C_1 C_2}$$

$$10K = \frac{1}{2\pi \sqrt{10K \times R_2} \times 0.001 \times 10^{-6}} = \frac{1}{5.0329212 \times 10^{-3} \sqrt{R_2}}$$

$$\sqrt{R_2} = \frac{1}{5.0329212 \times 10^{-3} \times 10^4}$$

$$\sqrt{R_2} = 5.032 \times 10^{-3}$$

R_2

$$10^4 \times 10^3 = 15911549.43 \frac{1}{\sqrt{R_2}}$$
$$10 \times 10^3 = 15.91 \times 10^6$$
$$\sqrt{R_2} = \frac{15.91 \times 10^6}{10}$$

31/1/22

LC Oscillators :- oscillators which use the elements L & C to produce oscillations are called LC oscillators.

⇒ The circuit using the elements (L & C) are called tank or oscillatory circuit, which is an important part in LC oscillators.

⇒ This circuit is also called Resonating / Tuned circuit.

⇒ This oscillators are used for very high frequency from

($200KHz$ to $100MHz$)

⇒ due to this (high) frequency range this oscillators are used in Radio receivers (or) Transmitters circuit.

Wien bridge

5) The frequency is

$$f = \frac{1}{2\pi RC}$$

6) It is a variable audio frequency oscillator.

arms of the Wien bridge oscillator

uses $C_1 = C_2 = 0.001 \mu F$ & $R_1 = 10K \Omega$, R_2 is kept variable. The

frequency is to varied from $10KHz$ to $50KHz$. Find min &

max value of R_2 ?

$$f = \frac{1}{2\pi \sqrt{R_1 R_2} C_1 C_2}$$

$$10K = \frac{1}{2\pi \sqrt{10K \times R_2} \times 0.001 \times 10^{-6}} = \frac{1}{5.0329212 \times 10^{-3} \sqrt{R_2}}$$

$$\sqrt{R_2} = \frac{1}{5.0329212 \times 10^{-3} \times 10^4}$$

$$\sqrt{R_2} = 5.032 \times 10^{-3}$$

$$10^4 \times 10^3 = 15911549.43 \frac{1}{\sqrt{R_2}}$$

$$10 \times 10^3 = 15.91 \times 10^6$$

$$\sqrt{R_2} = \frac{15.91 \times 10^6}{10}$$

$$\sqrt{R_2} = 15.91 \times 10^5$$

$$R_2 = (15.91 \times 10^5)^2$$

$$R_2 = 2531281 \times 10^5 \Omega$$

$$R_2 = 253128100000 \Omega$$

$$R_2 = 253128.1 K\Omega$$

$$R_2 = 253.1281 M\Omega$$

$$R_2 = 253.1281 \times 10^6 \Omega$$

$$R_2 = 253.1281 \times 10^6 \Omega$$

$$R_2 = 253.1281 \times 10^6 \Omega$$

$$R_2 = 253.1281 \times 10^6 \Omega$$


$$R_2 = 253.1281 \times 10^6 \Omega$$

$$R_2 = 253.1281 \times 10^6 \Omega$$

$$R_2 = 253.1281 \times 10^6 \Omega$$

$$R_2 = 253.1281 \times 10^6 \Omega$$

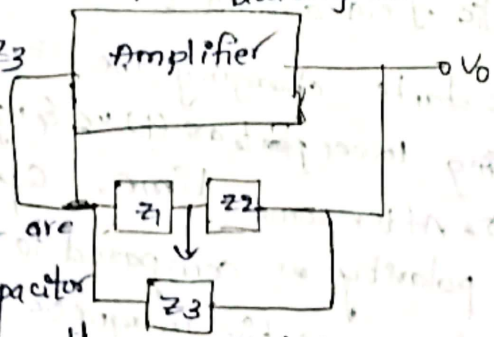→ In the fig, Z_1, Z_2, Z_3 are inductor (or) capacitor.






→ suppose if Z_1, Z_2 are inductors & Z_3 is capacitor then it is called **hastly oscillator**.

→ If Z_1, Z_2 are capacitors & Z_3 is inductor it is called **colpits oscillator**.



→ In the above fig. the amplifier provides 180° phase shift and the LC circuit feedback another 180° phase shift. Then overall phase shift around any loop either 0° or 360° .

Operation of LC circuit :-

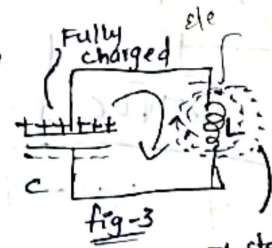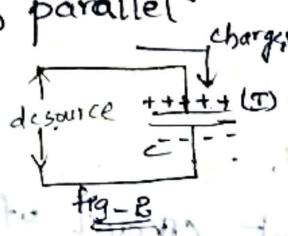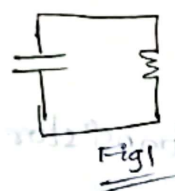Consider LC circuit as shown in fig 1, consists of LC are connected in parallel.



It starts charging so then discharging

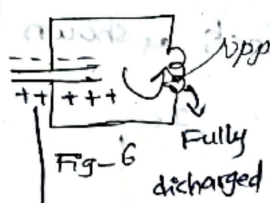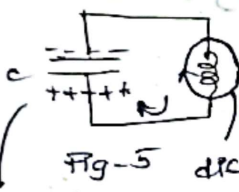

capacitor discharged → Inductor charged (continuously with (+)ve & (-)ve charging produce oscillations)
Indicates the oscillations

charging in reverse polarities

$$f = \frac{1}{2\pi\sqrt{LC}}$$

Let capacitor is initially charged from DC source with the polarities (+) as shown in fig 2. when the capacitor gets fully charged the energy stored in capacitor is called electrostatic energy. when such a charged capacitor is connected across inductor in a Tank circuit, then the capacitor discharges to (L) as shown in fig 3. The arrow indicates the direction of flow of conventional current. Due to such current flow the magnetic field gets setup around the inductor. Thus, inductor starts storing the energy (i.e. magnetic static energy). Then capacitor is fully discharged. The max current flows through the circuit. At that time all the electrostatic energy get stored as a electromagnetic energy in the inductor as shown in fig 4).


Now, the magnetic field around L starts collapsing as per Lenz's law. This starts charging the capacitor with opposite direction making lower plate as (+)ve & upper plate as (-)ve as shown in fig 5. After some time, capacitor is fully charged with opposite polarity as compared to initial polarity as shown in fig 6. Now, entire magnetic energy gets converted to electrostatic energy.

- The above process repeats by the proper care of polarities is taken in feedback also the LC circuit along with amplifier can be used to obtain oscillations called LC oscillations.
- The frequency of oscillations generated by LC tank ckt depends on the values of L & C .

$$f = \frac{1}{2\pi\sqrt{LC}}$$

General form of LC oscillators

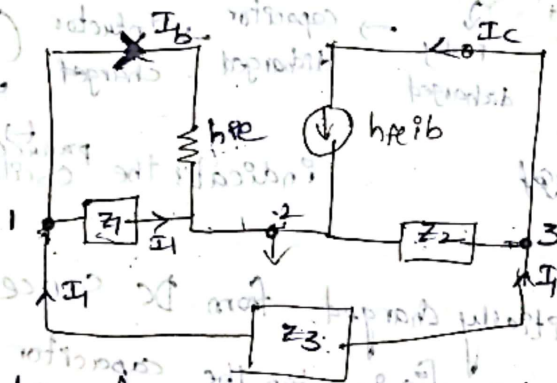Consider simplified equivalent circuit of a transistor with LC circuit as a feedback as shown in fig.



→ The load impedance (Z_L) b/w o/p terminals (2 & 3) node.

Here Z_1 & h_{ie} are in parallel, its resultant is in series with Z_3 & it is parallel to Z_2 .

$$\frac{1}{Z_1'} = \frac{1}{Z_1} + \frac{1}{h_{ie}} \Rightarrow Z_1' = \frac{Z_1 h_{ie}}{Z_1 + h_{ie}}$$

$$\begin{aligned} \text{Then } Z_1' + Z_3 \text{ (series)} &= \frac{Z_1 h_{ie}}{Z_1 + h_{ie}} + Z_3 \\ &= \frac{Z_1 h_{ie} + Z_3 (Z_1 + h_{ie})}{Z_1 + h_{ie}} \\ Z_1' + Z_3 &= \frac{h_{ie} (Z_1 + Z_3) + Z_1 Z_3}{Z_1 + h_{ie}} \end{aligned}$$

Equivalent load impedance

$$\frac{1}{Z_L} = \frac{1}{z_1 + z_3} + \frac{1}{z_2}$$

$$\frac{1}{Z_L} = \frac{(z_1 + z_3) + z_2}{z_2(z_1 + z_3)}$$

$$\frac{1}{Z_L} = \frac{1}{h_{ie}(z_1 + z_3) + z_1 z_3} + \frac{1}{z_2}$$

$$\frac{1}{Z_L} = \frac{(z_1 + h_{ie})}{h_{ie}(z_1 + z_3) + z_1 z_3} + \frac{1}{z_2}$$

$$\frac{1}{Z_L} = \frac{(z_2(z_1 + h_{ie}) + h_{ie}(z_1 + z_3) + z_1 z_3)}{z_2[h_{ie}(z_1 + z_3) + z_1 z_3]}$$

$$Z_L = \frac{z_2[h_{ie}(z_1 + z_3) + z_1 z_3]}{z_2 h_{ie}(z_1 + z_3) + z_1 z_2 + z_1 z_3}$$

⇒ Voltage gain (A_v) = $A_v = \frac{-h_{fe} R_L}{\beta_{ie}} = \frac{-h_{fe} Z_L}{h_{ie}}$

$$A_v = \frac{-h_{fe} R_L}{h_{ie}}$$

$$\therefore \beta = \frac{V_f}{V_o}$$

o/p voltage b/w 2 & 3 terminals is given by

$$V_o = (z_1 + z_3) I_1$$

$$V_o = \left[\frac{z_1(h_{ie})}{z_1 + h_{ie}} + z_3 \right] I_1$$

$$V_o = \left[\frac{z_1(h_{ie}) + z_3(z_1 + h_{ie})}{z_1 + h_{ie}} \right] I_1$$

$$V_o = \left[\frac{h_{ie}(z_1 + z_3) + z_1 z_3}{(z_1 + h_{ie})} \right] I_1$$

The feedback voltage b/w 1 & 2 terminals is

$$V_f = z_1 I_1$$

$$V_f = \left(\frac{z_1 h_{fe}}{z_1 + h_{ie}} \right) I_1 = \frac{z_1 h_{fe}}{(z_1 + h_{ie})} I_1$$

$$\beta = -\frac{V_f}{V_o}$$

$$\beta = \frac{1}{\left(\frac{h_{ie}(z_1+z_3) + z_1 z_3}{z_1 + h_{ie}} \right) \frac{z_1}{z_1 + h_{ie}}}$$

$$= \frac{1}{\left(\frac{z_1 h_{ie}}{z_1 + h_{ie}} \right)}$$

$$\beta = - \frac{1}{\left(\frac{h_{ie}(z_1+z_3) + z_1 z_3}{z_1 h_{ie}} \right)} = \frac{-z_1 h_{ie}}{h_{ie}(z_1+z_3) + z_1 z_3}$$

$$A\beta = -1$$

$$A\beta = -1$$

$$\frac{-h_{fe} z_1}{h_{ie}} = \frac{h_{fe} z_2 \left[\frac{h_{ie}(z_1+z_3) + z_1 z_3}{h_{ie}(z_1+z_2+z_3) + z_1 z_2 + z_1 z_3} \right] \times \frac{-z_1 h_{ie}}{h_{ie}(z_1+z_3) + z_1 z_3}}$$

\Rightarrow

$$\frac{h_{fe} z_1 z_2}{h_{ie}(z_1+z_2+z_3) + z_1 z_2 + z_1 z_3} = -1$$

$$h_{fe} z_1 z_2 = - \left[h_{ie}(z_1+z_2+z_3) + z_1 z_2 + z_1 z_3 \right]$$

$$h_{fe} z_1 z_2 + h_{ie}(z_1+z_2+z_3) + z_1 z_2 + z_1 z_3 = 0$$


$$z_1 z_2 (1 + h_{fe}) + z_1 z_3 + h_{ie}(z_1+z_2+z_3) = 0$$

For input, $z_1 = j\omega L_1$, $z_2 = j\omega L_2$, $z_3 = \frac{1}{j\omega C_3}$

For output, $z_1 = \frac{1}{j\omega C_1}$, $z_2 = \frac{1}{j\omega C_2}$, $z_3 = j\omega L$

The above eqn is general form of an LC oscillator that deriving frequency of oscillations & condition for sustained oscillations.

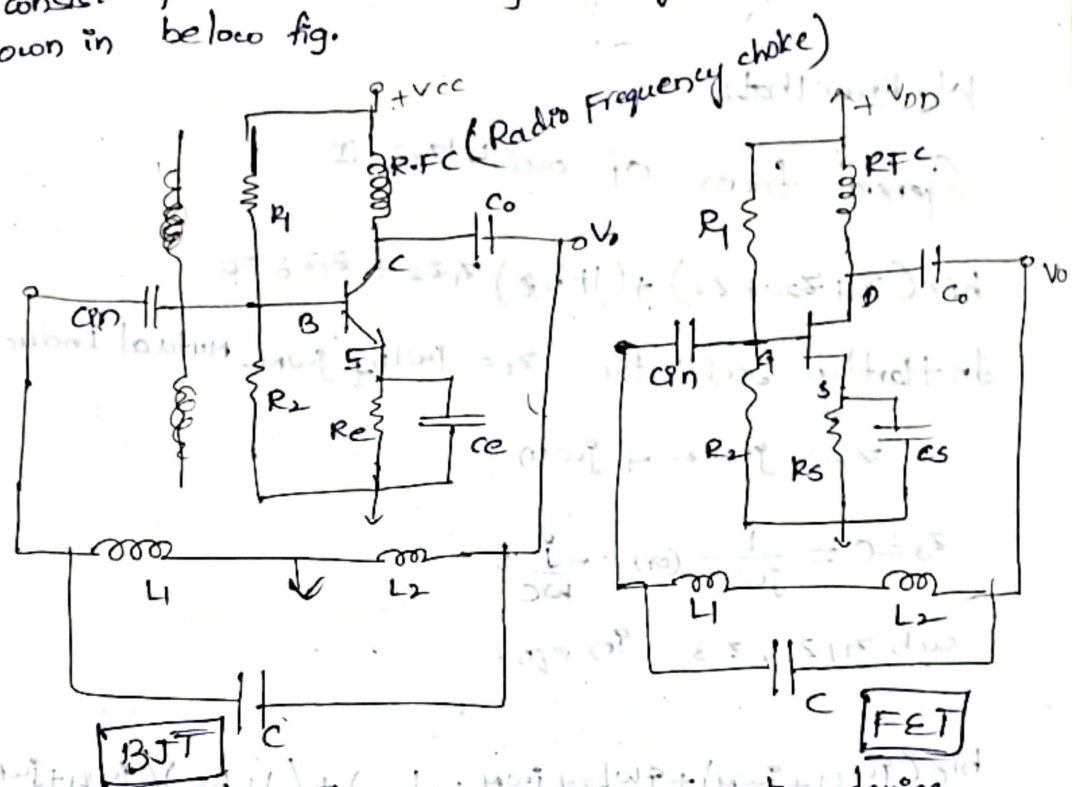Hartley Oscillator :- It is an example of LC oscillator, which consists of two inductors & one capacitor as feedback as shown in below fig.



- In fig 1, the amplifier stage uses an active device called BJT in CE configuration with voltage divider bias.
- Here R_1, R_2 are biasing resistors, the R.F.C. is the Radio frequency choke, its reactance value is very high for high frequencies. Hence it can withstand at large voltages (or) currents.
- It also provides isolation b/w AC & DC operation.
- R_e resistor provides stabilization and C_{B1}, C_{C1} are coupling capacitors.
- The feedback n/w consists of L_1 & L_2 and one capacitor C which are arranged in the form of Tank ckt.
- The CE amplifier provides a phase shift of 180° as the emitter is ground, the base & collector voltages are out of phase by 180° .
- As the centre of L_1 & L_2 are grounded, then upper end becomes (+)ve & lower end becomes (-)ve & vice-versa
- So LC feedback n/w gives an additional phase shift of 180°

necessary to satisfy oscillation conditions.
 Derivation for frequency of oscillations =

We know that,

General form of oscillations is

$$h_{ie}(z_1 + z_2 + z_3) + (1 + h_{fe})z_1 z_2 + z_1 z_3 = 0$$

In Hartley oscillator $z_1 = j\omega L_1 + j\omega M$ Mutual Inductance

$$z_2 = j\omega L_2 + j\omega M$$

$$z_3 = C = \frac{1}{j\omega C} \text{ (or) } \frac{-j}{\omega C}$$

sub z_1, z_2, z_3 in eqn.

$$h_{ie}(j\omega L_1 + j\omega M) + j\omega L_2 + j\omega M + \frac{1}{j\omega C} + (1 + h_{fe})(j\omega L_1 + j\omega M)(j\omega L_2 + j\omega M) + (j\omega L_1 + j\omega M)\left(\frac{1}{j\omega C}\right) = 0$$

$$= h_{ie}(j\omega(L_1 + L_2) + 2j\omega M) + \frac{1}{j\omega C} + (1 + h_{fe})(j^2\omega^2 L_1 L_2 + j^2\omega^2 L_1 M + j^2\omega^2 M L_2 + j^2\omega^2 M^2)$$

$$+ j\omega(L_1 + M)\left(\frac{1}{j\omega C}\right) = 0$$

$$= h_{ie} \left[L_1 + L_2 + 2M - \frac{1}{\omega^2 C} \right] + (1 + h_{fe})(-\omega^2) [L_1 L_2 + L_1 M + M L_2 + M^2] + (L_1 + M)\left(\frac{1}{C}\right) = 0$$

Equate imaginary to zero

$$h_{ie} \left[L_1 + L_2 + 2M - \frac{1}{\omega^2 C} \right] = 0$$

$$\omega(L_1 + L_2 + 2M) - \frac{1}{\omega^2 C} = 0$$

$$\frac{1}{\omega^2 C} = L_1 + L_2 + 2M$$

Two Inductors are in series

$$= \frac{1}{\omega} = \sqrt{L_{eq} C}$$

$$\frac{1}{2\pi f} = \sqrt{L_{eq} C}$$

$$\boxed{f = \frac{1}{2\pi \sqrt{L_{eq} C}}} \quad \text{where } L_{eq} = L_1 + L_2 + 2M$$

Equating real part to zero.

$$(-\omega^2)(1+hfe) \left[(L_1+M)(L_2+M) \right] + \frac{L_1+M}{C} = 0$$

$$-\omega^2(L_1+M) \left[(1+hfe)(L_2+M) - \frac{1}{\omega^2 C} \right] = 0$$

$$(1+hfe)(L_2+M) - \frac{1}{\omega^2 C} = 0$$

$$(1+hfe) = \frac{1}{\omega^2 C (L_2+M)}$$

$$\left| \frac{1}{\omega^2 C} = L_1 + L_2 + 2M \right.$$

$$\therefore (1+hfe) = \frac{L_1 + L_2 + 2M}{L_2 + M}$$

$$(1+hfe) = 1 + \frac{L_1 + M}{L_2 + M}$$

$$\boxed{hfe = \frac{L_1 + M}{L_2 + M}}$$

Gives condition for sustained oscillations.

Colpitts oscillators

$$z_1 = \frac{-j}{\omega C_1} ; z_2 = \frac{-j}{\omega C_2} ; z_3 = j\omega L$$

\therefore sub z_1, z_2, z_3 in general form of oscillators.

$$hfe(z_1 + z_2 + z_3) + (1+hfe)(z_1 z_2) + z_1 z_3 = 0$$

$$hfe \left(\frac{-j}{\omega C_1} + \frac{-j}{\omega C_2} + j\omega L \right) + (1+hfe) \left(\left(\frac{-j}{\omega C_1} \right) \left(\frac{-j}{\omega C_2} \right) \right) + \left(\frac{-j}{\omega C_1} \right) (j\omega L) = 0$$

$$\frac{hfe}{\omega} \left(\frac{j}{C_1} + \frac{j}{C_2} + \omega^2 L \right) + (1+hfe) \left(\frac{j}{\omega} \right) \left(\frac{j}{C_1} \right) \left(\frac{j}{C_2} \right) - \frac{j}{\omega C_1} (j\omega L) = 0$$

$$hfe \left(\frac{j}{\omega} \right) \left(\frac{j}{C_1} + \frac{j}{C_2} + \omega^2 L \right) + (1+hfe) \left(\frac{j}{\omega} \right) \left(\frac{j}{C_1} \right) \left(\frac{j}{C_2} \right) + \frac{L}{C_1} = 0$$

$$\frac{j hfe}{\omega} \left[\frac{j}{C_1} + \frac{j}{C_2} + \omega^2 L \right] + \frac{1}{\omega} \left[(1+hfe) \left(\frac{j}{C_1} \right) \left(\frac{j}{C_2} \right) \right] + \frac{L}{C_1} = 0$$

Equating imaginary to zero

$$\frac{hfe}{\omega} \left(\frac{1}{C_1} - \frac{1}{C_2} + \omega L \right) + (1+hfe) \left(\frac{1}{C_1} \right) \left(\frac{1}{C_2} \right) = 0$$

$$hfe \left(\frac{1}{C_1} - \frac{1}{C_2} + \omega L \right) - (1+hfe) \left(\frac{1}{C_1} \right) \left(\frac{1}{C_2} \right) = 0$$

$$-hfe \left(\frac{1}{\omega C_1} + \frac{1}{\omega C_2} - \omega L \right) = 0$$

$$\frac{1}{\omega C_1} + \frac{1}{\omega C_2} = \omega L$$

$$\omega = \frac{1}{L} \left(\frac{1}{\omega C_1} + \frac{1}{\omega C_2} \right) \Rightarrow \frac{1}{\omega^2} \left(\frac{1}{C_1} + \frac{1}{C_2} \right) = L$$

$$\therefore \omega = \frac{1}{L} \left(\frac{1}{\omega C_1} + \frac{1}{\omega C_2} \right)$$

$$\omega^2 = \frac{1}{L C_1} + \frac{1}{L C_2}$$

$$\omega = \sqrt{\frac{1}{L C_1} + \frac{1}{L C_2}}$$

$$2\pi f = \sqrt{\frac{1}{L C_1} + \frac{1}{L C_2}}$$

$$f = \frac{1}{2\pi} \sqrt{\frac{1}{L C_1} + \frac{1}{L C_2}}$$

Equating real part to zero

$$-(1+hfe) \left(\frac{1}{C_1} \right) \left(\frac{1}{C_2} \right) + \frac{1}{C_1} = 0$$

$$\frac{1}{C_1} \left[L - (1+hfe) \left(\frac{1}{C_2} \right) \right] = 0$$

$$L = (1+hfe) \left(\frac{1}{C_2} \right)$$

$$\omega^2 = \frac{1}{L C_1} + \frac{1}{L C_2}$$


$$\omega^2 = \frac{C_1 + C_2}{L C_1 C_2}$$

$$\frac{1}{\omega^2} \left(\frac{1}{C_1 C_2} \right) - \frac{hfe}{\omega^2 (C_1 C_2)} + \frac{1}{C_1} = 0$$

$$\frac{hfe}{\omega^2 C_1 C_2} = \frac{1}{\omega C_1} \left(\omega L - \frac{1}{\omega C_2} \right)$$

$$hfe = \omega C_2 \left(\omega L - \frac{1}{\omega C_2} \right)$$
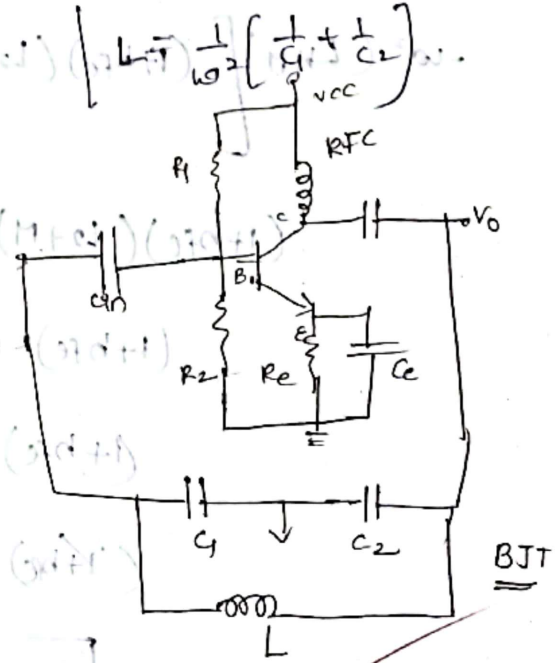
$$hfe = \frac{\omega^2 C_2 L - 1}{L C_2 - 1}$$



$$h_{fe} = \frac{C_1 + C_2}{C_1} \times \frac{L_1}{L_2} - 1$$

$$h_{fe} = \frac{C_1 + C_2 - C_1}{C_1}$$

$$h_{fe} = \frac{C_2}{C_1}$$

Advantages & disadvantages of Hartley ^{(LC) (or) Colpitts} oscillator =

→ It generates very high frequencies (200kHz - 2GHz)

→ It produces sinusoidal signal at radio frequency.

→ It has a variable oscillator by varying (C) (or) (L)

Disadvantages: The circuit becomes costly and bulky due to inductors.

→ It provides poor frequency stability.

Diff. b/w RC & LC oscillators

RC oscillators

The feedback also uses resistor and capacitor.

Frequency of oscillations depends on R & C

$$f = \frac{1}{2\pi\sqrt{RC}}$$

→ It produces audio/low frequency signals.

→ Load Resistor is RC

Find the frequency of a transistor Hartley oscillator if

$L_1 = 100\mu H$, $L_2 = 1\mu H$, Mutual inductance (M) = $20\mu H$ and

$C = 20pF$. Find the freq

$$L_{eq} = L_1 + L_2 + 2M = 100 \times 10^{-6} + 1 \times 10^{-6} + 2(20 \times 10^{-6})$$

$$C = 20 \times 10^{-12}$$

$$f = \frac{1}{2\pi\sqrt{L_{eq}C}} = \frac{1}{2\pi\sqrt{(100 \times 10^{-6} + 10^{-6} + 40 \times 10^{-6}) \times 20 \times 10^{-12}}}$$

$$f = 1054.029 \text{ kHz}$$

Find the frequency of Colpitts oscillator

$C_1 = 0.001\mu F$, $C_2 = 0.01\mu F$, $L = 15\mu H$

$$f = \frac{1}{2\pi} \sqrt{\frac{1}{L C_1} + \frac{1}{L C_2}} = \frac{1}{2\pi} \sqrt{\frac{1}{15 \times 10^{-6} \times 0.001 \times 10^{-6}} + \frac{1}{15 \times 10^{-6} \times 0.01 \times 10^{-6}}}$$

$$f = 1363.612 \text{ kHz}$$

In a transistorized Hartley oscillator, two inductances are 2mH & 20mH, while frequency is to be varied from 950kHz to 2050kHz. Calculate the range over which the capacitor is to be varied?

$M = 0$
 $L_{eq} = L_1 + L_2 = 0.002 + 0.02 = 0.022$
 $f = \frac{1}{2\pi\sqrt{L_{eq}C}}$
 $950\text{kHz} = \frac{1}{2\pi\sqrt{L_{eq}C}}$
 $\sqrt{L_{eq}C} = \frac{1}{2\pi(950\text{k})}$
 $C = \frac{1}{(2\pi(950\text{k}))^2 \times 0.022} = 1.3894\text{pF}$
 $C_1 = 0.00091$ $C_2 = 0.00066$

$2050\text{kHz} = \frac{1}{2\pi\sqrt{L_{eq}C_2}}$
 $C_2 = \frac{1}{(2\pi)^2 L_{eq} (2050\text{kHz})^2} = 2.98 \times 10^{-12} \text{ F} = 2.98\text{pF}$
 \therefore capacitor range is (2.98pF to 13.89pF)

In a Colpitts oscillator $C_1 = 0.001\mu\text{F}$, $C_2 = 0.01\mu\text{F}$, $L = 10\mu\text{H}$. Find the frequency of oscillations, f , voltage gain (A_v) ?

$f = \frac{1}{2\pi\sqrt{L\left(\frac{1}{C_1} + \frac{1}{C_2}\right)}}$
 $f = \frac{1}{2\pi\sqrt{10 \times 10^{-6} \left(\frac{1}{0.001 \times 10^{-6}} + \frac{1}{0.01 \times 10^{-6}}\right)}}$
 $f = 1670.077\text{kHz}$

$A_v = \frac{C_2}{C_1} = 10$

We know that $A\beta = 1 \Rightarrow \beta = \frac{1}{A} = 0.1$
 A FET RC phase shift oscillator has $g_m = 5\text{mA/V}$, $r_D = 50\text{k}\Omega$. Feedback resistance is $R = 100\text{k}\Omega$ and capacitance value is 64.79pF . Calculate the frequency of oscillations & $R_D = ?$

$f = \frac{1}{2\pi R C \sqrt{10}} = \frac{1}{2\pi \times 64.79 \times 10^{-12} \times 100 \times 10^3 \sqrt{10}} = 7.779\text{kHz}$
 $R_D =$

$|A| \geq 29$ $A \geq g_m R_L$

$$R_L = 2d \parallel R_D$$

$$f_m R_L > 29 \Rightarrow R_L > \frac{29}{f_m}$$

$$R_L > 5.8 \text{ k}\Omega$$

$$\text{Let } R_L = 6 \text{ k}\Omega$$

$$\therefore \text{By } R_L = 2d \parallel R_D$$

$$R_L = \frac{2d \times R_D}{2d + R_D}$$

$$(2d + R_D) 6 \text{ k}\Omega = 2d \times R_D$$

$$50 \times 10^3 \times 6 \times 10^3 + R_D \times 6 \text{ k}\Omega = 50 \times 10^3 \times R_D$$

$$6 \times 10^6 + R_D = 50 \times 10^3 R_D$$

$$44 \times 10^3 R_D = 300 \times 10^6$$

$$R_D = \frac{300 \times 10^6}{44 \times 10^3}$$

$$R_D = 6.818 \text{ k}\Omega$$


Drawbacks of RC & LC oscillators.

Crystal Oscillators:

In case of RC & LC oscillators, the frequency of ~~operations~~ operations does not remain strictly constant. The reason behind this is the values of R, C & L which are frequency determining factors. They may be changed due to so many reasons & they are not able to generate microwave frequencies.

→ To overcome the above disadvantages crystal oscillators are used, and its principle depends on piezo electric effect.

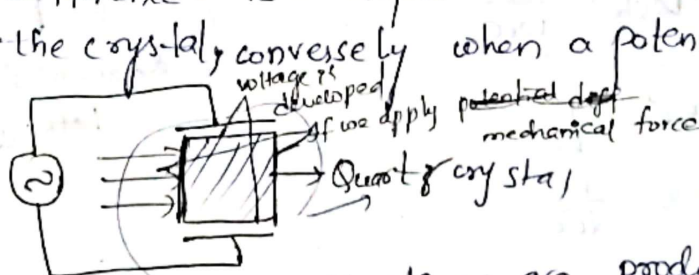
Piezo electric effect = It means when a mechanical stress/strain is applied across one faces of the crystal then a potential difference is developed across the opposite faces of the crystal, conversely when a potential difference



is applied mechanical vibrations are produced along the opposite faces, and that vibrations are in the form of oscillations



Working of Quartz crystal:

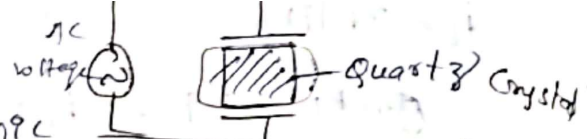

In order to use crystal in electronic circuit it is placed b/w two metals. This arrangement is equivalent to a capacitor with crystal as a dielectric as shown in fig. above.


⇒ When an AC voltage is applied crystal starts vibrating with the frequency of applied voltage. If frequency of applied voltage is equal to natural frequency of a crystal, resonance takes place and crystal starts vibrating with maximum amplitude.

⇒ The electrical equivalent of a crystal is shown in fig. b when the crystal is not vibrating, it is equivalent to capacitance C_m & when a crystal starts vibrating, it can be represented by a series RLC circuit, shunted (parallel) to C_m .

→ In this L is electrically equivalent to mass of the vibrating crystal.

→ C is equivalent to mechanical compliance

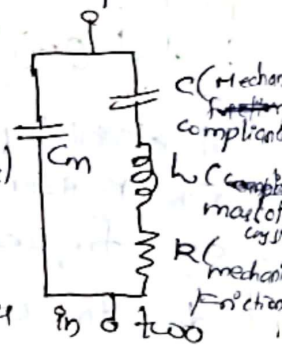and R is electrically equivalent to mechanical friction.



The above electrical equivalent crystal operates in 2 frequencies resonance conditions.

1) Series Resonance frequency:

Under this the reactance of Inductance (X_L) is equivalent to reactance of capacitance (X_C) in series RLC circuit

$$X_L = X_C$$

$$\omega_s L = \frac{1}{\omega_s C}$$

$$\omega_s^2 = \frac{1}{LC}$$

$$\omega_s = \frac{1}{\sqrt{LC}}$$

$$2\pi f_s = \frac{1}{\sqrt{LC}}$$

$$f_s = \frac{1}{2\pi\sqrt{LC}}$$

Series resonance frequency.

Working of Resonance with both \odot & \ominus

② parallel Resonance frequency: Under this frequency the total reactance of series RLC circuit is equal to Reactance of (C_m) mounting capacitance i.e) $\omega_p L - \frac{1}{\omega_p C} = \frac{1}{\omega_p C_m}$

$$\frac{\omega_p^2 LC - 1}{C} = \frac{1}{C_m}$$

$$\omega_p^2 L - \frac{1}{C} = \frac{1}{C_m}$$

$$\omega_p^2 L = \frac{1}{C_m} + \frac{1}{C}$$

$$\omega_p^2 = \frac{1}{L} \left[\frac{1}{C_m} + \frac{1}{C} \right]$$

$$\omega_p^2 = \frac{1}{L} (C_{eq})$$

$$\omega_p = \frac{1}{\sqrt{LC_{eq}}}$$

$$2\pi f_p = \frac{1}{\sqrt{LC_{eq}}}$$

$$f_p = \frac{1}{2\pi\sqrt{LC_{eq}}}$$


$$\left. \begin{array}{l} \frac{1}{C_m} + \frac{1}{C} \\ = \text{parallel} \\ C_{eq} = \frac{CC_m}{C+C_m} \end{array} \right\}$$

The below fig. shows the transistorized Crystal Oscillator with voltage divider bias:

⇒ This transistorized crystal oscillator is suggested by "Pierce".

⇒ In fig. 9, NPN transistor in CE configuration with voltage divider bias is used.

⇒ Here R_1 & R_2 provides biasing, R_e & C_e provides stabilization, RFC provides very high reactance path for Radiofrequency signals, C_o acts as output coupling capacitor to

block DC voltages and the crystal is connected in b/w collector to Base so it acts as feedback (or u can connect as ) and it operates in series resonance frequency because it is connected in a series element in feedback path from Collector to Base.

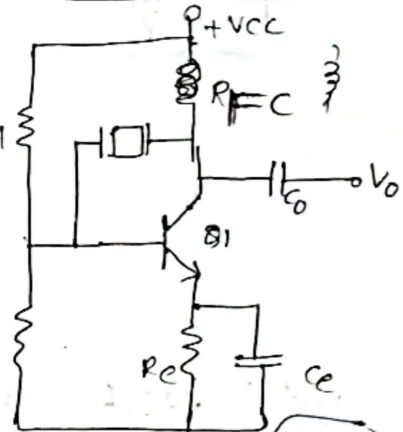


Fig 9

The frequency of oscillations is given by $f = \frac{1}{2\pi\sqrt{LC}}$


Advantages:

- As frequency of crystal is independent of temperature.
- These oscillators have higher order frequency stability.
- It is a fixed oscillator for generating microwave frequencies.
- Quality factor of crystal is very high.

Disadvantages:

- we cannot vary the oscillator because it is fixed.
- frequency of oscillations cannot be changed.
- It is a cost circuit.

Miller Crystal Oscillator:

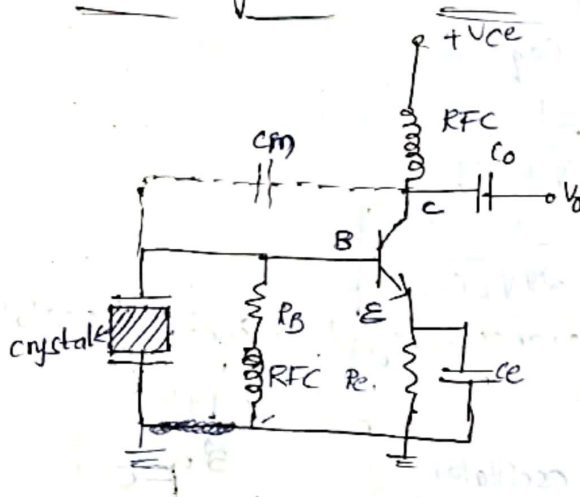

Crystal is connected in parallel to RFC. So it is called parallel resonance.

A crystal has $L = 0.1 \mu\text{H}$, $C = 0.08 \text{ pF}$, $C_m = 1 \text{ pF}$ with series resistance $(R_s) = 5 \text{ k}\Omega$, calculate series resonant frequency (f_s)

(f_p) parallel Resonant Frequency, Quality factor (Q) and by what percent that the parallel resonant frequency exceeds the series resonant frequency.

$$1) \quad f_s = \frac{1}{2\pi\sqrt{LC}} = \frac{1}{2\pi\sqrt{0.055 \times 10^{-12} \times 0.1}} = 4683 \text{ kHz}$$

$$f_p = \frac{1}{2\pi\sqrt{C_{eq} \cdot L}} = \frac{1}{2\pi\sqrt{\frac{C_m}{L+C_m} \times 0.1}} = 899.530 \text{ kHz}$$

$$3) Q = \frac{\omega_s L}{R} \quad \text{(or)} \quad \frac{2\pi f_s L}{R} = \frac{2\pi \times 863 \times 57610 \times 0.4}{5 \times 10^3} = 433.880$$

$$= \frac{1}{\omega_s CR} \quad \text{(or)}$$

4) % change = $\frac{f_p - f_s}{f_p} \times 100 = \frac{0.899 \times 10^6 - 0.893 \times 10^6}{0.899 \times 10^6} \times 100 = 4.004$

10M Frequency stability of oscillators :- = 4%

The ability of the circuit (oscillator) provides const. frequency over a period of time. is called frequency stability.

(or)
 \Rightarrow The ability of an oscillator to maintain the required frequency constant over a long time interval possible.

\rightarrow In transistor oscillators, the frequency of oscillations does not remain stable during long time because circuit parameters on which the oscillator frequency depends does not remain constant in time.

\rightarrow The frequency stability is affected due to following factors

1) change in temperature: The values of the components of feedback networks get affected. so changes in the values of R, L and C due to change in temp. is the main cause to which frequency does not remain stable.

2) Due to change in temp, the parameters of the active devices such as BJT (or) FET get affected, which changes frequency of oscillations.

3) Due to change in power supply: It affects the frequency.

4) Due to changes in atmospheric conditions, aging, unstable transistor parameters: It affects the frequency.

5) Due to changes in load connection: It affects the effective resistance of the feedback network.

6) Due to changes in capacitive effect in transistor at high frequencies such as stray capacitance (or) junction capacitances. It affects the capacitance of feedback circuit.

Based on change in temperature, frequency stability is defined as

$$S_{\omega-T} = \frac{\Delta\omega/\omega}{\Delta T} \text{ parts per million per } ^\circ\text{C}.$$

$\Delta\omega$ is change in frequency. ($\omega = 2\pi f$)

ω is desired frequency

ΔT is change in temperature

T is operating temperature.

→ Phase stability
 $S_{\omega} = \frac{d\phi}{d\omega}$ where $d\phi$ is change in phase shift (or) phase shift introduced by small change in frequency and $d\omega$ is change in frequency.

→ The frequency stability can be improved by the following Precautions

1) Enclosing the circuit in a constant temperature chamber.

2) Maintain constant power supply (supply voltage) by using Zener diode.


3) Load effect is reduced, by loosely connected to load.
(or)
with the help of a circuit having high i/p impedance & low output impedance.

Amplitude stability: It is defined as the ability of the oscillator to maintain constant amplitude over a long interval as possible.

→ The oscillator of amplitude if not limited/constant means which attains the extreme levels of saturation and it causes the distortion in output waveform due to either clipping of some portion/part of the wave form (or) it may drive amplifier into saturation.

→ To overcome above problems we can use circuit called amplitude limiting circuit two back to back zener diodes at the o/p of oscillator as shown in fig.

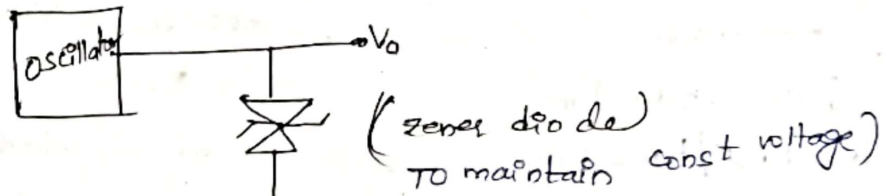→ This circuit makes the oscillations as a constant if the amplitude increases the behind limit.



Assign Write the differences b/n +ve & -ve feedback?

Tuned Amplifiers: To amplify the selective range of frequencies the resistive load (R_c) is replaced by a tuned circuit (tank circuit). The tuned circuit is capable of amplifying a signal over a narrow band of frequencies centered at resonance frequency.

Diff b/n normal Tuned amplifier


→ The amplifier with such a tuned circuit as a load are known as tuned amplifiers.

Below fig. shows the tuned parallel LC circuit which resonates at a particular frequency called as resonance frequency.


$$f_r = \frac{1}{2\pi\sqrt{LC}}$$

$$Z_r = \frac{L}{CR}$$

and impedance of tank circuit is

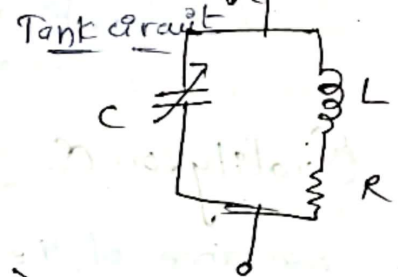

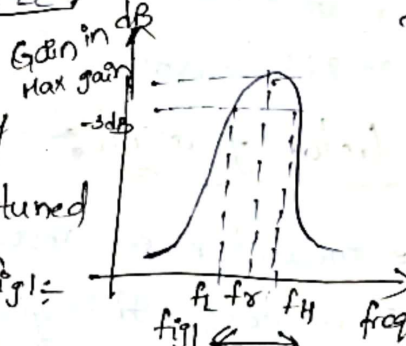At resonance frequency response of tuned circuit is shown in fig:



Q Why tuned circuit does not produce any oscillations?

When the applied signal frequency and tuned circuit frequency becomes, then reactance of inductance & reactance of capacitor cancelled, so circuit acts as pure resistive load, so no oscillations.

→ The frequency response of tuned circuit is shown in fig 1.

→ It is observed that max. gain is at Resonant frequency shortly below and above the resonant frequency (f_r).

→ At resonance the inductive and capacitive effect of tuned circuit cancelled each other as a result the tank circuit is acts like a resistive load, and it is able to amplify the i/p signal without oscillations.

Coil losses = (Inductor losses)



Pure Inductor

Inductor with series leakage resistor

In a tank/tuned circuit consists of coil/inductor, practically coil is not a purely inductive. It consists of few losses and they are represented in the form of leakage resistance in series with the inductor.

→ The losses in the coil are: copper, Eddy current, Hysteresis & copper losses. It appears at low frequencies and the coil is equivalent to DC resistance. These losses are inversely proportional

to frequency, $CL \propto \frac{1}{f}$

Eddy current losses: These are due to current flowing within the coil. As a result of eddy current, a loss due to heating the coil. These losses are \propto (directly pro) to frequency $(f \times f)$

Hysteresis losses: It is proportional to area enclosed by the hysteresis loop and to the rate at which the loop is traversed. It is a function of signal level and increases with frequency and however, it is independent of frequency.

Quality (or) Q-factor of a coil: It is defined as the ratio of reactance of the inductor at resonant frequency to its

resistance. It is unitless. It is given by $Q = \frac{\omega L_s}{R_s}$ or $\frac{R_p}{\omega L_p}$

$Q = \frac{\omega L_s}{R_s}$ series -

$Q = \frac{R_p}{\omega L_p}$ parallel

→ It is the measure of how much pure inductor contains only reactance.


→ The higher the Q-value of inductor, few/less losses are there, in inductor.

→ It is also defined as the measure of efficiency with which inductor can store the energy. (Q-factor)


Classification of Tuned amplifiers

- ① Based on No. of tuning stages
- a) single Tuned Amplifier
 - b) double Tuned Amplifier
 - c) stagger tuned / Synchronous
- ② Based on Coupling element
- a) capacitive coupled tuned amp.
 - b) inductive coupled tuned amplifier
 - c) Transformer coupled tuned amplifier

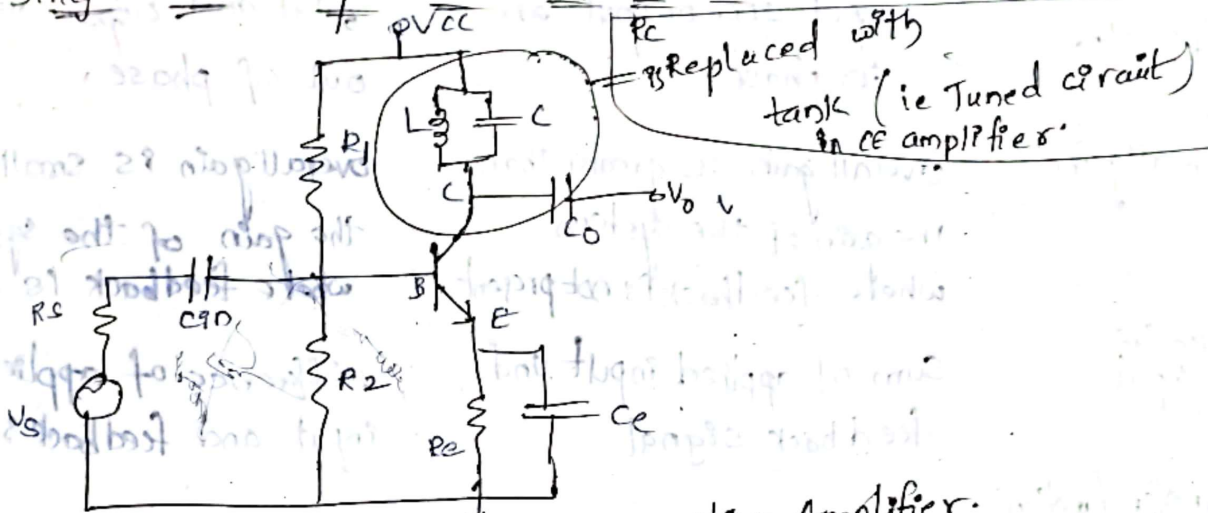Example of single Tuned capacitive Amplifier =



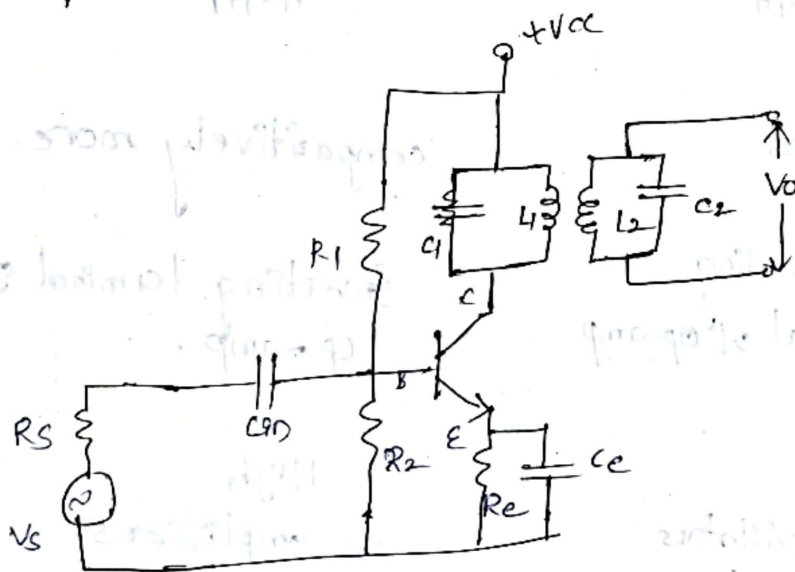Example of Double Tuned capacitive Amplifier.



Basis for comparison

Positive Feedback

Negative feedback

It is also called as regenerative feedback

It is also called as degenerative feedback.

Relation b/w i/p & o/p.

Input and output are in phase

Input and output are out of phase.

Overall gain

Overall gain is greater than the gain of the system where feedback is not present

Overall gain is smaller than the gain of the system where feedback is absent

Effective input

Sum of applied input and feedback signal

Difference of applied input and feedback signal.

Transfer function of system with respective feedback

$$\frac{G}{1-GH}$$

$$\frac{G}{1+GH}$$

stability

Less

Comparatively more.

Phase shift feedback is taken from

Non-inverting terminal of op-amp

Inverting terminal of op-amp.

Sensitivity

low

High

Use

In oscillators

In amplifiers

It increases the gain of the amplifier
It is regenerative or direct feedback

It decreases the gain of the amplifier.
It is degenerative or inverse feedback.

It makes the amplifier unstable

It makes the amplifier stable

It reduces the bandwidth

It increases the bandwidth

It is used in the oscillators

It is used in the small signal amplifiers.

Yes
relation

Rajeev Gandhi Memorial College of Engineering & Technology
Autonomous
NANDYAL-518501

Department of Electronics & Communication Engineering

Academic Year: 2022-23

Subject: Electronic Circuits-Analysis & Design (ECA&D)

Class: II B. Tech, II Sem

The following topics are covered beyond the syllabus as prescribed by RGM-R20 regulations:

1. Discrete- Circuit Amplifiers
2. Some useful transistor pairing in multistage amplifiers.
3. Effect of feedback on amplifier poles.
4. Amplifiers with Multiple Tuned Circuits

7.5 Discrete-Circuit Amplifiers

With our study of transistor amplifier basics complete, we now put everything together by presenting practical circuits for discrete-circuit amplifiers. These circuits, which utilize the amplifier configurations studied in Section 7.3 and the biasing methods of Section 7.4, can be assembled using off-the-shelf discrete transistors, resistors, and capacitors. Though practical and carefully selected to illustrate some important points, the circuits presented in this section should be regarded as examples of discrete-circuit transistor amplifiers. Indeed, there is a great variety of such circuits, a number of which are explored in the end-of-chapter problems.

As mentioned earlier, the vast majority of discrete-circuit amplifiers utilize BJTs. This is reflected in this section where all the circuits presented except for one utilize BJTs. Of course, if desired, one can utilize MOSFETs in the same amplifier configurations presented here. Also, the MOSFET is the device of choice in the design of integrated-circuit (IC) amplifiers. We begin our study of IC amplifiers in Chapter 8.

As will be seen shortly, the circuits presented in this section utilize large capacitors (in the μF range) to couple the signal source to the input of the amplifier, and to couple the amplifier output signal to a load resistance or to the input of another amplifier stage. As well, a large capacitor is employed to establish a signal ground at the desired terminal of the transistor (e.g., at the emitter of a CE amplifier). The use of capacitors for these purposes simplifies the design considerably: Since capacitors block dc, one is able to first carry out the dc bias design and then connect the signal source and load to the amplifier without disturbing the dc design. These amplifiers are therefore known as **capacitively coupled amplifiers**.

7.5.1 A Common-Source (CS) Amplifier

As mentioned in Section 7.3, the common-source (CS) configuration is the most widely used of all MOSFET amplifier circuits. A common-source amplifier realized using the bias circuit of Fig. 7.48(c) is shown in Fig. 7.55(a). Observe that to establish a **signal ground**, or an **ac ground** as it is sometimes called, at the source, we have connected a large capacitor, C_S , between the source and ground. This capacitor, usually in the microfarad range, is required to provide a very small impedance (ideally, zero impedance—i.e., in effect, a short circuit) at all signal frequencies of interest. In this way, the signal current passes through C_S to ground and thus *bypasses* the resistance R_S ; hence, C_S is called a **bypass capacitor**. Obviously, the lower the signal frequency, the less effective the bypass capacitor becomes. This issue will be studied in Section 10.1. For our purposes here we shall assume that C_S is acting as a perfect short circuit and thus is establishing a zero signal voltage at the MOSFET source.

To prevent disturbances to the dc bias current and voltages, the signal to be amplified, shown as voltage source v_{sig} with an internal resistance R_{sig} , is connected to the gate through a large capacitor C_{C1} . Capacitor C_{C1} , known as a **coupling capacitor**, is required to act as a perfect short circuit at all signal frequencies of interest while blocking dc. Here again, we note that as the signal frequency is lowered, the impedance of C_{C1} (i.e., $1/j\omega C_{C1}$) will increase and its effectiveness as a coupling capacitor will be correspondingly reduced. This problem, too, will be considered in Section 10.1 in connection with the dependence of the amplifier

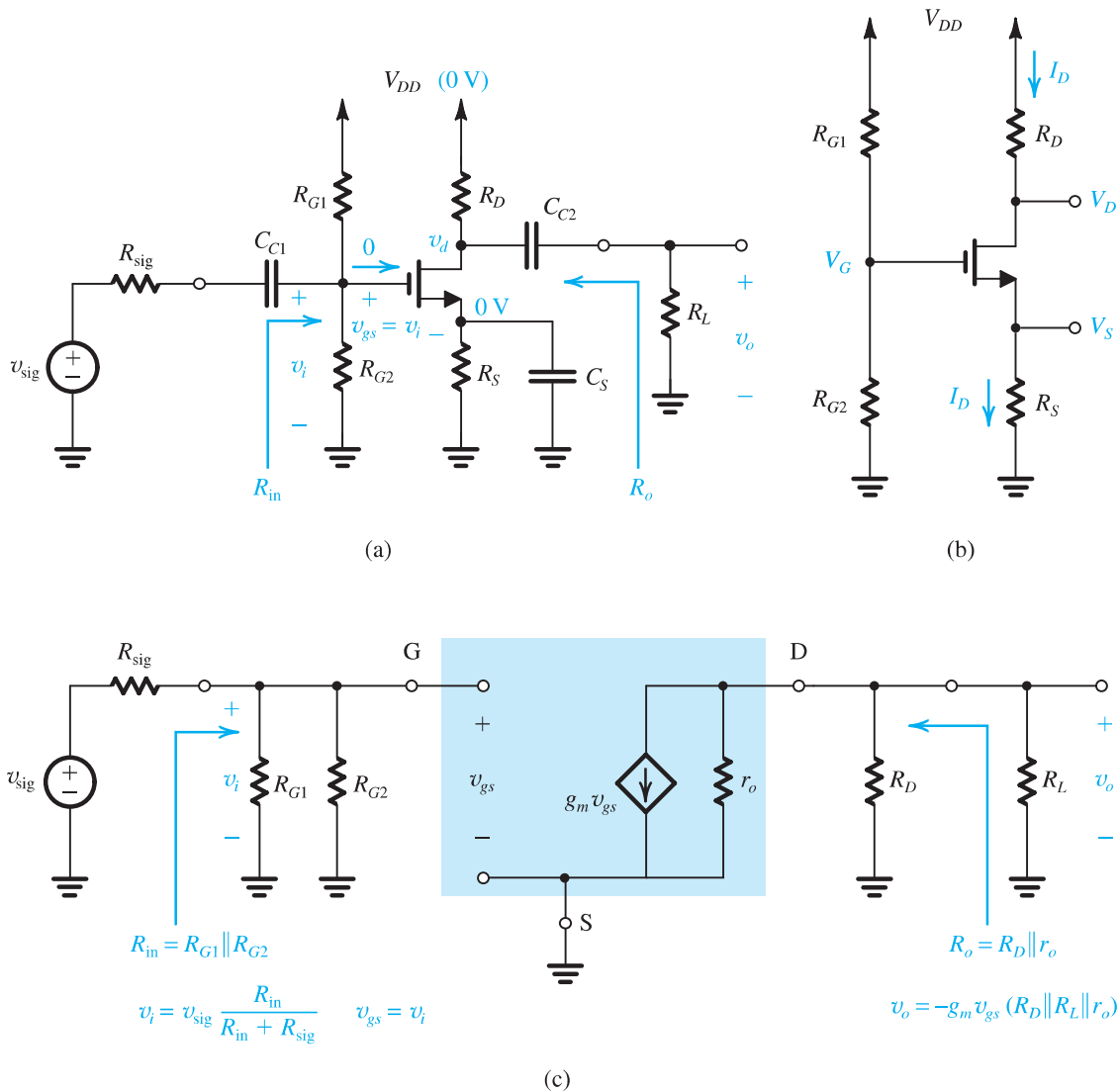


Figure 7.55 (a) A common-source amplifier using the classical biasing arrangement of Fig. 7.48(c). (b) Circuit for determining the bias point. (c) Equivalent circuit and analysis.

operation on frequency. For our purposes here we shall assume that C_{C1} is acting as a perfect short circuit as far as the signal is concerned.

The voltage signal resulting at the drain is coupled to the load resistance R_L via another coupling capacitor C_{C2} . We shall assume that C_{C2} acts as a perfect short circuit at all signal frequencies of interest and thus that the output voltage $v_o = v_d$. Note that R_L can be either an actual load resistor, to which the amplifier is required to provide its output voltage signal, or it can be the input resistance of another amplifier stage in cases where more than one stage of amplification is needed. (We will study multistage amplifiers in Chapter 9).

Since a capacitor behaves as an open circuit at dc, the circuit for performing the dc bias design and analysis is obtained by open-circuiting all capacitors. The resulting circuit is shown in Fig. 7.55(b) and can be designed as discussed in Section 7.4.1.

To determine the terminal characteristics of the CS amplifier of Fig. 7.55(a)—that is, its input resistance, voltage gain, and output resistance—we replace the MOSFET with its hybrid- π small-signal model, replace V_{DD} with a signal ground, and replace all coupling and bypass capacitors with short circuits. The result is the circuit in Fig. 7.55(c). Analysis is straightforward and is shown on the figure, thus

$$R_{in} = R_{G1} \parallel R_{G2} \quad (7.149)$$

which shows that to keep R_{in} high, large values should be used for R_{G1} and R_{G2} , usually in the megohm range. The overall voltage gain G_v is

$$G_v = -\frac{R_{in}}{R_{in} + R_{sig}} g_m (R_D \parallel R_L \parallel r_o) \quad (7.150)$$

Observe that we have taken r_o into account, simply because it is easy to do so. Its effect, however, is usually small (this is not the case for IC amplifiers, as will be explained in Chapter 8). Finally, to encourage the reader to do the small-signal analysis directly on the original circuit diagram, with the MOSFET model used implicitly, we show some of the analysis on the circuit of Fig. 7.55(a).

EXERCISES

D7.37 Design the bias circuit in Fig. 7.55(b) for the CS amplifier of Fig. 7.55(a). Assume the MOSFET is specified to have $V_t = 1$ V, $k_n = 4$ mA/V², and $V_A = 100$ V. Neglecting the Early effect, design for $I_D = 0.5$ mA, $V_S = 3.5$ V, and $V_D = 6$ V using a power-supply $V_{DD} = 15$ V. Specify the values of R_S and R_D . If a current of 2 μ A is used in the voltage divider, specify the values of R_{G1} and R_{G2} . Give the values of the MOSFET parameters g_m and r_o at the bias point.

Ans. $R_S = 7$ k Ω ; $R_D = 18$ k Ω ; $R_{G1} = 5$ M Ω ; $R_{G2} = 2.5$ M Ω ; $g_m = 2$ mA/V; $r_o = 200$ k Ω

7.38 For the CS amplifier of Fig. 7.55(a) use the design obtained in Exercise 7.37 to determine R_{in} , R_o , and the overall voltage gain G_v when $R_{sig} = 100$ k Ω and $R_L = 20$ k Ω .

Ans. 1.67 M Ω ; 16.5 k Ω ; -17.1 V/V

D7.39 As discussed in Section 7.3, beneficial effects can be realized by having an unbypassed resistance R_s in the source lead of the CS amplifier. This can be implemented in the circuit of Fig. 7.55(a) by splitting the resistance R_S into two resistances: R_s , which is left unbypassed, and $(R_S - R_s)$, across which the bypass capacitor C_S is connected. Now, if in order to improve linearity of the amplifier in Exercises 7.37 and 7.38, v_{gs} is to be reduced to half its value, what value should R_s have? What would the amplifier gain G_v become? Recall that when R_s is included it becomes difficult to include r_o in the analysis, so neglect it.

Ans. $R_s = 500$ Ω ; $G_v = -8.9$ V/V

7.5.2 A Common-Emitter Amplifier

The common-emitter (CE) amplifier is the most widely used of all BJT amplifier configurations. Figure 7.56(a) shows a CE amplifier utilizing the classical biasing arrangement of Fig. 7.48(c), the design of which was considered in Section 7.4. The CE circuit in Fig. 7.54(a) is the BJT counterpart of the CS amplifier of Fig. 7.55(a). It utilizes coupling capacitors C_{C1} and C_{C2} and bypass capacitor C_E . Here we assume that these capacitors, while blocking dc, behave as perfect short circuits at all signal frequencies of interest.

To determine the characteristic parameters of the CE amplifier, we replace the BJT with its hybrid- π model, replace V_{CC} with a short circuit to ground, and replace the coupling and bypass capacitor with short circuits. The resulting small-signal equivalent circuit of the CE amplifier is shown in Fig. 7.56(b). The analysis is straightforward and is given in the

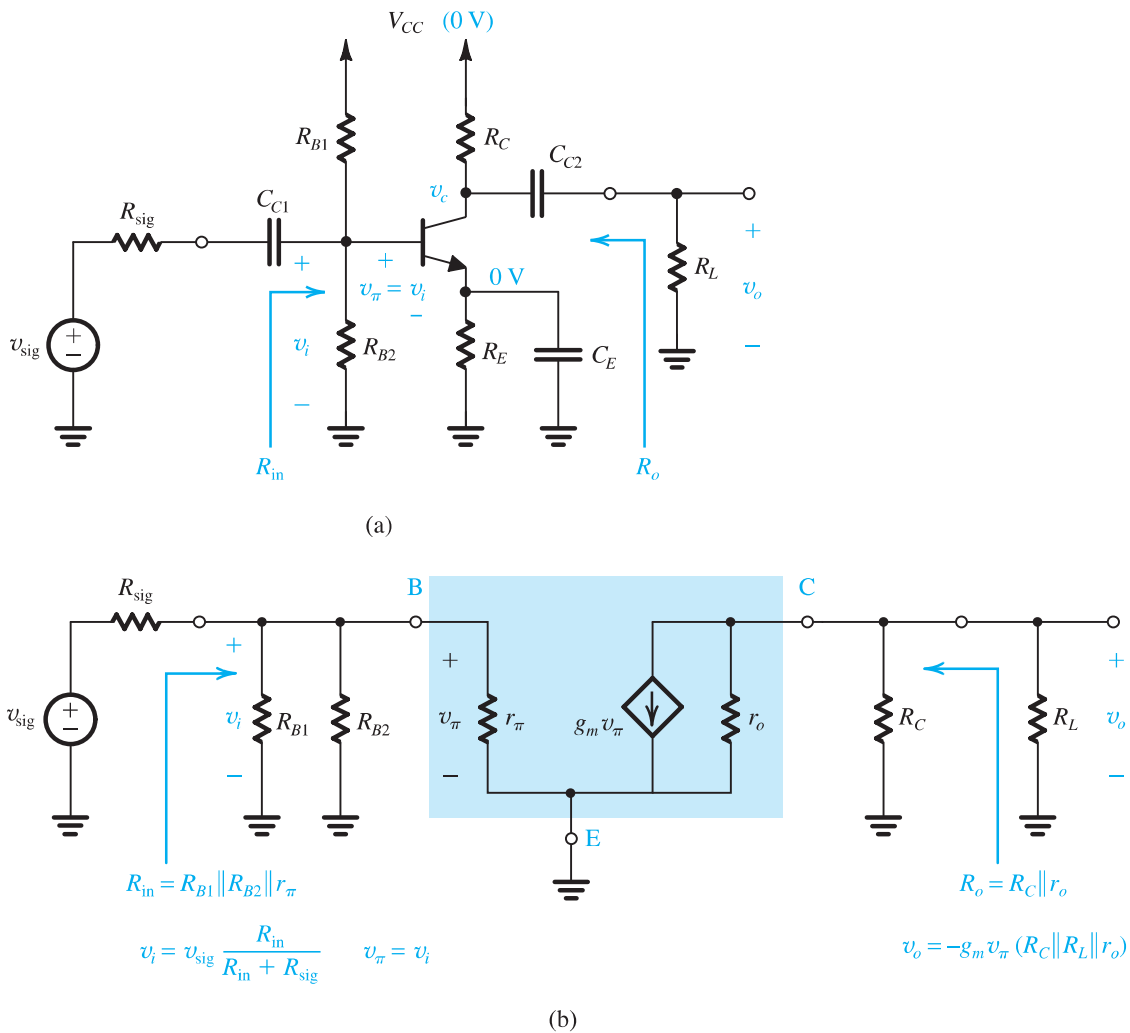


Figure 7.56 (a) A common-emitter amplifier using the classical biasing arrangement of Fig. 7.52(a). (b) Equivalent circuit and analysis.

figure, thus

$$R_{in} = R_{B1} \parallel R_{B2} \parallel r_{\pi} \quad (7.151)$$

which indicates that to keep R_{in} relatively high, R_{B1} and R_{B2} should be selected large (typically in the range of tens or hundreds of kilohms). This requirement conflicts with the need to keep R_{B1} and R_{B2} low so as to minimize the dependence of the dc current I_C on the transistor β . We discussed this design trade-off in Section 7.4.

The voltage gain G_v is given by

$$G_v = -\frac{R_{in}}{R_{in} + R_{sig}} g_m (R_C \parallel R_L \parallel r_o) \quad (7.152)$$

Note that we have taken r_o into account because it is easy to do so. However, as already mentioned, the effect of this parameter on discrete-circuit amplifier performance is usually small.

EXERCISES

D7.40 Design the bias circuit of the CE amplifier of Fig. 7.56(a) to obtain $I_E = 0.5$ mA and $V_C = +6$ V. Design for a dc voltage at the base of 5 V and a current through R_{B2} of 50 μ A. Let $V_{CC} = +15$ V, $\beta = 100$, and $V_{BE} \simeq 0.7$ V. Specify the values of R_{B1} , R_{B2} , R_E , and R_C . Also give the values of the BJT small-signal parameters g_m , r_{π} , and r_o at the bias point. (For the calculation of r_o , let $V_A = 100$ V.)

Ans. $R_{B1} = 182$ k Ω ; $R_{B2} = 100$ k Ω ; $R_E = 8.6$ k Ω ; $R_C = 18$ k Ω ; $g_m = 20$ mA/V, $r_{\pi} = 5$ k Ω , $r_o = 200$ k Ω

7.41 For the amplifier designed in Exercise 7.40, find R_{in} , R_o , and G_v when $R_{sig} = 10$ k Ω and $R_L = 20$ k Ω .

Ans. $R_{in} = 4.64$ k Ω ; $R_o = 16.51$ k Ω ; $G_v = -57.3$ V/V

7.5.3 A Common-Emitter Amplifier with an Emitter Resistance R_e

As discussed in Section 7.3.4, it is beneficial to include a small resistance in the transistor emitter lead. This can be implemented in the circuit of Fig. 7.56(a) by splitting the emitter bias resistance R_E into two components: an unbypassed resistance R_e , and a resistance ($R_E - R_e$) across which the bypass capacitor C_E is connected. The resulting circuit is shown in Fig. 7.57(a) and its small-signal model is shown in Fig. 7.57(b). In the latter we utilize the T model of the BJT because it results in much simpler analysis (recall that this is always the case when a resistance is connected in series with the emitter). Also note that we have not included r_o , for doing so would complicate the analysis significantly. This burden would not be justified given that r_o has little effect on the performance of discrete-circuit amplifiers.

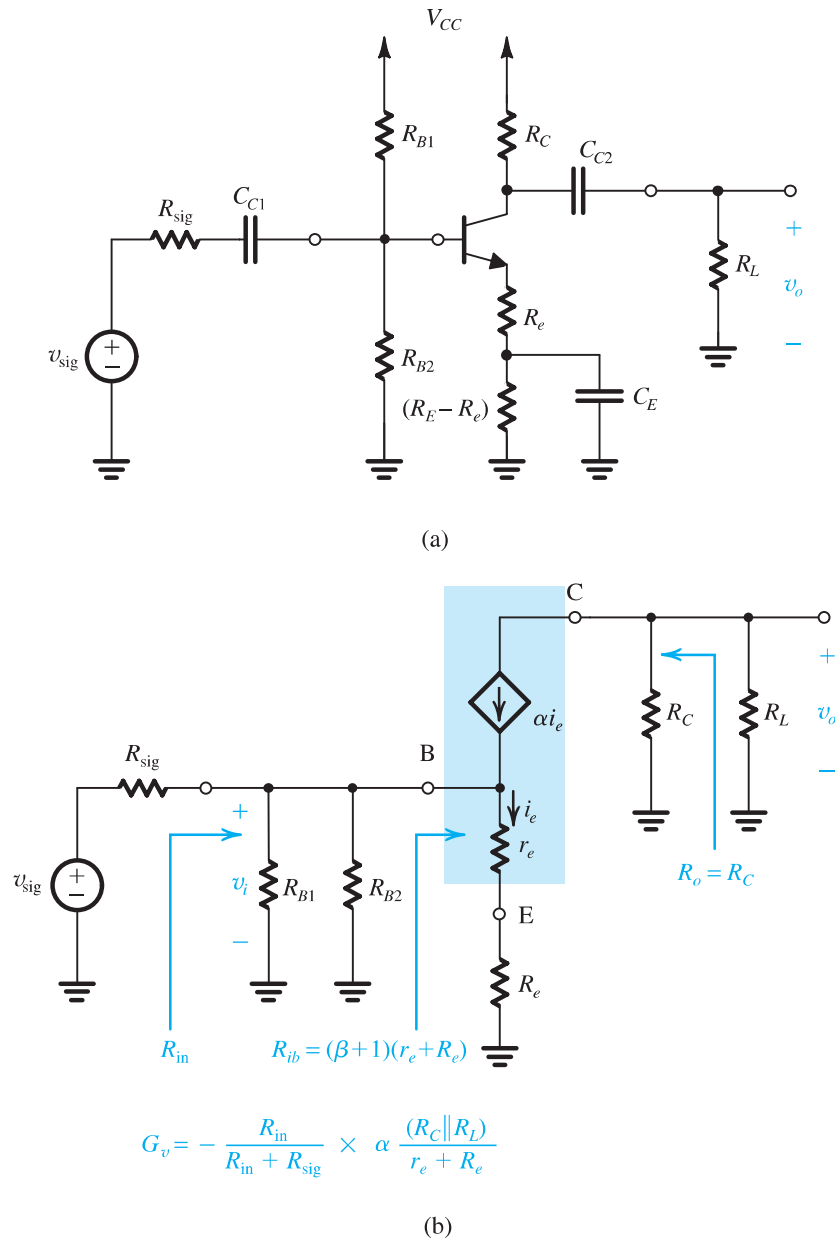


Figure 7.57 (a) A common-emitter amplifier with an unbiasing emitter resistance R_e . (b) The amplifier small-signal model and analysis.

Analysis of the circuit in Fig. 7.57(b) is straightforward and is shown in the figure. Thus,

$$\begin{aligned} R_{in} &= R_{B1} \parallel R_{B2} \parallel (\beta + 1)(r_e + R_e) \\ &= R_{B1} \parallel R_{B2} \parallel [r_{\pi} + (\beta + 1)R_e] \end{aligned} \quad (7.153)$$

from which we note that including R_e increases R_{in} because it increases the input resistance looking into the base by adding a component $(\beta + 1)R_e$ to r_π . The overall voltage gain G_v is

$$\begin{aligned} G_v &= -\frac{R_{in}}{R_{in} + R_{sig}} \times \alpha \frac{\text{Total resistance in collector}}{\text{Total resistance in emitter}} \\ &= -\alpha \frac{R_{in}}{R_{in} + R_{sig}} \frac{R_C \parallel R_L}{r_e + R_e} \end{aligned} \quad (7.154)$$

EXERCISE

7.42 For the amplifier designed in Exercise 7.40 and analyzed in Exercise 7.41, let it be required to raise R_{in} to 10 k Ω . What is the required value of R_e , and what does the overall voltage gain G_v become?

Ans. $R_e = 67.7 \Omega$; $G_v = -39.8 \text{ V/V}$

7.5.4 A Common-Base (CB) Amplifier

Figure 7.58(a) shows a CB amplifier designed using the biasing arrangement of Fig. 7.53. Note that the availability of two power supplies, V_{CC} and $-V_{EE}$, enables us to connect the base directly to ground, obviating the need for a large bypass capacitor to establish a signal ground at the base.

The small-signal equivalent circuit of the CB amplifier is shown in Fig. 7.58(b). As expected, we have utilized the T model of the BJT and have not included r_o . Including r_o would complicate the analysis significantly without making much difference to the results in the case of discrete-circuit amplifiers. From the circuit in Fig. 7.58(b) we find

$$R_{in} = r_e \parallel R_E \simeq r_e \simeq 1/g_m$$

which as expected can be very small, causing v_i to be a small fraction of v_{sig} ,

$$v_i = v_{sig} \frac{R_{in}}{R_{in} + R_{sig}}$$

Now,

$$i_e = -\frac{v_i}{r_e}$$

and

$$v_o = -\alpha i_e (R_C \parallel R_L)$$

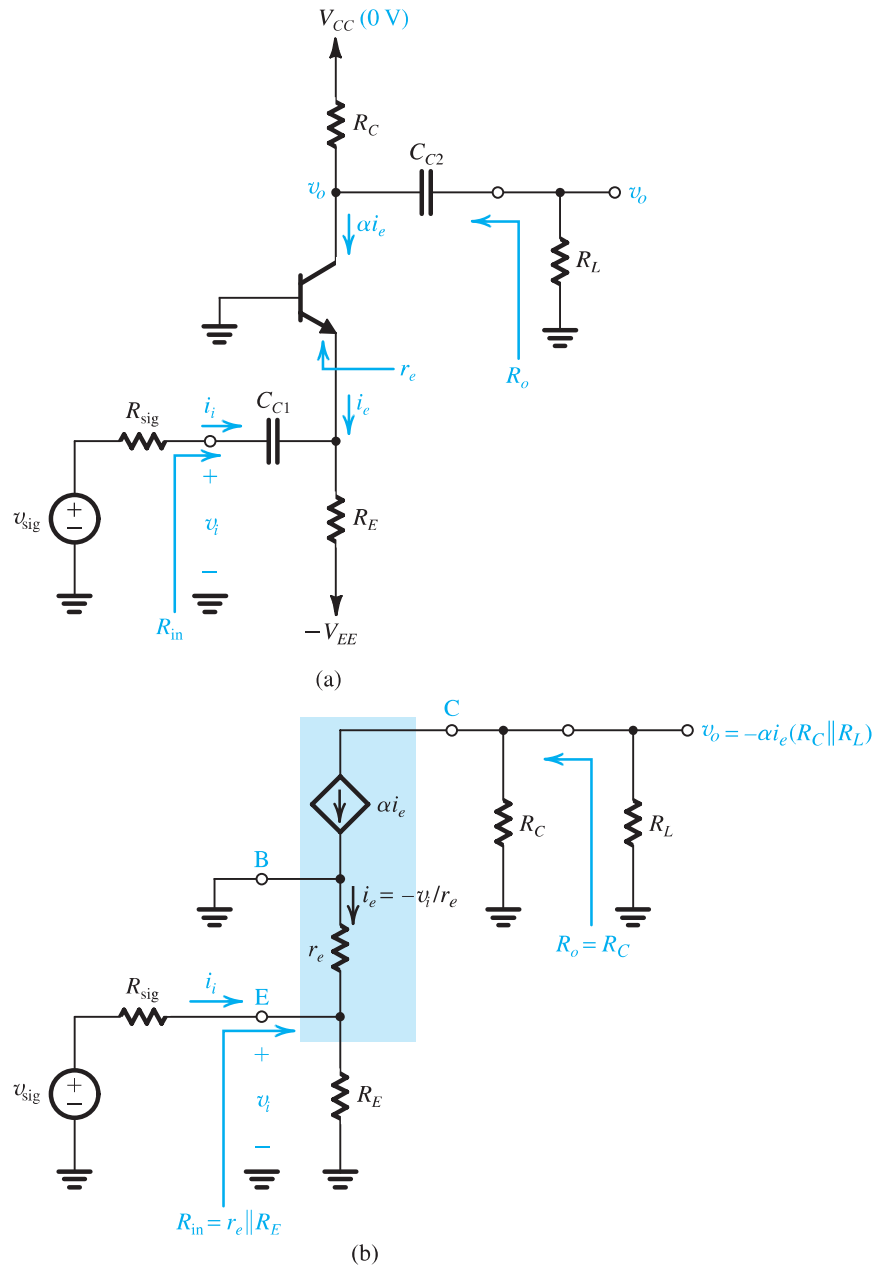


Figure 7.58 (a) A common-base amplifier using the structure of Fig. 7.53 with R_B omitted (since the base is grounded). (b) Equivalent circuit obtained by replacing the transistor with its T model.

Thus, the overall voltage gain is given by

$$G_v = \alpha \frac{R_{in}}{R_{in} + R_{sig}} \frac{R_C \parallel R_L}{r_e} = \frac{R_{in}}{R_{in} + R_{sig}} g_m (R_C \parallel R_L) \quad (7.155)$$

EXERCISE

D7.43 Design the CB amplifier of Fig. 7.58(a) to provide an input resistance R_{in} that matches the source resistance of a cable with a characteristic resistance of $50\ \Omega$. Assume that $R_E \gg r_e$. The available power supplies are $\pm 5\text{ V}$ and $R_L = 8\text{ k}\Omega$. Design for a dc collector voltage $V_C = +1\text{ V}$. Specify the values of R_C and R_E . What overall voltage gain is obtained? If v_{sig} is a sine wave with a peak amplitude of 10 mV , what is the peak amplitude of the output voltage? Let $\alpha \simeq 1$.

Ans. $R_C = 8\text{ k}\Omega$; $R_E = 8.6\text{ k}\Omega$; 40 V/V ; 0.4 V

7.5.5 An Emitter Follower

Figure 7.59(a) shows an emitter follower designed using the bias arrangement of Fig. 7.53 and two power supplies, V_{CC} and $-V_{EE}$. The bias resistance R_B affects the input resistance of the follower and should be chosen as large as possible while limiting the dc voltage drop across it to a small fraction of V_{EE} ; otherwise the dependence of the bias current I_C on β can become unacceptably large.

Figure 7.59(b) shows the small-signal equivalent circuit of the emitter follower. Here, as expected, we have replaced the BJT with its T model and included r_o (since this can be done very simply). The input resistance of the emitter follower can be seen to be

$$R_{in} = R_B \parallel R_{ib} \quad (7.156)$$

where R_{ib} , the input resistance looking into the base, can be obtained by using the resistance-reflection rule. Toward that end, note that r_o appears in parallel with R_E and R_L (which is why it can be easily taken into account). Thus,

$$R_{ib} = (\beta + 1)[r_e + (R_E \parallel r_o \parallel R_L)] \quad (7.157)$$

The overall voltage gain can be determined by tracking the signal transmission from source to load,

$$v_i = v_{sig} \frac{R_{in}}{R_{in} + R_{sig}} \quad (7.158)$$

and

$$v_o = v_i \frac{R_E \parallel r_o \parallel R_L}{r_e + (R_E \parallel r_o \parallel R_L)} \quad (7.159)$$

Thus,

$$G_v \equiv \frac{v_o}{v_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}} \frac{(R_E \parallel r_o \parallel R_L)}{r_e + (R_E \parallel r_o \parallel R_L)} \quad (7.160)$$

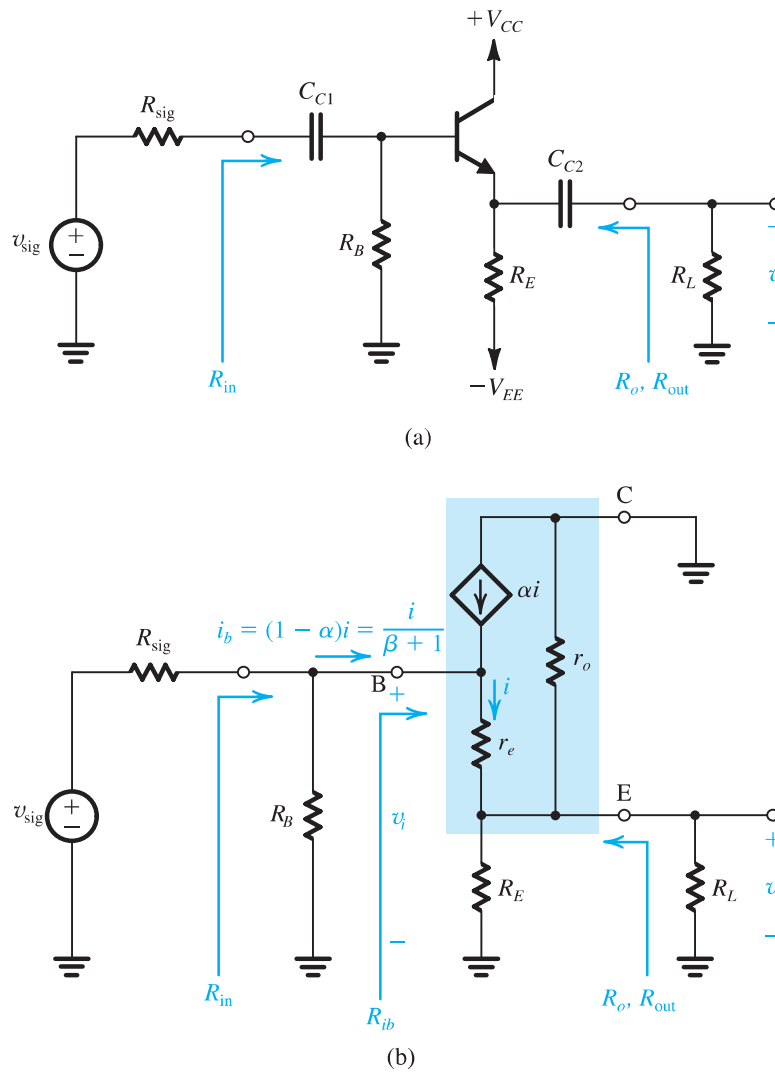


Figure 7.59 (a) An emitter-follower circuit. (b) Small-signal equivalent circuit of the emitter follower with the transistor replaced by its T model. Note that r_o is included because it is easy to do so. Normally, its effect on performance is small.

Finally, the output resistance R_{out} can be obtained by short-circuiting v_{sig} and looking back into the output terminal, excluding R_L , as

$$R_{out} = r_o \parallel R_E \parallel \left[r_e + \frac{R_B \parallel R_{sig}}{\beta + 1} \right] \quad (7.161)$$

Note that we have used the inverse resistance-reflection rule, namely, dividing the total resistance in the base, $(R_B \parallel R_{sig})$, by $(\beta + 1)$.

From the above example we observe that using the Widlar circuit allows the generation of a small constant current using relatively small resistors. This is an important advantage that results in considerable savings in chip area. In fact the circuit of Fig. 8.43(a), requiring a 942-k Ω resistance, is totally impractical for implementation in IC form because of the very high value of resistor R_1 .

Another important characteristic of the Widlar current source is that its output resistance is high. The increase in the output resistance, above that achieved in the basic current source, is due to the emitter-degeneration resistance R_E . To determine the output resistance of Q_2 , we assume that since the base of Q_2 is connected to ground via the small resistance r_e of Q_1 , the incremental voltage at the base will be small. Thus we can use the formula in Eq. (8.70) and adapt it for our purposes here as follows:

$$R_{\text{out}} \simeq [1 + g_m(R_E \parallel r_\pi)]r_o \quad (8.102)$$

Thus the output resistance is increased above r_o by a factor that can be significant.

EXERCISE

8.27 Find the output resistance of each of the two current sources designed in Example 8.6. Let $V_A = 100$ V and $\beta = 100$.

Ans. 10 M Ω ; 54 M Ω

8.7 Some Useful Transistor Pairings

The cascode configuration studied in Section 8.5 combines CS and CG MOS transistors (CE and CB bipolar transistors) to great advantage. The key to the superior performance of the resulting combination is that the transistor pairing is done in a way that maximizes the advantages and minimizes the shortcomings of each of the two individual configurations. In this section we present a number of other such transistor pairings. In each case the transistor pair can be thought of as a compound device; thus the resulting amplifier may be considered as a single stage.

8.7.1 The CC–CE, CD–CS, and CD–CE Configurations

Figure 8.44(a) shows an amplifier formed by cascading a common-collector (emitter-follower) transistor Q_1 with a common-emitter transistor Q_2 . This circuit has two main advantages over the CE amplifier. First, the emitter follower increases the input resistance by a factor equal to $(\beta_1 + 1)$. As a result, the overall voltage gain is increased, especially if the resistance of the signal source is large. Second, it will be shown in Chapter 10 that the CC–CE amplifier can exhibit much wider bandwidth than that obtained with the CE amplifier.

The MOS counterpart of the CC–CE amplifier, namely, the CD–CS configuration, is shown in Fig. 8.44(b). Here, since the CS amplifier alone has an infinite input resistance, the

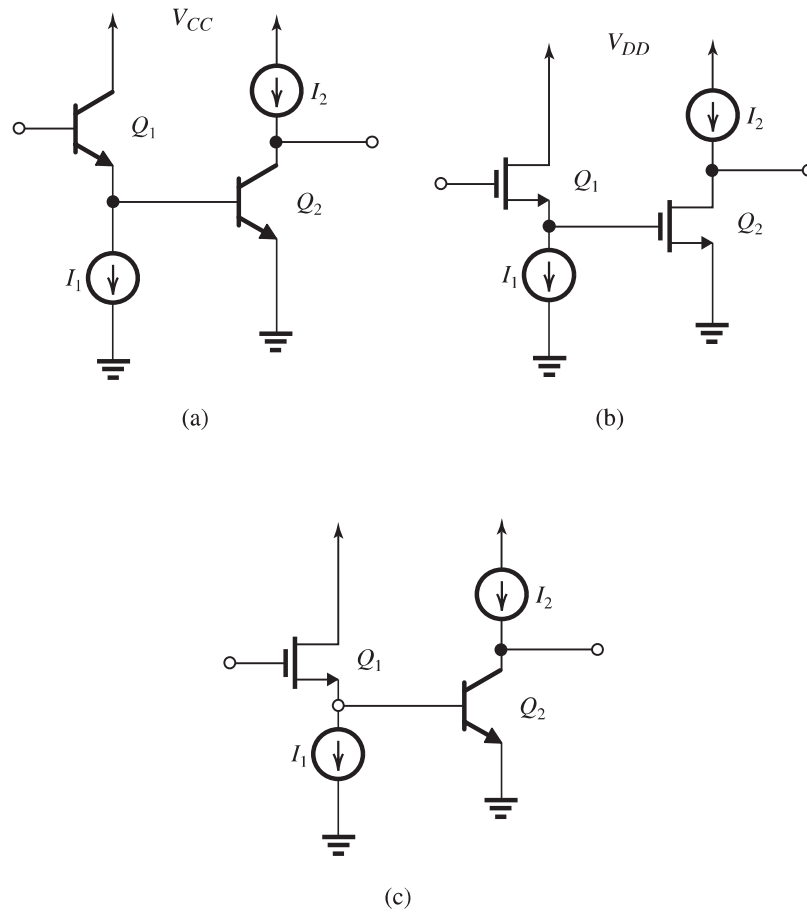


Figure 8.44 (a) CC–CE amplifier; (b) CD–CS amplifier; (c) CD–CE amplifier.

sole purpose for adding the source-follower stage is to increase the amplifier bandwidth, as will be seen in Chapter 10. Finally, Fig. 8.44(c) shows the BiCMOS version of this circuit type. Compared to the bipolar circuit in Fig. 8.44(a), the BiCMOS circuit has an infinite input resistance. Compared to the MOS circuit in Fig. 8.44(b), the BiCMOS circuit typically has a higher g_{m2} .

The IC Source Follower Since a number of the circuit configurations discussed in this section utilize an input source follower, we digress briefly to consider the IC source follower (the discrete-circuit source follower was studied in Section 7.3.6). Figure 8.45(a) shows a source follower formed by transistor Q_1 and biased by a constant-current supplied by the current mirror Q_2 – Q_3 . Observe that since the source of Q_1 cannot be connected to the body (which is at signal ground potential) a voltage signal v_{bs} develops between body and source and gives rise to a current signal $g_{mb}v_{bs}$, as indicated in the equivalent circuit in Fig. 8.45(b). The equivalent circuit shows also the output resistance r_{o3} of the bias current source Q_3 , which acts as a load resistance for the follower Q_1 .

An important observation to make from the equivalent circuit is that the controlled source ($g_{mb}v_{bs}$) appears across its control voltage v_{bs} . Thus we can use the source-absorption theorem (Appendix G) to replace the controlled source with a resistance $1/g_{mb}$. Next, note that the three

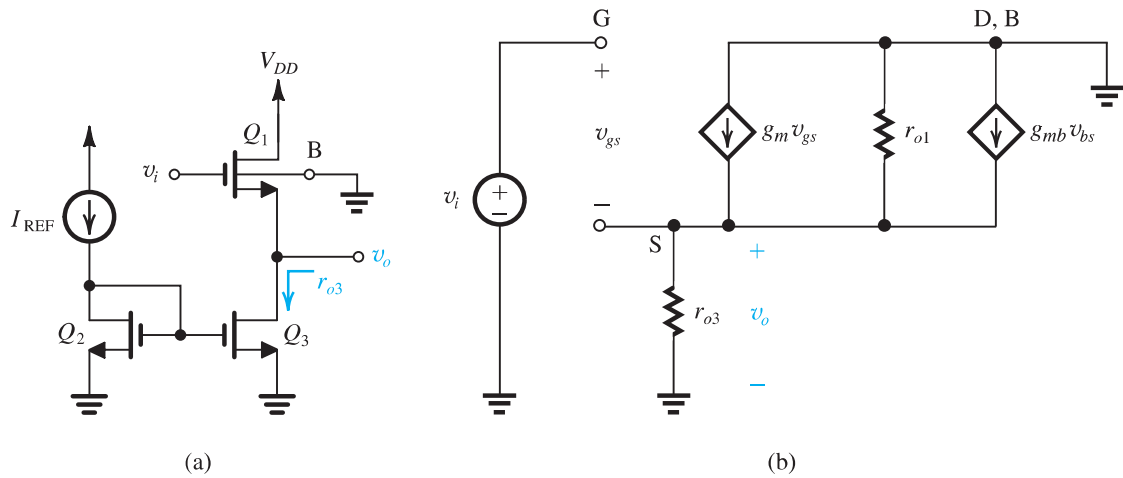


Figure 8.45 (a) A source follower biased with a current mirror Q_2 – Q_3 and with the body terminal indicated. Note that the source cannot be connected to the body and thus the body effect should be taken into account. (b) Equivalent circuit.

resistances $1/g_{mb}$, r_{o1} , and r_{o3} appear in parallel between the source and ground. If we denote their parallel equivalent R_L , we can easily show that the voltage gain of the source follower is given by

$$\frac{v_o}{v_i} = \frac{R_L}{R_L + \frac{1}{g_m}} \quad (8.103)$$

where

$$R_L = r_{o1} \parallel r_{o3} \parallel \frac{1}{g_{mb}} \quad (8.104)$$

In cases where $\frac{1}{g_{mb}} \ll r_{o1}, r_{o3}$,

$$R_L \simeq \frac{1}{g_{mb}}$$

and

$$\frac{v_o}{v_i} \simeq \frac{g_{mb}}{g_m + g_{mb}} \quad (8.105)$$

Substituting for $g_{mb} = \chi g_m$ where $\chi = 0.1$ to 0.2 ,

$$\frac{v_o}{v_i} \simeq \frac{1}{1 + \chi} \quad (8.106)$$

This is the maximum possible gain obtained from an IC source follower. The actual gain realized will usually be lower because of the effect of r_{o1} and r_{o3} .

EXERCISE

8.28 For the source follower in Fig. 8.45(a), let the bias current of Q_1 be $200 \mu\text{A}$ and assume Q_1 is operating at $V_{OV} = 0.2 \text{ V}$. If $V_A = 5 \text{ V}$ and $\chi = 0.2$, find the voltage gain of the source follower.

Ans. 0.81 V/V

Example 8.7

For the CC–CE amplifier in Fig. 8.44(a) let $I_1 = I_2 = 1\text{ mA}$ and assume identical transistors with $\beta = 100$. Find the input resistance R_{in} and the overall voltage gain obtained when the amplifier is fed with a signal source having $R_{sig} = 4\text{ k}\Omega$ and loaded with a resistance $R_L = 4\text{ k}\Omega$. Compare the results with those obtained with a common-emitter amplifier operating under the same conditions. Ignore r_o .

Solution

At an emitter current of 1 mA, Q_1 and Q_2 have

$$g_m = 40\text{ mA/V}$$

$$r_e = 25\ \Omega$$

$$r_\pi = \frac{\beta}{g_m} = \frac{100}{40} = 2.5\text{ k}\Omega$$

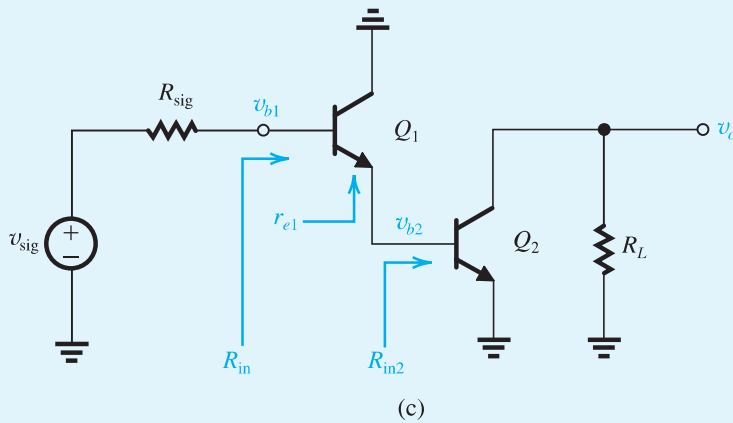


Figure 8.46 Circuit for Example 8.7.

Referring to Fig. 8.46 we can find

$$R_{in2} = r_{\pi2} = 2.5\text{ k}\Omega$$

$$R_{in} = (\beta_1 + 1)(r_{e1} + R_{in2})$$

$$= 101(0.025 + 2.5) = 255\text{ k}\Omega$$

$$\frac{v_{b1}}{v_{sig}} = \frac{R_{in}}{R_{in} + R_{sig}} = \frac{255}{255 + 4} = 0.98\text{ V/V}$$

$$\frac{v_{b2}}{v_{b1}} = \frac{R_{in2}}{R_{in2} + r_{e1}} = \frac{2.5}{2.5 + 0.025} = 0.99\text{ V/V}$$

$$\frac{v_o}{v_{b2}} = -g_{m2}R_L = -40 \times 4 = -160\text{ V/V}$$

Thus,

$$G_v = \frac{v_o}{v_{\text{sig}}} = -160 \times 0.99 \times 0.98 = -155 \text{ V/V}$$

For comparison, a CE amplifier operating under the same conditions will have

$$\begin{aligned} R_{\text{in}} &= r_{\pi} = 2.5 \text{ k}\Omega \\ G_v &= \frac{R_{\text{in}}}{R_{\text{in}} + R_{\text{sig}}} (-g_m R_L) \\ &= \frac{2.5}{2.5 + 4} (-40 \times 4) \\ &= -61.5 \text{ V/V} \end{aligned}$$

EXERCISE

8.29 Repeat Example 8.7 for the CD–CE configuration of Fig. 8.44(c). Let $I_1 = I_2 = 1 \text{ mA}$, $\beta_2 = 100$, $R_L = 4 \text{ k}\Omega$, and $k_{n1} = 8 \text{ mA/V}^2$; neglect the body effect in Q_1 and r_o of both transistors. Find R_{in} and G_v when $R_{\text{sig}} = 4 \text{ k}\Omega$ (as in Example 8.7) and $R_{\text{sig}} = 400 \text{ k}\Omega$. What would G_v of the CC–CE amplifier in Example 8.7 become for $R_{\text{sig}} = 400 \text{ k}\Omega$?

Ans. $R_{\text{in}} = \infty$; $G_v = -145.5 \text{ V/V}$, independent of R_{sig} ; -61.7 V/V

8.7.2 The Darlington Configuration⁵

Figure 8.47(a) shows a popular BJT circuit known as the **Darlington configuration**. It can be thought of as a variation of the CC–CE circuit with the collector of Q_1 connected to that of Q_2 . Alternatively, the **Darlington pair** can be thought of as a composite transistor with $\beta = \beta_1 \beta_2$. It can therefore be used to implement a high-performance voltage follower, as illustrated in Fig. 8.47(b). Note that in this application the circuit can be considered as the cascade connection of two common-collector transistors (i.e., a CC–CC configuration).

Since the transistor β depends on the dc bias current, it is possible that Q_1 will be operating at a very low β , rendering the β -multiplication effect of the Darlington pair rather ineffective. A simple solution to this problem is to provide a bias current for Q_1 , as shown in Fig. 8.47(c).

⁵Named after Sidney Darlington, a pioneer in filter design and transistor circuit design.

factor β is less than a critical value β_{cr} and unstable if $\beta \geq \beta_{cr}$, and find the value of β_{cr} . Hence, find the minimum value of the closed-loop gain for which the amplifier is stable.

Ans. $\omega_{180} = \sqrt{3} \times 10^4$ rad/s; $\beta_{cr} = 0.008$; $A_{f\min} = 111.1$

HARRY NYQUIST— A DIVERSE ELECTRONICS FUNDAMENTALIST:

Harry Nyquist, a Swedish-born electrical engineer working for Bell Labs and its predecessor, was responsible for developments in communications electronics involving thermal noise, feedback-amplifier stability, telegraphy, facsimile, television, and many other areas.

In *The Idea Factory*, an excellent book on the history of Bell Labs, Jon Gertner notes that

[S]ome lawyers in the patent office of the Bell Labs decided to study whether there was an organizing principle that could explain why certain individuals were more productive than others. They discerned only one common thread: Workers with the most patents often shared lunch or breakfast with a Bell Labs electrical engineer named Harry Nyquist. It wasn't the case that Nyquist gave them specific ideas. Rather, as one scientist recalled, "he drew people out, got them thinking." More than anything, Nyquist asked good questions.

11.8 Effect of Feedback on the Amplifier Poles

The amplifier frequency response and stability are determined directly by its poles. Therefore we shall investigate the effect of feedback on the poles of the amplifier.⁷

11.8.1 Stability and Pole Location

We shall begin by considering the relationship between stability and pole location. For an amplifier or any other system to be stable, its poles should lie in the left half of the s plane. A pair of complex-conjugate poles on the $j\omega$ axis gives rise to sustained sinusoidal oscillations. Poles in the right half of the s plane give rise to growing oscillations.

To verify the statement above, consider an amplifier with a pole pair at $s = \sigma_0 \pm j\omega_n$. If this amplifier is subjected to a disturbance, such as that caused by closure of the power-supply switch, its transient response will contain terms of the form

$$v(t) = e^{\sigma_0 t} [e^{+j\omega_n t} + e^{-j\omega_n t}] = 2e^{\sigma_0 t} \cos(\omega_n t) \quad (11.60)$$

This is a sinusoidal signal with an envelope $e^{\sigma_0 t}$. Now if the poles are in the left half of the s plane, then σ_0 will be negative and the oscillations will decay exponentially toward zero, as shown in Fig. 11.29(a), indicating that the system is stable. If, on the other hand, the poles are in

⁷For a brief review of poles and zeros and related concepts, refer to Appendix F.

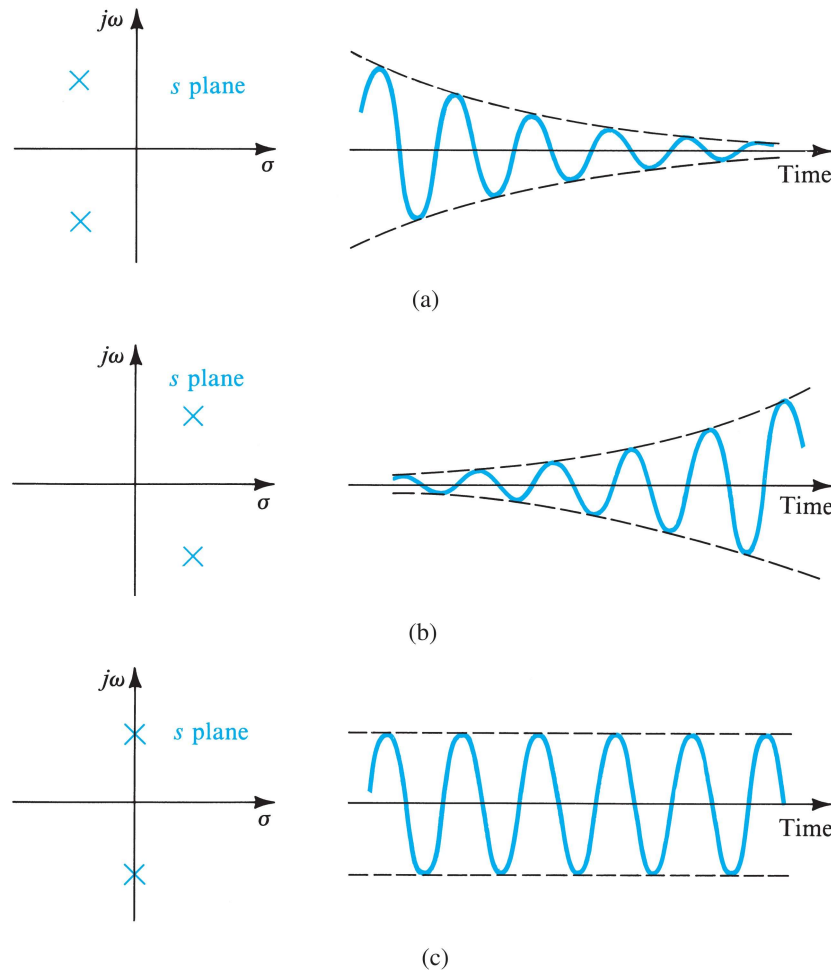


Figure 11.29 Relationship between pole location and transient response.

the right half-plane, then σ_0 will be positive, and the oscillations will grow exponentially (until some nonlinearity limits their growth), as shown in Fig. 11.29(b). Finally, if the poles are on the $j\omega$ axis, then σ_0 will be zero and the oscillations will be sustained, as shown in Fig. 11.29(c).

Although the discussion above is in terms of complex-conjugate poles, it can be shown that the existence of any right-half-plane poles results in instability.

11.8.2 Poles of the Feedback Amplifier

From the closed-loop transfer function in Eq. (11.57), we see that the poles of the feedback amplifier are the zeros of $1 + A(s)\beta(s)$. That is, the feedback amplifier poles are obtained by solving the equation



$$1 + A(s)\beta(s) = 0 \tag{11.61}$$

which is called the **characteristic equation** of the feedback loop. It should therefore be apparent that applying feedback to an amplifier changes its poles.

In the following, we shall consider how feedback affects the amplifier poles. For this purpose we shall assume that the open-loop amplifier has real poles and no finite zeros (i.e., all the zeros are at $s = \infty$). This will simplify the analysis and enable us to focus our attention on the fundamental concepts involved. We shall also assume that the feedback factor β is independent of frequency.

11.8.3 Amplifier with a Single-Pole Response

Consider first the case of an amplifier whose open-loop transfer function is characterized by a single pole:

$$A(s) = \frac{A_0}{1 + s/\omega_p} \quad (11.62)$$

The closed-loop transfer function is given by

$$A_f(s) = \frac{A_0/(1 + A_0\beta)}{1 + s/\omega_p(1 + A_0\beta)} \quad (11.63)$$

Thus the feedback moves the pole along the negative real axis to a frequency ω_{pf} ,

$$\omega_{pf} = \omega_p(1 + A_0\beta) \quad (11.64)$$

This process is illustrated in Fig. 11.30(a). Figure 11.30(b) shows Bode plots for $|A|$ and $|A_f|$. Note that while at low frequencies the difference between the two plots is $20 \log(1 + A_0\beta)$, the two curves coincide at high frequencies. One can show that this indeed is the case by approximating Eq. (11.63) for frequencies $\omega \gg \omega_p(1 + A_0\beta)$:

$$A_f(s) \simeq \frac{A_0\omega_p}{s} \simeq A(s) \quad (11.65)$$

Physically speaking, at such high frequencies the loop gain is much smaller than unity and the feedback is ineffective.

Figure 11.30(b) clearly illustrates the fact that applying negative feedback to an amplifier results in extending its bandwidth at the expense of a reduction in gain. Since the pole of the

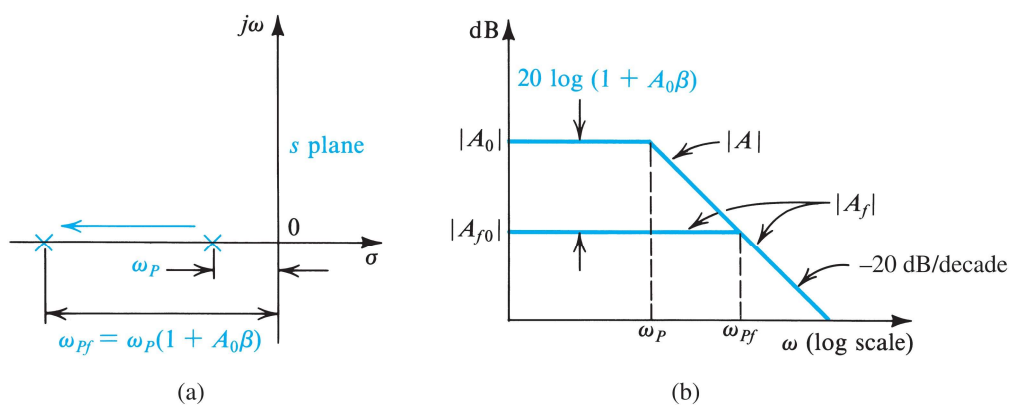


Figure 11.30 Effect of feedback on (a) the pole location and (b) the frequency response of an amplifier having a single-pole, open-loop response.

17.12.4 Amplifiers with Multiple Tuned Circuits

The selectivity achieved with the single tuned circuit of Fig. 17.42 is not sufficient in many applications—for instance, in the IF amplifier of a radio or a TV receiver. Greater selectivity is obtained by using additional tuned stages. Figure 17.46 shows a BJT with tuned circuits at both the input and the output.¹² In this circuit the bias details are shown, from which we note that biasing is quite similar to the classical arrangement employed in low-frequency, discrete-circuit design. However, to avoid the loading effect of the bias resistors R_{B1} and R_{B2} on the input tuned circuit, a **radio-frequency choke** (RFC) is inserted in series with each resistor. Such chokes have low resistance but high impedances at the frequencies of interest. The use of RFCs in biasing tuned RF amplifiers is common practice.

The analysis and design of the double-tuned amplifier of Fig. 17.46 is complicated by the Miller effect¹³ due to capacitance C_μ . Since the load is not simply resistive, as was the case in the amplifiers studied in Section 10.3.3, the Miller impedance at the input will be complex. This reflected impedance will cause detuning of the input circuit as well as “skewing” of the response of the input circuit. Needless to say, the coupling introduced by C_μ makes tuning (or aligning) the amplifier quite difficult. Worse still, the capacitor C_μ can cause oscillations to occur (see Gray and Searle, 1969, and Problem 17.101).

Methods exist for **neutralizing** the effect of C_μ , using additional circuits arranged to feed back a current equal and opposite to that through C_μ . An alternative, and preferred, approach is to use circuit configurations that do not suffer from the Miller effect. These are discussed later. Before leaving this section, however, we wish to point out that circuits of the type shown in Fig. 17.46 are usually designed utilizing the y -parameter model of the BJT (see

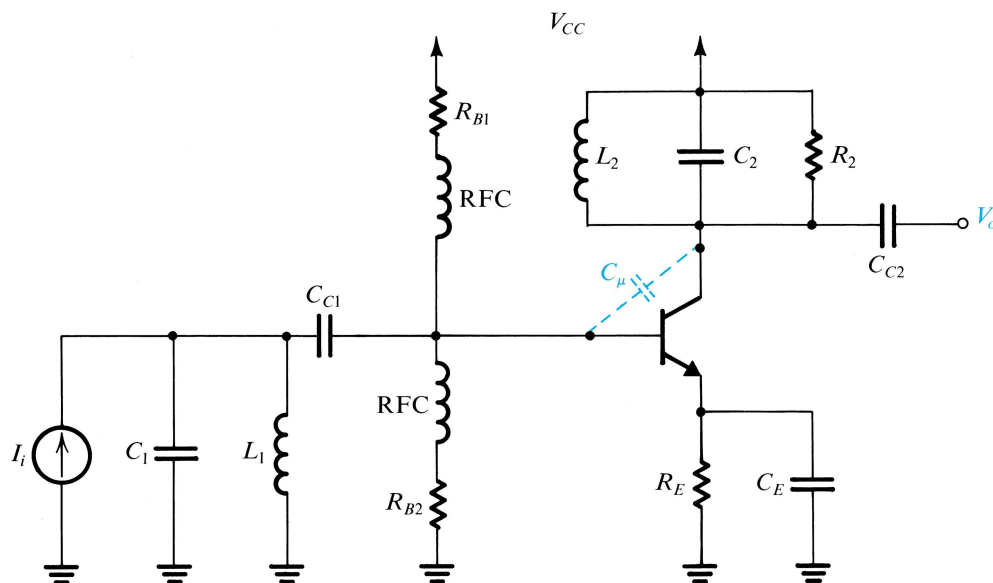


Figure 17.46 A BJT amplifier with tuned circuits at the input and the output.

¹²Note that because the input circuit is a parallel resonant circuit, an input current source (rather than voltage source) signal is utilized.

¹³Here we use “Miller effect” to refer to the effect of the feedback capacitance C_μ in reflecting back an input impedance that is a function of the amplifier load impedance.

Appendix C). This is done because here, in view of the fact that C_μ plays a significant role, the y -parameter model makes the analysis simpler (in comparison to that using the hybrid- π model). Also, the y parameters can easily be measured at the particular frequency of interest, ω_0 . For narrow-band amplifiers, the assumption is usually made that the y parameters remain approximately constant over the passband.

17.12.5 The Cascode and the CC–CB Cascade

From our study of amplifier frequency response in Chapter 10, we know that two amplifier configurations do not suffer from the Miller effect. These are the cascode configuration and the common-collector, common-base cascade. Figure 17.47 shows tuned amplifiers based on these two configurations. The CC–CB cascade is usually preferred in IC implementations because its differential structure makes it suitable for IC biasing techniques. (Note that the biasing details of the cascode circuit are not shown in Fig. 17.47(a). Biasing can be done using arrangements similar to those discussed in earlier chapters.)

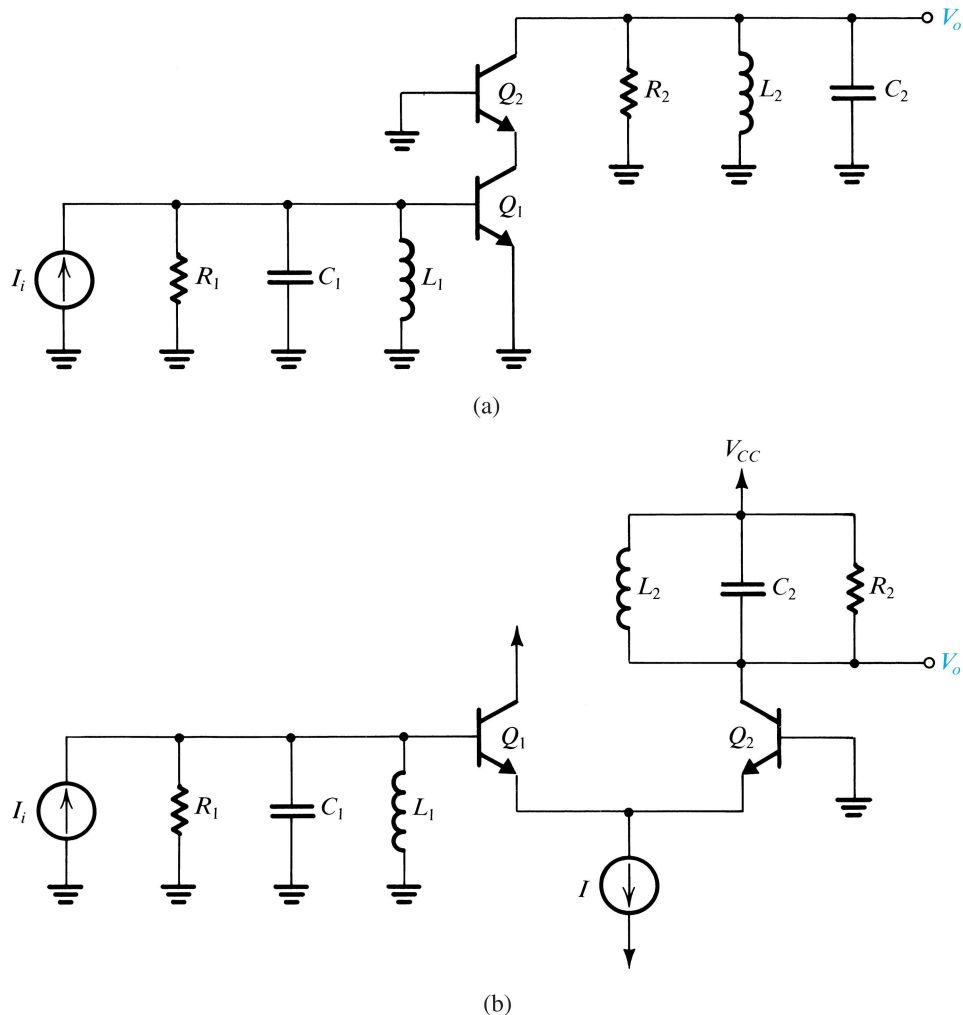


Figure 17.47 Two tuned-amplifier configurations that do not suffer from the Miller effect: (a) cascode and (b) common-collector, common-base cascade. (Note that bias details of the cascode circuit are not shown.)

17.12.6 Synchronous Tuning and Stagger Tuning

In the design of a tuned amplifier with multiple tuned circuits, the question of the frequency to which each circuit should be tuned arises. The objective, of course, is for the overall response to exhibit high passband flatness and skirt selectivity. To investigate this question, we shall assume that the overall response is the product of the individual responses: in other words, that the stages do not interact. This can easily be achieved using circuits such as those in Fig. 17.47.

Consider first the case of N identical resonant circuits, known as the **synchronously tuned** case. Figure 17.48 shows the response of an individual stage and that of the cascade. Observe the bandwidth “shrinkage” of the overall response. The 3-dB bandwidth B of the overall amplifier is related to that of the individual tuned circuits, ω_0/Q , by (see Problem 17.102)

$$B = \frac{\omega_0}{Q} \sqrt{2^{1/N} - 1} \quad (17.123)$$

The factor $\sqrt{2^{1/N} - 1}$ is known as the **bandwidth-shrinkage factor**. Given B and N , we can use Eq. (17.123) to determine the bandwidth required of the individual stages, ω_0/Q .

EXERCISE

D17.36 Consider the design of an IF amplifier for an FM radio receiver. Using two synchronously tuned stages with $f_0 = 10.7$ MHz, find the 3-dB bandwidth of each stage so that the overall bandwidth is 200 kHz. Using 3- μ H inductors find C and R for each stage.

Ans. 310.8 kHz; 73.7 pF; 6.95 k Ω

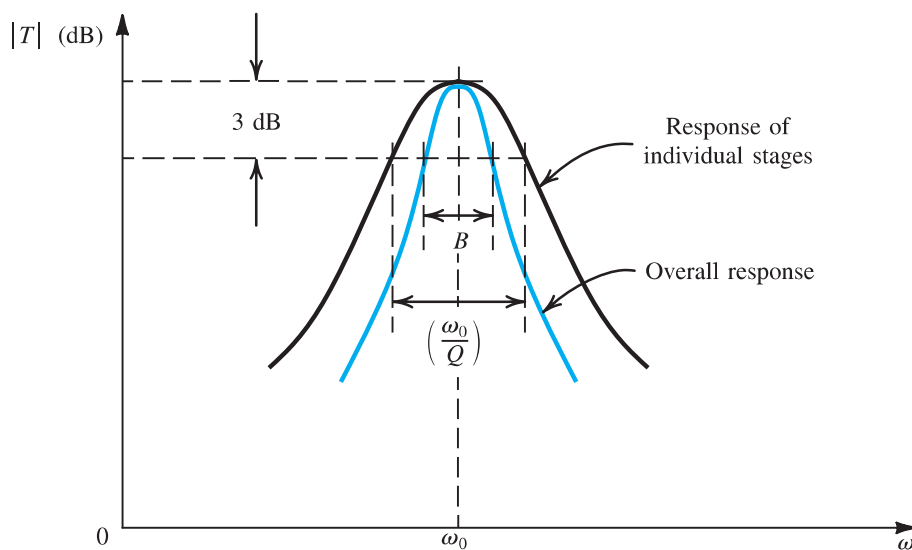


Figure 17.48 Frequency response of a synchronously tuned amplifier.

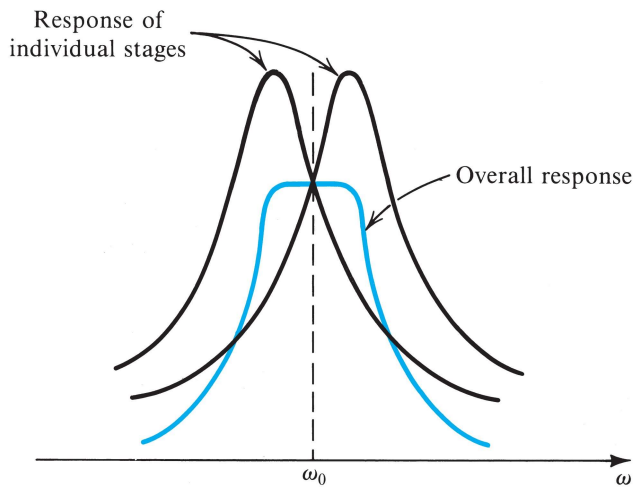


Figure 17.49 Stagger-tuning the individual resonant circuits can result in an overall response with a passband flatter than that obtained with synchronous tuning (Fig. 17.48).

A much better overall response is obtained by stagger-tuning the individual stages, as illustrated in Fig. 17.49. Stagger-tuned amplifiers are usually designed so that the overall response exhibits *maximal flatness* around the center frequency f_0 . Such a response can be obtained by transforming the response of a maximally flat (Butterworth) low-pass filter up the frequency axis to ω_0 . Appendix H shows how this can be done.

Summary

- A filter is a linear two-port network with a transfer function $T(s) = V_o(s)/V_i(s)$. For physical frequencies, the filter transmission is expressed as $T(j\omega) = |T(j\omega)|e^{j\phi(\omega)}$. The magnitude of transmission can be expressed in decibels using either the gain function $G(\omega) \equiv 20\log|T|$ or the attenuation function $A(\omega) \equiv -20\log|T|$.
- The transmission characteristics of a filter are specified in terms of the edges of the passband(s) and the stopband(s); the maximum allowed variation in passband transmission, A_{\max} (dB); and the minimum attenuation required in the stopband, A_{\min} (dB). In some applications, the phase characteristics are also specified.
- The filter transfer function can be expressed as the ratio of two polynomials in s ; the degree of the denominator polynomial, N , is the filter order. The N roots of the denominator polynomial are the poles (natural modes).
- To obtain a highly selective response, the poles are complex and occur in conjugate pairs (except for one real pole when N is odd). The zeros are placed on the $j\omega$ axis in the stopband(s) including $\omega = 0$ and $\omega = \infty$.
- The Butterworth filter approximation provides a low-pass response that is maximally flat at $\omega = 0$. The transmission decreases monotonically as ω increases, reaching 0 (infinite attenuation) at $\omega = \infty$, where all N transmission zeros lie. Eq. (17.11) gives $|T|$, where ϵ is given by Eq. (17.14) and the order N is determined using Eq. (17.15). The poles are found using the graphical construction of Fig. 17.10, and the transfer function is given by Eq. (17.16).
- The Chebyshev filter approximation provides a low-pass response that is equiripple in the passband with the transmission decreasing monotonically in the stopband. All the transmission zeros are at $s = \infty$. Eq. (17.18) gives $|T|$ in the passband and Eq. (17.19) gives $|T|$ in the stopband, where ϵ is given by Eq. (17.21). The order N can be determined using Eq. (17.22). The poles are given by Eq. (17.23) and the transfer function by Eq. (17.24).
- Figures 17.13 and 17.14 provide a summary of first-order filter functions and their realizations.
- Figure 17.16 provides the characteristics of seven special second-order filtering functions.
- The second-order LCR resonator of Fig. 17.17(a) realizes a pair of complex-conjugate poles with $\omega_0 = 1/\sqrt{LC}$ and $Q = \omega_0 CR$. This resonator can be used to realize the

Rajeev Gandhi Memorial College of Engineering & Technology

Autonomous
NANDYAL-518501

Department of Electronics & Communication Engineering

Academic Year: 2022-23

Subject: Electronic Circuits-Analysis & Design (ECA&D)


Class: II B. Tech, II Sem


Faculty member taught earlier: Dr. Kethepalli Mallikarjuna, Dr.C. Venkataiah

Suggestions:

As per the course structure of the UG (R20), ECA&D subject is completely based on the electronic circuits and its analysis based on the h-parameter model, simplified h-parameter model and also hybrid-pi parameter model. The subject also consists of analysis of feedback amplifier and its analysis based on its discrete components. It also consists of design of oscillator circuits using BJT and JFET. It also consists of different power amplifier and their efficiency calculations. Hence, following suggestions are made by subject experts:

1. As the subject comprises of theory and quantitative analysis and design earlier overall pass percentage was 85%. So, it is required to discuss more about designing problems to improve overall percentage further.
2. To improve the subject knowledge, this subject is to be demonstrated with prototype design models.
3. To improve the results, to take care of slow learners by taking extra classes and make them to practice more from previous year question papers as assignments.
4. Regular counseling and motivation should be given to the students to avoid the lacking in the subject knowledge.
5. The environment of the class should be interactive with respect to the subject discussion so that students can understand elaborately and may ask more questions.


Signature of the subject expert-1
Dr. Kethepalli Mallikarjuna
Professor and HOD
Dept. of ECE


Signature of the subject expert-2
Dr.C.Venkataiah
Associate Professor
Dept. of ECE

Assessment



Rajeev Gandhi Memorial College of Engineering & Technology

(Autonomous Institution | Approved by AICTE New Delhi | Affiliated to JNTU Anantapur)

Address : Nerawada 'X' Roads, Nandyal, Kurnool Dist, Andhra Pradesh, India

Counselling Code : RGIT



Dr. Y. Madhu Sudhana Reddy

Assoc. Prof.

Dept. of ECE

Phone: 9440486567

Email: ymsr1016@gmail.com

S.No.	Year (Batch)	Section	Subject	Branch	Registered	Appeared	Failed	Pass(%)	Highest
1	II B.Tech. II Sem. & 2021	B	ECAD Lab	ECE	73	72	8	88.89	10
2	II B.Tech. II Sem. & 2021	B	ECAD	ECE	73	72	14	80.56	9
3	II B.Tech. II Sem. & 2021	A	ECAD	ECE	73	70	18	74.29	9
4	IV B.Tech. II Sem. & 2019	D	SEM	ECE	64	64	0	100.00	9
5	IV B.Tech. II Sem. & 2019	A	SEM	ECE	71	71	0	100.00	10
6	IV B.Tech. I Sem. & 2019	A	DIP Lab	ECE	70	70	0	100.00	10
7	IV B.Tech. I Sem. & 2019	D	DIP	ECE	62	62	13	79.03	10
8	IV B.Tech. I Sem. & 2019	A	DIP	ECE	70	70	0	100.00	10
9	II B.Tech. II Sem. & 2020	A	ECAD Lab	ECE	66	66	3	95.45	10
10	II B.Tech. II Sem. & 2020	B	ECAD	ECE	61	61	3	95.08	10
11	II B.Tech. II Sem. & 2020	A	ECAD	ECE	66	66	4	93.94	10
12	IV B.Tech. I Sem. & 2018	D	DSP&IP Lab	ECE	60	55	3	94.55	9
13	IV B.Tech. I Sem. & 2018	B	DSP&IP Lab	ECE	69	69	0	100.00	10
14	IV B.Tech. I Sem. & 2018	D	DIP	ECE	60	55	13	76.36	7
15	IV B.Tech. I Sem. & 2018	B	DIP	ECE	69	69	2	97.10	9
16	III B.Tech. II Sem. & 2018	C	ECDT Lab	ECE	57	57	0	100.00	10
17	III B.Tech. II Sem. & 2018	C	DSP	ECE	57	57	3	94.74	7
18	III B.Tech. II Sem. & 2018	B	DSP	ECE	69	69	1	98.55	9
19	IV B.Tech. I Sem. & 2017	B	DSP&IP Lab	ECE	57	57	0	100.00	10
20	IV B.Tech. I Sem. & 2017	C	DIP	ECE	52	52	4	92.31	8
21	IV B.Tech. I Sem. & 2017	B	DIP	ECE	57	57	1	98.25	9
22	III B.Tech. II Sem. & 2017	B	S&T Lab	ECE	57	57	0	100.00	10

S.No.	Year (Batch)	Section	Subject	Branch	Registered	Appeared	Failed	Pass(%)	Highest
23	III B.Tech. II Sem. & 2017	B	EM&I	ECE	57	57	3	94.74	8
24	III B.Tech. II Sem. & 2017	A	DSP	ECE	57	57	1	98.25	10
25	II B.Tech. I Sem. & 2018	A	S&SS Lab	ECE	66	66	10	84.85	10
26	IV B.Tech. I Sem. & 2016	B	DSP	EEE	71	71	16	77.46	10
27	IV B.Tech. I Sem. & 2016	A	DSP	EEE	62	61	6	90.16	9
28	III B.Tech. II Sem. & 2016	C	ECDT Lab	ECE	56	51	0	100.00	10
29	II B.Tech. II Sem. & 2017	B	PDC	ECE	62	59	12	79.66	10
30	II B.Tech. II Sem. & 2017	A	PDC	ECE	60	59	11	81.36	10
31	II B.Tech. I Sem. & 2017	D	ECA Lab	ECE	59	51	2	96.08	10
32	II B.Tech. I Sem. & 2017	D	ECA	ECE	59	50	12	76.00	10
33	II B.Tech. I Sem. & 2017	B	ECA	ECE	64	59	18	69.49	9
34	III B.Tech. II Sem. & 2015	D	ECDT Lab	ECE	59	59	0	100.00	10
35	III B.Tech. II Sem. & 2015	D	DSP	ECE	59	59	7	88.14	10
36	II B.Tech. I Sem. & 2016	B	ECA Lab	ECE	61	54	3	94.44	10
37	II B.Tech. I Sem. & 2016	A	ECA Lab	ECE	62	58	3	94.83	10
38	II B.Tech. I Sem. & 2016	B	ECA	ECE	61	54	14	74.07	10
39	II B.Tech. I Sem. & 2016	A	ECA	ECE	62	58	11	81.03	9
40	II B.Tech. II Sem. & 2015	A	ECA Lab	ECE	65	3	0	100.00	8
41	II B.Tech. II Sem. & 2015	A	ECA	ECE	65	3	3	0.00	0
42	II B.Tech. II Sem. & 2015	D	PDC	ECE	62	62	19	69.35	10
43	II B.Tech. II Sem. & 2015	C	PDC	ECE	62	62	17	72.58	9
44	II B.Tech. I Sem. & 2015	D	ECA Lab	ECE	63	62	4	93.55	10
45	II B.Tech. I Sem. & 2015	C	ECA Lab	ECE	64	62	2	96.77	10
46	IV B.Tech. I Sem. & 2013	A	DIP	EIE	1	1	1	0.00	29
47	IV B.Tech. I Sem. & 2013	A	DSP	EEE	63	62	13	79.03	90
48	II B.Tech. I Sem. & 2015	D	ECA	ECE	63	62	15	75.81	10