
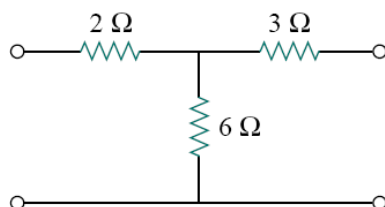


Note: 1. Answer first question compulsorily. (5 x 1 = 5 Marks)

2. Answer Any *THREE* from 2 to 5 questions. (3 x 5 = 15 Marks)

Q.No	M	CO	BL
Q.1 a) Define Natural response and Forced response.	1M	CO4	BL1
b) Write the conditions of Symmetry and Reciprocity for ABCD and h Parameters	1M	CO5	BL2
c) Define voltage Transfer ratio.	1M	CO6	BL1
d) Design a low pass Π -section filter with a cut off frequency of 2 KHz to operate with a load resistance of 400 Ω .	1M	CO6	BL3
e) Define Port	1M	CO5	BL2
Q.2 a) Find the short circuit admittance parameters for the circuit shown in Figure.	3M	CO5	BL2
b) Express h parameters in terms of ABCD parameters	2M	CO5	BL1
Q.3 a) Derive the inter relationship of Z in terms of Y, ABCD in terms of Y parameters.	3M	CO5	BL3
b) Find the Hybrid Parameters for circuit shown.	2M	CO5	BL1

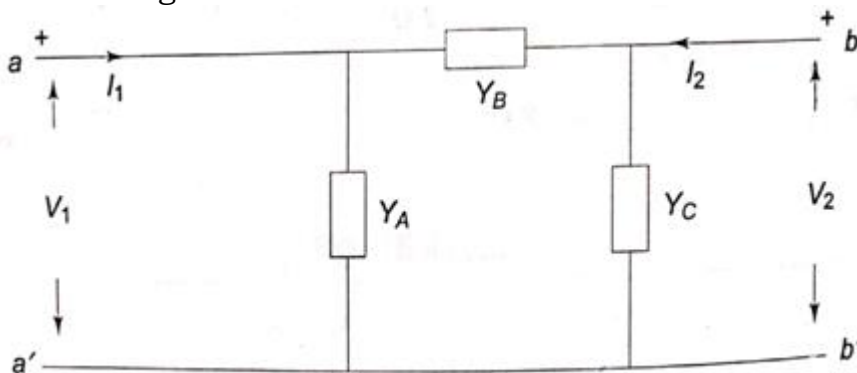

Q.4 a) Design a band elimination filter having a design impedance of **3M** CO6 BL1 600Ω and cut off frequencies $f_1=2$ KHz and $f_2=6$ KHz.

b) Explain in detail about classification of Filters **2M** CO6 BL2

Q.5 Determine the solution for the current when switch is closed **5M** CO4 BL1 at $\Phi=30$ degrees for a series RL circuit. Voltage $V=50\cos(100t+\Phi)$ volts is applied at $\Phi=30$. Resistance $R=150\Omega$ and $L=0.5H$.